

EDN[®]


Designer's guide to
flash-ADC testing—Pt 2

Engineering in Germany

New CASE packages
for embedded systems

Designing step-down
switching regulators

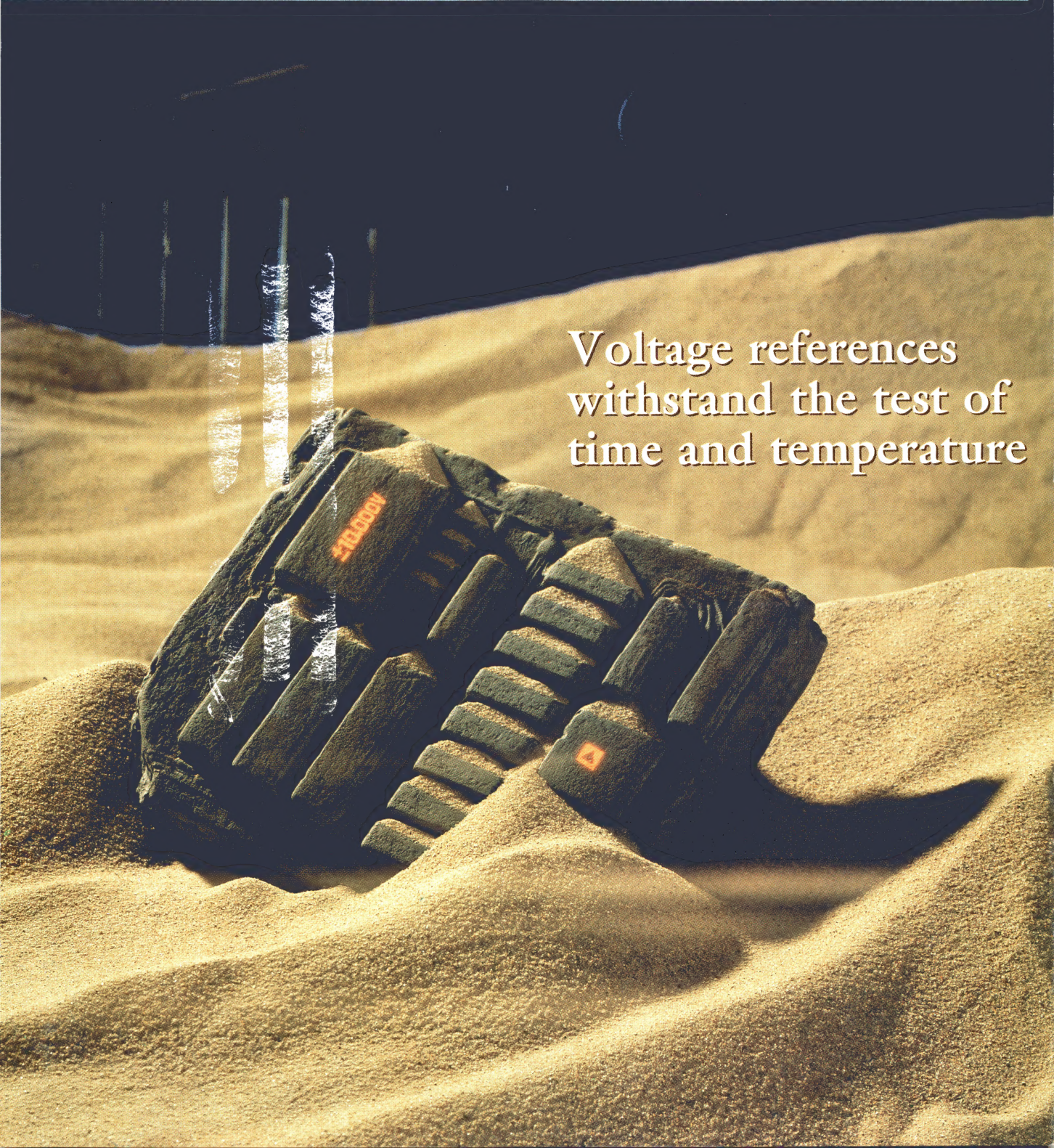ELECTRONIC TECHNOLOGY FOR ENGINEERS AND ENGINEERING MANAGERS



Voltage references
withstand the test of
time and temperature

TRUE POWER COMES FROM REAL CHOICE— FUJITSU MICROPROCESSORS

These two important facts should influence your choice of microprocessor supplier:

Fujitsu was the first vendor to implement the SPARC™ RISC architecture and has been shipping RISC products in volume since 1986.

Fujitsu's G_{MICRO} family of 32-Bit CISC microprocessors based on TRON architecture will offer performance nearly *double* that of the 32-Bit MPUs currently on the market.

In addition to the experience and leading edge technology one expects of Japan's largest computer company, and the world's No. 1 ASIC supplier, Fujitsu also offers choice—real choice in the form of a full range of microprocessor and controller products. You can choose from:

- 4-Bit CMOS microcontrollers
- 4/8-Bit CMOS F⁹MC™ flexible microcontrollers for tailor made solutions
- 8/16-Bit microprocessors and peripherals

To find out more about the Fujitsu range and about development support and training, call or fax your local Fujitsu office now for a free copy of their latest microprocessor selector guide—then make your choice.




MICROPROCESSOR



TELECOM




GATE ARRAY

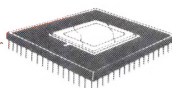


DRAM



DSP

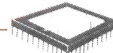

MICROPROCESSOR

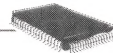

ITALY: Fujitsu Microelectronics, Italia S.R.L., Centro Direzionale Milanofiori, Strada 4—Palazzo A/2, 20094 Assago (Milano). Phone: (2) 8246170/176. Telex: 318546. Fax: (2) 8246189.
BENELUX: Fujitsu Mikroelektronik GmbH, Europalaan 26A, 5623 LJ Eindhoven, The Netherlands. Phone: (040) 447440. Telex: 59265. Fax: (040) 444158. SCANDINAVIA: Fujitsu Microelectronics Ltd., Tonggatan 8, 17154 Solna, Sweden. Phone: (8) 7646365. Telex: 13411. Fax: (8) 280345. UNITED KINGDOM: Fujitsu Microelectronics Ltd., Hargrave House, Belmont Road, Maidenhead, Berkshire SL6 6NE. Phone: (0628) 76100. Telex: 848955. Fax: (0628) 781484.

SPARC is a registered trademark of Sun Microsystems, Inc. TRON = The Real Time Operating systems Nucleus.



WEST GERMANY: Fujitsu Mikroelektronik GmbH, Lyoner Strasse 44-48, Arabella Center 9, OG 6000 Frankfurt 71. Phone: (069) 66320. Telex: 411963. Fax: (069) 6632122.
 SOUTH GERMANY: Fujitsu Mikroelektronik GmbH, Carl-Zeiss-Ring II, 8045 Ismaning. Phone: (089) 9609440. Teletex: (17) 897446. Fax: (089) 96094422. SOUTH WEST
 GERMANY: Fujitsu Mikroelektronik GmbH, Am Joachimsberg 10-12, 7033 Herrenberg. Phone: (07032) 4085. Fax: (07032) 4088. FRANCE: Fujitsu Microelectronics, Immeuble Le
 Trident, 3-5, Voie Félix Eboué, 94024 Creteil Cedex. Phone: (1) 42078200. Telex: 262861. Fax: (1) 42077933.



STD ROM

**A New ROM-based
Development
Standard from
Ziatech**



Put Your STD System to Bed

STD ROM streamlines the development of embedded applications. It combines Borland's Turbo Debugger with Ziatech's VIRTUAL TARGET INTERFACE and STD ROM LOCATE to provide an environment for easily "ROMMING" Microsoft C and Turbo C applications.

Single Board Selection

*Ziatech offers the best selection of single board computers in the business. These compact, cost-effective computers are compatible with existing STD Bus products and the new **STD 32** Bus introduced by Ziatech.*

Not Just Another STD Bus Company

Our on-line technical support, systems engineering courses, guaranteed product availability and superior documentation have made Ziatech the premier STD computer company.

FREE Demo and Data

STD ROM can be on your doorstep within days. Call today to arrange a free demonstration. STD ROM and Ziatech are ready to serve your embedded application needs.



8088

V20

V40

V50

80386SX

ZIATECH
CORPORATION

FAX (805) 541-5088

Telephone (805) 541-0488

© Copyright 1989 by Ziatech Corporation. All rights reserved.
Product names of other companies may be trademarks of those companies.



The VME Volksclosure. \$995. Ready to Run.

Finally. The economies of mass production catch up with VME and Multibus II enclosures.

Introducing the Volksclosure, Electronic Solutions' economy model enclosure with turbo performance. All you do is add cards and peripherals for a complete, attractive desktop computer.

With the Volksclosure (also known as our Model One) everything comes standard: six VME or Multibus II slots, space for three half-height 5 $\frac{1}{4}$ " disk drives, and a high-performance six-layer backplane all in a highly tooled enclosure with our handsome front panel that hides those ugly connectors and cables.



You do get a choice between two multiple-output power supplies: 190 Watts with 19A at +5V or 270 Watts with 30A at +5V. You can also choose a J2 backplane for VME extended addressing or iLBX II for a Multibus II system.


Most important, while the Volksclosure costs less, you

don't get less. It fully reflects Electronic Solutions' commitment to quality and performance. For example, it meets UL and CSA safety standards and FCC Class A EMI/RFI specs to the letter.

The New Volksclosure. How to get a lot more mileage from your packaging budget. Call right now for complete details.



We'll FAX you the facts

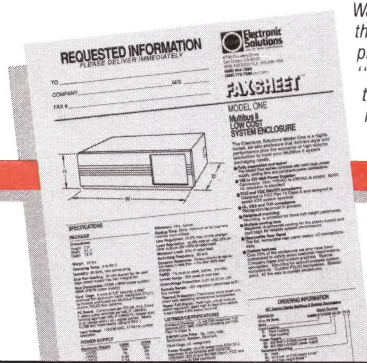

Want the latest data in a hurry? Nothing is faster than Electronic Solutions' new "FAX the FACTS" program. If you have a FAX machine, just call our "800" number, give us your FAX number and type of FAX machine, and the information you need from us. We'll FAX it to you immediately.




Electronic Solutions
UNIT OF ZERO CORPORATION

6790 Flanders Drive, San Diego, CA 92121 • (619) 452-9333 Telex II(TWX): 910-335-1169

Call Toll Free: (800)854-7086 In Calif: (800)772-7086

Circle No. 113

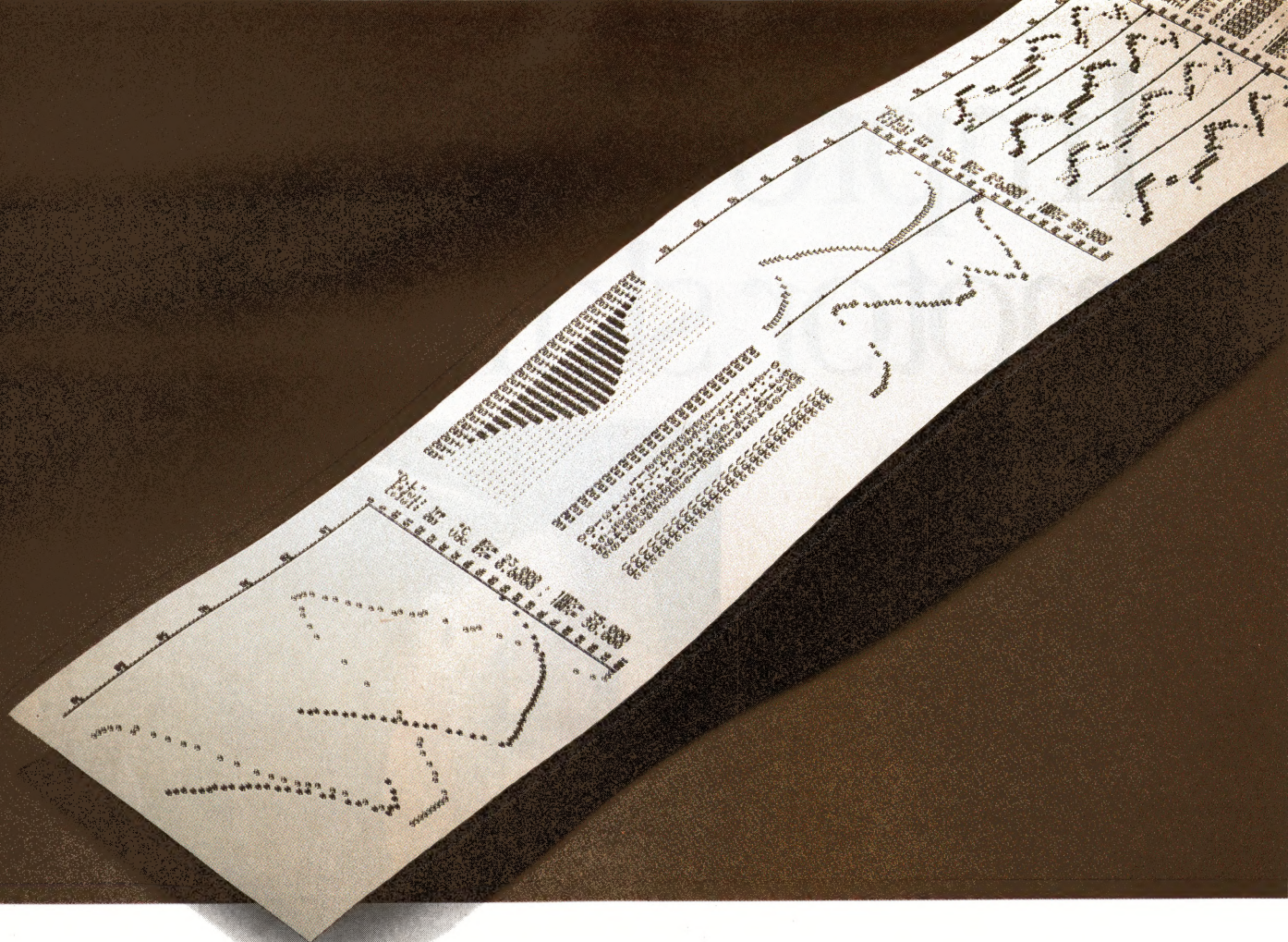

A plot to get you to buy our Data Logger.

As if you didn't have enough reasons already.

Our Series 50 Data Logger is a fraction the size of most other data loggers. Considerably less expensive. Completely portable.

And now, as you can see, Series 50 not only gathers data, it explains it.

You can plot from one to sixteen variables at a time. Divide the width of the page into one, two or four segments, with multiple variables in each.

If conditions change, Series 50 can be programmed to change the plot with them. For instance, it can switch to higher resolution and time-stamp data with messages during alarm conditions. And it does all this on its own, no computer needed. (On the other

hand, it can also be controlled by a computer via IEEE-488 or RS-232.)


Series 50 will plot bar graphs next to numerical data. Create

min/max plots. Or generate x-y graphs from stored data.

Speaking of stored data, Series 50 can keep up to 100,000 readings in memory. Which is a good thing, because with four independent A/D converters and up to 260 channel scanning capacity, you could be gathering plenty of data.


Data such as temperatures (6 thermocouple types and RTD's), AC/DC volts and current, resistance, frequency, time period, pulse width and more.

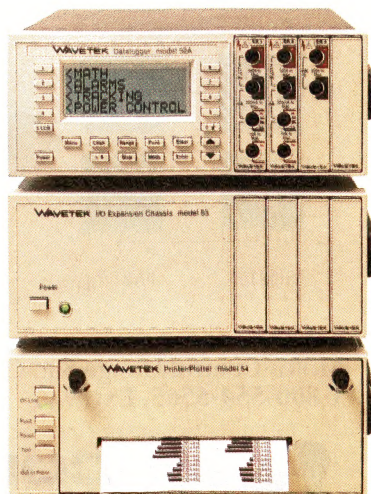If our plot is working, you'd probably like to know more about the Series 50 Data Logger. Just phone (619) 279-2200. We'll be expecting your call.




Improve your motor skills.

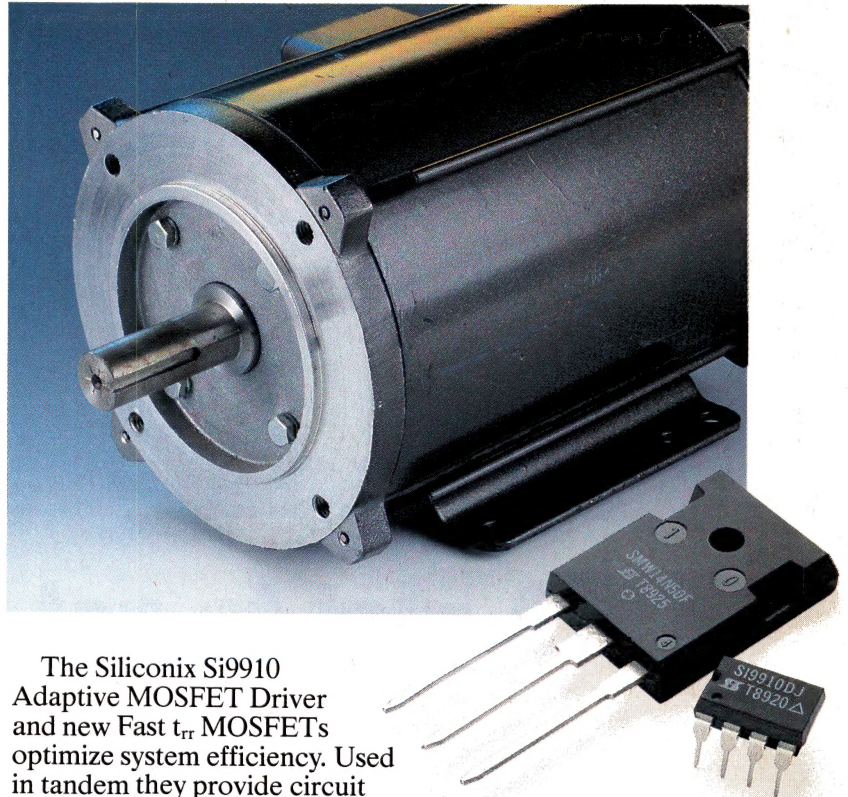Siliconix' new system solution for more efficient motor control. Combine an Adaptive MOSFET Driver with Fast t_{rr} MOSFETs.



The Siliconix Si9910 Adaptive MOSFET Driver and new Fast t_{rr} MOSFETs optimize system efficiency. Used in tandem they provide circuit protection and logic interface in off-line motor applications.

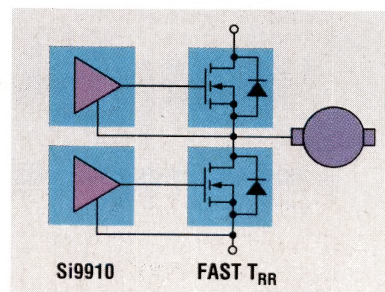This unique CMOS-compatible solution for variable-speed motor control significantly improves system performance. With five circuit protection features and lower power losses, the combined system results in higher reliability, smaller size, lower cost and reduced design time.



The Si9910 and Fast t_{rr} MOSFET family: system solutions for more efficient off-line control in motor drive and power supply applications such as major appliances, fans and blowers, industrial controllers, automobiles, power hand tools and UPS.


Improve your motor skills! Ask for your Si9910 and Fast t_{rr} Motor Control Design Kit. Call our toll-free hot line now! 1-800-554-5565, Ext. 946.

Siliconix
incorporated

2201 Laurelwood Road, Santa Clara, CA 95054

© 1989 Siliconix inc.

EDN January 18, 1990

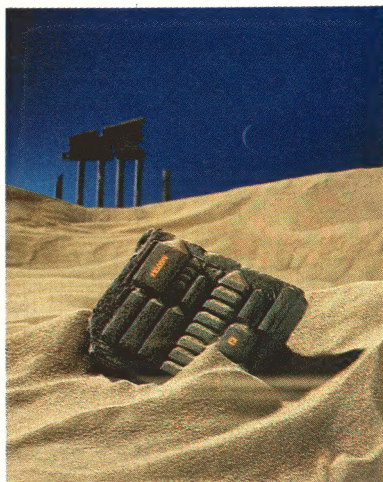

On the cover: Manufacturers offer a wide range of voltage references to suit various environments. Keep in mind the characteristics that are important to your particular application when you make your choice. See the Special Report on pg 120. (Photo courtesy Analog Devices Inc)

SPECIAL REPORT

Voltage references

120

Although seemingly mundane, voltage references play an important role in a wide range of applications. Manufacturers offer a variety of types from which to choose, but choose carefully and with an eye to what's important for your application.—*Dave Pryce, Associate Editor*

Measuring the cost of quality: German engineering at the crossroads

59

This article is the first in an occasional series that will examine the electronics-engineering profession in Europe. This installment describes how German electronics engineers, in an effort to become more competitive, try to keep quality high while reducing costs.

—*Gary Legg, Special Projects Editor*

DESIGN FEATURES

Designer's guide to flash-ADC testing—Part 2

133


By testing your flash A/D converter, you can ensure that it's faithful to all the specifications listed on its data sheet. Part 2 of this 3-part series presents a number of methods, including sine-wave curve fitting and the FFT, that you can use to test flash converters.—*Walt Kester, Analog Devices*

Basic principles and ingenious circuits yield stout switchers

151

A substantial percentage of power supplies are step-down regulators. Although the theory of step-down, "buck" switching regulators is well established, myriad practical details, if mishandled, can spoil the theory's pristine beauty. Luckily, convenient, easily applied switching-regulator ICs have recently become available.—*Jim Williams, Linear Technology Corp*

Continued on page 7

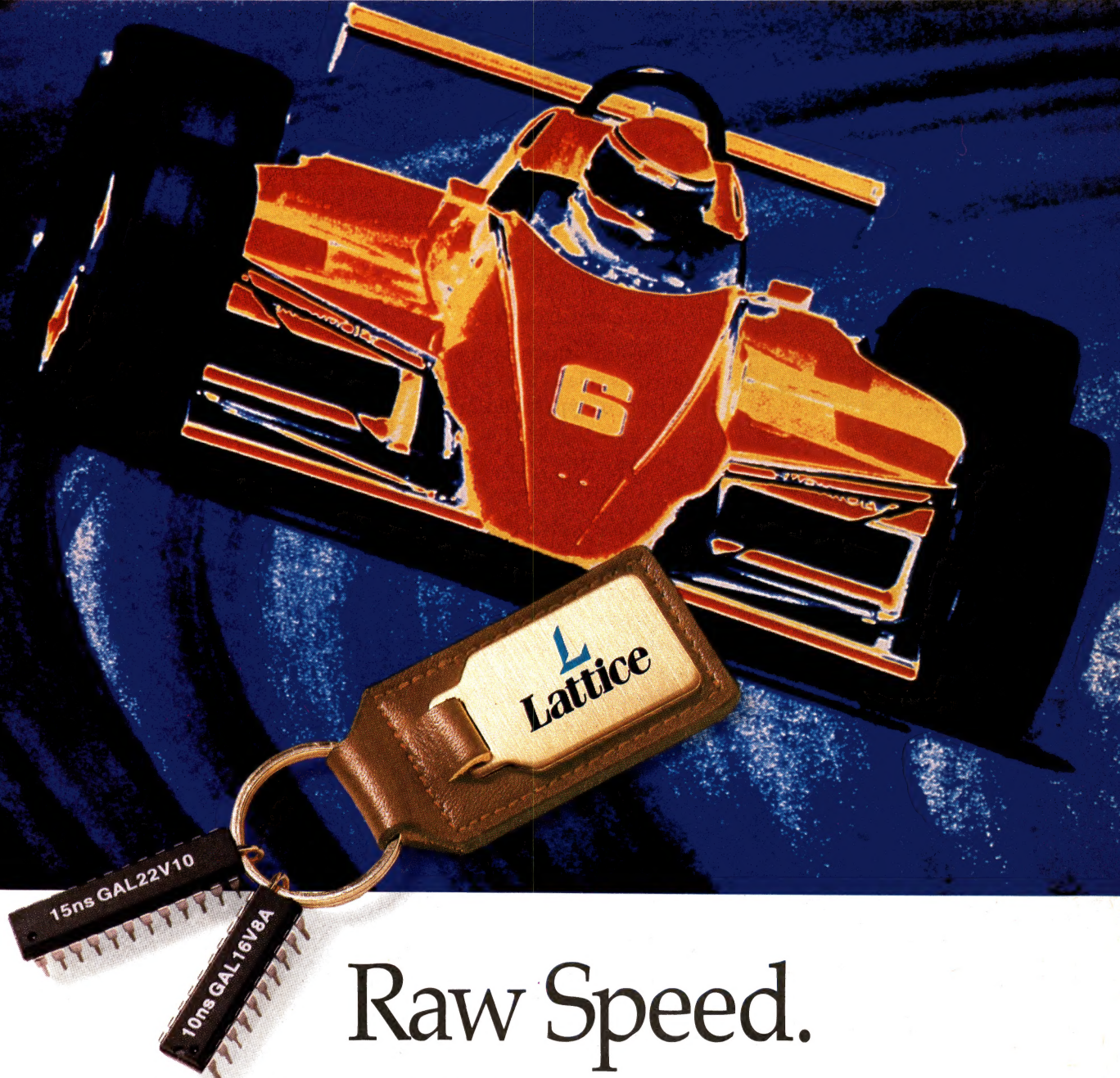

Raw Speed.

The world's fastest CMOS PLDs are the keys to your high performance design.

The leader in CMOS PLDs has done it again. Lattice's new 10ns GAL16V8A and GAL20V8A devices are the fastest on the track. With power consumption only one-fourth to one-half that of bipolar PLDs.

If you need higher functional integration, test drive our 15ns GAL22V10. It's the fastest user-programmable 22V10 available.

As if our superior speed/power product were not enough, our universal GAL® architecture makes conven-

tional PAL® devices—and huge inventories—obsolete. The 16V8A and 20V8A can replace 42 standard PAL devices.

Best of all, you know you've got a winner before you ever use a Lattice GAL device. Our proprietary electrically erasable CMOS (E²CMOS™) process lets us repeatedly test every characteristic before we ship the part. Which means 100% programming yields. Less board rework. And better system reliability.

Make sure your high-performance design has all the right parts. Get the fastest CMOS PLDs available. Only from Lattice, the leader in CMOS PLDs.



Lattice
Semiconductor
Corporation™

5555 N.E. Moore Ct. • Hillsboro, OR 97124

Inventors of the E²CMOS PLDSM


GAL is a registered trademark of Lattice Semiconductor Corporation.
E²CMOS is a trademark of Lattice Semiconductor Corporation.
PAL is a registered trademark of Advanced Micro Devices, Inc.

Circle 47 for Literature

Circle 48 for Employment Information

Copyright © 1989, Lattice Semiconductor Corporation.

EDN January 18, 1990

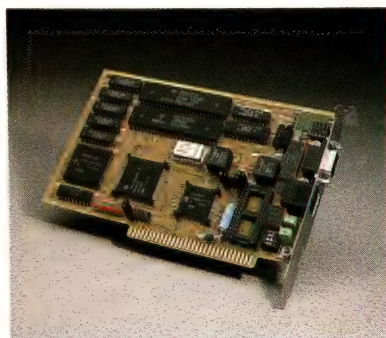

You can expect to see more token-ring LANs in non-IBM installations—the availability of faster boards is one reason why (pg 65).

EDN magazine
now offers
Express Request,
a convenient way
to retrieve product
information by
phone. See the
Reader Service
Card in the front
for details on how
to use this free
service.

Express Request 

TECHNOLOGY UPDATES

Token-ring boards: 65 Standard efficiently allocates channel use

Expect token-ring LANs to become more popular beyond IBM installations because of the benefits they offer compared with Ethernet networks. Speed, reliability, and improved bandwidth performance are a few reasons token-ring boards are expanding their realm of applications.—*Maury Wright, Regional Editor*

Optical-character-recognition software: 77 Inexpensive software reads printed material

Finally there's a worthwhile alternative to the time-consuming and tedious task of keying data and text into your personal computer by hand. Recently introduced, inexpensive software—optical-character-recognition packages—can accurately transform the printed output of high-resolution optical scanners into an ASCII file in your computer.—*Charles H Small, Senior Editor*

CASE for embedded systems: 95 New software tools speed design and debug

To avoid extensive redesign tasks, you must maintain a delicate balance between software and hardware development when designing for embedded systems. Four new computer-aided-software-engineering (CASE) packages, however, may simplify and speed the process. And unlike structured-analysis packages for batch-processing systems, these new tools concentrate specifically on code writing, debug, integration, and performance evaluation.—*Margery Conner, Regional Editor*

PRODUCT UPDATES

Custom-designed microcontrollers	113
Digital-storage-oscilloscope module	116


DESIGN IDEAS

Program plots transformer response	177
Op amp increases output impedance	178
Resistor isolates grounds	180
Routines give Quick Basic huge arrays	184
PLD expands arbiter chip	184

Continued on page 9

Cahners Publishing Company, A Division of Reed Publishing USA ☐ Specialized Business Magazines for Building & Construction ☐ Manufacturing ☐ Foodservice & Lodging ☐ Electronics & Computers ☐ Interior Design ☐ Printing ☐ Publishing ☐ Industrial Research & Technology ☐ Health Care ☐ and Entertainment. Specialized Consumer Magazines: ☐ American Baby ☐ and Modern Bride.

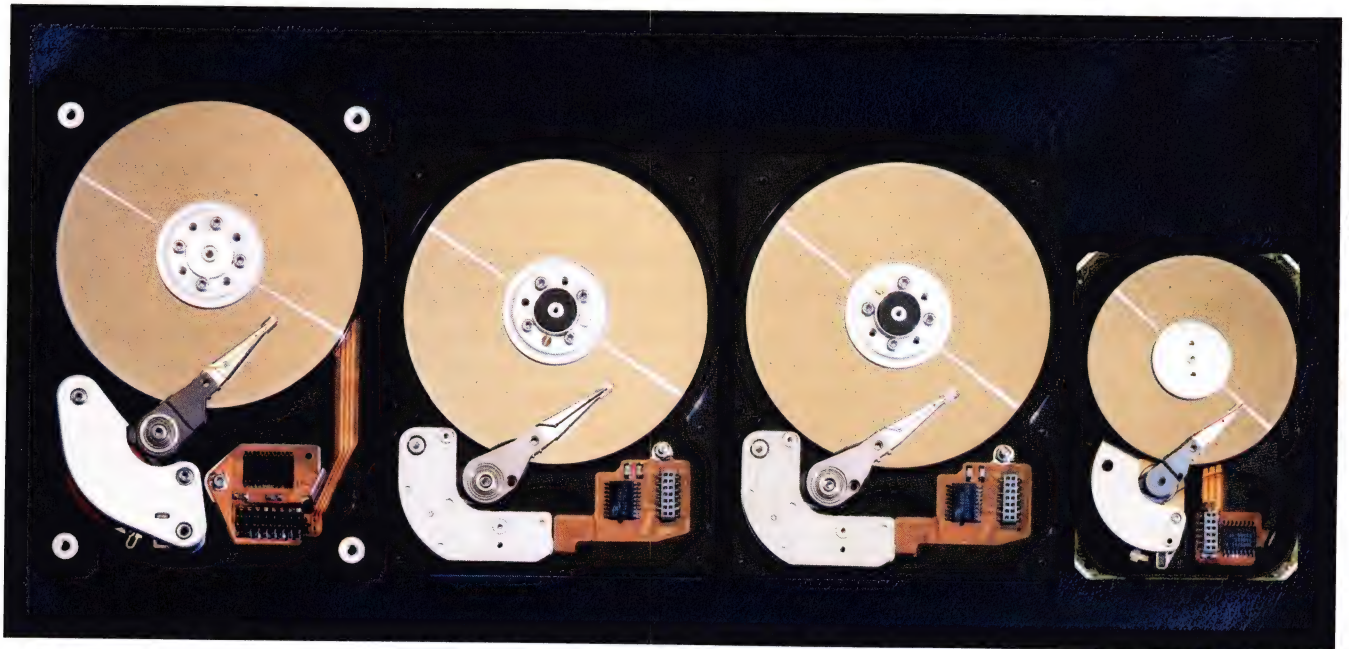WE'VE DECIDED TO CHANGE THE RULES. AGAIN.



© 1989 Conner Peripherals, Inc.

In just three short years, Conner Peripherals has earned a unique reputation as a company that responds to its customers with speed and innovation. With products that don't just follow the standards, but set them.

It began with a request for smaller, more capable storage for portable and desktop PCs. Conner responded with the first high-performance 3.5-inch Winchester. Then it was the first 1-inch high, low-profile drives, which turned laptops into serious business machines.

Today, Conner is prepared to deliver its third wave of innovative disk drives to its customers. Drives that, once again, change the rules.

Kato Series. Conner presents the first drive of the third wave. Our first pocket-sized disk drive, the 2.5-inch Kato represents a new standard for the emerging note-

book PC market. Providing 20MB of low power storage in an ultra-small, ultra-light, completely portable package.

Stubby Series. These entirely new 20 and 40MB *quarter-height* drives let designers pack their new laptop and notebook designs with desktop performance inside a reduced space. All, while operating at a cool 1.5 watts.

Hopi Series. In its 120MB configuration, Hopi becomes the industry's highest capacity 1-inch height drive. And the new standard for upgrading the storage capacity of today's premium laptop designs.

Lighter. Faster. Cooler. Thinner. Shorter. Conner has helped its customers to change the rules. Again. The next generation has begun. Call Conner and find out what we have in store for you.

CONNER
THE THIRD WAVE

World Headquarters: 3081 Zanker Road, San Jose, CA 95134, Telephone: (408) 433-3340 FAX: (408) 433-3303. Sales Offices: Boston: (508) 660-1088 Dallas: (214) 680-2913
Los Angeles: (714) 455-2777 San Jose: (408) 433-3340 Singapore: (65) 2845366 Taipei: (886) 2775-4352 Tokyo: (81) 3-597-8321 European Headquarters: (49) 89-811-2097

VP/Publisher

Peter D Coley

VP/Editor/Editorial Director

Jonathan Titus

Managing Editor

Joan Morrow

Assistant Managing Editor

Susan L Rastellini

Special Projects

Gary Legg

Home Office Editorial Staff

275 Washington St, Newton, MA 02158

(617) 964-3030

Tom Ormond, *Senior Editor*

Charles Small, *Senior Editor*

Jay Fraser, *Associate Editor*

John A Gallant, *Associate Editor*

Michael C Markowitz, *Associate Editor*

Dave Pryce, *Associate Editor*

James P Scanlan, *Associate Editor*

Julie Anne Schofield, *Associate Editor*

Dan Strassberg, *Associate Editor*

Anne Watson Swager, *Associate Editor*

Chris Terry, *Associate Editor*

Kathleen M Vejvoda, *Associate Editor*

Helen McElwee, *Senior Copy Editor*

Susan Bureau, *Copy Editor*

Christine McElvenny, *Senior Production Editor*

Gabriella A Fodor, *Production Editor*

Brian J Tobey, *Production Editor*

Editorial Field Offices

Steven H Leibson, *Senior Regional Editor*
Boulder, CO: (303) 494-2233

Margery S Conner, *Regional Editor*
Atascadero, CA: (805) 461-9549

Doug Conner, *Regional Editor*
Atascadero, CA: (805) 461-9669

J D Mosley, *Regional Editor*
Arlington, TX: (817) 465-4961

Richard A Quinnell, *Regional Editor*
Aptos, CA: (408) 685-8028

Maury Wright, *Regional Editor*
San Diego, CA: (619) 748-6785

Brian Kerridge, *European Editor*
011-44-603-630782

(St. Francis House, Queens Rd,
Norwich, NR1 3PN, UK)

Contributing Editors

Robert Pease, Don Powers,
Bill Travis

Editorial Coordinator

Kathy Leonard

Editorial Services

Helen Benedict, Nicky Woodlock

Art Staff

Ken Racicot, *Senior Art Director*

Chinsoo Chung, *Associate Art Director*

Cathy Madigan, *Staff Artist*

Martha Crowell, *Staff Artist*

Production/Manufacturing Staff

Andrew A Jantz, *Production Supervisor*

Michele R Weinberg, *Production Manager*

Deborah Hodin, *Production Assistant*

Lisa K. Mariano, *Production Assistant*

Diane Malone, *Composition*

Director of Art Department

Joan Kelly

Norman Graf, *Associate*

VP/Production/Manufacturing

Wayne Hulitzky

Director of Production/Manufacturing

John R Sanders

Business Director

Deborah Virtue

Marketing Communications

Anne Foley, *Promotion Manager*

Sara Morris, *Marketing Services Administrator*

Gordon Keegan, *Promotion Specialist*

EDITORIAL

47

Innovation, in addition to developing new things, involves developing your imagination.

NEW PRODUCTS

Computers & Peripherals	187
Integrated Circuits	193
Components & Power Supplies	201
CAE & Software Development Tools	207
Test & Measurement Instruments	211

PROFESSIONAL ISSUES

227

The new headhunters. —*Jay Fraser, Associate Editor*

LOOKING AHEAD


237

Engineering in the 1990s: EDN's editors predict how your job will change in the coming decade.—*Jay Fraser, Associate Editor*

DEPARTMENTS

News Breaks	21
Signals & Noise	32
Calendar	38
Literature	214
Business/Corporate Staff	216
Career Opportunities	232
EDN's International Advertisers Index	240





It's an Analog World.

Ultimately, all circuits are analog circuits. That's why you should step into the analog EDA world of Mentor Graphics.

Here you will find advanced design automation that guarantees high quality results. Gets you to market sooner. And still leaves you time to explore creative alternatives.


Start with AccuSim™, a robust analog simulator that consistently converges to a correct result—even on designs containing thousands of transistors.

Then turn to AccuParts™. This library of more than 2,400 discrete and integrated components includes a large selection of European and Pacific Rim parts. In fact, AccuParts is the most complete and accurate analog library available.

With AccuSim and AccuParts, you also enjoy full integration with the far-reaching Mentor Graphics suite of EDA tools. So you have direct links to logic simulation, IC and PCB layout, thermal analysis and more.


AccuSim and AccuParts draw you into a design environment that is analog at its core. So you can depend on the world's EDA leader to keep providing the tools and support you need.

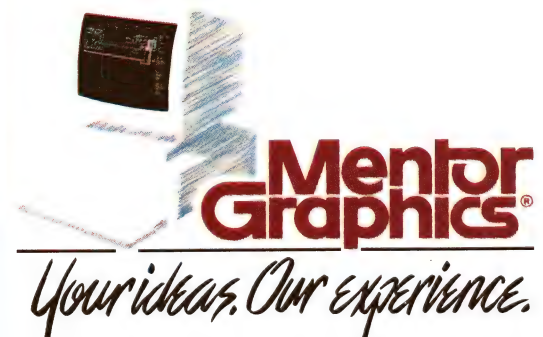For a brochure on the Mentor Graphics analog world, dial this digital, toll-free number: 1-800-547-7390.





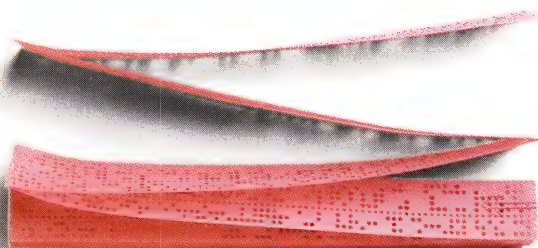The first computer graphics were created by these cards designed for use on the jacquard loom in the late 18th Century.




Each 25 x 21.5 cm section has a whopping 1360 possible digits. Users of paper tape were probably the first to pray for a paperless office.



The Selectron tube had random access to 256 bits of storage with a cycle time of a mere 20ms.

Keep up with with AMD's fast

Special thanks to The Computer Museum, Boston. © 1989 Advanced Micro Devices, Inc. Product or company mentioned herein may be trademarks and/or registered trademarks of their respective companies.
Bruxelles (02-2) 771 91 42 • Geneva (02) 2880025 • Hanover area (0511) 73 60 85 • Hong Kong (5) 8654525 • London area (0483) 740440 • Manchester area (0925) 828008 • Milano (02) 3533241 • München (089) 41 14-0 • Osaka (06) 243-3250 • Paris (1) 49 75 10 10 • Seoul (02) 784-7598 • Singapore (65) 348 1188 • Stockholm (08) 733 03 50 • Stuttgart (0711) 62 33 77 • Taiwan (02) 7213393 • Tokyo (03) 345-8241 • Latin America, Fort Lauderdale, Florida/U.S.A. Tel: (305) 484-8600 Tlx: (510) 955-4261 amd ftl

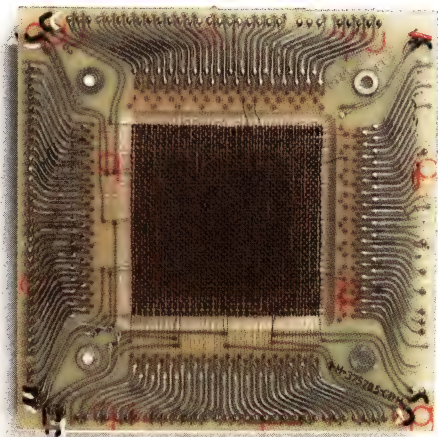

IBM® used 64 of these core memory planes in the 1958 SAGE.



This disk is one of six from a 1956 IBM 1316 disk pack which stored 2 million bits and accessed data at an astonishing 250ms.



AMD's 100ns 2Mb CMOS EPROM is 200,000 times faster and stores the same amount of data as over 8,000 Selectron tubes in under one centiliter.

the future CMOS EPROMs.

Now that you have your hands on that bat out of Hell microprocessor, don't let old memories turn your design into a nightmare.

All our CMOS EPROMs are the fastest in their class. And we have the widest range of densities. From our 55ns 64K device to our 100ns 2Mb device. In a configuration that matches any

system. Like the one you're designing.



And they're all in power-saving CMOS.

No one makes and sells more CMOS EPROMs than AMD. They're ready, in volume, at prices that won't put bugs in your budget.

Just contact us to find out how AMD can make wait states a mere memory for you.

Advanced Micro Devices

For more information write "CMOS EPROMS" on your letterhead and mail to: (In Europe) AMD Mail Operations, P.O. Box 4, Westbury-on-Trym, Bristol BS9 3DS United Kingdom (In Asia) Advanced Micro Devices Far East Ltd., Rm. 1201-2 Harcourt House, 39 Gloucester Road, Hong Kong, Attn: Andrew Ng (In Japan) Advanced Micro Devices Japan Ltd., Shinjuku Kokusai Bldg., 6-6-2 Nishi-Shinjuku, Shinjuku-ku, Tokyo 160, Japan.

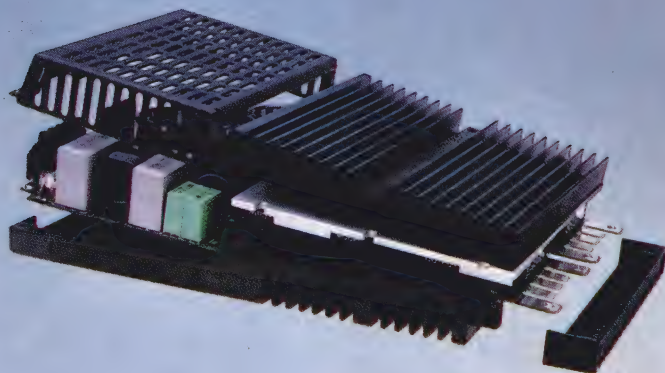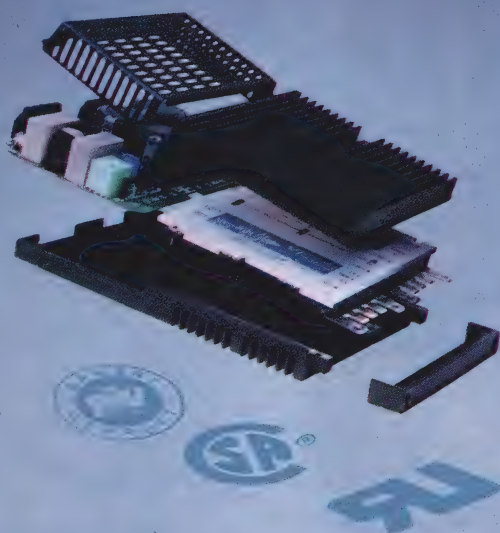

Celebrating The New Profile

Introducing the FlatPAC™ ... Vicor's Family of User Definable, Multiple Output, Switching Power Supplies

Until now, your power system decision meant choosing between costly and unpredictable custom development, or bulky and inflexible catalog supplies...or you had to design and manufacture it yourself. Taking the next step in the power-component revolution, Vicor introduces FlatPAC, the user-definable, "off-the-shelf" alternative to customs that's economical from single units to OEM quantities...and which fits in a fraction of the space required by conventional off-line supplies!

The Off-The-Shelf Alternative

FlatPAC's unique modular design allows Vicor to provide next day delivery on over 10,000 different FlatPAC configurations. You define your power requirements... Vicor does the rest — while eliminating the non-recurring costs, unpredictable lead times, risk, inflexibility, and reliability uncer-

tainties associated with conventional solutions. No other power product offers FlatPAC's combination of power density, economy, and "off-the-shelf" flexibility!

Power Cells


Sharing a distinctive, space saving flat package profile (1.37" high x 8.6" long), FlatPACs come in widths of 2.5", 4.9", and 7.4", and supply up to 200, 400, and 600 Watts of total output power...an unprecedented 7 Watts per cubic inch in an off-line switching power supply!

The three different packages provide one, two, or three user definable "Power Cells". Each Power Cell may be specified to be an independent, isolated output with a power rating of 50, 75, 100, 150, or 200 Watts, or cells may be combined to form higher power outputs...up to 600 Watts from a single output. Standard output voltages are 5, 12, 15, 24, and 48 Volts — and because all

FlatPAC outputs are field trimmable down to zero and up to 110% of nominal, a standard output can likely



FLATPAC

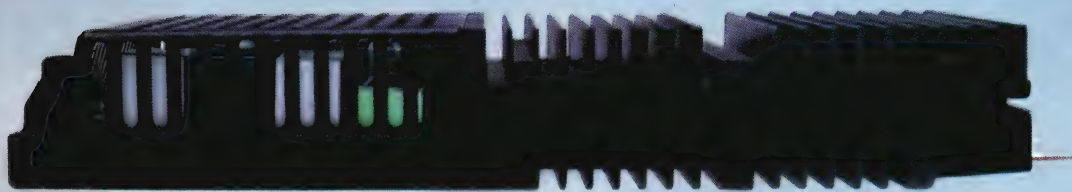

In Off-Line Switchers.

take care of even your most unusual voltage requirements. For special requirements, outputs as low as 2 Volts, and as high as 95 Volts can be provided.

And you don't give up features to get FlatPAC's advantages: besides being trimmable, all FlatPAC outputs have remote sensing and overvoltage and overcurrent protection. Individual FlatPAC outputs are totally isolated: there are no cross regulation issues; any output can be positive or negative; and output returns can float up to 500V, rms, apart. FlatPAC's run on either 110 or 220 Volt lines, meet "Class A" interference specs, have built in fusing, and conform to UL, CSA, and TUV safety agency requirements. Two and three cell units also provide two isolated, sequenced, logic outputs to indicate pending loss-of-line and pending loss-of-output for system housekeeping during power cycling or brownouts.

The key to FlatPAC's flexibility and power density is Vicor's VI-200 family of high density, high efficiency, UL, CSA, and TUV recognized, component level DC-DC converters. When you specify a FlatPAC, you benefit from the field reliability and predictability that's been established in an installed base approaching half a million units.

Join The Celebration Now

Call Vicor now to discuss your special needs...you'll be celebrating when you find how quickly Vicor can ship you the smallest, most efficient, most cost effective solution to your power system requirements...at prices as low as 85¢/Watt in OEM quantities.

To Receive A Complete Catalog, Including Information On Vicor Products, Applications And Accessories, Call Vicor Today At (508) 470-2900, 23 Frontage Road, Andover, MA 01810.



Component Solutions For Your Power System



Motorola ECL^{IN}PS is taking off

ECL with the shortest gate delays ever:
100 picoseconds.

ECLinPS is the low-fare, hypersonic ECL that shatters the price/performance barrier. Now fully qualified, ECLinPS is typically over 300% faster than previous ECL logic—at the same power level or less.

How fast? ECLinPS sets new performance standards with internal gate delays of just 100 picoseconds, and pin-to-pin delays of 330 picoseconds. Shorter gate delays are nearly impossible to measure.

And just as importantly, ECLinPS flies at 800MHz toggle rates to reach the boundaries of high frequency performance.



GaAs speed at a fraction of the cost

ECLinPS has the best performance cost ratio in the industry. Better than GaAs. Better than specialized ECL. And it's available now from the world's leader in ECL.

Making ECLinPS a much more logical logic for the long haul.

Speed without power penalties

For an equivalent function, ECLinPS is typically 300% faster than 100K ECL. Yet ECLinPS operates on about half of the supply current, at an average dissipation of just 0.5 W. So you can design for maximum speed but remain within practical air cooling design boundaries.

Choose your function and features

The ECLinPS logic family has expanded, now including some 30 circuits, with more under development. Applications? Supercomputers, minisupers, high-end workstations, advanced instrumentation, high performance ATE and digital communications. Anywhere speed and price make a difference.

Selected ECL^{IN}PS Functions

#	Function	min/max
E016	8-bit Synchronous Counter	700MHz
E101	Quad 4-Input OR/NOR Gate	500ps
E111	1:9 Differential Clock Driver	100ps skew*
E112	Quad Driver	700ps
E116	5-bit Diff. Line Rcvr.	500ps
E131	4-bit Flip-flop	800 MHz
E141	8-bit Shift Register	700 MHz
E241	8-bit Scannable Register	700 MHz
E151	6-bit D Register	800 MHz
E156	3-bit 4:1 Mux-Latch	950 ps
E163	2-bit 8:1 Mux	850 ps
E451	6-bit Diff. Register	800 MHz

*within-device skew



Packaged for performance

Available in 100K or 10KH compatible versions, ECLinPS is packaged for affordable performance. Its standard 28-lead surface mount PLCC helps keep noise to a minimum and eases design through multiple VCCO's.


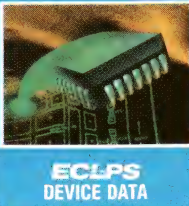
Your designs take off with ECL^{IN}PS

Design ECLinPS speed into your application. Product and data books are available now—just the ticket for a flying start.

For ECLinPS Logic information call or write to your Motorola Sales Office.



MOTOROLA

Write To: Motorola Ltd., European Literature Centre, 88 Tanners Drive
Blakelands, Milton Keynes MK14-5BP, United Kingdom

Please send me more information on Motorola ECLiPS.

411EDN011890

Name _____

Title _____



Company _____

Address _____

City _____

Country _____

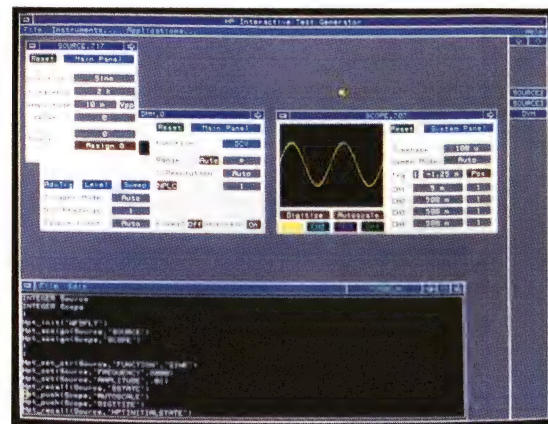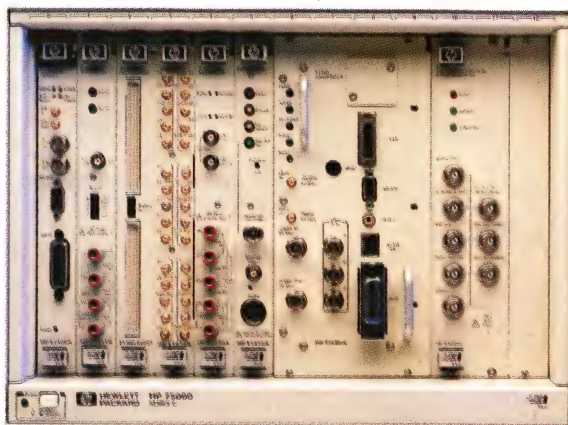“If all VXI systems are equal, how can one add up to faster test development?”



It's simple. By combining advanced VXI hardware, a powerful system language, and a common human interface, HP really puts your test development in motion.

Start with the hardware. HP 75000* Series B and C mainframes and modules give you a broad selection of price

and performance options. So you can tune a system to your needs in minimal time.

Then, the open Test & Measurement System Language (TMSL) lets you speed through test development as never before. It's a standardized

instrument language that insures compatibility with all HP 75000 modules, as well as other common system instruments. And it gives you a migration path for the future.

When you add the mouse-driven HP Interactive Test Generator software (HP ITG) to the equation, you really take off. Virtual front panels


+



=



©1989 Hewlett-Packard Co. TMLID936/F

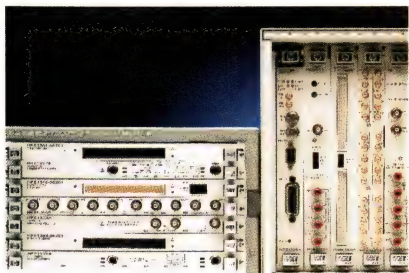

*The HP 75000 VXI is part of HP's Measurement System Architecture.

save time. Select a function by clicking the mouse and HP ITG sends the right command to the right module automatically. With pop-up windows and pull-down menus, the interface is simple and speedy.

So don't waste time. Call one of the countries listed below or our International Service

Line in The Netherlands at **(31) 20 809 809**. You may also write to Hewlett-Packard, Henk Van Lammeren, P.O. Box 999, 1180 AZ Amstelveen, The Netherlands.


There is a better way.



**HEWLETT
PACKARD**

• **Singapore** (65) 272 6677 • **Taiwan** (886-2) 717 9609 • **Hong Kong** (852-5) 848 7070 • **Korea** (82-2) 784 2666

No two alike.

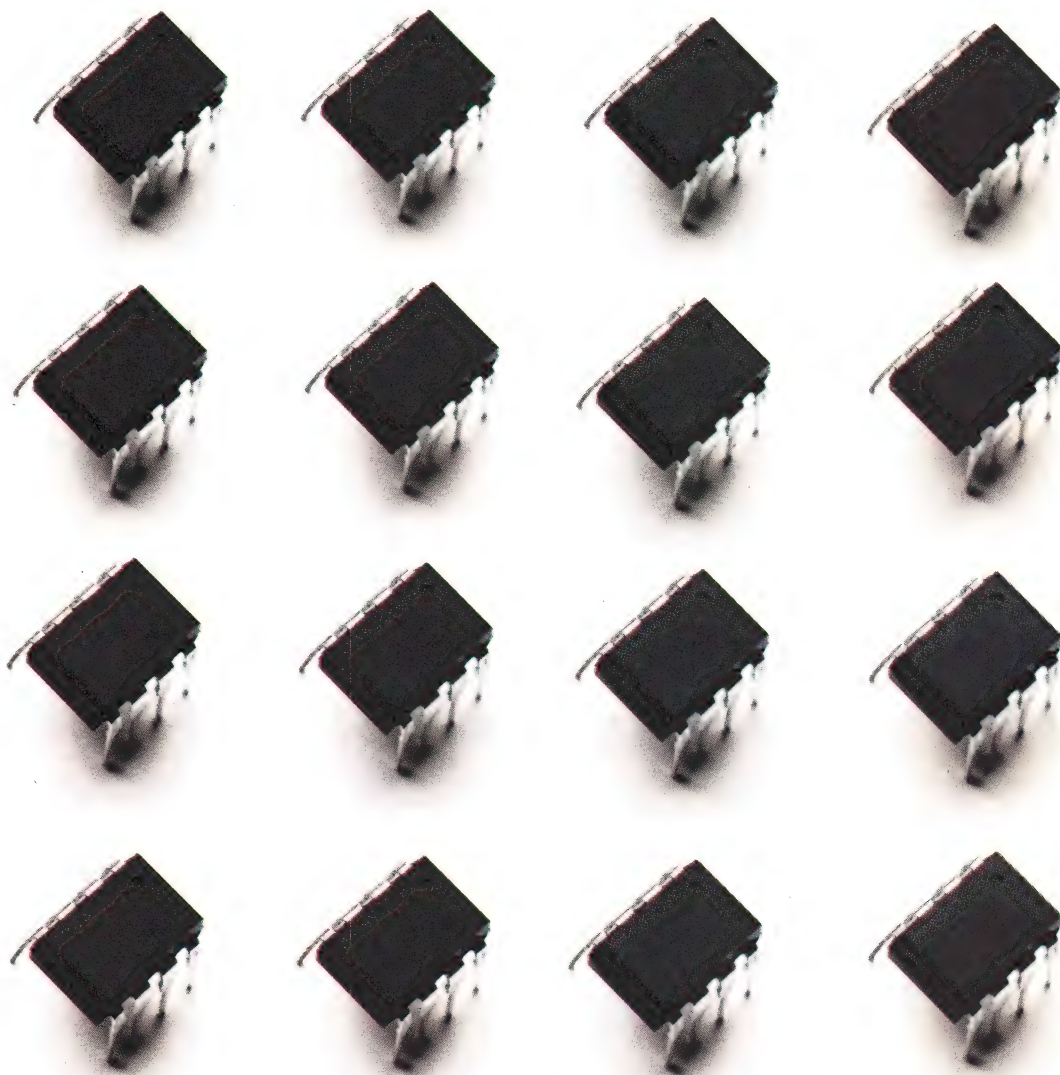

While HP's high-performance plastic optocouplers may all look alike, the similarity is only skin deep.

Because with five complete lines of plastic devices, there's clearly more to our optocouplers than meets the eye.

Like a wide variety of single- and dual-channel devices that provide you with an equally wide range of performance options.

Such as an innovative dual-channel design that combines a photon-emitting diode with a high-speed photon detector to produce data rates up to 40 MBd.

You also get high-output gain from low-input current or high-speed logic gates. Wide V_{cc} from 4.5 to 20 volts. And a unique AC/DC interface.

Plus they're compatible with TTL, STTL, LSTTL and, in many cases, CMOS logic families.

All of which makes HP's optocouplers the ideal solution for problems caused by ground loops and induced common mode noise.

Best of all, they're from HP. So you're assured of our commitment to excellence in service, support and reliability.

Which, come to think of it, is the one thing that makes all our optocouplers exactly alike.

To find out more about HP's optocouplers, call **1-800-752-0900, ext. 644G**. And see why looks aren't everything.

There is a better way.



**HEWLETT
PACKARD**

CG08907

NEWS BREAKS

EDITED BY JULIE ANNE SCHOFIELD

SINGLE-BOARD COMPUTER COMBINES 16-BIT μ P AND FORTH

Take a Motorola 68000 μ P and combine it with 64k bytes of battery-backed RAM; a battery-backed real-time clock; parallel ports for a printer, a keypad, and an LCD; two serial ports (one a multidrop RS-485); and an extended 32-bit version of the Forth-83 development environment burned into ROM, and you have the \$295 SBC68K single-board computer from Vesta Technology Inc (Wheatridge, CO, (303) 422-8088). The board measures 8×4 in. and requires 650 mA from a 5V power supply. You can plug as much as 128k bytes of RAM and 256k bytes of ROM into sockets on the board, which also incorporates an EPROM programmer.—Steven H Leibson

ETHERNET INTERFACE CONTROLLER FREES CPU POWER

The DP83932 systems-oriented network-interface controller (SONIC) from National Semiconductor (Santa Clara, CA, (408) 721-5000) frees your CPU from the drudgery of handling Ethernet messages. The DMA device includes an AUI-compatible analog-interface circuit and transmit and receive FIFO buffers. It also has a content-addressable memory that identifies, without CPU intervention, which incoming messages your system should receive. The controller can place incoming messages into system memory without CPU intervention and can transmit a string of messages from system memory with a single command. Multiple devices can share the same memory space, thus passing messages from one network to another without the CPU handling the message data. The device operates with system clocks as fast as 20 MHz and costs \$55 (100).—Richard A Quinnell

MEMORY SYSTEM PROVIDES FORMAT CHOICES

Mass-storage systems from Hewlett-Packard (Palo Alto, CA, (800) 752-0900) can integrate a 5¼-in. 332M-byte or 664M-byte hard-disk drive with two additional drives of your choice. You can choose among DAT (digital-audiotape) drives that can back up 1.3G bytes of data in two hours; CD-ROM drives with access to 600M-byte data disks; rewritable-optical-disk drives that conform to the ISO and ANSI definitions for the continuous-composite format and whose cartridges can store 650M bytes of data; or additional hard-disk drives. All these drives communicate via a SCSI, are supported on the HP 9000 Series 300 workstations, and fit into two full-height 5¼-in. slots. The costs of the systems range from \$4975 for a system with the 332M-byte hard-disk drive and two empty slots to \$21,475 for a system with three 664M-byte hard-disk drives.—Michael C Markowitz

PRINTER OFFERS BRAILLE FONTS

A modified version of Howtek's (Hudson, NH, (603) 882-5200) Pixelmaster color ink-jet printer prints raised graphics and braille fonts to provide tactile communications for the visually impaired. Developed with the National Federation of the Blind, the printer uses a thermal ink jet to produce a raised dot on standard office paper. The ink is a plastic that the printer melts into a liquid; it solidifies when it comes in contact with the paper. A software program, which comes with the unit, translates the alphanumeric keys on the keyboard to braille fonts. The printer, which costs about \$8000, also prints visual color graphics and text.—John Gallant

NEWS BREAKS

OP AMPS TAKE AIM AT VIDEO DESIGNS

Elantec (Milpitas, CA, (408) 945-1323) has announced several high-bandwidth op amps for video applications. The EL2423 quad 500-MHz op amp slews at 350V/ μ sec and draws 4 mA/amplifier. The op amp is stable for gains greater than 10. In a 14-pin plastic DIP, the part costs \$14.24 (100). The EL2232 is a dual version of the EL2020; the device integrates two current-feedback amps with unity-gain bandwidths of 60 MHz for the same power as the EL2020. The amplifier operates from ± 15 V supplies, and its output swings ± 12.5 V into a 500 Ω load. Other specifications include an offset voltage of 3 mV; a slew rate of 600V/ μ sec; and a 125-nsec 0.02% settling time to a 10V step. Prices start at \$7.50 (100) for an 8-pin plastic DIP. Both op-amp packages include short-circuit protection.—Anne Watson Swager

CACHE RAMs OPERATE AS FAST AS 50 MHz

A family of cache RAMs is available from Logic Devices (Sunnyvale, CA, (408) 720-8630). The family comprises 16 devices: three cache-tag memories, six 16k-bit static RAMs (SRAMs), and seven 64k-bit SRAMs. The cache-tag memories have 4k \times 4-bit (L7C180/181) or 8k \times 8-bit (L7C174) organizations. They signal a cache hit within 10 nsec. You can use these devices in parallel to accommodate wider addresses and wire-OR their match-output lines.

The SRAMs are available in 1-, 4-, and 8-bit-wide organizations. The 16k \times 1- (L7C167), 4k \times 4- (L7C168, L7C170/1/2), and 2k \times 8-bit (L6116) memories have access times of 10 nsec. These memories, coupled with a 10-nsec tag RAM, let your cache system operate as fast as 50 MHz. The 64k \times 1- (L7C187) and 16k \times 4-bit (L7C161/2, L7C164/5/6) memories have access times of 12 nsec; the 8k \times 8-bit (L7C185) memory has an access time of 15 nsec. These devices are available in a variety of package styles, including DIPs and surface-mount packages. Cache-tag RAMs cost from \$44.50 (100), and SRAMs cost from \$14.65 (100).—Richard A Quinnell

MEETING TO COVER SBCs AND REAL-TIME OPERATING SYSTEMS

DSP Associates (Newton, MA, (617) 964-3817) will hold a conference on single-board computers for a variety of bus architectures and real-time operating systems. The East Coast meeting will be March 5 to 8 at the Massachusetts Institute of Technology in Cambridge, MA; the West Coast meeting will be May 14 to 17 at Rickey's Hyatt Hotel in Palo Alto, CA. Participating companies will include Motorola's Microcomputer Div, Intel Corp, Force Computers, SBE Inc, and Wind River Systems. For more information, phone Alexander Chelmsky at (617) 964-3817. You can reach him by fax at 617-969-6689.—Julie Anne Schofield

DESKTOP-ENGINEERING CENTER OFFERS CLASSES

You can use many general-purpose PC-based software packages, such as spreadsheets and database managers, for scientific and engineering applications if you know the right tricks. Binary Engineering (Waltham, MA, (617) 290-5900) recently opened its Center for Desktop Engineering Training to help you learn some of those tricks. The center's next class, which will be taught February 6 to 7, is "Engineering Design and Analysis Using Lotus 1-2-3." Registration for the class costs \$695. The company will bring its classes to your site for approximately \$3500 plus travel expenses.—Steven H Leibson



TMC2310 Runs 1024-Point FFT in 0.5ms

Here's the FFT runner you need to win the race. It's the TMC2310 — the first single-chip FFT controller to be this fast and simple to use.

Imagine all of these capabilities on one chip: Arithmetic functions, FFT coefficients ("twiddle factors"), even built-in address generation. That's why the TMC2310 runs forward or inverse transformations, or multiple equal-length FFTs totalling 1024 points, in just 0.5ms. Or a complex radix-2 butterfly in only 100ns. The TMC2310 executes other functions just as quickly, including FIR filtering and vector operations. Even data windowing is included without impact on either performance or price.

Better still, no development system is required. The TMC2310 jumps into action with just two 13-bit control words. It's so simple. No complex, bit-slice, microcode-intensive building

blocks. No chip sets to contend with either.

You can qualify for a FREE sample. Just tell us about your application and we'll send you a TMC2310 to run in your system. You can build a complete spectrum analyzer with the TMC2310, our new 12-bit ADC (THC1200 Series), our TDC1012 DAC and external data and window memories. Be a winner. Try the TMC2310. Available now in 88-pin plastic pin grid array (PPGA) from TRW LSI Products or your nearest Hall-Mark or Hamilton/Avnet location.

1988-89
Emmy
Award
Winner



**TRW LSI Products — Bringing the worlds
of Data Acquisition and DSP together.**

TRW LSI Products Inc.
P.O. Box 2472, La Jolla, CA 92038
619.457.1000

In Europe, phone:
TRW LSI Products Inc.
Munich, 089.7103.115;
Guildford (U.K.), 0483.302364

In the Orient, phone:
Hong Kong, Tektron, 3.880629;
Tokyo, Dia Semicon, 3.439.2700,
Kawasaki, Teksel, 44.812.7430;
Taipei, Sea Union, 2.751.2062;
Seoul, M.S., 2.553.0901;
Singapore, Seamax, 65.445.1828;
Australia, Email, 613.544.8244

TRW

TRW LSI Products Inc.

©TRW Inc., 1989 — 712C01489

NEWS BREAKS

CONTRACTOR DEVELOPING REAL-TIME, DISTRIBUTED OS

Concurrent Computer Corp (Tinton Falls, NJ, (201) 758-7000) is under contract to the Air Force to develop a real-time, distributed operating system. The Alpha operating system will become part of the public domain upon completion. This extremely ambitious project, if completed successfully, will link virtually any computer system running any one of a number of common operating systems. Written in C++, Alpha will use the FDDI fiber-optic link as its backplane as well as support other common networks.

Concurrent seeks to form a consortium to promulgate Alpha. Research and Development Director E Douglas Jensen and Marketing Director William Blundon will answer any questions and provide any level of technical information in response to serious inquiries. Jensen forewarns that many basic real-time-system practices do not scale up to a distributed real-time system.—Charles H Small

SOFTWARE EXTENDS PC BUS ANALYZER ABILITIES


Release 2.60 of the AT BusTrak bus-analyzer software from Applied Physics Inc (West Lafayette, IN, (317) 497-1718) enables the company's IBM PC/XT/AT bus analyzer to disassemble captured trace files for both 8- and 16-bit μ Ps and display histograms showing bus utilization. Further, a validation filter eliminates invalid bus transfers from waveform displays. Present owners of bus analyzers that are still covered by the company's warranty can obtain the new software for free. The bus analyzer with the new software costs \$1995.—Steven H Leibson

FLASH A/D CONVERTER CAPTURES PULSE PEAKS

An 8-bit variant of the standard full-parallel flash converter captures the peak amplitude of square pulses without an additional peak-hold circuit. TRW LSI Products' (La Jolla, CA, (619) 457-1000) TDC1035 peak digitizer captures the maximum amplitude of one or more input pulses occurring between asynchronous reset pulses. For pulse widths of 30 nsec and greater, the converter digitizes peaks to its full dc linearity, which is $\frac{1}{2}$ LSB. The IC can also detect pulses as narrow as 12 nsec, although at this pulse width the converter underestimates the pulse's amplitude by about 15%. The digitization accuracy of any pulse's peak value depends on the shape of the pulse; the manufacturer characterized this ADC using square pulses with controlled rise and fall times of 8 nsec. You can estimate the device's performance with other pulse shapes by using an energy-above-threshold model. The 24-pin ceramic IC consumes 1W and includes an output register with 3-state outputs. All digital input and outputs are TTL compatible. Commercial and military versions of the part cost \$19 and \$95 (1000), respectively.—Anne Watson Swager

BUSCON SESSION TO HIGHLIGHT BUS ANALYSIS

A new session at Buscon/90-West—to be held on February 14 to 16 at the Long Beach Convention Center, CA—will explore some of the issues surrounding the use of bus analyzers. Speakers at session 503, "Applying Bus Analysis Tools in a Real-Time Development Environment," will address bus-analysis problems on IBM PC bus, NuBus, VMEbus, and Multibus systems. For more information about the convention, phone (203) 852-0500, ext 247.—Steven H Leibson

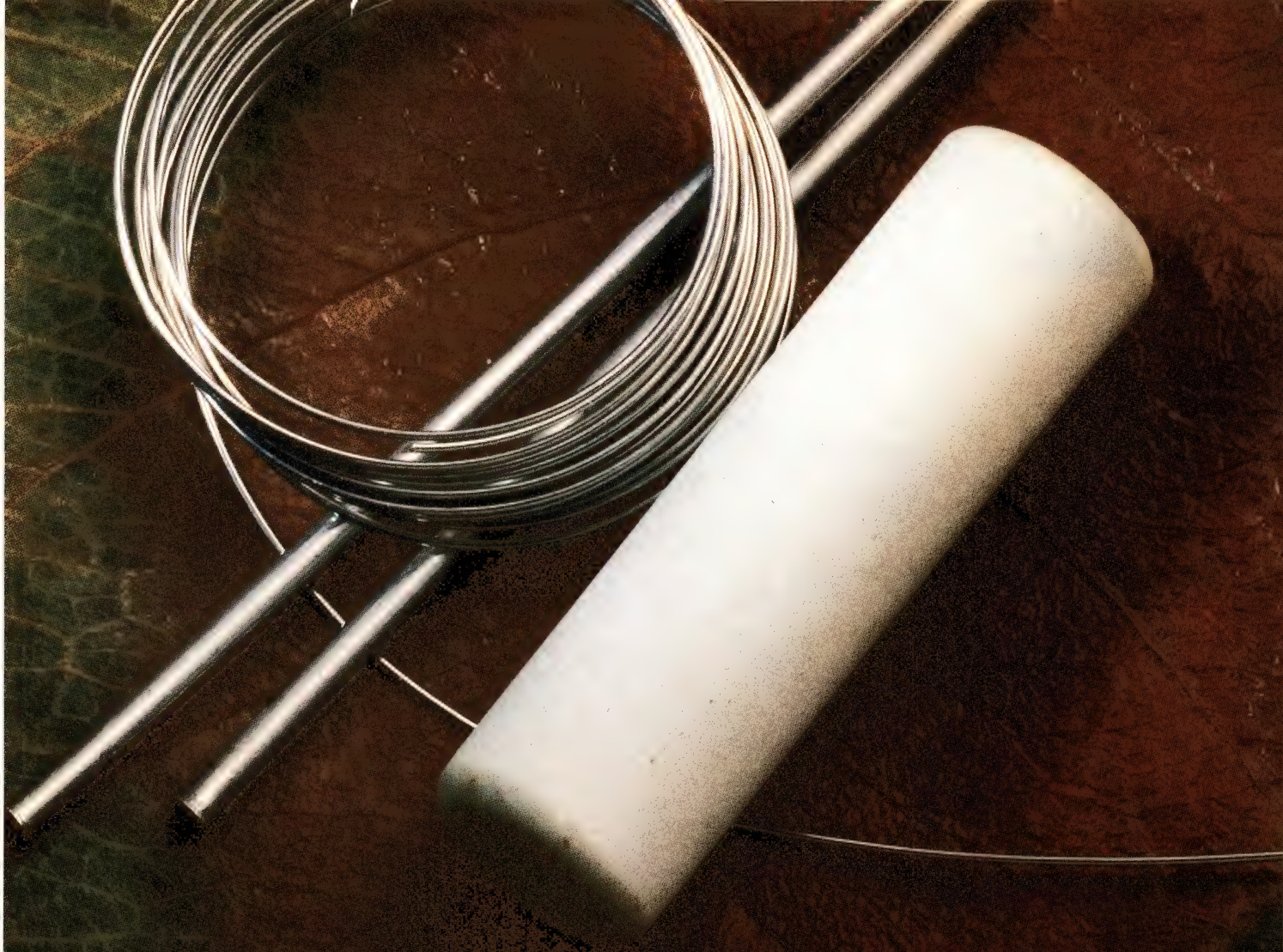

2 grams of ceramic and 18
inches of wire can't make you
more competitive.

There's only one real reason to specify Dale® wirewound resistors: We'll work harder turning something common into something uncommonly valuable. Up front, that means saving you selection time by producing every standard shape and size in the book. Plus, we give you immediate access to



Dale Makes Your Basics Better

Dale® Can.



design assistance and a wide range of proven special products.

It means factory and distributor stocking programs that can be quickly fine-tuned to your Just-In-Time delivery programs.

CIRCLE NO. 54


And, it means making reliability the least of your worries with well-established Statistical Process Control and Quality Assurance systems to give you ship-to-stock capability.

Dale wirewound resistors. They're not commodities — they're the power you need to help make your products more competitive. Contact your Dale representative or distributor, or phone: 402-563-6283. Dale Electronics, Inc., 1122 23rd Street, Columbus, NE 68601-3647.

DALE ELECTRONICS, INC.
... a VISHAY Company

RF TRANS

Over 50 off-the-shelf models...

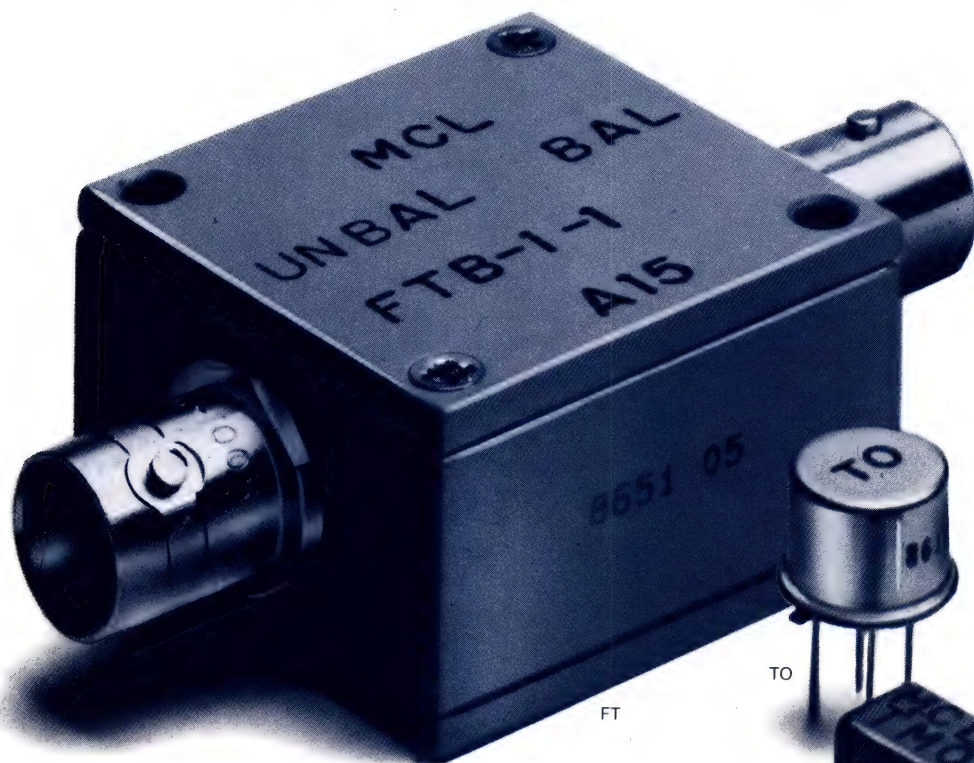


Having difficulty locating RF or pulse transformers with low droop, fast risetime or a particular impedance ratio over a specific frequency range? ... Mini-Circuits offers a solution.

Choose impedance ratios from 1:1 to 36:1, connector or pin versions (plastic or metal case built to meet MIL-T-21038 and MIL-T-55831 requirements*). Ultra-wideband response achieves low droop and fast risetime for pulse applications. Ratings up to 1000M ohms insulation resistance and up to 1000V dielectric voltage. For wide dynamic range applications involving up to 100 mA DC primary current, use the T-H series. Coaxial connector models are offered with 50 and 75 ohm impedance; BNC standard; request other types. Available for immediate delivery with one-year guarantee.

Call or write for 68-page catalog or see our catalog in EEM, or Microwaves Product Data Directory.

*units are not QPL listed

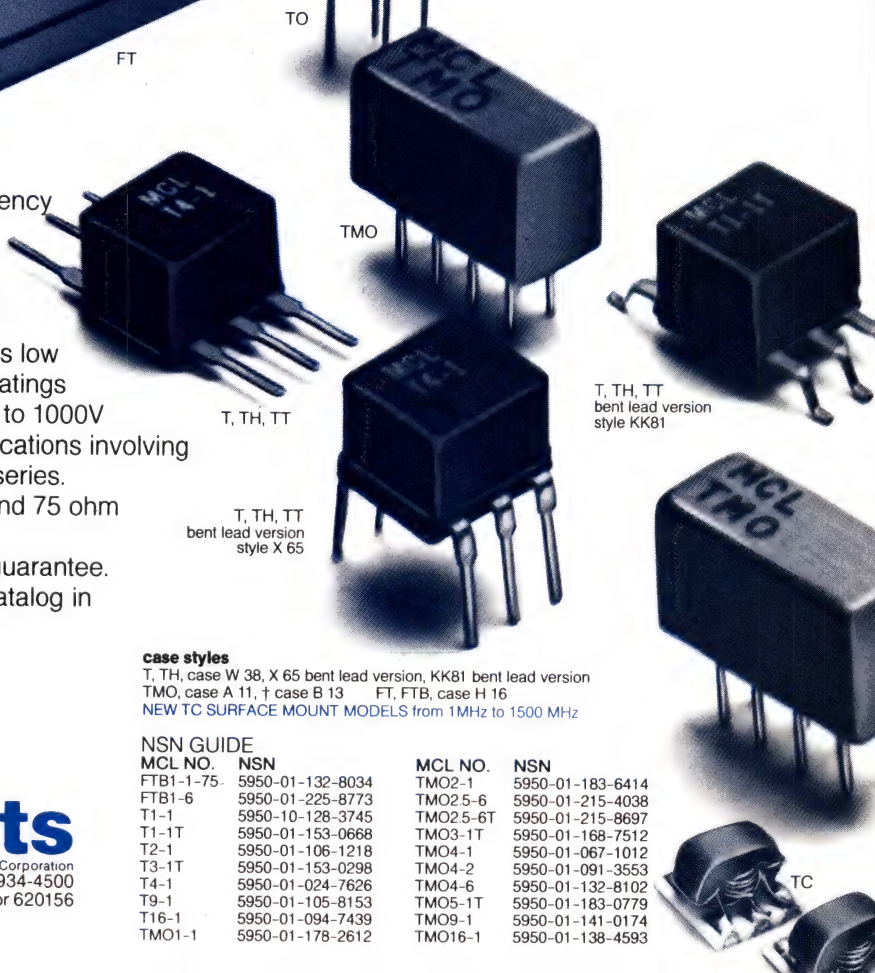

case styles

T, TH, case W 38, X 65 bent lead version, KK81 bent lead version
TMO, case A 11, † case B 13 FT, FTB, case H 16

NEW TC SURFACE MOUNT MODELS from 1MHz to 1500 MHz

NSN GUIDE

MCL NO.	NSN
FTB1-1-75	5950-01-132-8034
FTB1-6	5950-01-225-8773
T1-1	5950-10-128-3745
T1-1T	5950-01-153-0668
T2-1	5950-01-106-1218
T3-1T	5950-01-153-0298
T4-1	5950-01-024-7626
T9-1	5950-01-105-8153
T16-1	5950-01-094-7439
TMO1-1	5950-01-178-2612

MCL NO.	NSN
TMO2-1	5950-01-183-6414
TMO2.5-6	5950-01-215-4038
TMO2.5-6T	5950-01-215-8697
TMO3-1T	5950-01-168-7512
TMO4-1	5950-01-067-1012
TMO4-2	5950-01-091-3553
TMO4-6	5950-01-132-8102
TMO5-1T	5950-01-183-0779
TMO9-1	5950-01-141-0174
TMO16-1	5950-01-138-4593

finding new ways ...
setting higher standards

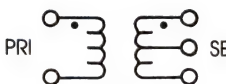
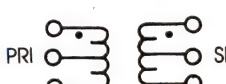

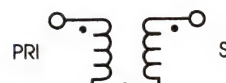
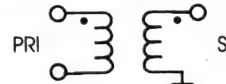
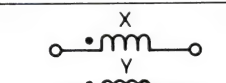
Mini-Circuits

A Division of Scientific Components Corporation

P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500
Fax (718) 332-4661 Domestic and International Telexes: 6852844 or 620156

FORMERS

3KHz-800MHz from \$3²⁵

case style number see opposite page		MODEL NO.	Ω RATIO	FREQUENCY MHz	INSERTION LOSS			PRICE \$
					3dB MHz	2dB MHz	1dB MHz	Qty. (1-9)
A*		T T1-1T	1	05-200	05-200	08-150	2-80	4.45
		T T1-6T	1	003-300	003-300	01-150	02-50	6.95
		T T2-1T	2	07-200	07-200	1-100	5-50	4.95
		T T2.5-6T	2.5	01-100	01-100	02-50	50-20	4.95
		T T3-1T	3	05-250	05-200	1-200	5-70	4.95
		T T4-1	4	2-350	2-350	35-300	2-100	3.25
		T T4-6T	4	02-250	02-250	05-150	01-100	4.45
		T T5-1T	5	3-300	3-300	6-200	5-100	4.95
		T T8-1T	8	03-140	03-140	10-90	1-60	7.95
		T T13-1T	13	3-120	3-120	7-80	5-20	4.95
	TH TMO	T T16-6T	16	03-75	03-75	06-30	1-20	5.65
		T T4-1H	4	10-350	10-350	15-300	25-200	5.95
		T TMO1-1T	1	05-200	05-200	08-150	2-80	7.95
		T TMO2-1T	2	07-200	07-200	1-100	5-50	8.45
		T TMO2.5-6T	2.5	01-100	01-100	02-50	05-20	8.45
		T TMO3-1T	3	05-250	05-250	1-200	5-70	7.95
		T TMO4-1	4	2-350	2-350	35-300	2-100	6.25
		T TMO5-1T	5	3-300	3-300	6-200	5-100	8.45
		T TMO13-1T	13	3-120	3-120	7-80	5-20	8.45
B*		TT TT1-6	1	004-500	004-500	02-200	1-50	6.95
		TT TT1.5-1	1.5	075-500	075-500	2-100	1-50	5.95
		TT TT2.5-6	2.5	01-50	01-50	025-25	05-10	6.45
		TT TT4-1	3	05-200	01-50	2-50	1-30	5.95
		TT TT4-1A	4	01-300	01-300	02-250	03-180	6.95
		TT TT25-1	25	02-30	02-30	05-20	1-10	9.95
		TT TMO25-1	25	02-30	02-30	05-20	1-10	11.95
		TT TMO1-1	1	005-100	005-100	01-75	05-40	11.45
		TT TMO4-1A	4	01-300	01-300	02-250	03-180	13.95
C		T T1-1	1	15-400	15-400	35-200	2-50	3.25
		T T1.18-3	1.18	001-250	001-250	002-200	003-50	5.65
		T T1-6	1	01-150	01-150	02-100	05-50	5.65
		T T1.5-1	1.5	1-300	1-300	2-150	5-80	4.45
		T T1.5-6	1.5	02-100	02-100	05-50	01-25	5.65
		T T2.5-6	2.5	01-100	01-100	02-50	05-20	4.45
		T T4-6	4	02-200	02-200	05-150	1-100	4.45
		T T9-1	9	15-200	15-200	3-150	2-40	3.95
		T T16-1	16	3-120	3-120	7-80	5-20	4.45
		T T36-1	36	03-20	03-20	05-10	1-5	6.95
	TO TH TMO	T TO-75	1	10-500	—	10-500	40-250	6.95
		T T1-1H	1	8-300	8-300	10-200	25-100	5.95
		T T9-1H	9	2-90	2-90	3-75	6-50	6.45
		T T16-H	16	7-85	7-85	10-65	15-40	6.45
		T TMO1-02	1	1-800	1-800	2-500	—	9.45
		T TMO1-1	1	15-400	15-400	35-200	2-50	6.25
		T TMO1.5-1	1.5	1-300	1-300	2-150	5-8	8.45
		T TMO2.5-6	2.5	01-100	01-100	02-50	05-20	7.95
		T TMO4-6	4	02-200	02-200	05-150	1-100	7.95
		T TMO6-1	6	3-200	3-200	5-150	5-50	7.95
D		T T2-1	2	050-600	050-600	1-400	5-200	3.95
		T T3-1	3	5-800	5-800	2-400	—	4.45
		T T4-2	4	2-600	2-600	5-500	2-250	3.95
		T T8-1	8	15-250	15-250	25-200	2-100	3.95
		T T14-1	14	2-150	2-150	5-100	2-50	4.95
	TMO	T TMO2-1	2	050-600	050-600	1-400	5-200	7.95
		T TMO3-1	3	5-800	5-800	2-400	—	8.45
		T TMO4-2	4	2-600	2-600	5-500	2-250	7.95
		T TMO8-1	8	15-250	15-250	25-200	2-100	7.95
		T TMO14-1	14	2-150	2-150	5-100	2-50	8.45
	FT	T FT1.22-1	1.22	005-100	005-100	01-50	05-25	35.95
		T FT1.5-1	1.5	1-400	1-400	5-200	1-100	35.95
E		FTB FTB-1	1	2-500	2-500	5-300	1-100	36.95
		FTB FTB1-6	1	01-125	01-125	05-50	1-25	36.95
		FTB FTB-1-75	1	5-500	5-500	5-300	10-100	36.95
F		T T-622	1	01-200	01-200	05-100	5-80	3.25
		T T626	1	001-10	001-10	02-5	04-2	3.95

■ Denotes 75 ohm models

* FOR A AND B CONFIGURATIONS


Maximum Amplitude Unbalance
0.1 dB over 1 dB frequency range
0.5 dB over entire frequency range

Maximum Phase Unbalance
1.0° over 1 dB frequency range
5.0° over entire frequency range

CIRCLE NO. 55

C72-2 REV. B

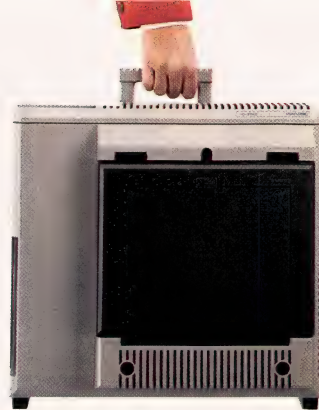HIGH-SPEED HARDWARE ANALYSIS MODULES: THE NEWEST PAYOFF TO YOUR PRISM INVESTMENT.




Visualize a logic analyzer that not only acquires microprocessor state and timing data, but adds emulation capabilities... real-time performance analysis... high-speed timing for hardware analysis... and more—all usable in precise, time-correlated combination. All configurable to your needs.

That's the visible edge of the Prism 3000 Series from Tektronix.

The new dimension of integrated analysis.


MPM/MPX Module	Microprocessor control Real-time performance analysis 200 MHz hardware analysis 8K deep state analysis Multiple Microprocessor support
HSM Module	2 GHz hardware analysis 300 MHz state analysis 1.5 ns glitch capture 12K transitionally-stored memory (up to 120K effective memory)

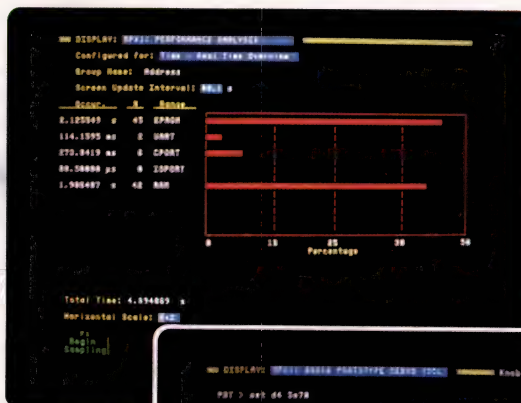Now, just months after introduction, Prism breaks *new* barriers with a module specifically designed for hardware analysis—for detecting glitches, metastability, and the other common problems of state machines, busses, and sequential logic.



Start with up to 96 channels and the exceptional resources of Prism's 8/16/32-bit microprocessor integration modules.

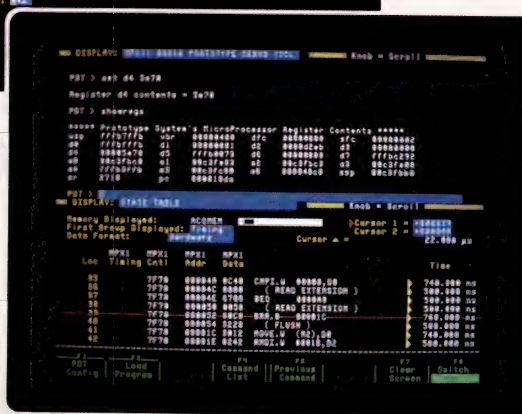You can view 200 MHz timing and 8K of state data per channel,



(Above, left) Real-time performance analysis as displayed on the Prism color monitor. (Left) The Prototype Debug Tool provides easy access to microprocessor control and debug functions, including the ability to set hardware and software breakpoints, and to patch registers and memory.





(Left) Prism microprocessor and hardware analysis modules are user-installable in minutes. These application modules can be configured in any combination, up to a maximum of ten cards per system.

all time-correlated and integrated on the same display. Set up state and timing sections to cross-

trigger, synchronize and arm each other, so you know exactly when and in what time relationship events occur.

Push beyond microprocessor observation into microprocessor control.

With its unprecedented Prototype Debug Tool, Prism lets you easily set breakpoints, patch registers and memory, restart the system—all without an emulator's intrusiveness.



Use real-time performance analysis to get a true, non-statistical view of system performance.


Designers of embedded control systems will especially benefit from histograms of uncompromising accuracy.

Now, with Prism's HSM high-speed hardware analysis module, you can add capabilities like 2 GHz timing and 300 MHz state analysis—and use these tools in tight time-correlation with other Prism modules.

Detect race conditions, setup and hold time violations, and glitches as small as 1.5 ns. Switch to dual threshold or digitizing modes to get a quick look at intermittent problems like ringing or undershoot.

Memory constraints are virtually eliminated: the HSM's 12K of transitionally-stored memory offers the equivalent of as much as 120K of conventional memory!

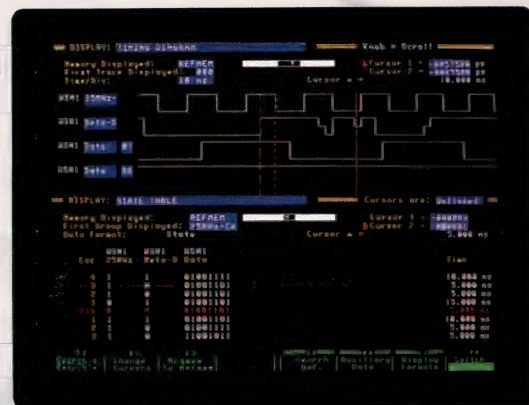(Below) The Prism HSM's dual threshold mode triggers on and displays a metastable condition. Middle thresholds are displayed as "M" in the time-correlated state table. Cursors measure the setup time violation that caused the metastable state.



Choose from a stand-alone Prism, expandable main-frame-and-monitor, even a portable model with fold-up flat panel screen.

Features like autoload, split-screen displays, smooth scrolling and on-line help make Prism refreshingly simple to learn and use.


The clincher? You can step into this new generation of logic analyzers at prices starting at \$8600.

Call 1-800-426-2200 for our free video demo and literature packet. For a hands-on introduction, call your Tek sales engineer soon.

Circle 114 for Literature
Circle 115 for Sales Contact

Tektronix
YOUR VISIBLE EDGE

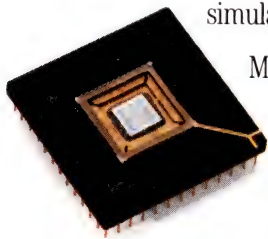If your CAE tools are telling you too little too late, consider this news from Teradyne. Now you can capture and analyze complex ASIC and VLSI board designs with unprecedented accuracy and ease, using our Vanguard™ schematic entry software and LASAR



simulator in Teradyne's

MultiSim™

environment.

Here are CAE

tools that work the

way you like to work.


They'll help you move

quickly between

schematic and simu-

lation, and let you control simulation interactively. You'll get immediate feedback at every step.

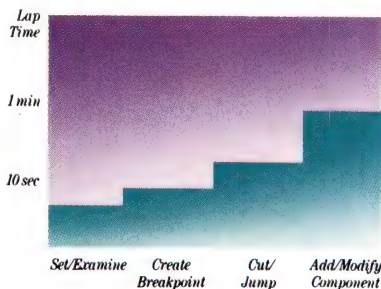Click on nodes you want to monitor and watch signal activity "live" on the schematic or in the logic analyzer window. By setting breakpoints, you can freeze the action when results aren't what you expect. In no time, you'll know where your design is



If you find a problem, fix it and see the results in seconds, because we eliminate compilation for most common design changes.


working and where it's not.

Got a glitch? Need to invert a signal?



Make cuts or jumps on schematic interconnections. Add or delete components.

You'll see the effects of design changes instantly because we shortcut compilation for the modifications you make most frequently. This means you can try out "what-ifs" with record speed, reducing design-loop time from tens of minutes to tens of seconds.

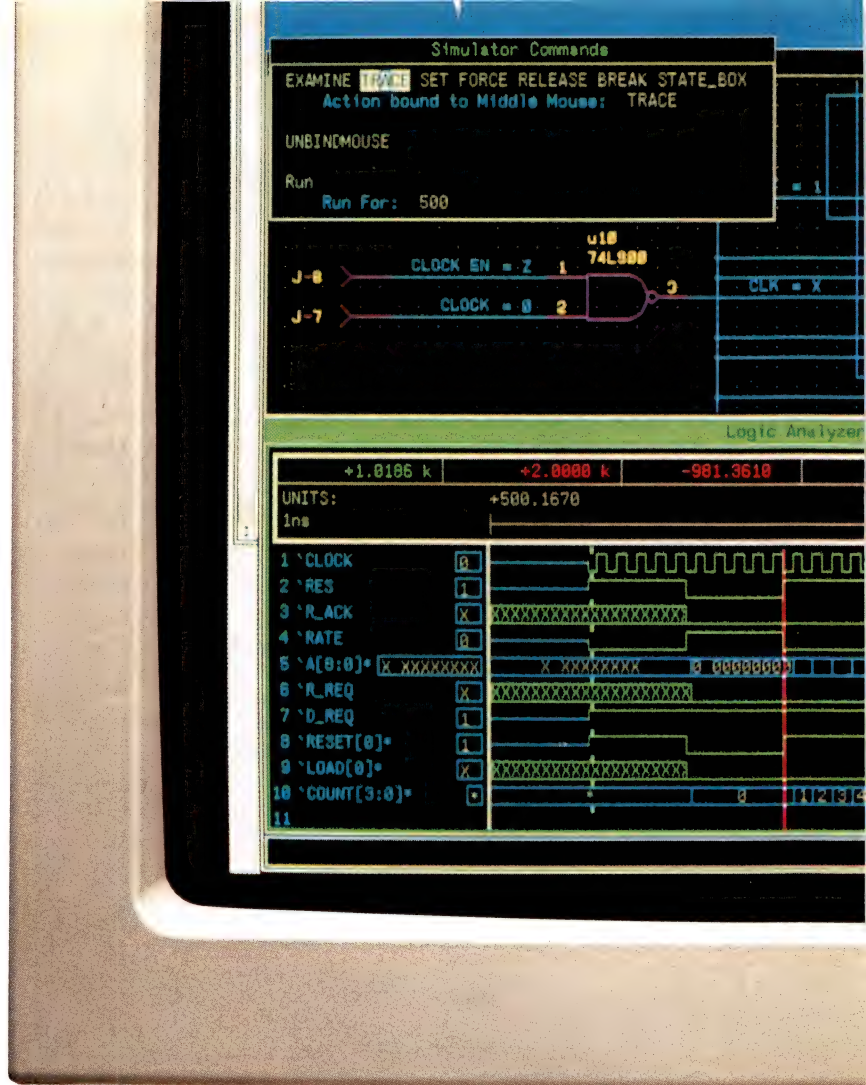Best of all, with CAE tools from Teradyne you can be sure that what



CAE for people to see how their

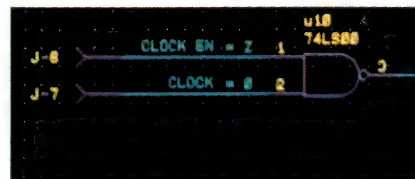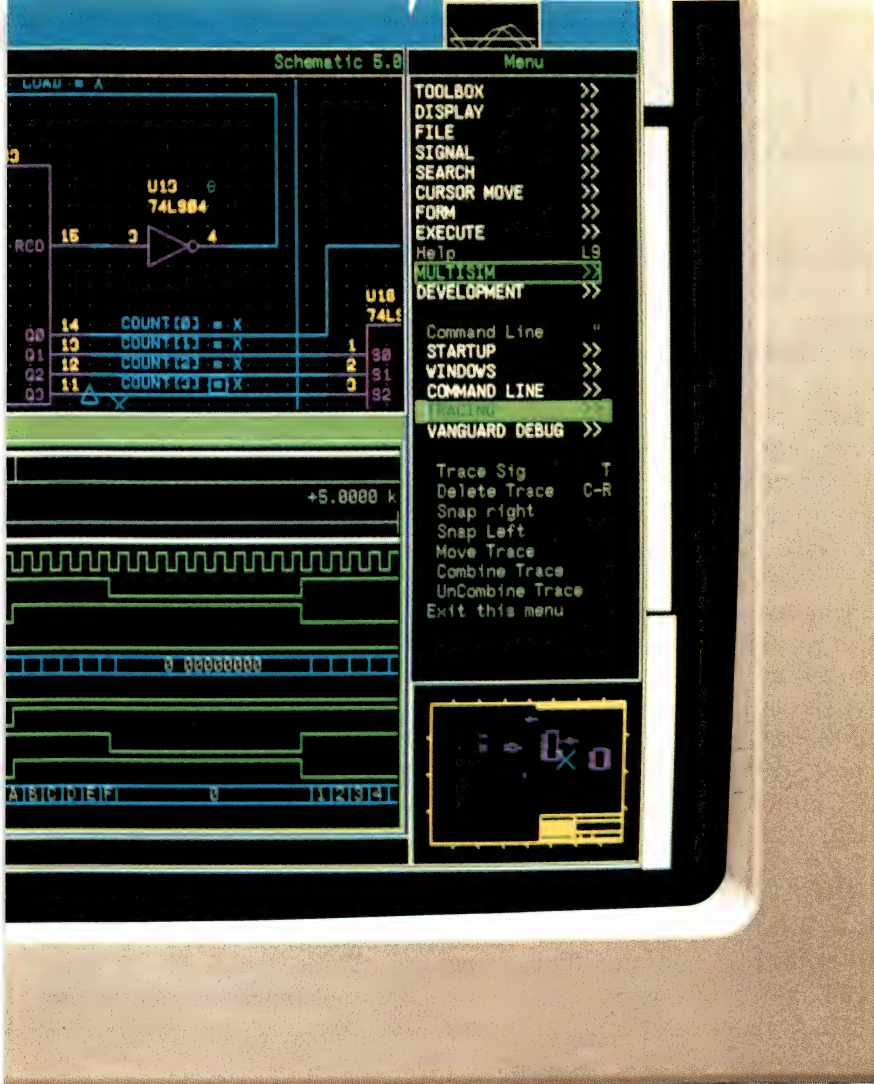


*Interactive
commands execute
instantly so it's easy
to try out new ideas.*

hurry for results,
you'll appreciate
how easily Teradyne

tools integrate into your current design process. EDIF, VHDL and commercial-tool interfaces let you build on existing databases. Then tie all your design and analysis tools running on PCs, Suns® or VAXs™ into one multiwindow design environment using Vanguard's graphical framework.

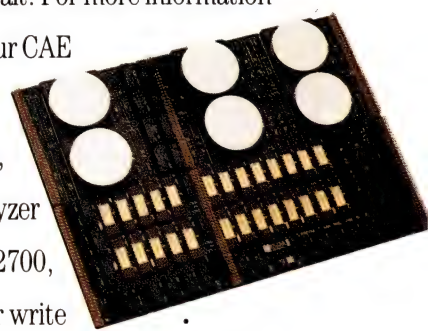So don't wait. For more information about how our CAE tools can work for you, call Daryl Layzer at (617) 482-2700, ext. 2808. Or write Teradyne, 5155 Old Ironsides Drive, Santa Clara, CA 95054.



LASAR lets you combine structural, behavioral, and hardware models for simulation efficiency with exceptional accuracy.

who can't wait designs work.

you see in design is what you'll get in manufacturing. How so? Because our LASAR system is more accurate than other event-based simulators. LASAR's worst-case algorithms precisely simulate the operation of gate arrays, high-speed



micros and time-multiplexed buses, including the effects of process variations. You can zero-in on troublespots efficiently, and be confident that LASAR-verified designs will work—reliably and repeatably.

The same user interface and file format on PCs, Suns and VAXs simplifies training and communications when you're mixing platforms.

If you're in a

TERADYNE

SIGNALS & NOISE

Bob Pease sends corrections

Thank you for printing my letter about ICs that are nonstandard (EDN, October 26, 1989, pg 33). However, the statement reading, "The following list of parts all share the same pinout" contains an error. It should read, "The following list of parts all *have a nonstandard* pinout."

An error also crept into Fig 1, Part 12 of the series on troubleshooting analog circuits (EDN, October 26, 1989, pg 176). VA does connect to two diodes and to R₂, but VA does not connect to the op-amp input. Therefore, this path should be broken. Similarly, the bottom of R₂ does not connect to ground, but it does connect to the input of the amplifier.

Finally, in Part 11 of the series (EDN, October 12, 1989, pg 177),

the original text of a statement in the lower left column read: "...features as good a temperature coefficient as you'd probably ever be willing to pay for." I realize the EDN Stylebook frowns on using "good" in statements about specifications, so the editors changed it to "high." Unfortunately, "good" in this case means "low." The sentence should read: "These bandgap references feature as low a temperature coefficient as you'd probably ever be willing to pay for."

*Robert Pease
Staff Scientist
National Semiconductor
Santa Clara, CA*

Tell them "We won't take it anymore"

Yes, I'm mad as hell. Jon Titus's editorial "She'll be right, mate"

(EDN, October 12, 1989, pg 49) touches on a problem that I find more and more unsettling as time goes by. From busboy to president, everybody relies on a "Santa Claus" to make things right. Worse yet, without a "Santa," Americans are getting ever more helpless. Recently, the TV show, "Hidden Video," set up a phony Canadian border crossing outside a California desert town and made people swear to uphold the laws of Canada. I find it very hard to visualize one of the Founding Fathers falling for such a prank.

What has turned a proud, self-reliant nation into a bunch of nitwits that needs to be told what to do and not to do every step of the way? Not only responsibility seems to have vanished, but common sense as well. While one might construe the "Don't blame me!" syndrome as



THE NEW-EVENT MACHINE.

Introducing the Analytek Series 2000 2 GS/s, 12 bit, Multichannel Waveform Sampling System.

It's a dazzling new way to take a better look at fast and rare events where every little bit counts. Analyze, record, measure. Unprecedented 63 dB signal to noise.

Compact, flexible, and modular. Mix and match sampling modules to trade off channel count for record length and speed. Install up to 96 channels in a single VXI/VME mainframe. Mouse driven. Programming via IEEE 488.2. Autocalibration, variable time base.


For a demo or more information.

Call Analytek at **(800) 366-5060**. FAX (408) 725-8562. For more information, contact your nearest Tektronix sales office, or Analytek, 10261 Bubb Road, Cupertino, CA 95014.



CIRCLE NO. 1

THE FINE ART OF DISC DRIVES

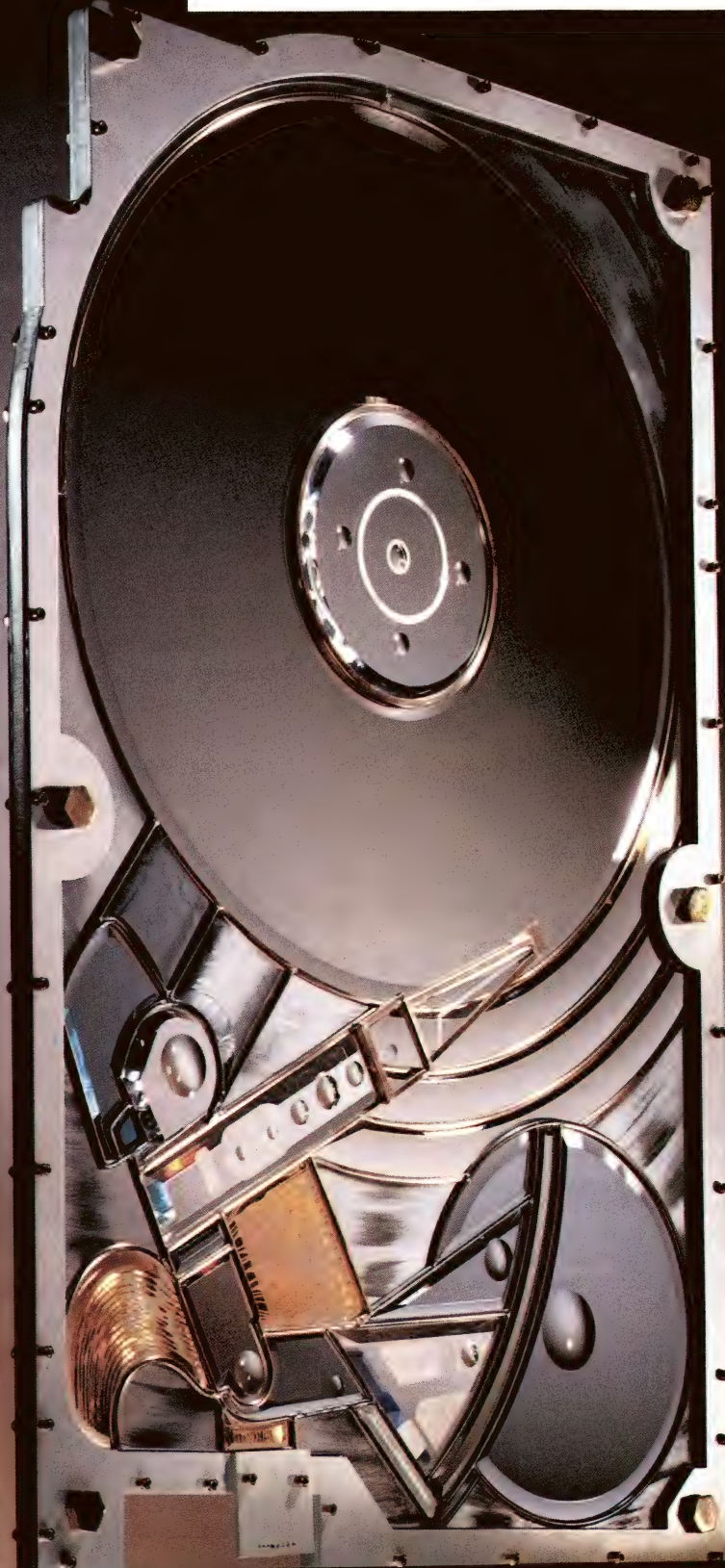

*Beveled Glass Window by
Thomas Tisch & Andreas Lehmann
Oakland, California*

Even to the experienced observer, a disc drive is a technological marvel. With discs spinning at 60 revolutions per second, the mechanics involved are astounding. It takes a company with a unique level of skill and experience to produce drives in volume that perform reliably year after year. A company like Seagate.

Our 3.5" ST1096 family is a great example of Seagate craftsmanship. Featuring a choice of 42, 60 or 83 formatted megabytes, these high performance (24 msec average access time) drives are ready for demanding PC and Apple® applications. The family offers ST412/MFM and SCSI interfaces for application flexibility. And they all feature a 50,000 hour mean-time-between-failure rate.

Like the artist who spends years perfecting his craft, Seagate has spent the past decade mastering the fine art of disc drives. For more information on our multi-faceted product line, contact your authorized Seagate distributor, or call Seagate directly at 800-468-DISC, or 408-438-6550.

 **Seagate**

Apple is a registered trademark of Apple Computer, Inc.
Seagate and the Seagate logo are registered trademarks of Seagate Technology, Inc.
© 1989 Seagate Technology, Inc.

merely a side effect of the pursuit of happiness, what can account for the simultaneous urge to become victims?

Could the Founding Fathers have unwittingly built a time bomb? The Constitution was constructed to safeguard against arbitrary rule by an aristocracy, an oligarchy, or any

other elite. By setting up a government "not of men, but of laws," the framers may have planted a dangerous seed: The guardians of these laws would eventually usurp the power of the people to rule themselves.

It's taken 200 years for the seed to grow into a clear and present

danger, but today there can be little doubt that many of us live in daily fear, not of law, but of lawyers, much as earlier civilizations trembled in fear of their High Priests. "The law" has been turned into a monster that only the Anointed can understand and keep at bay—after adequate sacrifices. We have by now been trained to seek our lawyer's blessing not just before embarking on any journey, but also upon returning. If anything went awry, he'll tell us who was "at fault" and how to cash in on every mishap.

Innovators, producers, and their sponsors have become prime targets for the modern witch hunters. Naturally, the litigators line their pockets with the wealth that should have benefited our industries' (and the country's) growth. The message "Don't take chances" pervades our business world. A clique of unproductive tea-leaf readers, pretending to "make her right, mate," is paralyzing progress and goading the nation into a mindless stupor.


What can we, as innovators and as citizens, do to break the spell? We must tell our legislators in no uncertain terms, "We're mad as hell, and we won't take it anymore." If we yell loud enough, they might listen—at least the few who aren't lawyers.

*Max J Schindler
Prime Technology
Boonton, NJ*

Correct phone number and location

In the Technology Update (EDN, October 26, 1989, pg 115) entitled "CAD tools aren't yet on speaking terms," two errors appear in the box on pg 116. The phone number for Honeywell Systems Inc should be (612) 782-7322, and the company is located in Minneapolis, MN, rather than in Boston, MA.

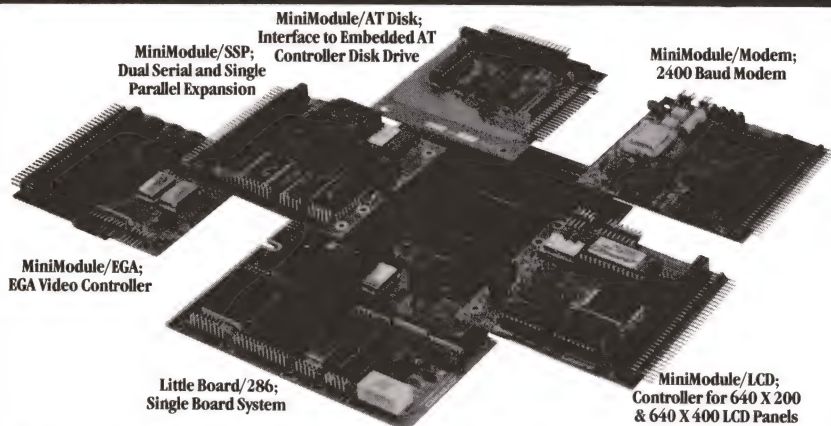Build your embedded PC or AT any way but big.



Little Board plus Minimodules™

Embedded applications. Ampro's Little Board PC and AT compatible single board systems are ideal for embedded or dedicated applications. Specifically, applications which demand small size, high reliability, rugged design and low power consumption. Now, Ampro MiniModules allow you to build Little Board systems into a wider range of applications while meeting these same requirements. **Little Board/PC or /286.** Take your pick. PC compatible or AT compatible. Both single board systems are equivalent to a mother-board and four expansion cards in a single 5.75" X 8" card. Both offer low power consumption, single 5V supply operation and 0 to 70°C operating range.

MiniModule Expansion. Extend your Little Board based embedded system using Ampro MiniModules. These compact 3.5" X 3.8" boards provide CGA or EGA video interfaces,

LCD or EL panel controllers, Arcnet LAN controller, 2400 baud modem, serial/parallel port expansion or an interface to hard disks with embedded AT controllers. Stack 'em vertically or side by side. Build a big system in small space.

Complete information. Fast. Call us at the number below. We'll immediately forward specifications and details on the Little Board family of single board systems and MiniModules. Then, you can build your embedded system. Any way but big.

All trademarks are the property of their respective owners


408-734-2800

AMPRO

SINGLE BOARD SYSTEMS
Ampro Computers, Inc., 1130 Mountain View/Alviso Road
Sunnyvale, CA 94089. FAX (408) 734-2939. TLX 4940302

Distributors: Reqs: USA - contact AMPRO for the name of your nearest rep. Australia - 61 3 720-3298; Austria - 43 222/3109110; Canada - (604) 438-0028; Denmark - 455 3 66 20 20; Finland - 358 0 585-322; France - 331 4842-2222; Germany - West - 49 6151 7305-35; Hong Kong/P.R.C. - 5 8613118; Israel - 972 3 49-16-95; Italy - 39 6 811-9406; Japan - 81 3 257-2630; Netherlands - 31 10-411 8521; Norway - 46 8 28-72-86; Sweden - 46 8 28-72-86; Switzerland - 41 1 740-41-05; United Kingdom - 44 2 964 5551

High Performance Reading

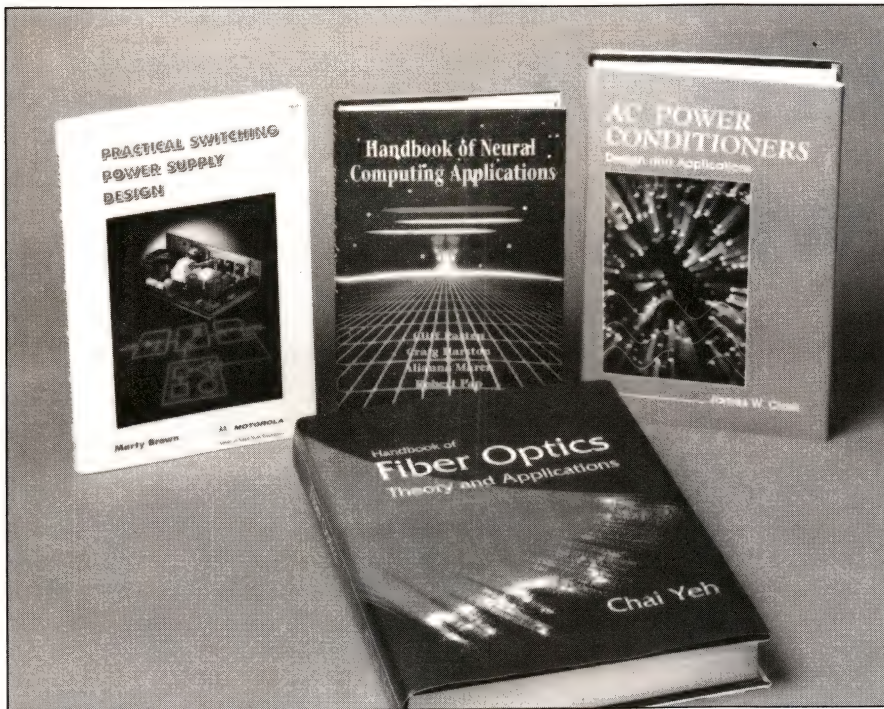

Practical Switching Power Supply Design

Marty Brown

Take the "black magic" out of switching power supplies with this complete "hands-on" guide to the theory behind, and design of, PWM and resonant switching supplies. You'll find:

- details on switching supply operation
- advice on how to select an appropriate topology for your application
- extensive coverage of buck, boost, flyback, push-pull, half and full bridge regulator circuits
- special attention on semiconductors used in switching supplies
- explanations of RFI/EMI reduction, grounding, testing, and safety standards.

March 1990, c. 240 pages
\$39.95 (tentative)/ISBN: 0-12-137030-5

Handbook of Neural Computing Applications

Cliff Parten, Craig Hartson,
Alianna Maren, and Robert Pap

This book is a detailed guide to the essential architectures, processes, implementation methods, and applications of neural computing systems. Unlike purely theoretical books, this handbook shows how to apply neural processing systems to problems in neurophysiology, control theory, learning theory, pattern recognition, and similar areas. This book fully discusses neural network theories, and also shows where they came from, how they can be used, and how they can be developed for future applications.

February 1990, c. 400 pages
\$69.95 (tentative)/ISBN: 0-12-546090-2

AC Power Conditioners

Design and Applications

James W. Clark

Written by a working professional, this detailed guide describes the theory and design of AC power conditioners and provides you with application techniques, presents original design equations, and working circuit examples.

December 1989, 208 pages, \$44.95
ISBN: 0-12-175460-X

Handbook of Fiber Optics

Theory and Applications

Chai Yeh

Here's a comprehensive reference with state-of-the-art information on fiber optics including:

- optic fibers and fiber materials
- light sources and detectors
- coupler, LEDs, and other individual components
- coherent optics
- lasers and
- the development of fiber optics-based telecommunications systems.

February 1990, 382 pages
\$79.95 (tentative)/ISBN: 0-12-770455-8

Order from your local bookseller
or directly from



ACADEMIC PRESS

Harcourt Brace Jovanovich, Publishers
Book Marketing Department #29010,
1250 Sixth Avenue, San Diego, CA 92101

CALL TOLL FREE

1-800-321-5068


Quote this reference number for *free postage and handling* on your prepaid order — 29010

Prices subject to change without notice. ©1990 by Academic Press, Inc.
All Rights Reserved. CB/KR — 29010.

**These speech
synthesizers
can be difficult
to work with...**



these aren't.

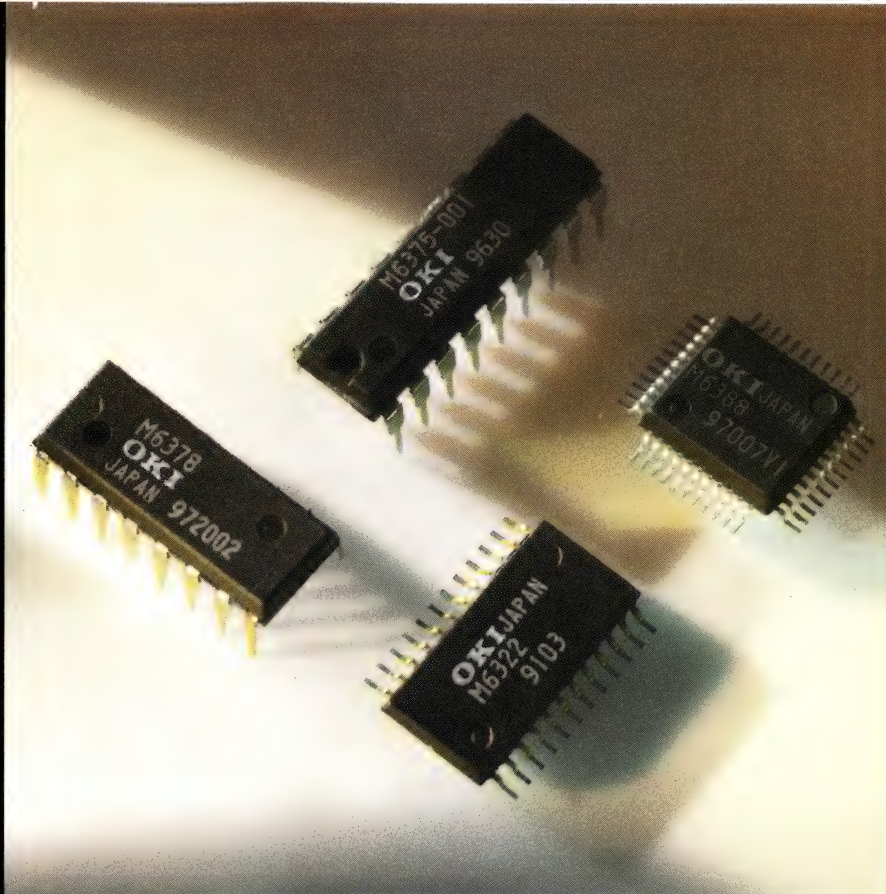

Tired of working with speech synthesizers that squawk or screech or sound like tinny talking toys? Do your high-tech applications demand high-quality sound reproduction?

If so, you need to sound out Oki's easy-to-use speech synthesizers. The superior quality of our chips quickly demonstrates that it's one thing to imitate sound. It's another to synthesize it.

Our state-of-the-art synthesizers offer the high integration and realistic sound you expect, with features like these:

- on-chip low pass filter
- on-chip 12-bit D/A converter

• 4-bit ADPCM algorithm for better than FM signal-to-noise ratio


And we have the range of products to meet your varied applications: Three masked ROM chips with 10- to 40-second message options. A ROMless development chip. A one-time programmable chip. A real-time pitch control chip. And a solid-state recorder.

If you like the sound of our offerings, you'll love the sound of our chips. Order a demo board from Oki today. And you'll design us in tomorrow.

So. Calif.
(Irvine)
714/752-1843
(Sherman Oaks)
818/990-3394
No. Calif.
(San Jose)
408/244-9666
Boca Raton, FL
407/394-6099

Atlanta, GA
(Norcross)
404/448-7111
Chicago, IL
(Rolling Meadows)
708/870-1400
Boston, MA
(Stoneham)
617/279-0293
Detroit, MI
(Livonia)
313/464-7200

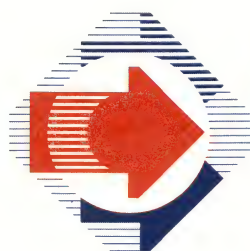New York, NY
(Poughkeepsie)
914/473-8044
Philadelphia, PA
(Horsham)
215/674-9511
Dallas, TX
(Richardson)
214/690-6868



OKI

Semiconductor

Quality that speaks for itself.

ULTRA QUALITY, ULTRA ECONOMY POCKET DMMS



AT YOUR FINGERTIPS

**\$29⁹⁵_{LIST} and \$44⁹⁵_{LIST} . . . Take Your Choice
and Save With The Best!**

So small you carry them on-the-spot in your shirt pocket, so precise you'll think they're bench models with numerous features. The model 3060 offers 3200 counts, full scale, analog bar graph display and 3½ digits . . . plus fast auto/manual ranging; automatic power shut down; high speed sampling; range hold and continuity beeper.

Of course, the companion Model 3020 also measures Volts, Amps, Ohms, tests diodes, and includes continuity beeper. Both models come with heavy duty carrying case, "button" cell batteries, test leads, and manual.

Send for New Catalog

CARLO GAVAZZI
Instruments

CG Instruments Corp.

434 Windsor Park Drive, Dayton, OH 45459
TEL: (513) 434-6952 • FAX: 513-434-7643

CALENDAR

Designing for Electromagnetic Compatibility (short course), Various locations and dates. Hewlett-Packard Co, Signal Analysis Div, 1212 Valley House Dr, Rohnert Park, CA 94928. (800) 247-3382; in CA, (707) 794-1212. Through June 5.

Winter 1990 UNIX Technical Conference, Washington, DC. Judith DesHarnais, USENIX Conference Office, 22672 Lambert St, Suite 613, El Toro, CA 92630. (714) 588-8649. January 22 to 26.

SaudiComputer '90, Saudi Arabia. Gerald G Kallman, Kallman Associates, 5 Maple Ct, Ridgewood, NJ 07450. (201) 652-7070. FAX 201-652-3898. January 28 to February 1.

SEMICON/Southwest, Dallas, TX. Semiconductor Equipment and Materials International, Shows Dept, 805 E Middlefield Rd, Mountain View, CA 94043. (415) 964-5111. January 31 to February 1.


SECS Communications Seminar, Dallas, TX. GW Associates Inc, 1183 Bordeaux Dr, Suite 27, Sunnyvale, CA 94089. (408) 745-1844. February 2.

1990 6th IEEE/CHMT Semiconductor Thermal & Temperature Measurement Symposium, Scottsdale, AZ. C/S Communications, Box 23899, Tempe, AZ 85285. (602) 967-7444. February 4 to 8.

2nd International Tape Automated Bonding (TAB) Symposium, San Jose, CA. Dr Subash Khadpe, Semiconductor Technology Center, Box 38, Neffs, PA 18065. (215) 799-0919. FAX 215-799-2677. February 5 to 7.

Communication Networks '90, Washington, DC. IDG Conference Management Group, Box 9171, 20 Speen St, Framingham, MA 01701. (508) 879-6700. February 5 to 8.

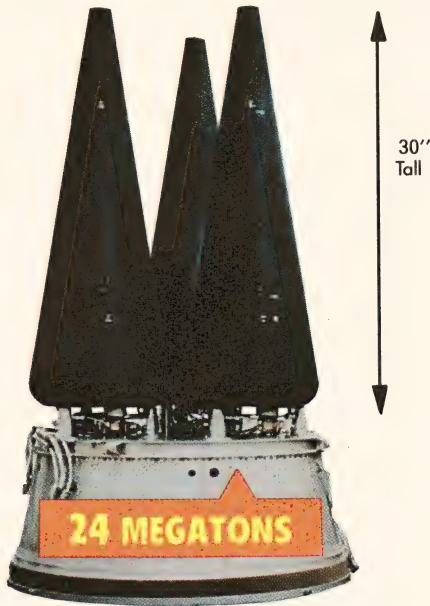Awesome Power Often Comes in Small Packages





If you thought GESPAC makes small boards, you are right! Every product we make fits on a 25 square inch single height Eurocard. Now, if you think a small board cannot be powerful enough for your application, it may be that you have not seen our latest products. The G-64 bus now supports full 32-bit data transfer at 40 Mbytes per second and we have introduced a series of very high performance boards, including the most compact implementation of the 68030 microprocessor. We also offer high-end, add-on functions such as: 8 Mbyte RAM boards, X.25 and Ethernet network controllers, high resolution graphics, and the widest selection of general purpose I/O functions and real-time software under the sun.

All in all, no one packs more power per square inch than GESPAC.

Our boards are small and use our unique fine line, single layer dual sided PC board technology. They are more reliable and cost less, which should make them the obvious choice for your next OEM system design.

To receive your free data sheet and full line catalog,

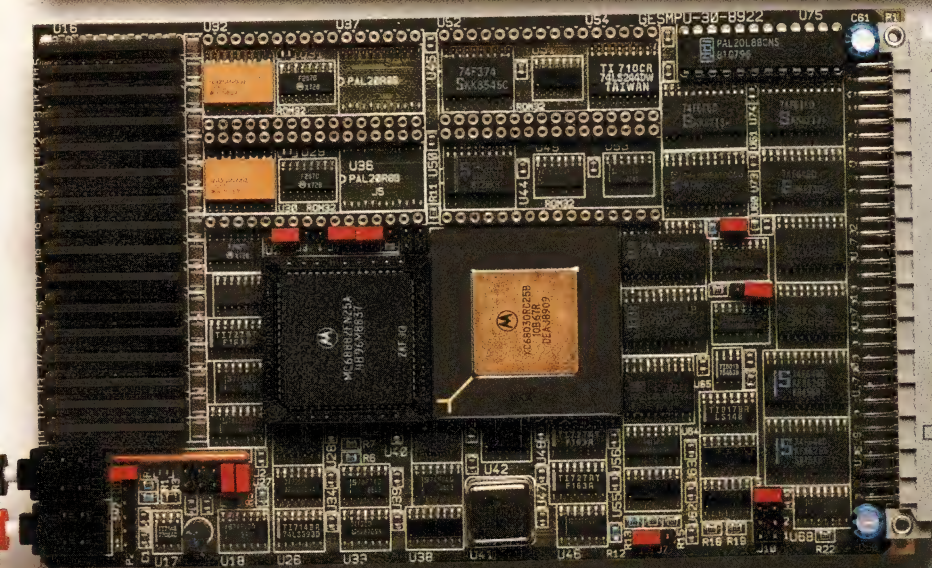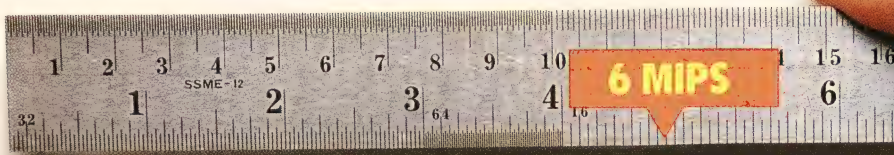**Call Toll Free 1-800-4-GESPAC
or (602) 962-5559.**



GESMPU-30H

Processor	MC68030
Speed	25 MHz
FPU	68882
#JEDEC Sockets	4
EPROM Capacity	512 Kbytes
RAM Supplied	2 Mbytes
# Serial Ports	2 *
# TTL I/O	20
# Timers/# Bits	3 x 16-bit *
Clock/Calendar	Yes *
Watchdog	Yes *
Ext. Addressing	32 Mbytes

USA - CANADA
50 West Hoover Ave.
Mesa, Arizona
85210 USA
Tel. (602) 962-5559
Fax. (602) 962-5750

EUROPE
Z.I. les Playes
83500 La Seyne
France
Tel. 94 30 34 34
Fax. 94 87 35 52

INTERNATIONAL
18, Chemin des Aulx
CH-1228 Geneva
Switzerland
Tel. (022) 794 3400
Fax. (022) 794 6477

GESPAC

* Using GESMFI-1 Multi-function board.

CIRCLE NO. 58

This ad is by no means an endorsement for nuclear weaponry.

"MATHCAD IS THE BEST THING TO HAPPEN TO THE ENGINEER SINCE THE POCKET PROTECTOR."

— PC Magazine

For problems involving engineering calculations or scientific analysis, the answer is MathCAD®

MathCAD is the only PC-based software package specifically designed to give technical professionals the freedom to follow their own scientific intuition. You decide how to solve the problem – MathCAD does the "grunt work."

- Ends tedious programming and debugging.
- Displays instant answers as you change variables.
- Generates quick plots to help you view results.

MathCAD includes such built-in features as:

- Matrix operations
- Simultaneous equation solver
- Real and complex numbers
- Dynamic error flagging
- Automatic unit conversions
- Greek character set
- Fast Fourier Transform and much more

To find out what MathCAD can do for you, call us today for a **free demo disk: 1-800-MathCAD** (in MA, 617-577-1017). Or write to MathSoft, Inc., One Kendall Square, Cambridge, Massachusetts 02139.


Requires IBM® PC or compatible, 512KB RAM, graphics card.

Math Soft

$\Sigma + \sqrt{-} = \times j \div \delta$


Software Tools for Calculating Minds #13

CIRCLE NO. 4

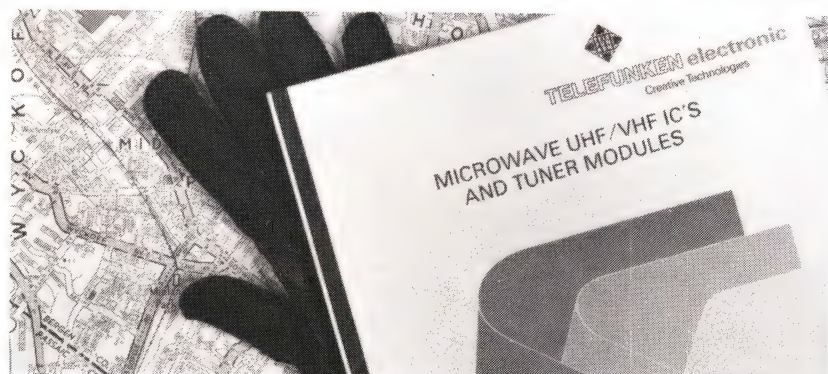

A Road Map to VHF, UHF & Microwave Component Design

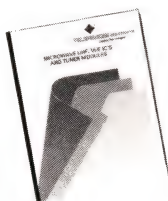Our "Atlas" is loaded with specs and engineering data describing Microwave UHF/VHF ICs and Tuner Modules. For information concerning Microwave Frequency Dividers (prescalers), PLL ICs, UHF/VHF front end ICs for communications, Video and FM Tuners, contact: AEG Corporation, 3140 Rte. 22, PO Box 3800, Somerville, NJ 08876-1269; (201) 231-8493; Fax: (201) 231-8353.



TELEFUNKEN electronic
Creative Technologies

CIRCLE NO. 5

CALENDAR

Hands-on UNIX for Programmers (short course), Seattle, WA. Specialized Systems Consultants Inc, Box 55549, Seattle, WA 98155. (206) 527-3385. FAX 206-527-2806. February 7 to 9.

1990 Symposium on Electronic Imaging: Science and Technology/Exhibit, Santa Clara, CA. The International Society for Optical Engineering, Box 10, Bellingham, WA 98227. (206) 676-3290. FAX 206-647-1445. February 11 to 16.

IEEE Instrumentation and Measurement Technology Conference, San Jose, CA. Robert Myers, IEEE Instrumentation and Measurement Society and IEEE Santa Clara Valley Section, 3685 Motor Ave, Suite 240, Los Angeles, CA 90034. (213) 287-1463. FAX 213-287-1851. February 13 to 15.


Systems/USA, San Jose, CA. Chuck Jungi, American Electronics Association, 5201 Great America Pkwy, Santa Clara, CA 95054. (408) 987-4204. February 13 to 15.

Buscon West, Long Beach, CA. Sharon Salvo, Conference Management Corp, 200 Connecticut Ave, Norwalk, CT 06856. (203) 852-0500, ext 253. February 14 to 16.

Modern Power Conversion Design Techniques (short course), San Diego, CA. Joy Bloom, Bloom Associates Inc, Educational Div, 115 Duran Dr, San Rafael, CA 94903. (415) 492-1239. FAX 415-492-1239. February 19 to 23.

SECS Communications Seminar, San Jose, CA. GW Associates Inc, 1183 Bordeaux Dr, Suite 27, Sunnyvale, CA 94089. (408) 745-1844. February 26.

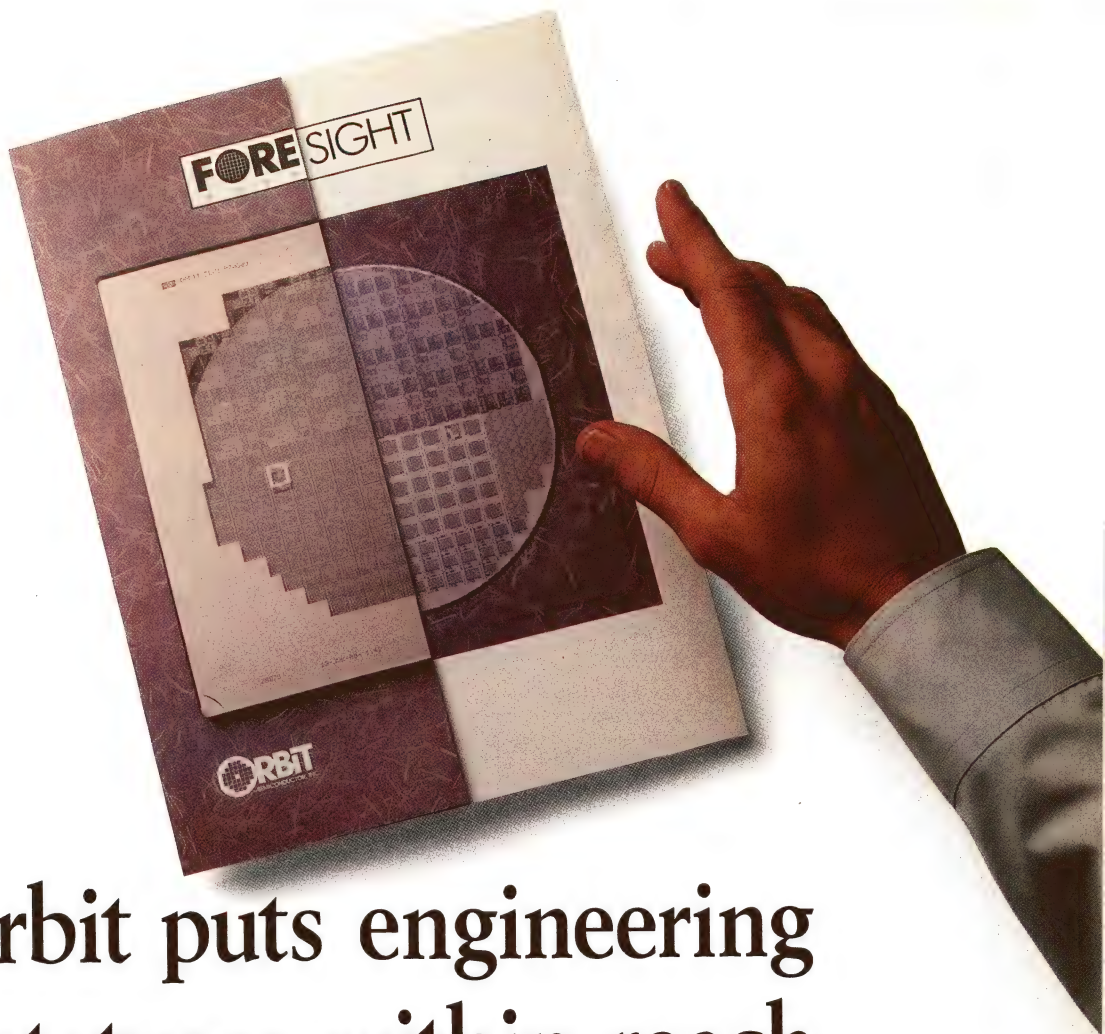Electronic Imaging West, Pasadena, CA. MG Expositions Group, 1050 Commonwealth Ave, Boston, MA 02215. (800) 223-7126; in MA, (617) 232-3976. February 27 to March 1.



Orbit puts engineering prototypes within reach.

Now you can cut NRE expense and save valuable time on engineering prototype runs just by using a little foresight. Foresight, Orbit's new multi-project wafer processing service, puts the engineering prototypes you need within reach. In record time. And at a record low cost.

Orbit's new Foresight accommodates generic CMOS processes with feature sizes down to 1.2 microns with maximum die sizes of 300 mils on a side. Getting in on a run is as easy as supplying a database tape by our monthly start date.

Available processes:

- Single Poly/Single Metal
- Double Poly/Single Metal
- Single Poly/Double Metal
- Double Poly/Double Metal

Don't wait until high NRE costs and slipped deadlines put you in a bind. Design rules and information on Orbit's new Foresight service are within reach today by contacting Foresight Marketing or the international rep nearest you. Orbit Semiconductor, Inc. 1230 Bordeaux Drive. Sunnyvale, CA 94089. FAX (408) 747-1263. Or call (800) 331-4617. In California (800) 647-0222 or (408) 744-1800.



A subsidiary of Orbit Instrument Corporation.




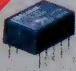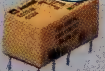

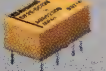

What others promise, we guarantee.

CIRCLE NO. 29

For your next design application...

15 great reasons for Aromat's leadership



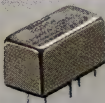
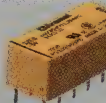
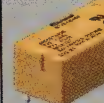
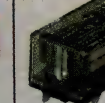

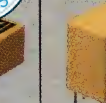


• Dimension (inches) L x W x H								
		.551 x .354 x .197	.551 x .354 x .307	.551 x .220 x .386	.787 x .390 x .366	.795 x .433 x .394	.630 x .390 x .276	.787 x .394 x .323
• Type of relay		NEW T-SERIES			High Breakdown Voltage Capacity	Miniature Power	Ultra-Miniature	Highly Reliable DIP
		TQ	TF	TN	DS	DSP	DF	DR
• Features		<ul style="list-style-type: none"> Most advanced polarized relay High sensitivity 1500V FCC surge satisfied 4 pole model available 	<ul style="list-style-type: none"> 80mW nominal operating power 48VDC coil available Surface mount models available 1500V FCC surge satisfied 	<ul style="list-style-type: none"> Vertical TQ Relay Ultra-slim size High sensitivity 1500V FCC surge withstand voltage 	<ul style="list-style-type: none"> 1500 FCC surge satisfied High sensitivity High switching power Ag-Pd contact type available 	<ul style="list-style-type: none"> 1500V FCC surge satisfied High sensitivity High switching capacity 	<ul style="list-style-type: none"> Ultra-small type .28" x .63" x .39" High sensitivity DIL Terminal 	<ul style="list-style-type: none"> High sensitivity High sticking resistance High breakdown voltage High speed operation—1msec
• Sealed types		●	●	●	●	●	●	●
• Latching types		●	●	●	●	●	●	●
• Contact arrangement		2C, 4C	2C	2C	1C, 2C, 4C	1a, 1a1b, 2a	2C	1C
• Contact rating		0.3A, 110VDC 0.5A, 125VAC 1A 30VDC	0.3A 110VAC 0.5A 125VAC 1A 30VDC	0.3A 110VDC 0.5A 125VAC 1A 30VDC	0.6A 125VAC 0.6A 110VDC 2A 30VDC	(1a): 8A, 250VAC (1a1b, 2a): 5A, 250VAC	0.3A 125VAC 1A, 30VDC	0.3A 110VAC 1A 20VDC
• Life (min. operations)	Electrical (at rated load)	2 × 10 ⁵	2 × 10 ⁵	2 × 10 ⁵	5 × 10 ⁵	10 ⁵	10 ⁵	10 ⁶
	Mech.	10 ⁸	10 ⁸	10 ⁸	10 ⁶	5 × 10 ⁷	5 × 10 ⁶	10 ⁹
• Breakdown voltage		1000Vrms	1000Vrms	1000Vrms	1500Vrms	3000Vrms	1000Vrms	1500Vrms
• Surge withstand voltage		1500V FCC	1500V FCC	1500V FCC	1500V FCC	1500V FCC	—	1500V FCC
• Coil voltage		(DC) 3, 5, 6, 9, 12, 24V	(DC) 1.5, 3, 5, 6, 9, 12, 24V, 48V	(DC) 3, 4.5, 5, 6, 9, 12, 24V	(DC) 1.5, 3, 5, 6, 9, 12, 24, 48V	(DC) 3, 5, 6, 9, 12, 24V	(DC) 1.5, 3, 5, 6, 9, 12, 24V	(DC) 3, 5, 6, 12, 24, 48V
• Nominal operating power		(Single) 140mW (-L) 100mW (-L2) 200mW	(Single) 80mW (-L) 55mW (-L2) 110mW	(Single) 140mW (-L) 100mW (-L2) 200mW	Standard: 400mW Sensitive: 200mW	(Single): 300mW (-L): 150mW (-L2): 300mW	(Single) 200mW (-L) 100mW (-L2) 200mW	(Single) 96mW (-L) 50mW (-L2) 111mW
• UL, CSA, VDE		UL/CSA	UL/CSA	UL/CSA	UL/CSA	UL/CSA	UL/CSA	—



Relays totally produced in our advanced manufacturing facility in San Jose, Ca.

in relay technology.



							
787 x .394 x .394	1.102 x .472 x .394	1.220 x .551 x .433	1.969 x 1.008 x .807	1.189 x .787 x .425	.787 x .433 x .618	.600 x .906 x .370	.795 x .441 x .358
Half-Size Amber	High Density Amber	Field Switching Power	Compact Power Sensitive	Flatpack	Subminiature DIP	High Frequency	Miniature High Frequency
R	SEB	STE	SP	NF	HB	RG	RK
<ul style="list-style-type: none"> • Magnetically shielded • High sensitivity • High speed operation—1 msec (max) 	<ul style="list-style-type: none"> • High sensitivity • High vibration and shock resistance • Low thermal electromotive force—3μV • DIL terminal 	<ul style="list-style-type: none"> • High sensitivity • Large capacity in small size • Capable of switching field inductive loads • High inrush capability 	<ul style="list-style-type: none"> • High sensitivity • High vibration and shock resistance • Wide switching range 	<ul style="list-style-type: none"> • 1500V FCC surge satisfied • Low profile • High sensitivity • MBB contacts available • Ag-Pd contacts type available 	<ul style="list-style-type: none"> • DIP terminal • Flux-resistant • Ag-Pd contacts type available 	<ul style="list-style-type: none"> • Excellent high frequency characteristics • Characteristic impedance 50Ω & 75Ω types 	<ul style="list-style-type: none"> • Isolation 60dB min. at 1.5GHz • Insertion loss 0.3dB max. at 900MHz
IC Relay option	IC Relay option	IC Relay option	IC Relay option				
●	●	●	●	●	●	●	●
1C	2a2b, 4a	1a1b, 2a	2C, 4C	2C, 4C,	1C, 2C	1C, 2C	1C
0.3A 110VAC 1A 20VDC	4A 250VAC 3A 30VDC	8A 250VAC 5A 30VDC	(2C) 15A 250VAC (4C) 10A 250VAC	0.5A 125VAC 2A 30VDC	1A 125VAC 2A 30VDC	1A 24VDC	0.01A 24VDC
10 ⁶	10 ⁶	10 ⁶	10 ⁶	10 ⁶	2 x 10 ⁵	10 ⁵	3 x 10 ⁵
10 ⁹	10 ⁹	10 ⁷	5 x 10 ⁷	(2C) 3 x 10 ⁹ (4C) 10 ⁶	10 ⁷	5 x 10 ⁶	5 x 10 ⁶
1000Vrms	1500Vrms	3750Vrms	3000Vrms	1000Vrms	1000Vrms	2000Vrms	1000Vrms
—	—	—	—	1500V FCC	—	—	—
(DC) 5, 6, 12, 24, 48V	(DC) 5, 6, 12, 24, 48V	(DC) 3, 5, 6, 12, 24, 48V	(DC) 3, 5, 6, 12, 24, 48V	(DC) 5, 6, 12, 24, 48V	(DC) 3, 5, 6, 12, 24, 48V	(DC) 3, 5, 6, 9, 12, 24, 48V	(DC) 3, 5, 6, 9, 12, 24V
(Single) 150mW (-L) 70mW (-L2) 150mW	192 to 355mW	240mW	300mW	(2C) 300mW (4C) 480mW	(1C) 360mW (2C) 580mW	(Single) 350-400mW (-L) 180-200mW (-L2) 350-400mW	(Single) 200mW (-L) 200mW (-L2) 400mW
UL/CSA	UL/CSA	UL/CSA	UL/CSA	UL/CSA or VDE	UL/CSA	—	—

Advanced switching technology.

For further information, contact your nearest Aromat sales office:

New Providence, NJ

Tel: (201) 464-3550

Marlboro, MA

Tel: (508) 481-1995

Orlando, FL

Tel: (407) 855-1075

Elk Grove Village, IL

Tel: (708) 593-8535

Richardson, TX

Tel: (214) 235-0415

San Jose, CA

Tel: (408) 433-0466

Garden Grove, CA

Tel: (714) 895-7707

Aromat Canada Inc.

Mississauga, Ontario

Tel: (416) 624-3777



Aromat

Member of Matsushita Group




What's

No matter what frequencies you work, you want everything in your connectors that engineering can deliver.

From AMP, that's a great deal.

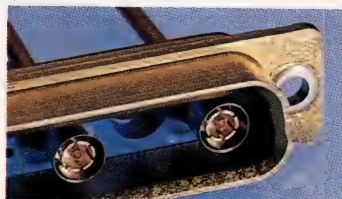Our entire line delivers the advanced design and controlled, precision




manufacturing you need for top performance, and top productivity. That kind of engineering care is why our "old

standards"—from dual-crimp BNCs on

up—consistently exhibit Mil-equivalent electrical characteristics. And you can enhance performance even further with a choice of 50 ohm or 75 ohm versions.

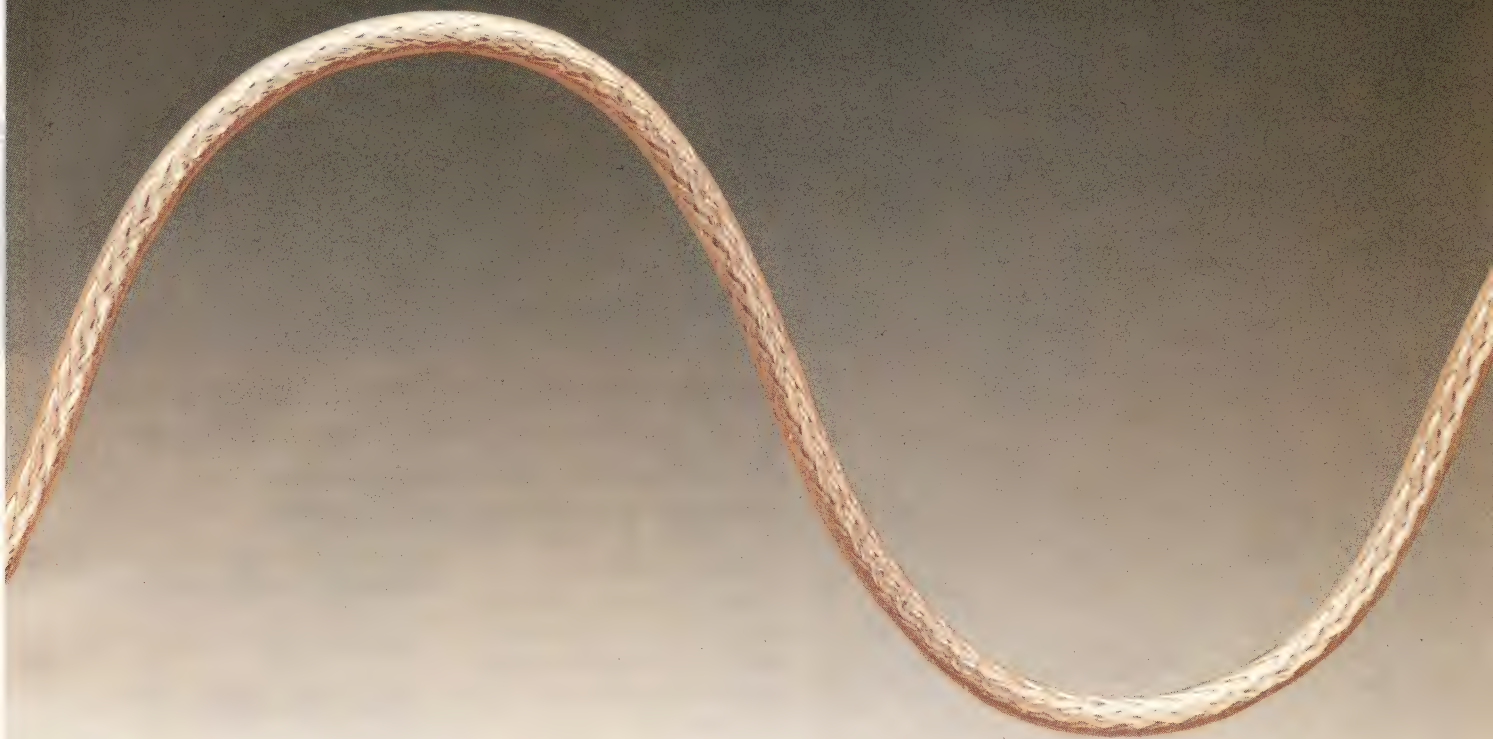
Our product offerings cover the spectrum, pushing performance on out





your sine?

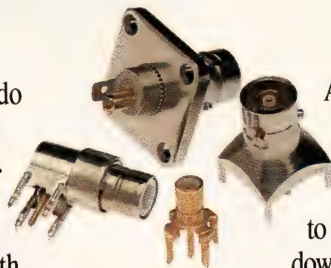to 26 GHz. And they do it time after time, with unbeatable consistency. All the while saving *you* time—on the line or in the field—with proven crimp/seal technology.



And with AMP, you get the broadest selection available anywhere, in *every* range. From cable to bulkhead and panel, right down to the board—and now including custom and semi-custom high-speed coax and transmission cable assemblies. And our field and

production tooling is second to none in dependable, repeatable terminations.

Call 1-800-522-6752 for technical literature on AMP RF connectors, or for the name of your local AMP Distributor. AMP Incorporated, Harrisburg, PA 17105-3608.



AMP Interconnecting ideas

How to get 32-bit Cache into a restricted area:

Running out of board space? Here is high-performance SRAM, organized for 32-bit systems, with density that delivers up to 80% savings in real estate. Call today for a FREE mechanical sample.

32-bit SRAM.

Here are five very fast ways to simplify the implementation of 32-bit SRAM for high performance applications like RISC and DSP.

These ultra-fast, low-power 32-bit CMOS *modules* give you the word-width and density you need, but with a reduced area and pin count. That translates to routing

efficiency and performance efficiency. Interconnect capacitance is reduced. Crosstalk is reduced.

Most important, board space requirements are reduced, *dramatically*.

With edgemount versions under 1/2" in height (easily meeting VME slot requirements) the space savings can really add up.

So if you are feeling cramped for board space, please call our hotline for immediate relief.




CYPRESS
SEMICONDUCTOR



1. CYM1822HV-16K x 32 SRAM w/Sep. I/O, 15 ns. 88-Pin VDIP. 0.9" Sq. req.



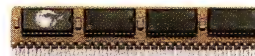2. CYM1821PZ-16K x 32 SRAM w/OE, 15ns. 64-pin ZIP. 1.2" Sq. req.



3. CYM1832PZ-64K x 32 SRAM, 25ns. 60-pin ZIP. 1.0" Sq. req.



4. CYM1831PZ-64K x 32 SRAM w/OE, 25ns. 64-pin ZIP. 1.2" Sq. req.



5. Mil-Spec! CYM1830HD-64K x 32 SRAM, 25ns. 60-pin DIP. 1.8" Sq. req.

**Pick your FREE
mechanical sample
then call:**

1-800-952-6300.*

Ask for dept. C43

**We'll send your
part, and our
new Multichip
data book.**



*1-(800)-387-7599 in Canada. (32)2-672-2220 in Europe.

©1989 Cypress Semiconductor, 3901 North First Street, San Jose, CA 95134.

Phone: (408) 943-2600, Telex: 821032 CYPRESS SNJ UD, TWX: 910-997-0753.

EDITORIAL

Innovation is imagination realized



Jesse H Neal
Editorial Achievement Awards
1987, 1981 (2), 1978 (2),
1977, 1976, 1975
American Society of
Business Press Editors Award
1988, 1983, 1981

We're pleased to be launching EDN's Crusade for Innovation—a program that will recognize innovative designs, products, and people. Soon you'll see our Innovation and Innovator logos associated with technical articles, products, and people. We believe that innovation is the key to keeping the electronics industry dynamic, healthy, and profitable.

People often ask, though, what is innovation? Isn't it something more than simply developing new things? In truth, yes. Not every new product is an innovation, nor is every engineer an innovator. To me, the heart of innovation is imagination and the ideas that spring from it. No one can be an innovator without having—and using—a fertile imagination, for without one you cannot see the future and how to reach it.

If you want to be an innovator, start using your imagination right now. Conjure images of

- an organization in which divisions and departments communicate with each other, coordinate their efforts, and pursue common overall goals outside normal "compartments"
- a company that has no managers, only leaders who champion and sponsor people and ideas
- a company that promotes and encourages entrepreneurial spin-offs and new ventures and developments when it can't exploit them itself
- a business that encourages people to pursue ideas and to make intellectual leaps—even though they might sometimes fail.
- an enterprise in which engineers aren't stuffed into a Black Hole of Calcutta to do "engineering," but are encouraged to help set market, service, and product-definition goals
- a venture that does less market research and decides to "just do it" and get the market's reaction to a real product
- a company that encourages or demands that people think of what they can do, rather than what they cannot
- a firm that encourages employees to use their imaginations.

Forming images is the easy part. But, to become truly innovative, you must put your ideas and the ideas of others into action. You must try to bring the future up to the present. You'll never be an innovator unless you set *real* goals and strive to reach them.

A stylized, handwritten signature in black ink.

Jon Titus
Editor

FULL SPE



For the name of your nearest distributor in Europe, call 44-296-625462. Or contact Applied Microsystems Corporation Ltd., Chiltern Court, High Street, Wendover, Aylesbury, Bucks HP22 6EP, United Kingdom. **In Japan, call 03-493-0770.** Or contact Applied Microsystems Japan Ltd., Nihon Seimei, Nishi-Gotanda Building, 7-24-5 Nishi-Gotanda, Shinagawa-KU, Tokyo T141, Japan.

AMC 240

ED AHEAD.

INTRODUCING THE FIRST 33-60 MHz MICROPROCESSOR EMULATOR FOR THE 68020 AND 68030.

Put your phone in front of you and get ready. You're about to get in touch with the future of high speed microprocessor emulation.

For quite some time Applied Microsystems has been designing a radical new concept in 32-bit development. Now it's ready. The EL 3200.

It's capable of not only matching current speeds, but can efficiently expand to support faster speeds and advanced 32-bit microprocessors of the future.

The news is not just speed, but how the EL 3200 gets up to speed.

It runs at full target clock speed—33 MHz for 68020 and 68030. It fully supports 68030 cache burst and synchronous bus cycles. And, since it sits as a node right on the trunk of your Ethernet network, the EL 3200 can be accessed from any workstation.

The EL 3200 offers your choice of source level or symbolic debugging. Whether you want to work in Assembly or C, we can provide the software tools for your exact needs.

The sophisticated breakpoint system has hundreds of real-time access breakpoints, six real-time execution breakpoints and unlimited software execution breakpoints. As an option, you can have up 2MB of no wait state overlay memory that runs at full clock speed, so there are no restrictions on memory, software or interrupts. The 16K deep by 139 bit wide trace provides true 32 bit support.

Seeing is believing. For a demonstration or more information, pick up your phone.

Dial full speed ahead and ask for Telemarketing. In WA (206) 882-2000.

Applied Microsystems Corporation, P.O. Box 97002, Redmond, Washington, USA 98073-9702.

1-800-343-3659



Applied Microsystems Corporation



Marshall Boasts A Fine Lineage.



TLC549
1985
8 Bit A/D

Introduction of LinCMOS Technology



TLC1540
1986
10 Bit A/D

12 Channel LinCMOS Technology



TLC7524 (AD7524)
1987

1st D/A Converter

Introduction of Advanced LinCMOS Technology



TLC7528 (AD7528)
1987

1st 8-bit D/A Dual Channel

Advanced LinCMOS Technology



TLC10 (MF10)
1988

1st Dual-switched Capacitor With Filter
Advanced LinCMOS Technology



TLC32044
1989

1st 14 Bit A/D, D/A And Filter On Same Chip
Advanced LinCMOS Technology*

At Marshall, we have a history of making history in linear technology. Like supporting each new generation from Texas Instruments. Now our line includes TI's family of Advanced Linear components. With higher performance, higher levels of integration and merging of analog and digital signals. So whether your applications

are mainframes and modems or terminals and test equipment, Marshall stocks the TI Linear and Advanced Linear parts you need.

After all, we've been doing it for generations.

Marshall



(*Authorized Locations)
AL Huntsville (205) 881-9235*
AZ Phoenix (602) 496-0290*
Tucson (602) 790-5687*
CA Irvine (714) 458-5311*
Los Angeles (818) 407-4100*
Sacramento (916) 635-9700*

San Diego (619) 578-9600*
San Francisco (408) 942-4600*
CO Denver (303) 451-8383*
CT Connecticut (203) 265-3622*
FL Ft. Lauderdale (305) 877-4880*
Orlando (407) 767-8585*
Tampa (813) 573-1399*

GA Atlanta (404) 923-5750*
IL Chicago (312) 490-0155*
IN Indianapolis (317) 297-0483*
KS Kansas City (913) 492-3121*
MA Boston (617) 658-8811*
MD Maryland (301) 622-1118*
MI Michigan (313) 525-5550*

MN Minneapolis (612) 559-2211*
MO St. Louis (314) 291-4650*
NC Raleigh (919) 878-9882*
NJ N. New Jersey (201) 862-0300*
Philadelphia (609) 234-9100*
NY Binghamton (507) 798-1611*
Long Island (516) 273-2424*

Rochester (716) 235-7820*
OH Cleveland (216) 248-1788*
Dayton (513) 898-4480*
OK Tulsa (918) 622-7151*
OR Portland (503) 644-5050*
PA Philadelphia (609) 234-9100*
Pittsburgh (412) 788-0441*

TX Austin (512) 837-1991*
Dallas (214) 233-5200*
El Paso (915) 593-0706*
Hartford (617) 542-4588*
Houston (713) 865-9000*
San Antonio (512) 734-5100*
UT Salt Lake City (801) 485-1551*

WA Seattle (206) 486-5747*
WI Wisconsin (414) 797-8400*
In Canada: G.S. Marshall Co.
Montreal/Ottawa (514) 694-8142*
Toronto (416) 458-8046*

* For a free sample and information kit of TI's latest family member call (818) 459-5594, while supplies last.

OPEN SYSTEMS::OPEN TOOLS™

MAXIMUM POWER FOR REAL-TIME DEVELOPMENT

Whether over the backplane or network, Heurikon has your VME and Multibus targets. VxWorks • VADSWorks • OS-9 • VRTX • Ada • Unix V.3 • Network solutions • Just a few of the Open Tools™ Heurikon has to speed your application to market. Call now for real-time response.



1-800-356-9602

HEURIKON
CORP
MICROCOMPUTERS FOR INDUSTRY

VxWorks is a trademark of Wind River Systems, Inc. VADSWorks is a trademark of Wind River Systems, Inc. and Verdix Corporation. VRTX is a trademark of Ready Systems, Inc. OS-9 is a trademark of Microware Systems, Inc. Unix is a trademark of AT&T Bell Laboratories, Inc. Multibus is a trademark of Intel Corporation. Open Systems: Open Tools is a trademark of Heurikon Corporation. Open Tools is a trademark of Heurikon Corporation.


CIRCLE NO. 60



The ADSP-2100.

- The ADSP-2100 computes a 1024-point complex FFT in less than 3 ms with a total memory requirement of less than 4k bytes. It also computes a 2×2 D convolution in 1.2 μ s and executes ADPCM in only 68 μ s.
- The ADSP-2100 can access two words of external data every cycle.
- The ADSP-2100 supports zero-overhead loops of any length. So our looped code – which is the easiest to write – is also the fastest.
- The ADSP-2100's two dedicated data address generators can auto-increment/decrement by any offset value, and they have automatic circular buffer wraparound.
- The ADSP-2100 Assembler supports the easiest language in the business. So you code a multiplication/accumulation the same way you'd write the original algorithm. For example, the algebraic $R = R + X*Y$ codes as $MR = MR + MX*MY0$.

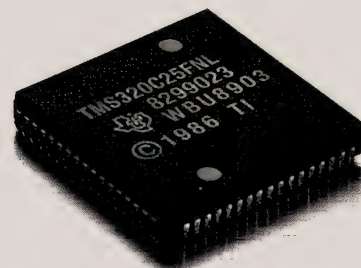Given
enough
time, the
TMS320C25
can do
almost
everything
the
ADSP-2100
can.



The TMS320C25.

- The TMS320C25 takes more than three times as long to compute the same size FFT, while it devours over 47k bytes of memory.¹
- The TMS320C25 is limited to one access of external data every two cycles.
- The only zero-overhead loop the TMS320C25 can execute is one instruction repeated no more than 256 times.
- Circular buffers? The TMS320C25 doesn't support them.
- The TMS320C25 is programmed with 133 mnemonics like SPAC, BGEZ, MACD, XORX, and SBRK. A multiplication/accumulation is coded as $MACD > FF03, -$. While this might not scare the XORX out of you, it's not the easiest thing to debug or maintain.

We're not saying the TMS320C25 is slow. But even if it were twice as efficient as it is now, it'd still be a lot slower at DSP than the ADSP-2100. The fact is, the ADSP-2100 is out in front of the TMS320C25 in performance, readability of code, and development tools.

Just how far out front? Get our free technical booklet and read about it. Or better yet, get an ADSP-2100 sample kit for only \$49.95 and see for yourself. To request either, call DSP Marketing at 1-617-461-3771.



Analog Devices, Inc., One Technology Way, P.O. Box 9106, Norwood, MA 02062-9106; Headquarters: (617) 329-4700; California: (714) 641-9391, (619) 268-4621, (408) 559-2037; Colorado: (719) 590-9952; Maryland: (301) 992-1994; Ohio: (614) 764-8795; Pennsylvania: (215) 643-7790; Texas: (214) 231-5094; Washington: (206) 575-6344; Austria: (222) 885504-0; Belgium: (3) 237 1672; Denmark: (2) 845800; France (1) 4666-25-25; Holland: (1620) 81500; Israel: (052) 911415; Italy: (2) 6883831, (2) 6883832, (2) 6883833; Japan: (3) 263-6826; Sweden: (8) 282740; Switzerland: (22) 31 57 60; United Kingdom: (932) 232222; West Germany: (89) 570050.

¹EDN, "EDN's DSP Benchmarks," September 29, 1988.

Measuring the cost of quality: German engineering at the crossroads



Article and photographs by Gary Legg,
Special Projects Editor

This article is the first in an occasional series about engineering in Europe.

On the Autobahn, traveling from Munich to Regensburg at 170 kilometers an hour, you get a feeling for what German quality is all about. Even at that high speed, the BMW rumbles softly like a large, lithe cat. When a sudden stop is necessary to avoid two cars that have been involved in an accident, braking is fast, smooth, and precise. Later, talking with engineers at Siemens AG, the international electronics giant whose headquarters are in Munich, the German attitude toward quality becomes apparent. It's more than respect; it's almost a reverence.

And yet, as markets become more global and more competitive, that attitude is changing. Increasingly, in order to remain competitive, German engineers speak of shortening product-development times. Again and again, though it seems to go against their nature, they mention "stopping the design" when it's "good enough" and of reducing component costs. More and more, they're concerned with lowering overall costs. Their challenge, of course, is to reduce costs while still keeping quality at

an acceptable level. And for a German, "acceptable level" means "high."

Quality—or reliability, at least—isn't even negotiable for Dr. Alfons Härtl, group leader of airbag electronics for Siemens at the company's automotive-electronics division in Regensburg. Härtl explains that an airbag must fully inflate in 30 milliseconds during an accident, and then it must quickly deflate.



For Dr. Alfons Härtl, group leader of airbag electronics at Siemens AG, product quality isn't negotiable. In many car accidents, airbag deployment can mean the difference between life and death.

The bag must work perfectly when it's needed, and it must never inflate when it's not needed. Still, Härtl says, airbag prices must come down. The use of passive restraints—either airbags or special seat belts—has been mandated for cars sold in the US beginning with 1990 models. Airbags produced in

high volumes are potentially cheaper than passive seat belts, and because several major companies are supplying airbag systems, price competition will be fierce.

In the US, Härtl continues, manufacturing volumes are much higher in the automotive industry (and thus in the automotive-electronics industry) than in Europe. Consequently, reducing the price of each individual component is important.

"They stop the design," he says of some US engineers, "before [German engineers] would say it is finished. There are some [US] products on the market that we would not normally accept." To be competitive, he says, German engineers now have to "reconsider in our minds the design of such products if we want to have success in the US market. We have to think differently and figure out how to stop a design a little bit earlier and bring a product to market in the right

time and at the right price."

Giuliano Visintini, a researcher for Siemens in Munich, concurs with Härtl's assessment of German versus American quality. A native Italian who attended the Technische Universität Wien (Technical University of Vienna) in Austria and is pursuing a doctorate there, Vis-

intini has visited a number of American companies on two trips to the US. "In the US," he says, "engineers are able to get acceptable quality in a very fast time and at a low cost, and then they start something new. In Germany, we work longer and try to get better quality, but at the same time we increase the cost."

Surface-acoustic-wave (SAW) devices, for which Visintini develops simulation models, illustrate his point. Siemens makes superior SAW devices, the researcher says, but they compete with products from other companies that are cheaper. In many companies, he says, "production cost is the first thing and quality is second."

But it isn't simply a desire to keep improving a product that fosters German quality. Often, improvements occur simply as a result of continued, long-term involvement by individuals. Because German engineers change jobs less often than their American counterparts, they frequently have more opportunities to apply their understanding and insight to improvements. On the average, German engineers work for only three employers during an entire career.

In his observations of US companies and engineers, Visintini has noticed what he feels is a detrimental effect of personnel changes on quality. Viable approaches to problems often get discarded in favor of new approaches, he says, simply because a person who best understands an approach leaves for a new job. "If you're in a company for only two years," Visintini says, "you need the first year to understand what your problem is and the second year to solve it. If you stay a third year, you can make improvements, but if you go somewhere else, you can't." Engineers tend to stay at Siemens a long time, Vis-



Giuliano Visintini, an Italian who studied at the University of Vienna, now works for Siemens in Munich developing simulation models for surface-acoustic-wave (SAW) devices. German engineers' concerns for quality, Visintini notes, often result in high development costs.

intini notes; he and his colleagues are able to use and improve software that was first developed 10 years ago, because some of its original developers still work there.

Another factor that encourages quality work, according to Härtl, is that employees at German companies expand their responsibilities across defined job boundaries. Because boundaries between engineering jobs in Germany tend to be blurred, he says, an individual engineer is apt to tackle any problem that becomes apparent, even if it's nominally someone else's problem. At an American aerospace company with which he worked closely for three years as a supplier, Härtl observed just the opposite. There, he says, "Everyone looks for a well defined position and defines his boundaries. When a problem falls between boundaries, no one takes care of it unless it becomes very visible."

To Wolf Jaenecke, a Siemens project manager for telephone switch-

ing systems, quality stems from a basic attitude. The US is market driven, he says, and Germany is quality driven. "Sometimes," Jaenecke comments, "Germans and Americans just don't understand each other."

The difference in outlook became apparent to Jaenecke a few months ago during an in-house seminar for cross-cultural training. In one of the seminar's exercises, Siemens engineers were divided into an American team and a German team and instructed to develop marketing plans for a fictional "fitness monitor," a device to be worn on the wrist like a watch. The German plan resulted in an expensive, high-quality product whose technical merits were to be heralded in advertisements in upscale magazines; the American plan, in contrast, called for an inexpensive product to be sold in discount stores.

The German and American teams even worked in different ways. The Germans' first activity was to organize their team, determining who would lead it and then deciding who would work on each of the tasks. Once they had established a structure, the team members worked individually. The Americans, on the other hand, hardly bothered with structure or individual tasks; their marketing plan was almost entirely the result of brainstorming.

Structure with flexibility

At Siemens, weekly meetings that last from two hours to half a day are obligatory as you move up the chain of engineering management. At lower levels, meetings are less likely to be required, but they're still fairly common. Nevertheless, Jaenecke believes that in one sense, at least, German managers are less rigid than Americans. American managers, he says, sometimes exert undue pressure on

American dream, German reality: a 37½-hour work week and six weeks or more of annual vacation.

schedules to get a product to market on time. In general, however, Jaenecke gives American managers high marks; within American organizations that he has observed, he has admired the clear lines of reporting, the strong group identity, and the overall friendly, casual work atmosphere.

Härtl, who supervises half a dozen or so engineers and is "about 50% engineer" himself, seems anything but rigidly structured. Gregarious and energetic (he was an avid sky diver and hang glider before marriage and children), he favors unscheduled, day-to-day contact over formal meetings. "For me," he says, "it's important to have good relations with the engineers." Härtl also stresses the importance of listening to the engineers' ideas and not forcing his own upon them. The notion that "we're going to do this—no discussion—is the past. It's no longer working."

What does work in Germany, in sharp contrast with the US, is a strong engineers' union. Union achievements, in fact, may contribute to the much praised German technical quality; with a standard 37½-hour work week and six weeks or more of vacation each year, few engineers are likely to be burned out on the job. Not all German engineers belong to a union, but those who do can't be forced to work more than a certain number of hours per day (usually 10) or to work an excessive number of overtime hours per month (usually 20). In some cases, the union may agree to additional overtime, but engineers either get paid extra or get additional vacation time for their efforts. At Siemens, engineers can earn as much as 10 additional vacation days per year for working overtime, thus accruing a total of eight weeks.

Often, however, German engi-

neers donate a certain amount of overtime out of expediency. In most cases, they can receive extra pay or vacation time only if they apply in the preceding month, so in short-term crunches, they may work some additional time without extra pay. Many engineers, especially those who are young and ambitious, may also work overtime voluntarily to advance their projects. At Siemens' Regensburg automotive-electronics division, for example, many engineers have only two or three years of experience. "They want to solve problems," says Härtl. "All you have to do is give them some guidance so that they work in a common direction."

Most German engineers, in fact, are accustomed to being self starters, because their university education requires them to be. A student must pass an examination to get a diploma, but the education program is remarkably unstructured. Attendance isn't required at lectures, for example, and a professor probably


won't even notice a student's absence. There aren't even required textbooks. Härtl, who undertook some graduate study at the State University of New York at Albany, was amazed that exams there were based on specified pages of specified books.

Assessing a new Europe

The flexibility that is so evident in German education, and which appears to be reflected in companies such as Siemens, may be the key to the future for German electronics companies. West Germany is already the dominant economic power in Europe, and it's poised to increase its commercial standing through opportunities that are now appearing in a realigned Eastern Europe. Nevertheless, the country's electronics industry faces a continual struggle against larger American and Japanese industries. And even though the united Europe of 1992 will make pan-European trading easier for its members, the resulting common market will also create opportunities for non-European companies.

Many Japanese companies in particular are well prepared for the changing European marketplace. Long accustomed to selling abroad, they have been quietly gearing up for a post-1992 Europe. Even the one area where German industry has long reigned supreme now faces a Japanese threat: New luxury cars from Japan are competing directly against the classic Mercedes and BMW.

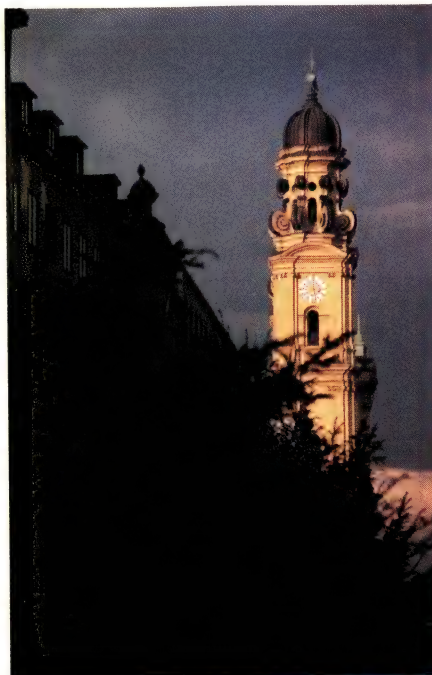A major problem the Germans face, and one that they fully recognize, is that the Japanese are able to produce quality that's "good enough" (or better) at an attractive price. Although many German engineers dispute the notion of Japanese quality being equal to German, they concede that it's nevertheless



Spire of the 17th-century Theatinerkirche in Munich, located near the headquarters of Siemens.

SURFACE MOUNT DIP SWITCH

SURFACE MOUNT



J' OR GULL WING

2 TO 8 POSITION



BIFURCATED SLIDE CONTACTS

LOW PROFILE




SAME SIZE AS AN I.C.

PROVIDED ON REELS




NO HAND LABOR

INFRARED REFLOW

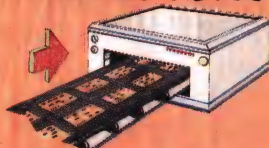

INFRARED REFLOW SOLDERING

REMOVABLE TAPE SEAL

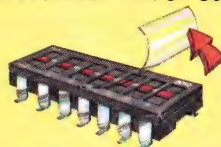

PREVENTS CONTAMINATION

**FOR A FREE SAMPLE
CALL 312-888-7245**

**AMERICAN RESEARCH
& ENGINEERING
1500 EXECUTIVE DR. ELGIN IL 60123**

high and, more significantly, less expensive to produce.

Still, old attitudes die hard. Pride makes it difficult to design a product that's just "good enough" when the traditional design goal has always been "the best." But if engineers at Siemens are typical of those throughout the German electronics industry, then a new attitude is emerging that could make the difference between a future of growth and one of decline.

Quality will remain high, according to the new attitude, and the old reverence for quality certainly won't disappear. Most German engineers will probably continue to strive for quality that's more than just "good enough." The difference now is that, to be more competitive, they may have to settle for less than perfect.

EDN

Article Interest Quotient
(Circle One)


High 506 Medium 507 Low 508

WHAT'S COMING IN EDN

EDN Magazine's February 1, 1990, issue will feature a staff-written Special Report on how add-on buses let you attach small I/O boards to your computer at low cost. Part 3 of the designer's guide to flash-ADC testing concludes this design series with a discussion of the measurements you'll need to fully characterize flash A/D converters. Also, Contributing Editor Bill Travis looks at analog comparators that address TTL and ECL ICs.

Remember to look for our regular departments, and in EDN's February 15 issue, look for coverage of static RAMs.

Intelligent Data Acquisition

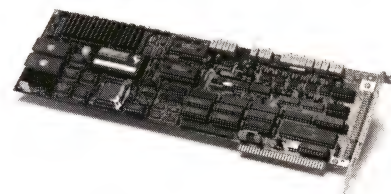

DAP 1200™

Data Acquisition Processor™ for IBM PC/XT/AT/386

Microstar's DAP™ manages the entire data acquisition and control interface inside a PC. Onboard intelligence in the DAP speeds development and increases performance.

- Onboard intelligence: 80186 coprocessor
- Acquires analog and digital inputs to 156,000 samples/seconds
- Buffers and processes input data
- More than 100 commands without programming
- Commands include: Average, Scale, Peak Detection, Logic, Integration, Differentiation, Thermocouple Linearization, Closed Loop Control (PID), Event Detection, Auto-Range, Waveform Generation
- FFT and FIR filtering without programming
- Custom commands may be written in C

DAP 2400™ also includes:

- 10 MHz or 16 MHz 80C186
- 20 MHz DSP56001 for 10 MIPS digital signal processing
- Acquires analog and digital inputs to 235,000 samples/seconds
- Updates analog or digital outputs to 250,000 values/seconds
- Performs 1,024 point complex FFT in under 10 milliseconds
- Executes FIR filters in less than 200 nanoseconds per tap

Call for FREE Demo Diskette

MICROSTAR


LABORATORIES™

(206) 881-4286
2863 152 Ave. N.E.
Redmond, WA 98052
Fax (206) 881-5494

CIRCLE NO. 15

EDN January 18, 1990

SIEMENS

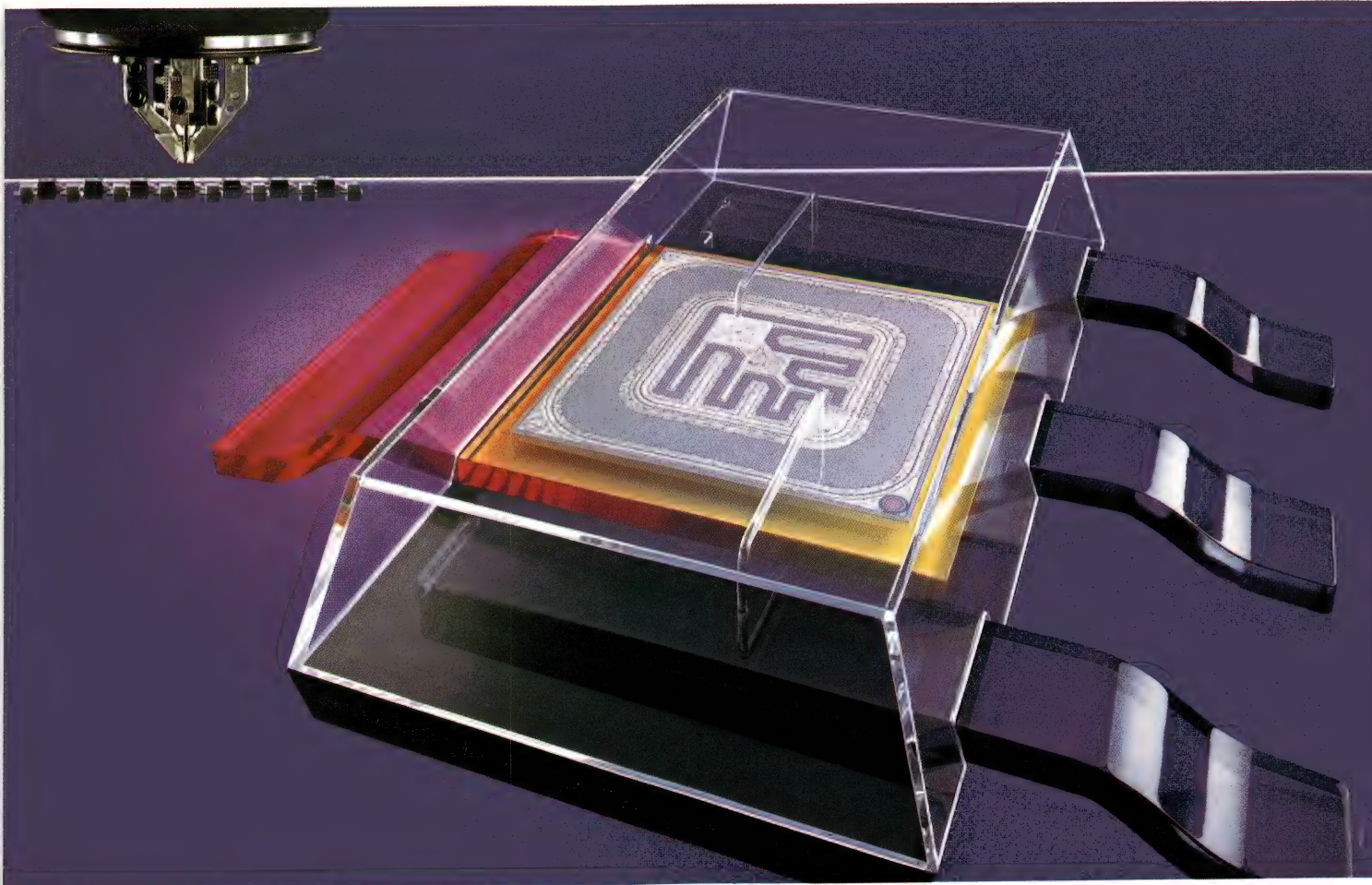

Powerful chips packaged right


**New SMD package SOT 223 –
for power up to 1.5 W**

The new SOT 223 package from Siemens was created with powerful chips in mind. Without any extra cooling it can dissipate up to 1.5 W.

SOT 223 is ideal for all substrates – even epoxy. And you can put it through any kind of soldering process, wave soldering too. The package measures 6.5 by 3.5 by 1.6 mm and is available right away on 12-mm tapes.

SOT 223 comes with a variety of powerful chips, for applications in industrial, automotive, consumer and entertainment electronics.

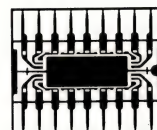For full details by return post write Siemens AG, Infoservice, HL 3206, Postfach 2348, D-8510 Fürth quoting "SOT 223 power package".



**TopTech
Semiconductors
Siemens**

The future is in the cards.




Pick a Star Card IC memory device and something rather magical happens:

A world of possibilities is placed in the palm of your hand.

Holding the Star Card gives you the industry's most complete portable data storage and retrieval system.

Unlike other devices, the Star Card has such features as an optional Card Disk File, a removable storage unit that can input or output data with as many as eight cards instantly. In addition, the Star Card System is available in a wide variety of RAM and ROM versions.

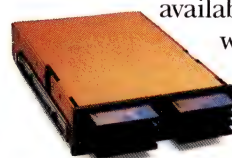ITT Cannon is the only IC memory card manufacturer producing in the United States, with additional production and customer service in Europe and Asia to assure you multi-source



availability worldwide. And the only company that manufactures its own interconnect system, designed specifically for the Star Card, and rated for dependable performance up to 10,000 mating/unmating cycles.

Since the connector is one of the most vital components to your IC memory card system, this kind of performance is critical.

With such reliability, your applications for the Star Card are endless. Virtually any environment where the space is confined, the conditions are rugged or the technology advanced.

The future is yours to design with Star Card—the only complete IC memory card system available. For more information, please contact:

*ITT Cannon Components
1851 East Deere Avenue
P.O. Box 35000
Santa Ana, CA 92705-6500
Telephone: (714) 261-5300
FAX: (714) 757-8301*

CIRCLE NO. 35

ITT Cannon
AN ITT EMC WORLDWIDE COMPANY
Discover our strengths.

TOKEN-RING BOARDS

Standard efficiently allocates channel use



Expect token-ring LANs to become popular beyond IBM installations as designers take advantage of the technical benefits they offer compared with Ethernet networks.

Maury Wright,
Regional Editor


LANs based on the IEEE 802.5 token-ring standard offer system designers a way to implement an extremely reliable network with a guaranteed allocation of network bandwidth to each node. Furthermore, signal collisions on busy networks do not degrade the bandwidth of token-ring LANs. However, most people use the token-ring standard because it is IBM's network of choice. Outside of IBM installations, Ethernet LANs are more popular for office-automation applications. But expect to see more token-ring LANs in nonIBM installations.

Six months ago only a few manufacturers offered token-ring boards for IBM-compatible PCs. After Comdex, the number of manufacturers tripled. Likewise, more companies now offer token-ring cabling systems and multistation access units (MAUs), or wiring centers. Companies have also begun offering token-ring boards for architectures other than the IBM PC/AT and Microchannel Architecture (MCA) buses.

Token-ring LANs transmit data at 4M or 16M bps, but products that support the faster rate are just emerging. The availability of faster token-ring boards will serve to further boost the popularity of the network.

Token-ring- and Ethernet-based LANs differ only at the physical- and data-link layers of the ISO's 7-layer OSI model. For more information on the basics of the token-ring standard, see **box**, "The token-ring standard—IEEE 802.5," and **Ref 1**. Popular network protocols such as TCP/IP (Transmission Control Protocol/Internet Protocol), TOP (Technical and Office Protocol), NetBIOS, and the evolving ISO protocols run on token-ring, Ethernet, and other physical- and data-link layers.

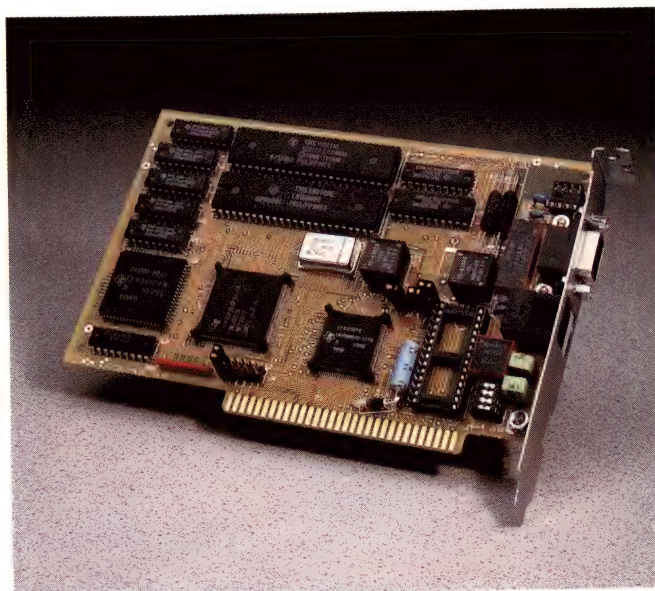The Ethernet technique offers a maximum data-transfer rate of 10M bps but employs a CSMA/CD (carrier sense multiple access with collision detection) scheme to allocate network bandwidth. In a heavily loaded network, collisions waste network bandwidth and, there-



Shielded cable is not required for the TokenCard from Western Digital to achieve its 4M-bps transfer rate. The card is compatible with popular network software such as Netware and NetBIOS.


FAX'n Easy

Designing Group 3 FAX capabilities into a laptop or other portable device has just been made faster and easier. All it takes is the new YM7109, a true single-chip 9600bps FAX MODEM, and FAXSIM™ (FAX Software Integration Module) by Yamaha LSI.

It's in there.

With the YM7109, the solution to your Group 3 FAX design is suddenly no bigger than a 40-pin DIP or 64-pin QFP. And, FAXSIM can cut weeks, even months off your design time. Because FAXSIM allows you to sidestep thick manuals and detailed T.4 or T.30 documentation. There's no need to interpret chip specs and study

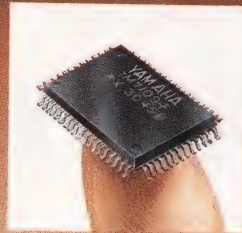the idiosyncrasies of communication protocol or training sequences because we make the source code (developed in Borland Turbo C) available. FAXSIM gives you what you need to beat the competition — a head start.



It takes so little power.

The YM7109 typically consumes only 200mW \pm 25mW, so batteries will last longer. And, the YM7109 needs only one +5V supply. DTMF detect for remote control or security, flag pattern detect, selectable cable equalization, receive signal monitoring, programmable receive level adjust and auto equalization are all in the chip. Of course, the YM7109 meets CCITT V.29, V.27ter, V.21 channel 2, V.23 backward channel, V.21 and Bell 103 standards. It's compatible with industry-standard chip sets and has been tested on both domestic and international telephone lines.

Get the FAX. Just call 1-800-543-7457

YAMAHA® LSI

Systems Technology Division
981 Ridder Park Drive
San Jose, CA 95131
(408) 437-3133 FAX (408) 437-8791

CIRCLE NO. 62

©Yamaha LSI, Systems Technology Division, 1989. Yamaha LSI, Systems Technology Division and the Yamaha logo are registered trademarks of Yamaha Corporation of America. FAXSIM is a trademark of Yamaha Corporation of America. Turbo C is a trademark of Borland Corporation.

805-A-004-89

TECHNOLOGY UPDATE

Token-ring boards


fore, reduce efficiency. The token-ring technique guarantees bandwidth for priority transmissions and, based on its implementation, can fairly allocate bandwidth to all nodes.

In a heavily loaded network application, token-ring networks approach 100% efficiency. Each consecutive node captures the token in turn, and only overhead in the token, addressing, and status bytes wastes bandwidth. Conversely, on a LAN with sparse traffic, the Ethernet technique offers the advantage of immediate access to the channel. Expect to see 16M-bps token-ring LANs providing high-speed backbones between departmental Ethernet LANs due to the different operational characteristics of the two techniques.

The token-ring technique also offers advantages in reliability and maintenance compared with the Ethernet technique. Ethernet LANs employ either bused coaxial cable to connect nodes in a bus wiring scheme or a star-configured twisted-pair medium with active hubs. The bused connections make the initial installation simple but make maintaining and changing the wiring and diagnosing problems difficult.

Token-ring LANs typically employ a star configuration with passive hubs, commonly called MAUs. You can isolate any node on a token-ring network by unplugging a cable or throwing a switch in the wiring closet. Likewise, you can isolate one MAU from a network and therefore isolate a group of nodes for testing. An MAU and the token-ring cabling scheme also let the network self-heal. Relays in MAUs and on interface cards and the shorting connectors used on MAUs and cables automatically eliminate problems with powered-down stations or disconnected cables.

Token-ring interface cards should

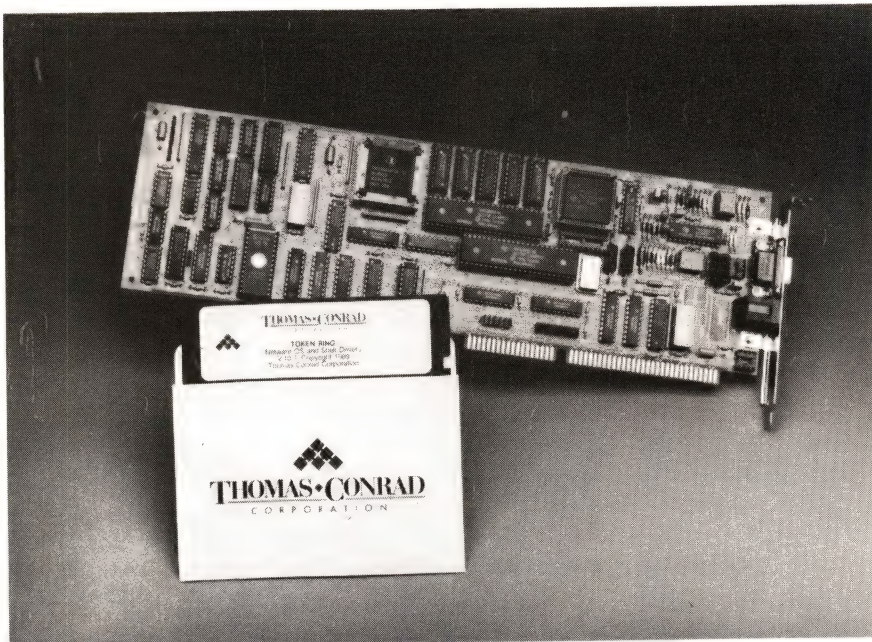

The bus-master capability built into Thomas Conrad's TC4035 token-ring card speeds data transfers across the host IBM PC/AT-compatible bus.

cost less than Ethernet cards. The Ethernet interface requires a digital component to both transmit and receive data and an analog component to detect collisions. A token-ring interface only requires a digital receive and a digital transmit component. The popularity and volume of Ethernet parts, however, make them less costly. A token-ring board for a personal computer typically costs 50 to 100% more than an Ethernet board.

Until recently, you had only a few products to choose from to implement token-ring LANs. IBM offers this LAN for all its system products. In addition, IBM offers its Token-Ring Adapter II (\$650) for IBM PC/XT- and PC/AT-compatible systems and the Token-Ring Adapter II/A (\$750) for MCA-based systems. These boards only support 4M-bps token-ring operation. The Token-Ring Adapter II only transfers data across the host bus in 8-bit increments. Neither product offers bus-master capabilities.

These boards are compatible with IBM's LAN Manager and the

NetBIOS transport protocol. They use a 9-pin DB-type connector, and you can use shielded or unshielded dual twisted-pair cable with them. IBM also offers a 4-channel token-ring MAU that costs \$727 and occupies a 1¾-in.-high space in a 19-in. rack. The IBM MAU includes connectors that short automatically when disconnected.

Western Digital offers lower-priced alternatives to the IBM products. The TokenCard WS costs \$499, includes a 3k-byte static-RAM buffer, and suits applications in NetBIOS or Novell (Provo, UT) Netware workstations. Western Digital also offers the TokenCard, which it recommends for servers and all IBM software environments. It costs \$599 and includes the features of the TokenCard WS as well as a 128k-byte dynamic-RAM buffer and local protocol store. Both cards offer an 8-bit host interface. The cards include both a 9-pin connector and an RJ-11 phone interface.

Gateway Communications also offers lower-priced alternatives to

TECHNOLOGY UPDATE

Token-ring boards

IBM products. The company offers an 8-bit IBM PC-compatible card for \$595 and a 16-bit IBM PC/AT card for \$695. The cards include both connector types and support Netware and NetBIOS.

Racore Computer Products offers an 8-bit token-ring board for only \$399. The company also offers a 16-bit IBM PC/AT board and an MCA board for \$499 each. You can specify a \$70 18k-byte buffer that sup-

ports the downloading of protocol software as an option.

Bus masters speed DMA

Recent announcements centering around boards that support 16M-bps operation and the host-bus-master capability also promise to spur interest in token-ring LANs. Both features will let system designers take advantage of the performance potential of token-ring

networks. Proteon has an IBM PC/AT card that can act as a bus master; several other companies have similar new products.

The IBM PC/AT bus has no provision for bus masters to arbitrate for the bus, but a bus master can take over the bus and perform DMA transfers independently of the mother-board DMA controller. This technique, often called first-party DMA, increases the effective

The token-ring standard—IEEE 802.5

IEEE 802.5 defines a LAN based on token passing and a physical ring that connects the nodes of the network. Each node can only access the network communication channel while holding the token. Therefore, this LAN automatically implements a guaranteed channel-access allocation scheme. This LAN also happens to be the network that IBM offers across its line of computer systems.

The token-ring standard deals with the lowest two layers—the physical layer and the data-link layer—of the ISO OSI model. The physical layer of a network includes connectors, cables, and the transmission of raw bits of data. The data-link layer ensures that the basic transmission facility is free of errors. The medium-access-control (MAC) sublayer corresponds to the upper portion of the physical layer and lower portion of the data-link layer.

Above the MAC sublayer, the token-ring network is compatible with the popular Ethernet (IEEE 802.3) network and with the token bus (IEEE 802.4) used in manufacturing-automation-protocol (MAP) LANs. Token-ring LANs encode data using a differential Manchester scheme and employ twisted-pair wiring. Most installed token-ring LANs transmit data at 4M bps, but expect the newer 16M-bps addition to the standard to grow in popularity.

Token propagates around ring

A 3-byte token circulates around a token-ring LAN. Each LAN node retransmits all bits received with a 1-bit delay. A node captures the token by inverting a bit in the second byte of a free token. The first two bytes of the token then become a start-of-frame sequence. A station that captures the token follows the start-of-frame bytes with addressing information, a data frame or frames, check-sum

bytes, an ending delimiter byte, and a frame-status byte. The node that captures the token and transmits data removes the data bits after they propagate around the ring.

The token-holding time parameter, typically 10 msec, specifies the length of time any node can hold the token. Only the token-holding time limits the size of frames transmitted, and a node can transmit multiple short frames in one token-holding time. After completing a data transfer, the station holding the token places a new token on the ring.

A priority field in the middle byte of the token can prioritize frames. An inactive node must wait to capture the token until the priority of the frame waiting for transmission is higher than the frame priority set in the rotating token. During retransmission, any node can set the priority field in the active token, providing that the node sets the field to a higher-priority status than the token previously held. Thus, the node holding the highest-priority frame reserves the next free token. A station that raises the priority of a token and captures it must lower the priority again when it is done. A system designer can set up a network with a completely fair allocation scheme or one that allocates a large part of the network bandwidth to high-priority traffic.

One node on the LAN acts as a monitor station and supervises the ring, thus setting up a centralized maintenance facility. The monitor ensures that the token isn't lost, handles problems with garbled frames, and drains the ring of orphan frames (frames left on the ring if a transmitting station loses power). On power up or after the failure of a monitor, a node assumes the role of monitor by issuing a claim-token control frame. All stations must be able to

TECHNOLOGY UPDATE

bandwidth of the host bus. The potential for conflict exists, however, if you put several boards that can become bus masters in one system. Single-tasking MS DOS-based systems can typically operate with multiple bus-master cards.

Thomas Conrad Corp offers an IBM PC/AT-compatible board that supports bus mastering. The TC4035 board costs \$595 and operates at 4M bps. It includes Netware

and NetBIOS drivers and is compatible with IBM LAN software. You can also buy MAUs that support as many as 16 stations from Thomas Conrad. The company has reaffirmed its plans to offer a token-ring board for EISA systems, but has no time table to introduce such a product.

In the 16M-bps arena, IBM has been the first to ship products. The company offers the Token-Ring

Network 4/16 Adapter for IBM PC/AT compatibles and the Token-Ring Network 4/16 Adapter/A for MCA-based systems. The boards cost \$895 each and operate at 4M or 16M bps, but they do not have bus-master capabilities.

Although other companies have also introduced 16M-bps products, don't expect volume shipments of such products until about midyear because board manufacturers ha-

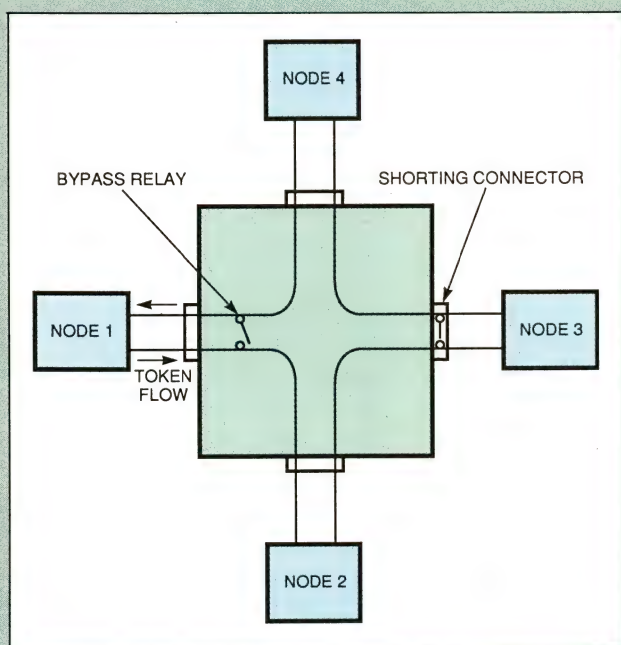


Fig A—An MAU offers fault tolerance by including shorting connectors or relays that isolate a station that powers down. You can buy MAUs that include as many as 48 ports.

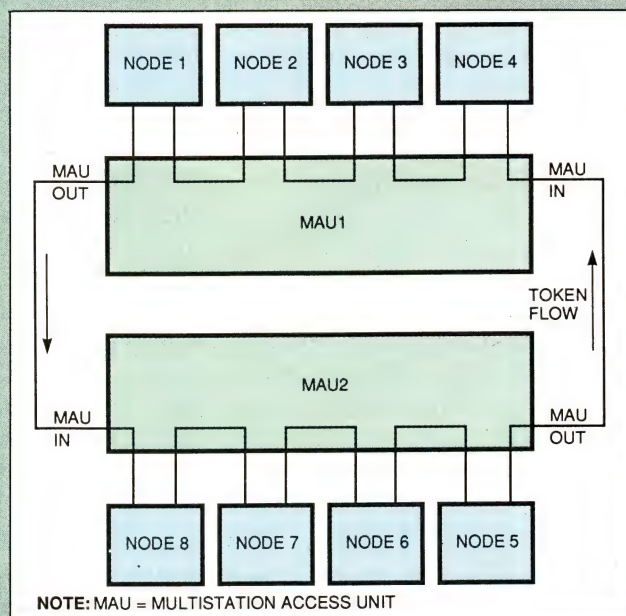


Fig B—MAUs form a physical ring with input and output signals that connect to other units. You can isolate the subnetwork connected to any MAU with switches or by disconnecting the in and out cables.

become monitors. A contention protocol sets up a new monitor if several nodes issue a claim token.

Figs A and B show typical token-ring wiring schemes. Most installations use a star configuration and wiring centers or MAUs (multistation access units) that connect stations. A single cable between an MAU and a station includes two twisted pairs to implement the ring. **Fig B** shows how to connect two or more MAUs.

MAUs typically reside in wiring closets with phone equipment, and they increase the reliability and maintainability of token-ring LANs. MAUs are passive parts and, therefore, are only subject to the mechanical failures of relays, connectors, and wir-

ing. The MAU shown in **Fig A** depicts two different ways to ensure reliability. Some MAUs include a relay dedicated to and powered by each station on the network. The relays bypass a station that is powered down or disconnected. Likewise, token-ring interface cards that reside in stations typically include a bypass relay to short input and output signals on power down. Some MAUs, including those offered by IBM, employ connectors that automatically short input and output signals when disconnected.


TECHNOLOGY UPDATE

Token-ring boards

ven't been able to get token-ring chips. IBM developed a token-ring IC for 16M-bps operation and licensed Texas Instruments to manufacture the IC for sale to other board vendors. Texas Instruments, however, has met delays in producing the IC. The company recently pushed back the schedule for volume shipments until late this quarter. IBM builds its own chips, but virtually every other company's 16M-bps token-ring products use Texas Instruments' IC.

Manufacturers can soon expect other options for token-ring ICs. Toshiba America (Irvine, CA) introduced a 16M-bps IC and should have production volume about the same time Texas Instruments does. The Toshiba IC isn't compatible with Texas Instruments', but it will offer board manufacturers an alternative. In addition, Ungermann-Bass (Santa Clara, CA) offers a 16M-bps token-ring board based on a proprietary chip. However, the company only sells it as part of a bundled network system.

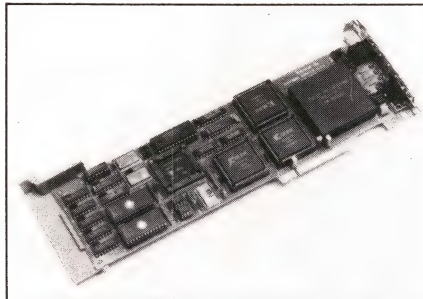Proteon, Lantana Technology, Racore Computer Products, and



Microchannel Architecture-compatible token-ring cards that offer bus-master capability combine with IBM PC/AT-compatible cards in Lantana Technology's Cypress family of token-ring products.

Gateway Communications all recently introduced token-ring boards that support 16M-bps transfers. Furthermore, Western Digital and Thomas Conrad have made it clear that they are simply waiting for ICs before they announce similar products.

Lantana Technology became the first company to introduce an MCA bus-master card for 4M-bps token-ring networks last year. The company recently introduced 16M-bps boards for the IBM PC/AT architecture and MCA. The boards should ship during the first half of the

year. Proteon recently previewed EISA and MCA boards that run at 16M bps but has not announced pricing or availability.

Several recent announcements also point to the growing popularity of token-ring products outside the personal-computer market. Interphase now offers a token-ring board for VMEbus systems. The V/Token Ring 4212 Owl operates at 4M or 16M bps and costs \$3595. The board includes a 68020 μ P that manages the network interface. Furthermore, the board employs the MACSI (Multiple Active Command Software Interface) command interface, which all Interphase I/O boards use. MACSI simplifies the integration of token-ring LANs into systems that use other Interphase communication boards.

You can also buy token-ring interface boards for DEC Q-bus and BI-bus systems. Simpac offers hardware/software combinations that range from \$7900 to \$17,150. The boards support IBM's LAN protocols and TCP/IP.

Finally, MAU units are starting to go high tech. In the past, MAUs

For more information . . .

For more information on the token ring products discussed in this article, circle the appropriate numbers on the Information Retrieval Service card or use EDN's Express Request service. When you contact any of the following manufacturers directly, please let them know you saw their products in EDN.

Gateway Communications Inc
2941 Alton Ave
Irvine, CA 92714
(714) 553-1555
FAX 714-553-1616
Circle No. 699

IBM
Dept 804
900 King St
Rye Brook, NY 10573
(914) 934-4000
Circle No. 700

Interphase Corp
2925 Merrell Rd
Dallas, TX 75229
(214) 350-9000
FAX 214-352-4124
Circle No. 701

Lantana Technology Inc
4393 Viewridge Ave, Suite A
San Diego, CA 92123
(619) 565-6400
FAX 619-565-0798
Circle No. 702

Mux Lab Inc
165 Gravelin St
Laurent, Quebec, Canada, H4T 1R3
(514) 735-2741
FAX 514-735-8057
Circle No. 703

Proteon Inc
2 Technology Dr
Westborough, MA 01581
(508) 898-2800
Circle No. 704

Racore Computer Products Inc
170 Knowles Dr
Los Gatos, CA 95030
(408) 374-8290
FAX 408-374-6653
Circle No. 705

Simpac Associates Inc
9210 Sky Park Ct
San Diego, CA 92123
(619) 565-1865
Circle No. 706

VOTE . . .


Please also use the Information Retrieval Service card to rate this article (circle one):

High Interest 512
Medium Interest 513
Low Interest 514

Thomas Conrad Corp
1908-R Kramer Lane
Austin, TX 78758
(512) 836-1935
FAX 512-836-2840
Circle No. 707

Western Digital Corp
2445 McCabe Way
Irvine, CA 92714
(714) 863-0102
Circle No. 708

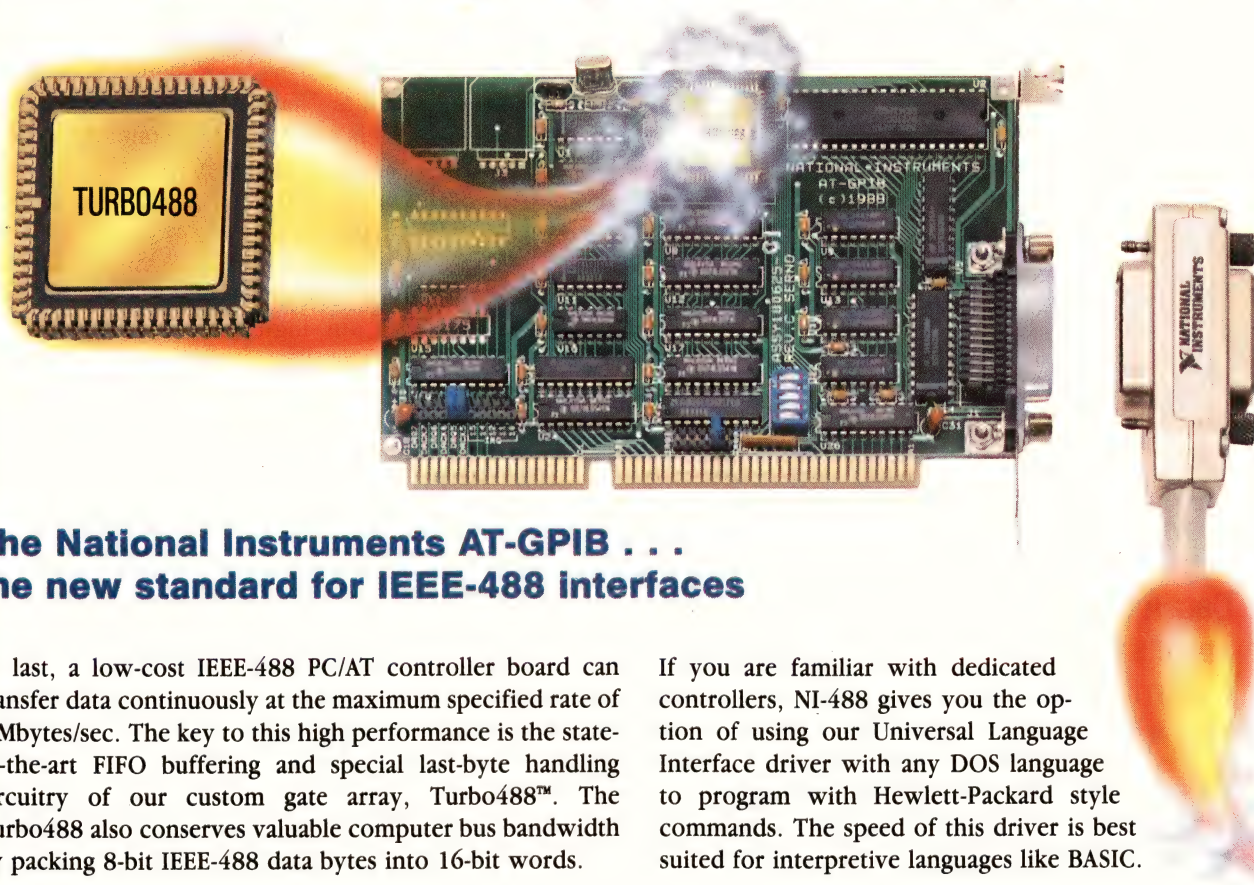Maximum **IEEE-488** Performance for Your High-Speed AT Computer




The National Instruments AT-GPIB . . . the new standard for IEEE-488 interfaces

At last, a low-cost IEEE-488 PC/AT controller board can transfer data continuously at the maximum specified rate of 1 Mbytes/sec. The key to this high performance is the state-of-the-art FIFO buffering and special last-byte handling circuitry of our custom gate array, Turbo488™. The Turbo488 also conserves valuable computer bus bandwidth by packing 8-bit IEEE-488 data bytes into 16-bit words.

By moving time consuming software functions into hardware, the Turbo488 significantly reduces the overhead of a software driver too. The combination of the AT-GPIB and our streamlined software driver gives you the power needed for today's high speed digitizers.

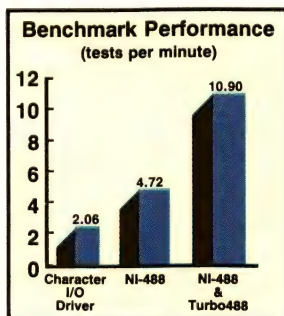The AT-GPIB is controlled by the *de facto* industry standard NI-488 software. NI-488 has high-level routines that transparently handle IEEE-488 protocol and buffered DMA transfers. These routines can be used with any popular language and are the perfect match for the structured, hierarchical programming style preferred by users of high-speed, compiled languages such as C and Pascal.



If you are familiar with dedicated controllers, NI-488 gives you the option of using our Universal Language Interface driver with any DOS language to program with Hewlett-Packard style commands. The speed of this driver is best suited for interpretive languages like BASIC.

Your investment in National Instruments is a sound one. You can still run your existing NI-488 programs yet automatically take full advantage of the Turbo488. If you're just getting started, our interactive instrument control and menu-driven configuration utilities will get you up and running in no time.

Your relationship with National Instruments does not end when you purchase our products. A staff of applications engineers is always a free phone call away. Demand the best IEEE-488 controller available . . . give us a call today at (800) IEEE-488.

Ask for a *FREE* Catalog

Turbo488 technology is standard on our boards for Micro Channel and Macintosh computers



12109 Technology Blvd.
Austin, Texas 78727-6204
(512) 794-0100

NATIONAL INSTRUMENTS OF JAPAN (03) 788-1921 • NATIONAL INSTRUMENTS OF FRANCE (1) 486 53370 •
NATIONAL INSTRUMENTS UNITED KINGDOM (06) 355-23545 • ARGENTINA (1) 46-5776 • AUSTRALIA (2) 736-2888 •
BELGIUM (2) 466-8199 • CANADA (416) 890-2010, (613) 596-9300, (514) 747-7878, (403) 295-0822, (604) 988-2195 •
CHILE (2) 225 3689 • DENMARK (2) 251-122 • FINLAND (0) 372-144 • GREECE (1) 361-1283 • HONG KONG (2) 0426-2707 •
IRELAND (846) 661414, (3) 427-2282 • ISRAEL (3) 324 298 • ITALY (2) 984-91071-2-3 • KOREA (2) 776-5340 •
MEXICO (5) 660-4323 • THE NETHERLANDS (7) 099-6360 • NEW ZEALAND (9) 444-2645 • NORWAY (2) 53-1250 •
PORTUGAL (1) 545-313 • SINGAPORE (65) 336-4713 • SOUTH AFRICA (011) 787-0473 • SPAIN (1) 455-8112 •
SWEDEN (8) 792-1100 • SWITZERLAND (6) 552-8949 • TAIWAN/THE REPUBLIC OF CHINA (02) 703-6280 •
THAILAND (2) 234-9330 • WEST GERMANY (89) 80-7081

See Us at ATE Booth #108

CIRCLE NO. 63

AT YOUR COMMAND.



Data Acquisition and Instrument Control at Your Fingertips

With the CEC genie your wishes come true. You can control any IEEE-488 (HP-IB, GP-IB) instrument, printer, or plotter from your PC. CEC's plug-in cards come with a software library of example programs and utilities that let you spend more time solving problems than programming. CEC provides software support for BASIC, Pascal, C, and FORTRAN.

If your wish is for a custom program, CEC also offers software that writes '488 programs.



Simply pop up our software over your program editor and choose a control function or library for your instrument. Code is automatically generated from your choices. Press a key and the magic begins.

The code appears where you want it in your program.

Now, make your wishes come true by calling 800-234-4232 for your FREE demo disk.



Capital Equipment Corp.

99 South Bedford Street
Burlington, MA 01803
Tel: 617-273-1818 Fax: 617-273-9057

CIRCLE NO. 6

EDN INFO CARDS

DONNA PONO (617) 558-4282

THE 2¢ SOLUTION

EDN Magazine
Edition
News
Edition

A Partnership in Power and Prestige Worldwide

UPDATE

Token-ring boards

included little more than connectors and wiring, but now you can buy units that have status LEDs and relays powered by connected nodes. Companies have also begun to offer units that surpass IBM's 4-node capability.

Mux Lab, for example, offers a 16-node unit that fits in the same 1³/₄-in.-high rack as IBM's 4-node MAU. The company plans to add a 48-node unit that stands 3¹/₂-in. high by the end of the first quarter of this year. The 16-node device sells for \$2590; the 48-node unit will cost \$7500. The Mux Lab products include a shorting relay dedicated to each node and status LEDs. The units also have trunk-routing switches and employ RJ11 or RJ45 connectors.

IBM's products require shielded wiring for 16M-bps operation, but for \$50 Mux Lab will sell you a signal conditioner that plugs into an IBM token-ring card and lets you use unshielded phone wire for 16M-bps needs. For customers who own IBM MAUs, the company offers signal conditioners for the interface between an MAU and an unshielded twisted-pair cable for \$90.

Expect the companies that offer 16M-bps cards to include similar signal-conditioning capabilities. By midyear, such cards will be readily available for use with unshielded cable, and the token-ring alternative will emerge from its IBM shadow to claim its place as a legitimate choice for all office networks.

EDN

References

1. Tanenbaum, Andrew, *Computer Networks*, Prentice-Hall, Englewood Cliffs, NJ, 1988.

Article Interest Quotient
(Circle One)

High 512 Medium 513 Low 514

**"CERTAINLY, OUR
DMMs GIVE YOU ACCURATE
READINGS. THAT'S A GIVEN.
BUT THERE'S MORE TO
THEM THAN MEETS THE EYE.
DROP ME A NOTE AND
I'LL SHOW YOU."**

Joseph F. Keithley, Chairman

Joseph F. Keithley

SEE FOR YOURSELF.

From the outside they may look like your standard digital multimeters. They're not. Keithley doesn't make standard instruments. Quality — that's what we're known for. And that's a given with these DMMs.

They're designed, engineered, built to give you more features, more value. And as a result, more performance benefits at less cost than other DMMs.

Put them on your bench or in an automated test system. They'll give you 100pA and 100nV sensitivity. Reading rates up to one million per second. Memory


to store readings. And even the portable units have automatic calibration over the IEEE bus.

And anytime you want assistance, make one phone call and you'll get the answers you need from our Applications Department. This dedicated staff of engineers has the experience to help you with equipment selection and test system design.

Drop us a note at 28775 Aurora Road, Cleveland, Ohio 44139. Or call 1-800-552-1115, Ext. 394, for all the facts. You'll see what you've been missing.



KEITHLEY INSTRUMENTS

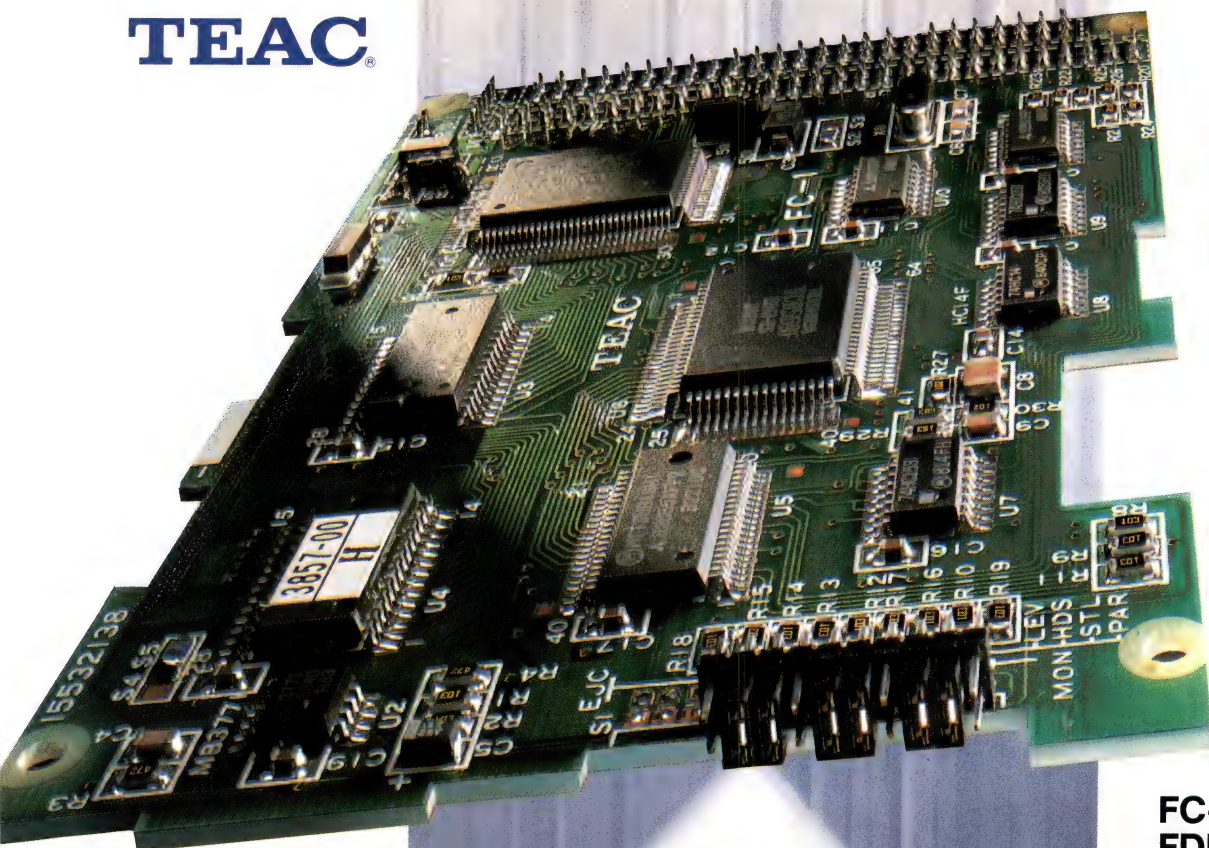TEAC

FC-1
FDD SCSI Interface
Controller

The FC-1: A Fast and Flexible SCSI FDD Controller

The Easy Way to Make Your Floppy Disk Drives Intelligent

An FC-1, small enough to fit inside a 3.5" FDD, has the intelligence to handle device-independent control of 3.5 and 5¼" FDDs for the host computer. At its best with 4MB perpendicular recording method drives like the TEAC FD-235J, and equally happy with formats down to 0.5MB, it is compact, lightweight, and competitively priced. Also offering expansibility and reduced host loads, the FC-1 is ideal for the widest possible range of applications.

TEAC FDDs with built-in FC-1 SCSI controllers, including the FD-235HS and FD-235JS, are also available.

CIRCLE NO. 40



FD-235J
3.5" Micro Floppy Disk Drive

TEAC CORPORATION 3-7-3 NAKA-CHO, MUSASHINO, TOKYO, JAPAN TEL: (0422)52-5041 TLX: 2822451 FAX: (0422)55-2554

■Hong Kong, Nissei Sangyo Co., Ltd. Hong Kong Branch Tel: 3-343441-6; KARIN ELECTRONIC SUPPLIES CO., LTD. Tel: 3-898252 ■Singapore, NISSEI ELECTRONICS, LTD. SINGAPORE BRANCH OFFICE Tel: 2357900; UAC SINGAPORE REP. OFFICE Tel: 2922608 ■New Zealand, DATAMATIC NETWORKS LIMITED Tel: 09-444-0760 ■Australia, AWA DISTRIBUTION Tel: 02-888-9000 ■Indonesia, CHUGAI BOYEKI CO., LTD. Tel: 370824 ■Philippines, COMPEX INTERNATIONAL INC. Tel: 213020 ■India, Priya Electronics & Chemicals Limited Tel: 2863611 ■Kuwait, Bader Al Mulla & Brothers Co. W.L.L. Tel: 2423250 ■United Kingdom, TEKDATA LIMITED Tel: 0782577677; Data Peripherals (UK) Limited Tel: 078557050 ■F.R. Germany, nbn Elektronik GmbH Tel: 08152/390 ■Austria, nbn Elektronik GmbH Tel: 0316/40 28 05 ■Netherlands, SIMAC DATA B.V. Tel: 040-582933 ■Belgium & Luxembourg, SIMAC ELECTRONICS SPRL/BVBA Tel: 02/252.36.90 ■France, TEKELEC AIRTRONIC S.A. Tel: (1)4534-75-35 ■Italy, A.E.S.S.E. S.p.A. Tel: 02/54.64.741 ■Spain, ATAIO INSTRUMENTOS S.A. Tel: 733 05 62 ■Portugal, BASF PORTUGUESA LDA. Tel: (351) 1-562511 ■Switzerland, WENGER PERIPHERALS AG Tel: 01/830 75 55 ■Denmark, Dansk Binær Teknik A/S Tel: 03/66 20 20 ■Sweden, MACROTEC AB Tel: 08-733 02 20 ■Norway, SCANTELE A/S Tel: (02)65 69 20 ■Finland, INSTRUMENTARIUM CORPORATION Tel: 90-528 4338

*If no distributor listed above is in your area, please contact us directly for further details about our products.

OPTICAL-CHARACTER-RECOGNITION SOFTWARE

Inexpensive software reads printed material



Powerful personal computers run software that transforms a raw bit map, derived from an optical scan of a page of printed text, into an ASCII file.

*Charles H Small,
Senior Editor*

In the aftermath of the computer revolution it's clear that touch typists—not the meek—shall inherit the Earth. If you're one of the unfortunate hunt-and-peckers who find that keying in text or data is a burdensome chore, take heart. You can now let your personal computer do this onerous job for you. Recently introduced, inexpensive software packages can transform the output of high-resolution optical scanners into an ASCII file.

Optical-character recognition (OCR) offers the promise of painless, completely accurate data entry from printed material directly into your computer. Despite all the nifty things that imaginative people suggest you *could* do with your personal computer, EDN's research reveals that engineers devote a major portion of their personal computer time to plain old word processing and spreadsheets.

Engineers find themselves having to enter bits and pieces of text and data into their word processors and spreadsheets from a variety of sources. These sources include spec sheets, price lists, printouts from mainframe computers, official and voluntary standards documents, as well as reports from manufacturing, quality assurance, and field service. This list isn't exhaustive. No doubt each engineer could think of many more such sources.

Heretofore, OCR equipment was both expensive and not particularly useful. Early OCR equipment couldn't read just any printed material; you had to prepare your copy on special paper and use a special IBM Selectric typewriter ball. Even the slightest smudge or mistrike could confuse the computer. Later, special, computer-readable character sets (or fonts) came along—the most recognizable being the MR11 (Fig 1).

Such fonts are still very much with us. And you can get hand-held scanners with which to read them from makers such as Caere Corp. You can design these handheld scanners into applications where you might alternatively use a bar-code or a magnetic-strip reader.

Although high-resolution scanning hardware has been available for some time, low-cost OCR systems that can read an entire page have not. That's be-



The OmniScan omnifont OCR software from Caere Corp can translate the output of handheld scanners as well as conventional page scanners.

PACK MORE PERFORMANCE INTO YOUR SYSTEM...



With PlanarPak™ Microwave Surface Mount Components... DC to 18 GHz

Your next microwave system needs more functions in less space. You're ready for the advantages of microwave surface mount technology (SMT)... Avantek's PlanarPak™ components. You'll get smaller size†... lighter weight... increased board density... and, circuits on both sides of the board. Your design team can put the system you need together faster... with lower risk and more control, with off-the-shelf PlanarPak components. More than thirty different high performance

PlanarPak components provide DC to 18 GHz coverage. All are 50 ohm matched for easy microstrip integration. Avantek offers the widest range of microwave functions in surface mount packages —

- Amplifiers — .01 to 18.0 GHz
 - Attenuators — .1 to 2.0 GHz
 - Detectors — .02 to 6.0 GHz
 - Limiting Amplifiers — .01 to 1.0 GHz
 - Mixers — .05 to 2.5 GHz
 - Switches — .01 to 2.0 GHz
- with more functions on the way. PlanarPak components make complete surface mount microwave systems a reality.

Designed for High Volume Applications in Demanding Environments

These hermetically sealed, thin-film MIC components are designed for rugged operating environments... missiles... smart munitions... expendables... and RPVs. Wherever size and performance are critical.

PlanarPak products are ideal for automated manufacturing. A proven technology... in volume production today at Avantek.

SMT Application Assistance and Off- the-Shelf Delivery...

Avantek, the world leader in microwave SMT, offers a comprehensive selection of literature, test fixtures, and technical assistance. And, all PlanarPak components are in stock at your local Avantek distributor for immediate delivery. Contact us today to receive PlanarPak products literature and the name and address of your local Avantek distributor.

†Three sizes: .25 x .25 x .11 in, .375 x .375 x .15 in and .4 x .8 x .15 in

Avantek Regional Offices

North America


Eastern: (301) 381-2600

Central: (708) 358-8963

Western: (805) 373-3870

Europe: (44) 276-685753

Asia: (01) (408) 943-5484

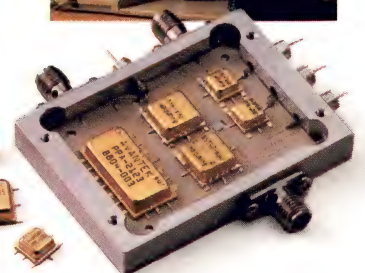

TECHNOLOGY UPDATE

Optical-character-recognition software

cause the real trick to reading fonts not expressly designed for computer input is lots of processing power and memory capacity in the computer, which mulls over the scanner's output.


Reading isn't easy

Consider the magnitude of the task the computer faces. First, a high-resolution, 300-dpi scanner will produce a 1M- to 2M-byte data file from a single 8×11-in. page.

Also consider that the conservative estimate of the number of commonly encountered fonts is 2000. And, if the sheer number of different fonts isn't enough of a problem, typesetters have their own little tricks that further complicate the OCR software's job. In addition to proportional spacing, typesetters execute a process called kerning to slightly squeeze or expand the letters on a given line to make a column's margins exactly even. Thus, on a given page, even if the page's printing uses only one font, not all of the letters on the page will be exactly the same shape.

But if you look closely at printed material, such as the copy of EDN you're reading now, you will become aware that typesetters and magazine designers use a variety of fonts and character sizes on a given page to dress it up. And, while typewritten material generally has only one large column per page, typeset material often has multiple columns that snake hither and yon around the page. We've all had the experience of getting lost while trying to follow the column breaks around a badly laid-out page. OCR software can find such pages equally confusing.

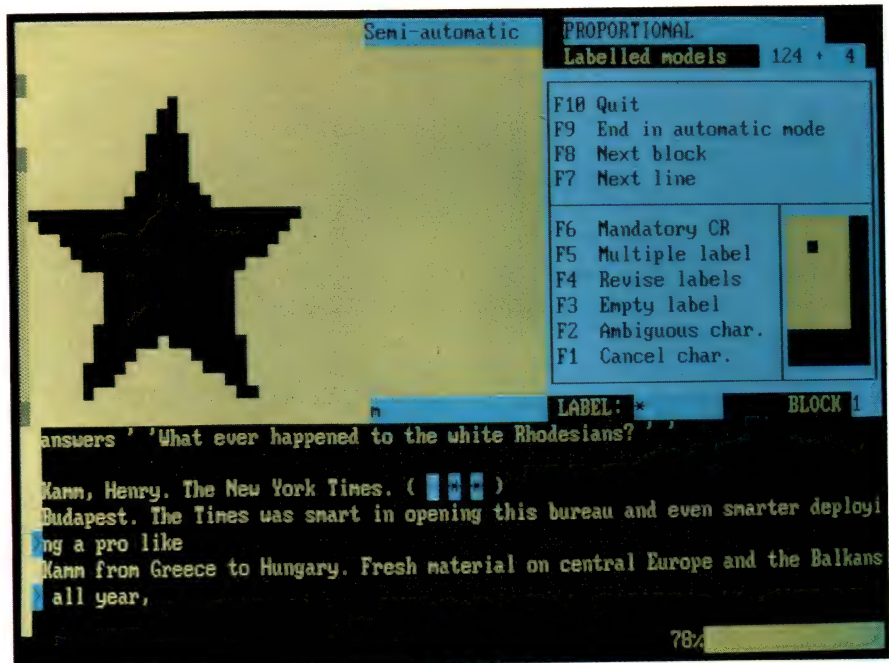To be useful to engineers, OCR software also has to be able to read tabular material. And with the advent of the laser printer and desktop-publishing systems, typewritten documents having nothing but



The ReadStar Express OCR program combines omnifont scanning with optional training sessions to allow the program to recognize special characters.

simple, consistent letters and no line drawings, tables, or photos are fast disappearing. Virtually anyone can now produce documents that have a variety of typefaces and type sizes, along with a rich variety of tables and artwork.

Additionally, OCR software has

to contend with a lot of artifacts on the page that are *not* text. Magazine pages and spec sheets have photographs and line drawings; they also have other embellishments and decorations (called dingbats, believe it or not). Depending on a font's design, OCR software can have trouble separating letters because between 10 and 50% of the letters in a given font can be joined. What's more, the ASCII character set has far fewer total characters available than do fonts for typeset material. For example, typeset material uses different characters for opening and closing quotes where the ASCII character set has only one quote character. Typeset material uses different characters for minus signs, dashes, and hyphens where, again, ASCII has only one.

You should not be surprised to learn that effective, low-cost OCR software awaited the arrival of the more powerful versions of the IBM PC and the Macintosh.

Right now, inexpensive OCR software for personal computers

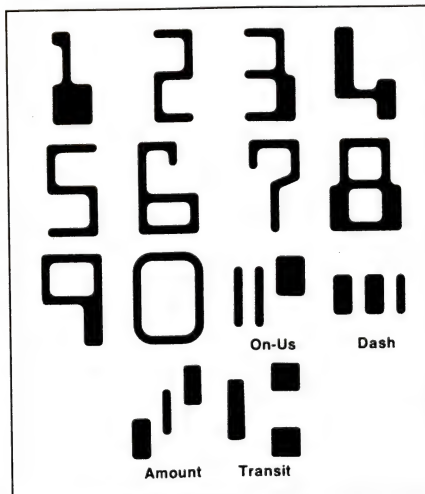


Fig 1—Computers have an easy time reading specially designed characters such as these. Recognizing printed characters such as those used in this magazine is much harder to do.

TECHNOLOGY UPDATE

Optical-character-recognition software

breaks down into two basic categories: "omnifont" software, which automatically recognizes any font, and "trainable" software, which you must train to recognize each new font as the software encounters it.


Historically, OCR software progressed from programs that recognized only a few, preprogrammed, computer-readable fonts, to trainable programs with which you could develop a library of fonts that the software could read. Using a trainable OCR program, you need to spend 5 to 15 minutes going over a page or two of text interactively before the program will be able to read the new font reliably. Consequently, trainable OCR programs prove bothersome for some short documents or uncommon fonts. To make OCR programs useful for even a single page and to reduce the headaches associated with managing a library of fonts, vendors developed omnifont OCR software.

Companies keep secrets

The inner workings of OCR software would probably be fascinating to learn about—if only the vendors would reveal them. Alas, they regard their algorithms as proprietary company secrets and will not discuss them in public.

According to one OCR-software maker, Inovatic, first-generation OCR software uses matrix-matching techniques to recognize characters. First-generation OCR software compares the bit map of a character, pixel by pixel, with a table of pre-defined matrices, looking for a match. Because two scans of the same image rarely yield identical bit maps, matrix-matching OCR software must have a relatively high tolerance for near matches. After all, the files comprise millions of bits.

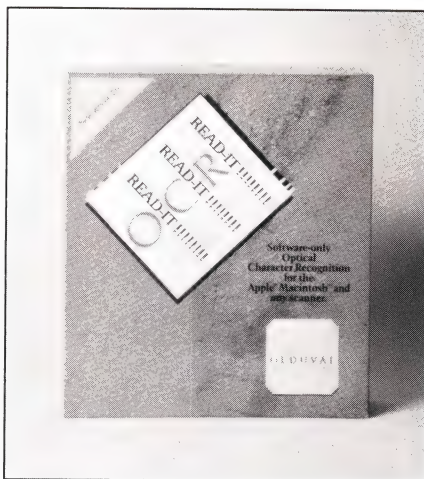This requirement results in a degradation of accuracy as the fine information required to discrimi-



The Read-It! OCR software from Olduvai Corp comes with many common fonts already entered into its libraries.

nate between innately similar characters such as a "b" and a "6" often gets lost within wide tolerance limits. The associated matrices of the more complex fonts must perforce become more complicated; therefore both recognition speed and accuracy tend to fall when these fonts are used.

The next step for OCR software was the development of feature-extraction methods. Feature-extraction software uses a set of rules about characters based on the char-

acters' appearance. A character comprising an arc attached to the top and mid-point of a vertical line, for example, could be a "p" or a "P."

The task of finding unique descriptions for all characters and then translating the descriptions into terms a computer can understand can be monumental. Try, for example, to describe the difference between "5" and "S" while keeping in mind that your description must apply to a wide variety of fonts. And consider that concepts such as "straight" and "vertical" can often be ambiguous when dealing with 300-dpi representations of pages that are not always laid perfectly squarely on the scanner.

Your instruction must also be able to distinguish between serifs (the decorative flourishes found on the endpoints of many characters), and truly distinguishing features. Handling all possible exceptions often results in a large feature-extraction rule base, which in turn consumes more memory than most PCs have.

Inovatic claims to use proprietary "elastic" mathematical models in its "third-generation" OCR software, which it considers to be a better



The Datacopy AccuText OCR program recognizes indents, tabs, margins, returns, and other page-formatting commands. The Xerox Imaging Systems' program inserts the appropriate codes for these page-formatting commands into the ASCII file it passes on to the computer's word-processing program.



The program in a switch.

Introducing Vivisun Series 2000, the programmable display pushbutton system that interfaces the operator with the host computer. The user friendly LED dot-matrix displays can display any graphics or alpha-numerics and are available in green, red or amber. They can efficiently guide the operator through any complex sequence, such as a checklist, with no errors and no wasted time.

They also simplify operator training as well as control panel design. Four Vivisun Series 2000

switches can replace 50 or more dedicated switches and the wiring that goes with them. In short, Vivisun Series 2000 gives you more control over everything including your costs.

Contact us today.



AEROSPACE OPTICS INC.

3201 Sandy Lane, Fort Worth, Texas 76112

(817) 451-1141 • Telex 75-8461 • Fax (817) 654-3405

SERIES
VIVISUN 2000™



Programmable display switches. Making the complex simple.

TECHNOLOGY UPDATE

Optical-character-recognition software

method of character extraction.

Presently, four vendors have low-cost OCR software. The software packages differ in two ways: some are omnifont while some are trainable, and some require an add-in board while some do not. Most claim to be able to digest the output of virtually all commercially available, high-resolution scanners.

Caere Corp claims its OmniScan omnifont OCR software can translate 40 to 115 cps from a consistent font. The characters being read can range in size from 8 to 72 points (one point $\approx 1/72$ in.). In addition to automatically recognizing any font, OmniScan can separate drawings from text and read tabular material. You can also set it up to ignore certain portions of a page and to follow column breaks.

The software can accept files

from fax modems; it produces files compatible with Lotus 1-2-3, Microsoft Excell, and Ashton-Tate dBASE, as well as files for most common word processors.

OmniScan requires an IBM PC with 640k bytes of RAM, a hard disk, and MS-DOS 3.1 or later. It requires a mouse and runs under Microsoft's Windows 2.0 or later. The package for 80286-based PCs comes with a Motorola 68020-based add-in board, which has 2M bytes of RAM. The version for 80386-based PCs requires no add-in board and runs under either MS-DOS or OS/2.

Recently announced add-ons for OmniScan claim to enhance its accuracy and expand its usefulness. OmniSpell is a \$99 spell checker that goes over the output of OmniScan looking for spelling errors. Omni-

Spell has dictionaries for 10 popular Indo-European languages and Finnish.

OmniDraft also costs \$99 and can make sense of the otherwise hard-to-scan output from dot-matrix, draft-quality printers. OmniTrace costs \$150 and it converts bit-mapped artwork into PostScript-compatible artwork files. With OmniTrace, you can scan both text and drawings and submit the converted files to the PostScript desktop-publishing program.

Caere offers package deals that include software, an add-in board (as needed), and a Cannon scanner. Prices for 80286 PCs range from \$3185 to \$4380, depending on the scanner selected, and \$2085 to \$3280 for 80386 PCs.

Inovatic, on the other hand, does not package scanners with its Read-

Sealed Process Compatible Switches

■ Toggle ■ Rocker ■ Pushbutton ■ DIP

- Sealed to eliminate the intrusion of flux during cleaning processes
- O-Ring actuator seal, epoxy terminal seal and tape DIP seal
- Withstands vapor phase and infrared reflow soldering temperatures

Call or write for literature and a free sample
(617) 964-6400
FAX (617) 527-3062.



C&K Components, Inc.
15 Riverdale Avenue
Newton, MA 02158

The Primary Source Worldwide®.

Introducing 750kHz VME data acquisition.



— Fred Molinari, President

Once again, we've left everyone in the dust.

Plug in one of our new DT1492 Series boards, and your Sun or VMEbus computer can capture and output data at an astonishing 750kHz. Which makes our VMEbus boards ideal for those really tough applications that require you to track lots of data—fast.

More surprising, though, is the flexibility you get with the DT1492 Series. 9 different high performance models are available.

Each features onboard memory for gap-free data collection at high speeds. Flexible channel and gain selection, deglitched DACs, an external trigger, pacer clock, and 16 digital I/O lines are standard features too.

As you might expect, DT1492 models can perform A/D, D/A, and digital I/O functions simultaneously! With our

DT1498, you can even collect data from up to 4 inputs simultaneously.

When it comes to data acquisition speed and accuracy, we finish first. To raise your speed limits, call today.

Call (508) 481-3700
In Canada, call (800) 268-0427

FREE 1990 Data Acquisition Handbook.



Model	Channels	Resolution bits	Gain	Throughput kHz	Analog Output Chls	Throughput kHz	Digital I/O
DT1492	16SE/8DI	12	1, 2, 4, 8	40	2	130/DAC	16
DT1492-F	16SE	12	1, 2, 4, 8	150	2	130/DAC	16
DT1492-F	8DI	12	1, 2, 4, 8	150	2	130/DAC	16
DT1492-G	16SE	12	1, 2, 4, 8	250	2	130/DAC	16
DT1492-G	8DI	12	1, 2, 4, 8	250	2	130/DAC	16
DT1492-L	4DI	12	1	750	2	130/DAC	16
DT1495	16SE/8DI	12	1, 10, 100, 500	40/2.5	2	130/DAC	16
DT1497	4DI	16	1	100	2	130/DAC	16
DT1498	4SE(SS&H)	12	1	100	2	130/DAC	16

DATA TRANSLATION®

World Headquarters: Data Translation, Inc., 100 Locke Drive, Marlboro, MA 01752-1192 USA (508) 481-3700 Tlx 951646

United Kingdom Headquarters: Data Translation Ltd., The Mulberry Business Park, Wokingham, Berkshire RG11 2QJ U.K. (0734) 793838 Tlx 94011914

West Germany Headquarters: Data Translation GmbH, Stuttgarter Strasse 66, 7120 Bietigheim-Bissingen, West Germany 07142-54025

International Sales Offices: Australia (2) 662-4255; Belgium (2) 466-8199; Canada (416) 625-1907; China (1) 868-721 x4017; Denmark (42) 274511; Finland (0) 372144; France (1) 69077802; Greece (1) 361-4300; Hong Kong (5) 448963; India (22) 23-1040; Israel (52) 545685; Italy (2) 824701; Japan (3) 502-5550, (3) 348-8301, (3) 555-1111; Korea (2) 756-9954; Netherlands (70) 99-6360; New Zealand (64) 9-545313; Norway (2) 53 12 50; Portugal (1) 545313; Singapore (65) 7797621; South Africa (12) 8037680/93; Spain (1) 455-8112; Sweden (8) 761-7820; Switzerland (1) 723-1410; Taiwan (2) 702-0405.

Data Translation is a registered trademark of Data Translation, Inc. All other trademarks and registered trademarks are the property of their respective holders.

TECHNOLOGY UPDATE

Optical-character-recognition software

Star Express omnifont OCR software. Nor does it require an add-in board. The \$995 program, unlike other OCR software, first compresses the scanner's output down from a megabyte-range file into a hundred or so "signs"—to use the term fashionable among semioticians.

As a result of this compression, ReadStar Express can run on 80286-based PCs without an add-in processor board because the compressed page file does not overwhelm such PCs' 640k-byte memories. Inovatic does not quote a character-conversion rate for its program.

The program automatically differentiates between text, graphics, headlines, and multiple columns. It can also recognize tables and automatically suppress images and lo-

gos. One minor detail: You can supplement the program's automatic analysis of a page with a manual training session.


Olduvai Corp has two versions of its Read-It! OCR software: a \$195 version for hand scanners and a \$495 version for page scanners. The trainable software runs on both IBM PCs and Macintoshes. The IBM edition runs under Microsoft's Windows Graphical User Interface (GUI).

The programs come with many common fonts already entered into libraries. It takes about 15 minutes for you to train the programs to recognize another font, the company claims. The programs can handle from 6- to 48-point type. The hand-held-scanner version doesn't just recognize special, computer-readable fonts; you can use it, in con-

junction with a hand-held scanner, to enter text and data from virtually any source. You can also set it up to read tables.

The software can read standard files from many common hand-held scanners, including the Logitech ScanMan, DFI, and The Complete PC scanner. It also works with page scanners such as those from Canon/Princeton, Microtek, and Hewlett-Packard's Scanjet. The text files it produces are compatible with most word processors, database programs, spreadsheets, and desktop-publishing systems. The program will run on an 80286-based IBM PC without an add-in processor board.

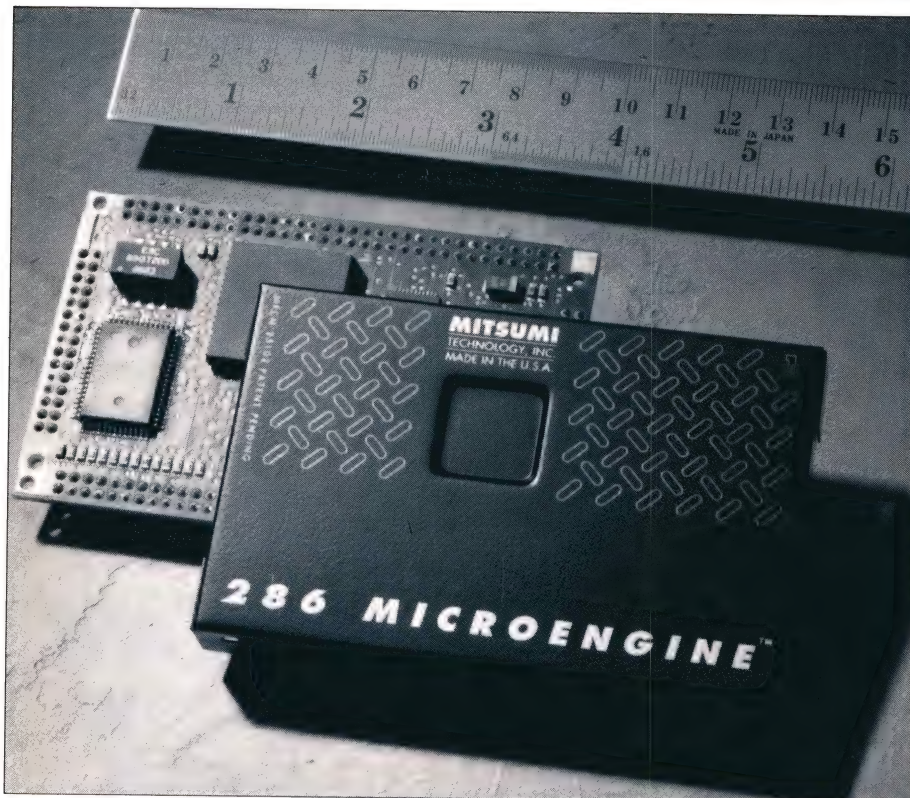Datacopy AccuText software from Xerox Imaging Systems (formed by a merger of Datacopy and Kurzweil Computer Products), purportedly brings artificial-intelli-



THE 286 MICROENGINE™ measures 4 by 2.6 by 0.5 inches, weighs 5 oz. and uses less than 3 watts, yet it includes the electronic equivalent to the original IBM PC AT. An AWARD™ BIOS and access to all AT bus signals guarantee complete compatibility. IBM PC/XT/AT is a registered trademark of International Business Machines Corporation.

286 MICROENGINE™

PACKED WITH POWER

PC AT IN A POCKET

THE 286 MICROENGINE IS A MINIATURIZED AT-COMPATIBLE COMPUTER MODULE INCLUDING:


- 10MHz 286 • 512K RAM
- ROM BIOS • AT BUS
- KEYBOARD CONTROLLER
- REAL TIME CLOCK

FOR
INFORMATION CALL:
1 408 980-5400
1 800 736-7736

MITSUMI
TECHNOLOGY, INC.

3295 Scott Boulevard
Santa Clara, CA 95054

KILL THE NOISE WITH

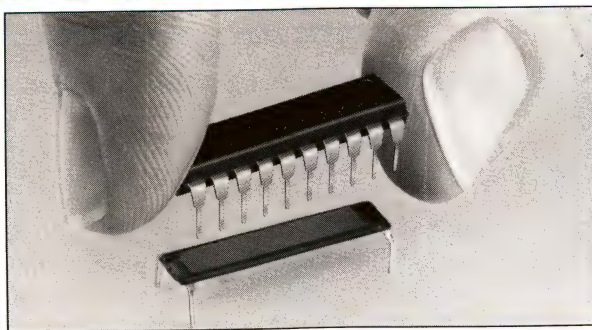

MICRO/Q® CAPACITORS

Reduce voltage noise spikes in ICs by as much as a factor of 10. Without redesign. Without using additional space.

With Micro/Q® decoupling capacitors from Rogers. Micro/Q capacitors mount under the IC. Share mounting holes. To improve noise suppression where it's most effective—at the source.

Best of all, Micro/Q capacitors kill the noise without killing a lot of valuable time.

Micro/Q® is a registered trademark of Rogers Corporation. Another MEKTRON® Interconnection Product.

For all the facts, including the Micro/Q capacitor track record for noise-reduction in dynamic RAMs, EPROMs, static RAMs and boards that need EMI/RFI fix, call a Rogers' Product Specialist today at (602) 967-0624 (Fax 602-967-9385). And ask for a free sample.

Technology for tomorrow built on TQC today.



ROGERS

Rogers Corporation
Circuit Components Division
2400 S. Roosevelt Street
Tempe, AZ 85282

DISTRIBUTION: Europe, Japan, Taiwan, Singapore, Hong Kong, Korea, Brazil, Australia

CIRCLE NO. 107

MICRO/Q 1000 STANDARD CAPACITORS

Improve board performance without redesign. Noise problems are solved by retrofitting on existing boards.



CIRCLE NO. 108

MICRO/Q 1000 CUSTOM CAPACITORS


Special pinouts are available to address the wide variety of specialty DIPs such as analog devices, op-amps, and the center pinout advanced CMOS devices. Applications include: decoupling, EMI/RFI filtering, and compensation.



CIRCLE NO. 109

MICRO/Q 2000 CAPACITORS

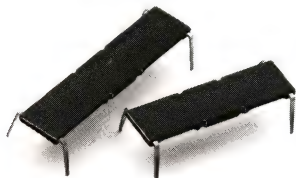
Capacitance levels from 0.01 μ F to 0.3 μ F in Z5V and X7R temperature stable dielectrics. The unique molded construction provides for maximum environmental protection. Suitable for use in both commercial and military applications.



CIRCLE NO. 110

MICRO/Q 3000 CAPACITORS

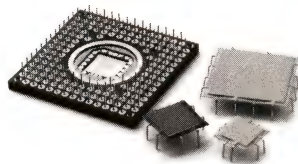Reduces noise associated with the use of PGA and PLCC devices. Several part sizes are available to address a variety of package sizes. Micro/Q 3000 is designed to be used with all 16/32-bit MPUs, DSPs, GSPs, FPPs, gate arrays, standard cells, and fully custom ASICs.



CIRCLE NO. 111

✓ Check List for Selecting a Data Acquisition System

Are you looking for

- ☐ 1 to 32 Channels per rack unit
- ☐ Plug-in Digitizers up to 200 Msps
- ☐ Memory to 512k pts / Channel
- ☐ Eight- to Sixteen-bit Digitizers
- ☐ MS-DOS Floppy & Hard Disk

Call Hi-Techniques

- ☐ Pre - and Post - Trigger Viewing
- ☐ Complex Trigger Arrangements
- ☐ On-screen Trigger Parameters

Call Hi-Techniques


- ☐ Internal Processing
- ☐ Keyboard Data Manipulation
- ☐ Complete Computer Control from IEEE-488 (GPIB) & RS232

Call Hi-Techniques

- ☐ Live Displays and Readouts
- ☐ Cursors - Absolute & Delta readouts
- ☐ User units for transducers & probes
- ☐ User-selectable labels for channels

Call Hi-Techniques

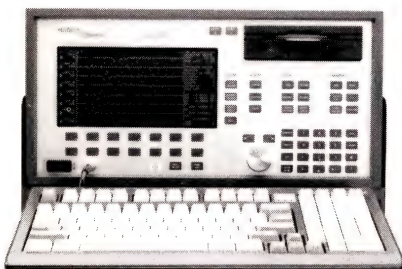- ☐ Internal registers for stored results
- ☐ Printer/Plotter connections
- ☐ Hi-Res plots with user comments
- ☐ Applications Programming Support
- ☐ Immediate Service Help via Toll Free Number
- ☐ On-site Training



1-800-248-1633

Call TOLL FREE today

**Hi-Tech
Techniques**

152 Owen Road, Madison WI 53716
In Wisc: 608-221-7500

TECHNOLOGY UPDATE

Optical-character-recognition software

gence techniques to bear on the task of reading text. The \$995 program runs with a 68020 accelerator card on either the Macintosh II or the Macintosh SE and requires 4M bytes of system memory.

The program handles the output of most scanners including the company's various JetRead models, the Apple Scanner, and HP Scanjets. It can translate 6- to 24-point type. In addition to text, the software develops a range of formatting information, "hard" carriage returns, bulleted lists, and tabs for material organized in columns.

AccuText can capture line-art images, along with printed text, and generate user-specified half-tone images in standard image-output formats such as the one used for MacPaint. You can vary the resolution of artwork from 75 to 400 lpi.

The program also has a 50,000-entry dictionary. It employs usage information in the dictionary to resolve ambiguous translations at the word level based on the word's context. Most other OCR software simply tries to recognize each letter individually. The firm offers programs with context-sensitive dic-

tionaries for English, Spanish, Italian, German, Dutch, Swedish, Norwegian, and French. You can add up to 10,000 words of your own to the program's dictionary. Revealingly, the program is so automatic that it has no provision for user training.

Scanner cost is high

Although low-cost OCR software is now available, high-resolution optical scanners are still rather expensive. Perhaps hardware designers will be inspired to re-design high-resolution scanners to bring their prices down in line with the software's. What's more likely is that scanner prices will remain expensive while their performance will increase. Scanners' resolution will increase from 300 to 400 dpi or even 600 dpi, grey-scale resolutions will increase from 4 to 8 bits or 16 bits, and color scanners may even appear soon.

EDN

Article Interest Quotient
(Circle One)

High 515 Medium 516 Low 517

For more information . . .

For more information on the OCR software discussed in this article, circle the appropriate numbers on the Information Retrieval Service card or use EDN's Express Request service. When you contact any of the following manufacturers directly, please let them know you saw their products in EDN.

Caere Corp
101 Medford-Mt Holly Rd
Medford, NJ 08055
(609) 953-0223
Circle No. 716

Olduvai Corp
7520 Red Rd, Ste A
South Miami, FL 33143
(305) 665-4665
Circle No. 718


Xerox Imaging Systems
1215 Terra Bella Ave
Mountain View, CA 94043
(415) 965-7900
FAX 415-965-3474
Circle No. 719

Inovatic
1911 N Fort Meyer Dr, Ste 798
Arlington, VA 22209
(703) 522-3053
Circle No. 717

Twice the Power:

PCB II

PC Board Layout
on your PC

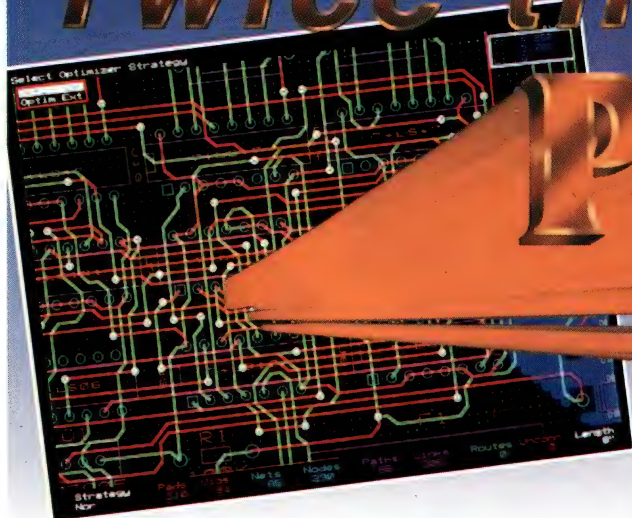

OrCAD Systems Corporation, the world's largest marketer of PC-based CAE software, has completely upgraded it's popular printed circuit board layout software. Now you can have all the power features you need for your board designs on the PC you already own.

Twice the capacity

OrCAD/PCB II has over double the capacity using a flexible, user-definable memory allocation system. The product now supports over 270 14-pin IC equivalent designs, 6000+ pads, 16,000+ equivalent track segments.

Twice the options

OrCAD/PCB II comes with over 50 different printer drivers including most popular dot matrix and laser printers, over a dozen plotter drivers and over 50 display drivers. We conform to your system better than anyone.

Twice the features

- Improved autorouting strategies means a faster route with more completions.
- Design Rule Check available as OrCAD/PCB II runs. Parameters are user configurable.
- Via and Track Optimization. Minimize vias and improve routing automatically.

OR8944-Intl.

- On-Line module browsing and reading. Call up modules and browse through their graphic descriptions.
- Gerber Viewer generates screen version of Gerber file to check output.

Twice the value

OrCAD's commitment to you is that all of our powerful software will give you workstation performance without extra hardware, all handled within 640k RAM.

And the price? The package comes complete with autorouter, printer and plotter support, excellent documentation and more for a very reasonable price.

The price also includes one year of technical support, free product updates and access to our 24 hour BBS.

Curious? Try it yourself with our demo disk.

Call for our demonstration disk and information packet. You'll see why more designers look to OrCAD for their design solutions.

OrCAD 
Systems Corporation

3175 NW Alcock Drive
Hillsboro, Oregon 97124
(503) 690-9881

If you would like more information about this or any other OrCAD product, contact your local OrCAD representative.

AUSTRIA
**Dahms
Elektronik**
0316/64030-0
Fax: 64030-29

ITALY
BRM Italiana
TEL: 011/771.00.10
FAX: 011/771.01.98

BELGIUM
INEX
(02) 649.99.91
Fax: (02) 649.27.92

ITALY
**MicroData
Systems**
0187/966123
Fax: 0187/988322

DENMARK/
NORWAY
NordCAD
98 17 32 99
Fax: 98 17 37 41

SPAIN
Next-For S.A.
504 02 01
Fax: 504 00 69

UK
**ARS Micro-
systems**
(0276) 685005
Fax: (0276) 61524

SWEDEN
**Technology
Partners**
(468)790 97 75
Fax: (468)16 77 86

FINLAND
Elektrotel OY
(358 0)754-3122
Fax: 754-2593

SWITZERLAND
Logmatic AG
056/83 38 38
Fax: 056/83 38 40

FRANCE
ALS Design
(331) 46 04.30.47
Fax: 48 25.93.60


W. GERMANY
**Compware,
GmbH**
4940/81 80 74
Fax: 4940/81 10 37

Call today for your demo disk

No matter what you high performance logic



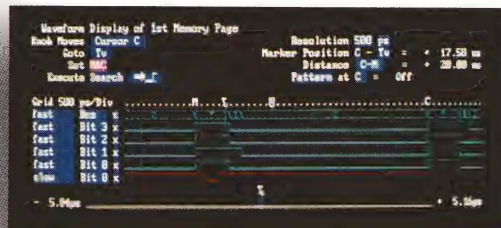Our Rotary Mouse™ gives you the easy, intuitive performance of a mouse with no mouse mess on your bench.




With 500 pS timing resolution, no variation is too subtle for detection.




A clustered-channel bus display simplifies the timing diagram so you always know exactly where you are on multiple buses at a glance.



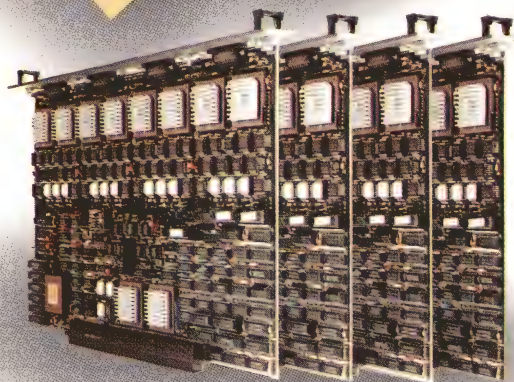
Advanced transitional recording techniques give you at least 5 times more recording time, with more high speed channels.



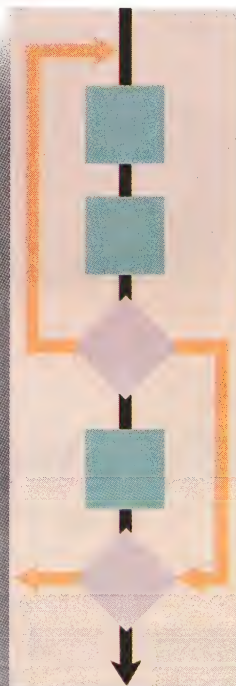
All the channels you'll need at 100 MHz are in one mainframe. Configure them as up to 4 independent logic analyzers and disassemble up to 4 microprocessors at a time.



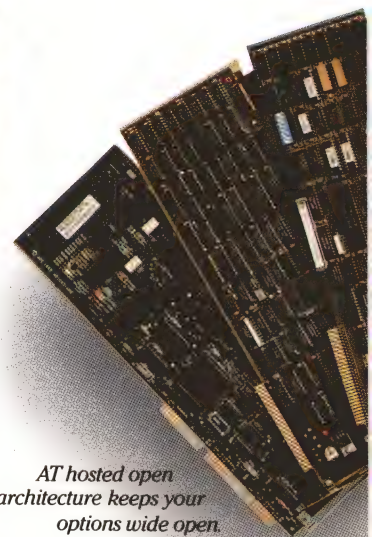MetaTrigger™, a patented, proprietary, custom ASIC for Logic Analyzer triggering, instantaneously links unrelated events.




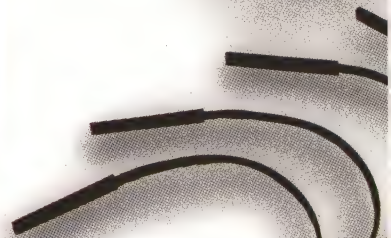
AT hosted open architecture keeps your options wide open.




Even the most elusive signals can't escape VHSTA probes with 800 pS pulse capture.



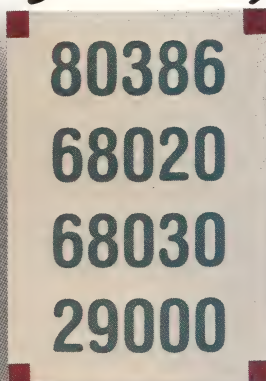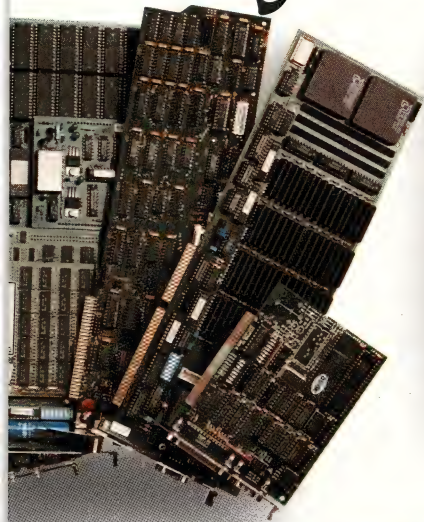
are looking for in a analyzer, you just found it.



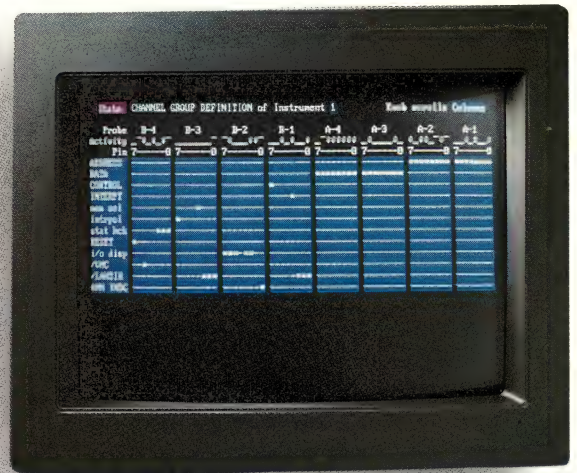
You get disassembly for the fastest, most complex microprocessors, with the architecture to support up to 50 MHz performance.



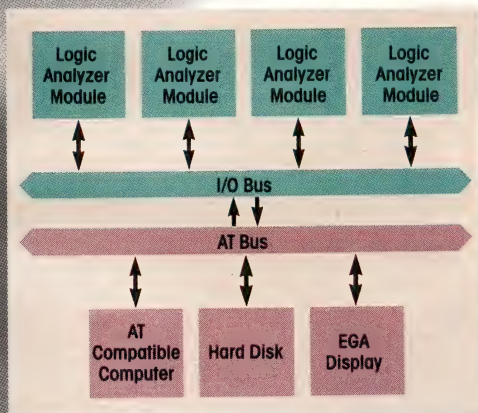
Open channel assignment with labeling gives you complete flexibility in reconfiguring.



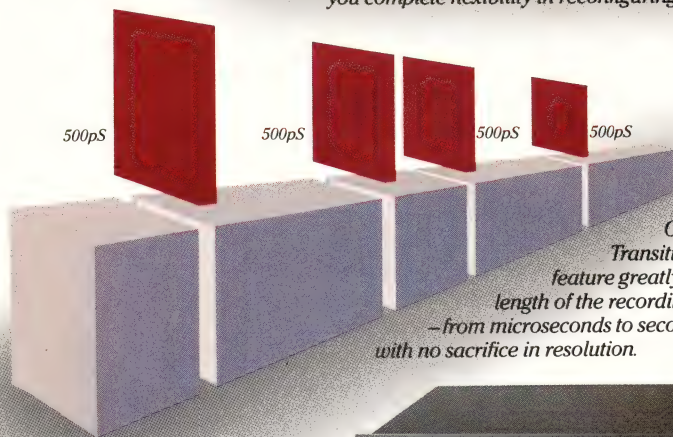Kontron's modular design grows into new applications, so you buy only what you need now.



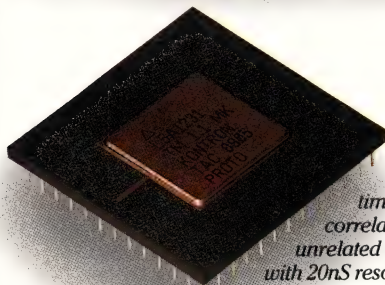Our exclusive Transitional Recording feature greatly extends the length of the recording window — from microseconds to seconds — with no sacrifice in resolution.



Our custom time tag chip correlates multiple unrelated events with 20ns resolution.

Kontron's high performance logic analyzers give you every power feature on your list, including some you didn't know you could get. And some you can't get anywhere else.

Like 96 channel width in a machine that also delivers 500 pS resolution. Advanced disassembly and transitional timing. Sophisticated trigger control and timing correlation for unrelated events, all managed with the simplicity of our exclusive Rotary Mouse.

KONTRON ELECTRONICS, 244 Sobrante Way, Sunnyvale, CA 94086, Telephone (800) 227-8834



You'll find it all in our extraordinary new PLA/2 and KLA/2 high performance logic analyzers, including your choice of portable, rack mount and desktop configurations.

Interested in performance? Call 800-227-8834 now. We'll express you the specs. No matter where else you've looked so far, we

promise you'll be impressed. **KONTRON ELECTRONICS**

Kontron Technical Centers Boston (508) 921-4700, Baltimore (301) 792-4987, San Jose (408) 733-0272

Meet the

Complete, real-time emulation solutions...

EZ-PRO 1.5

PRICE/PERFORMANCE LEADER

For 8-bit in-circuit emulation, EZ-Pro 1.5 provides large scale system support at a modest price. This includes an assembler, linker and debugger with each emulator at no extra charge. C compilers are also available. Processors emulated:

46 different versions of the popular 8051 family; 6301/03 family; 6309/E, 64180R0; 6502, 65C02; 6800/02/08, 6801/03/U4, 6805/E2/E3/D2/C4/C8, 6809/E, 68HC11/A0/A1/A8/E1/E2/E9; 8035, 8039, 80C39, 8040, 8048, 8748, 8049, 80C49, 8050, 8085, 80C85, Z80A/B/H, NSC800, plus continual additions such as 68HC11 D3 and F1.

EZ-PRO 2.1

INDUSTRY WORKHORSE

For 16-bit and 8-bit design support, Series 2.1 systems couple the most versatility with the greatest reliability. They emulate all devices supported by EZ-Pro 1.5 plus:

1802, 1805AC, 1806; 64180R0/R1/Z, Z180; 68000, 68HC000, 68008, 68010; 8086, 8088, 80C88, 80186, 80188, 80C188; 8096/BH/90, 8396/BH/90, 8796/BH/90, 80196/BH/90, 80C196; 8X300, 8X305; V20, V30 and more processors as they come to market.



Family.

EZ-PRO 3.7

THE POWER-PLUS SYSTEM

For 32-bit CISC & RISC development, the sophistication, power and speed of EZ-Pro 3.7 assure important advantages for your embedded system designs. Call our marketing department for information and availability.

EZ-PRO S/W

AA-AUTHORED SOFTWARE

EZ-Pro software optimizes your emulation solutions, with or without our hardware. It includes ANSI standard C compilers, assemblers & linkers for MS-DOS/PC-DOS host machines.

Depth of the offer includes an emulation executive with C-source level debugging; optional 4K deep trace, performance analyzer, EPROM programmers and more.

Our benefits continue with service programs, sales, leases, trials, trade-ins, rentals—all for customer satisfaction.

Look at it from our 'family' to yours. We're an employee-owned company. We have a personal reason to treat you better. So please talk with us today:

714-731-1661.



CIRCLE NO. 44

Headquarters: 2651 Dow Avenue, Tustin, California

92680-7207, Telephone (714) 731-1661. European Headquarters: UK Oxford 0993-778991. Distributors: Australia 35-601011, Belgium 02-468-1400, France 1-69308050, India 44-417423, Indonesia 02-271880, Korea 02-784-9942, Spain 1-729-1155, Switzerland 1-435-4111, Taiwan 02-7061271, West Germany/Netherlands/Austria 089-6127087.

RISC PROCESSORS



CISC PROCESSORS

C-COMPILERS

LINKERS

MICROSOFT
SUPPORT

UTILITIES

ASSEMBLERS

EMULATION EXECUTIVES



Introducing AvCase™ 8051.

Three finely-tuned instruments for embedded-system development.

AvCase™ 8051 C Compiler, Assembler, and Simulator from Avocet. Play them solo, for peak performance. Or bring them together in perfect harmony as an integrated system. AvCase will manage all the steps—from editing source code, compiling,

assembling, and linking, all the way to debugging. ■ *High-level language in the key of C.* AvCase C Compiler is our biggest seller. It produces fast, tight, optimized code that helps speed development time.

■ *Clear, concise scoring.* AvCase Assembler is the classic Avocet assembler tuned-up and ready for your most demanding applications.

AvCase Simulator lets you test code on debugging feature you can work at both the C and assembly *begin*. If you want to meet your project deadlines—come in on bug-free product—you simply can't do better than AvCase.

Fax, write, or call toll-free 1-800-448-8500 for complete information, including a free AvCase Brochure and Avocet Catalog.

■ *Full dress rehearsal without leaving your desk.*

your own PC. With the new source-level language level. ■ *Let the music*

budget—and develop a high-quality,

Find out more about these finely-

AVOCET
SYSTEMS, INC.

CASE FOR EMBEDDED SYSTEMS

New software tools speed design and debug



Four recently introduced CASE packages may help speed design, debug, and integration chores for your embedded system.

Margery Conner,
Regional Editor

Embedded-systems design requires a delicate hardware-software balancing act. The two must be designed to complement each other. If you spend too much effort in the design of one before checking it against the other, you'll face extensive redesign chores. Although excellent CAE tools exist to aid hardware design and simulation, similar tools for software design and integration have lagged. In the past six months, however, four vendors have introduced computer-aided-software-engineering (CASE) tools specifically for embedded systems software design and integration.


CASE tools have been around for a long time for batch-processing systems. Most of these tools, however, are for the code-design step, and are tools for documenting code design using a structured-design methodology. Projects that use these CASE tools tend to have large teams of programmers who write millions of lines of code. Typical applications are in banking or the military.

Many of these structured-analysis packages address embedded systems by including extensions for real-time programming. The Yourdon-DeMarco method, for example, is one of the most popular structured-analysis methodologies, and the Hatley real-time extensions are the conventions used for indicating how a software mod-

ule reacts to a real-time interrupt. Indeed, the prevalence of these tools labeled as "CASE" has made CASE synonymous with structured analysis. However, for many reasons, few embedded-systems designers use structured analysis. First, most embedded-systems designers view structured analysis as a method to coordinate and document a project among many engineers. Also, relatively few engineers, perhaps 15%, are familiar with a structured-analysis methodology.

In addition, there's much more to embedded-systems software than code design (Fig 1). Unlike traditional CASE tools for batch-processing systems, the embedded-system tools introduced recently by Mentor, Ready Systems, Archimedes Software, and Integrated Systems Inc (ISI) concentrate on the steps that follow code design: code writing, debug, integration, and performance evaluation.

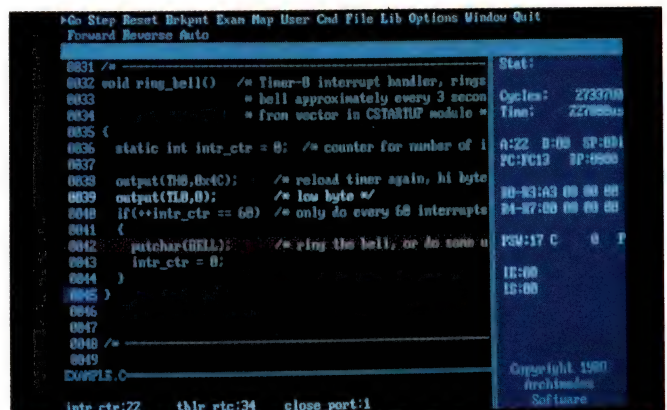The four packages, which are listed in Table 1, are aimed at fairly specific



Running on an IBM PC or compatible, SimCASE uses multiple windows to provide information about its simulation of an 8051 μ C running your C code.



THREE NAMES ARE STACKING UP BIG IN THE BUS BUSINESS.

If you're designing for bus systems, you should know these names: *VIC*, *VAC*, and *ACL*. They're IC building blocks that can drive your system to maximum performance levels.

The VIC068 brings real plug-and-play compatibility to the VME world. It's a complete VMEbus Interface Controller on a single chip. Developed with a consortium of VMEbus International Trade Association (VITA) member firms, it's fast becoming the standard for VME developers, worldwide.

Since it's a single-chip solution, the VIC068 gives VME designers more board space for other features. And, it guarantees compatibility for boards from different suppliers.

The VAC068 is a VMEbus Address Controller, designed as a complementary chip to the VIC. It provides address counters and the necessary hand-shake signals for block transfers. It also provides memory address decoding and, like the VIC chip, is highly programmable. The VIC068 truly raises the level of integration for high-performance systems.


The VIC-VAC architecture provides a complete master interface, with unrestricted memory access to and from the VMEbus. Both chips are packaged in a 144-pin plastic or ceramic PGA.

The VIC and VAC chips drive the bus directly, using the patented output drivers from VTC's ACL (Advanced CMOS Logic) family. Our ACL parts — both FCT and ACT — have up to 64mA drive, making them ideal for *any* high-performance bus system. And, with significantly less ground bounce than competitive products, our FCT gives you better system performance.

VIC, VAC, and ACL are available in commercial grade, or MIL-STD-883C compliant.

And, these three names are just the beginning. There's more to come in the "total VTC bus solution." So, get on board! And start driving *your* system to the maximum.

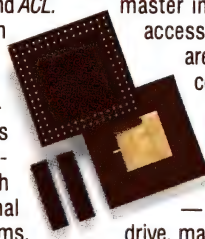VTC Incorporated, 2401 East 86th Street, Bloomington, MN 55425 USA. Fax 612/851-5199. Telex 857113. (In Minnesota, please call 612/851-5200.)



VTC Incorporated

Hard-Driving Bus Solutions™

CIRCLE NO. 65

CALL 1-800-VTC-CMOS

TECHNOLOGY UPDATE

CASE for embedded systems

kinds of embedded systems, so you'll need to know which package best suits your application. For example, Mentor's Codelink Station is aimed at simpler systems operating without a kernel; Ready Systems' CARDtools is aimed at systems operating under the company's real-time kernel. Archimedes' SimCASE supports only systems running on an 8051 μ C (microcontroller); Integrated Systems Inc's Matrix tools can handle most general kinds of systems.

Codelink does not assume that you have used a structured-analysis methodology for your code design. As long as your C code complies with IEEE-695A, Codelink's Structure Recovery portion reverse engineers your code to create a structure chart. This structure chart serves as a graphical road map of your software that you use to select any portion of the code. Once you've selected the code, you can examine, modify, or run it on simulated hardware. In Codelink's virtual mode, ISS (Instruction Set Simulator) generates object code from the source code you write. The object code then serves as the stimulus to the company's hardware simulator, QuickSim, which flags any logic er-

rors. QuickSim runs in batch mode using the ISS-derived signal as the input stimulus to a bus-functional hardware model.

De facto division of labor

Be aware that timing conflicts are not automatically flagged; rather, they must be caught by the astute hardware designer. According to Rick Potter, general manager of Mentor's CASE division, there is a wall between software and hardware development in most embedded-systems designs. Usually, the software engineer writes code independently of the hardware designer. He added that the most likely scenario for coding is where the programmer hands the code off to the hardware designer, who will supervise the integration of hardware and software.

Thus, you cannot specify the software's behavior at the system level. The hardware simulator only tells you that it didn't get the expected output for a given input vector; it doesn't give you any analysis as to why you didn't get the correct output vector.

Also, be aware that if you should change the code, the structure chart is no longer any good. You

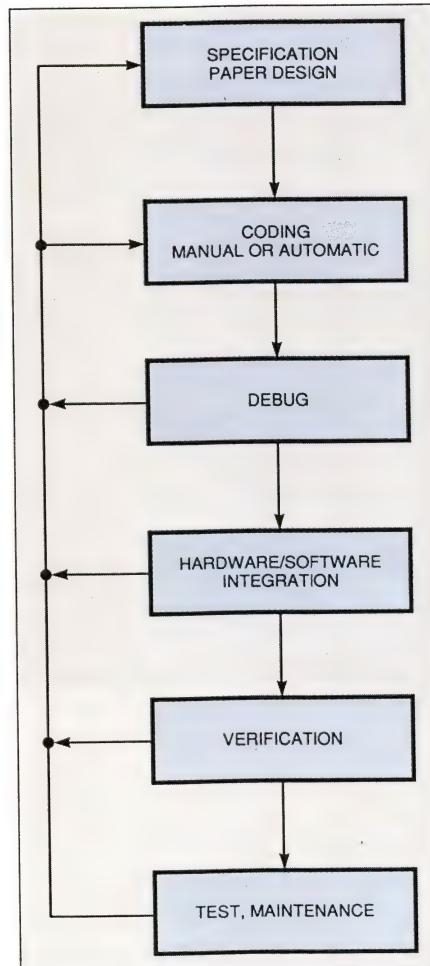


Fig 1—Embedded-systems software design tools differ from traditional CASE tools for batch-processing systems in that they concentrate on the steps that follow code design.

Table 1—Representative CASE tools for embedded systems

Vendor/Tool	Real-time operating-system support	μ P	Workstation	Languages	Price	Comments
Archimedes Software SimCASE	Intel	8051	PC/AT	C	\$995	SimCASE is an 8051 simulator.
Integrated Systems matrix	All	μ P independent	Sun, DEC, Apollo, PC/AT, PS/2	C, Fortran, Ada	\$20,000-120,000	Matrix is an analysis, design, modeling, code generation and simulation package.
Mentor Graphics Codelink station	None	All	Apollo	C (IEEE-695A)	From \$27,900	Codelink performs behavioral and timing analysis through Mentor's QuickSIM hardware simulator. It also links to Hewlett-Packard's 64700-series emulators.
Ready Systems CARDtools	VRTX	680X0, 80X86, 29000	Sun 3, VAX mainframes and VAX-stations	Not language dependent	From \$7000	CARDtools TaskTimer combines user estimates of application module and hardware timing with its calculations of VRTX timing requirements to generate a system timing simulation.


TECHNOLOGY UPDATE

CASE for embedded systems

must rerun the structure-recovery software to have a valid chart. There is neither back annotation nor automatic checks to make sure that you indeed do rerun the structure recovery software.

Codelink supports embedded systems that do not require an operating-system kernel. Ready Systems' CARDtools, on the other hand, supports complex multitasking systems that use the company's VRTX real-time operating system. And unlike Mentor's approach, which assumes that the ultimate responsibility for system integration is the hardware designer's, CARDtools supports system design from a software designer's point of view. For example, hardware is represented in simulations as a black box, whose only characteristics you know are its timing characteristics, such as response time.

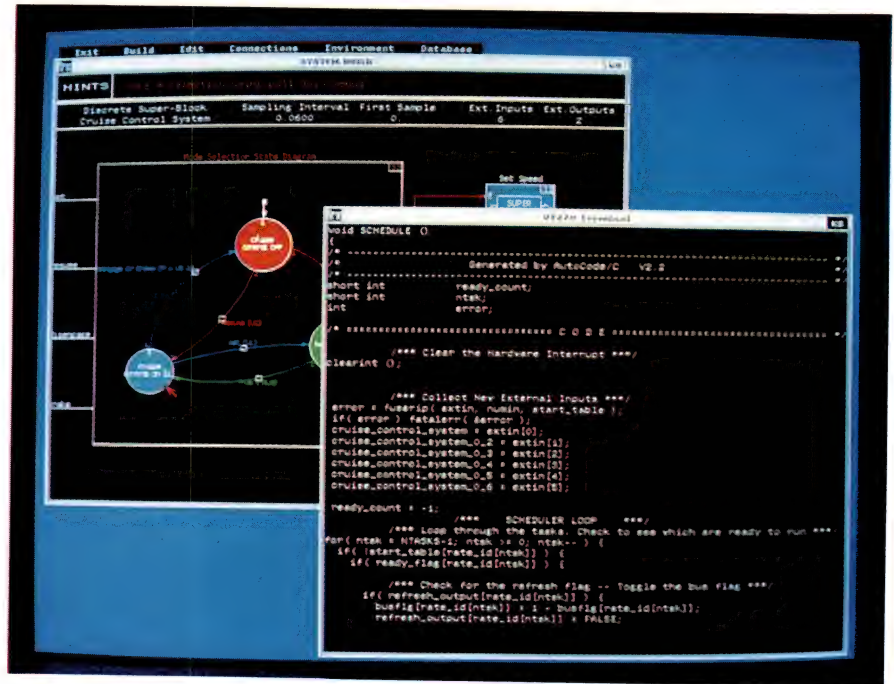CARDtools contains TaskTimer, a system timing performance simulator. System timing depends on two factors: the application software and the operating system. TaskTimer derives the VRTX operating system's response time, but



By automatically generating C code, ISI's AutoCode lets you try several different versions of your software before selecting the final one.


you must estimate the time each module in your application software will take to run.

Thus, TaskTimer's simulation is only as good as your timing estimates for your application software and your hardware black boxes.

But, by forcing you to perform a timing analysis at the very beginning of your design cycle, TaskTimer can point out ambiguities and potential trouble spots before any code is written or hardware designed. Also, as you refine the estimates, you can play a "what-if" analysis and evaluate your hardware.

Software tradeoffs

TaskTimer includes the pertinent specifications of target processors, such as cycle times or any required RAM or ROM wait states. By including these hardware parameters in a system-timing simulation, TaskTimer lets you evaluate your options in processor hardware. For example, you can check if a 68010 is fast enough. If not, you may be able to raise the system speed by using a 20-MHz version, rather than a 68020. Keep in mind that TaskTimer is concerned only with processor timing that affects how fast VRTX runs, so it doesn't need to know about other system proces-

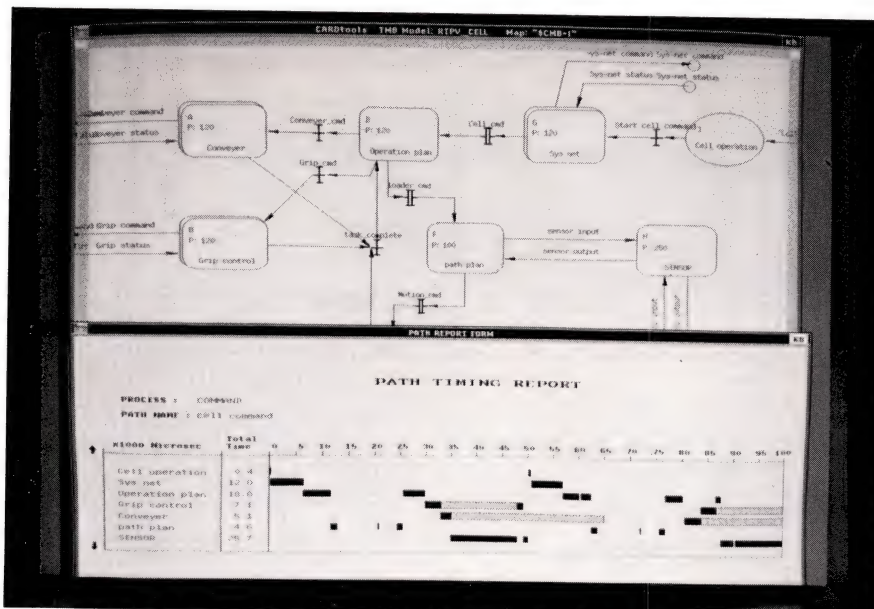

By displaying system timing results in a Gantt chart, TaskTimer lets you consider multiple paths, priorities, and shared resources in your embedded system.

Visit us at the Design Engineering
Show in Chicago at Booth #1423.

Its vast, electronic nervous system will transmit enormous amounts of information at the speed of light thanks to surface-mountable electronic components constructed of materials from Eastman Performance Plastics, such as the advanced Ektar® Filled Blend PCT Polymer.


Eastman is the only manufacturer of PCT, a material that allows the most efficient and economical manufacture of surface mounted components for vapor phase and infrared reflow-solderable printed circuit boards – the circuit boards of the future.

If miniaturization and surface mount technology are driving your need for better performance, greater reliability and increased economy, talk to us about Ektar® FB PCT Polymer and our full range of performing plastics. Call A. Laws at 1-800-EASTMAN or write to Eastman Performance Plastics, P.O. Box 1969, Kingsport, Tennessee 37664.

PERFORMING PLASTICS FROM EASTMAN

© 1989 Eastman Kodak Company

CIRCLE NO. 46

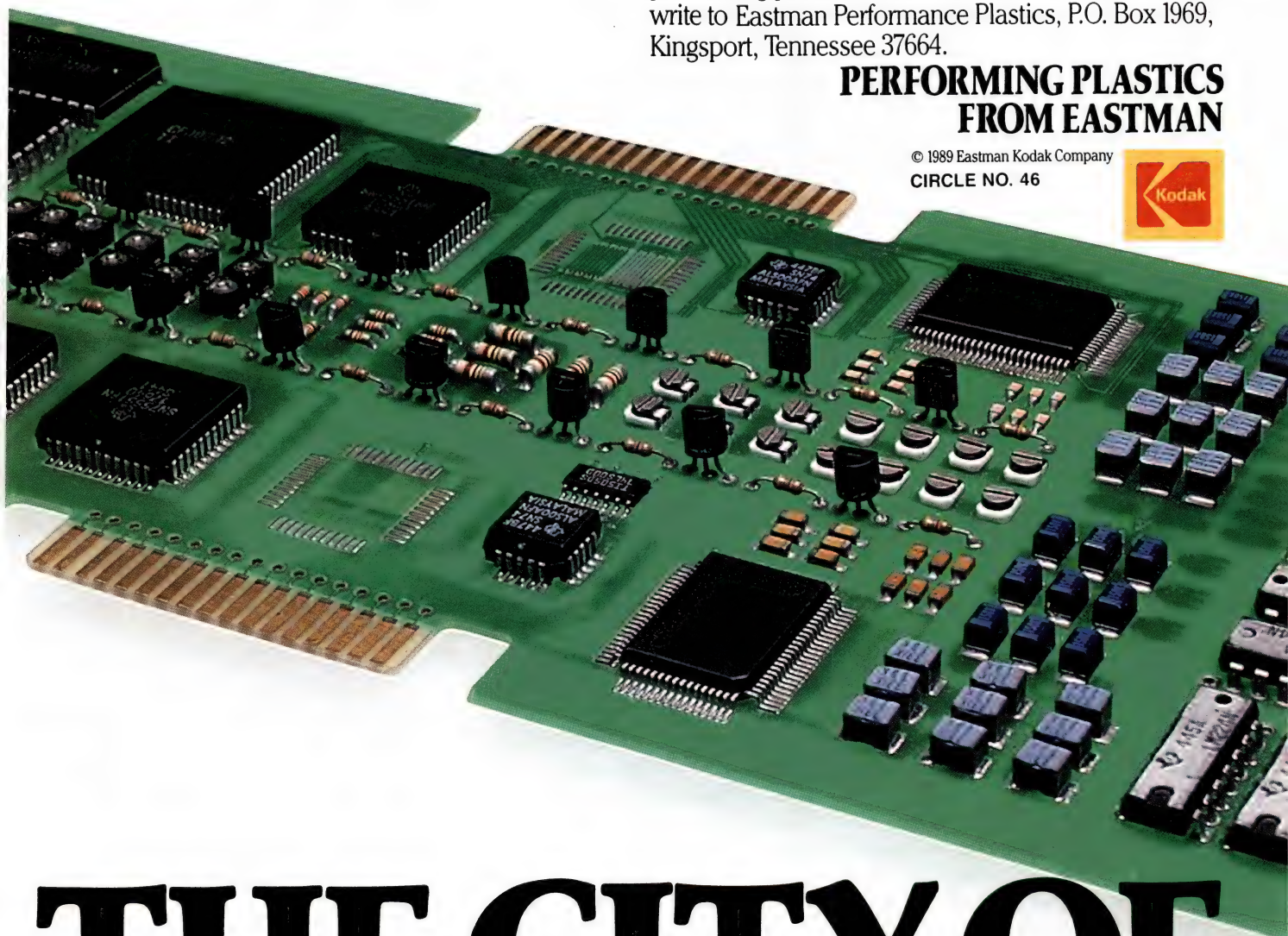

THE CITY OF THE FUTURE

* Ektar is a registered trademark of Eastman Kodak Company for its poly (1,4-cyclohexylene dimethylene terephthalate)

TECHNOLOGY UPDATE


CASE for embedded systems

sors, such as a dedicated DMA controller. Note too that in the design phase you can assume multiple processors, but in simulation, only one.

Along with its knowledge of the processor speeds, TaskTimer also can apply knowledge of external devices and their drivers. You can either define the external devices as drivers with a specified delay, which are completely opaque to VRTX, or you can define the devices as being under the control of VRTX. When these type of drivers run, VRTX essentially goes to sleep as long as the device is active. Nothing else can occur in parallel as far as VRTX is concerned. By involving VRTX, the operating system is able to let something else run in parallel with the device's activity.

CARDtools doesn't have the degree of accuracy that Codelink offers, but you can use it on much more complex multitasking systems. It also allows you to easily change software and hardware timing characteristics while you're still in the planning stage. An advantage to this flexibility is that you can closely examine your design partitioning—which tasks are done in hardware, and which in software.

You probably won't find this flexibility in most structured-analysis design packages, because structured-analysis methodologies are usually in the form of data-flow diagrams, which are concerned only with input. That is, through some transformation, the input becomes output. Real-time systems are concerned with the transformation itself because the time the transformation takes is critical. And the timing of the transformation will affect the software design. By estimating software and hardware module timing very early in your design, you can determine which

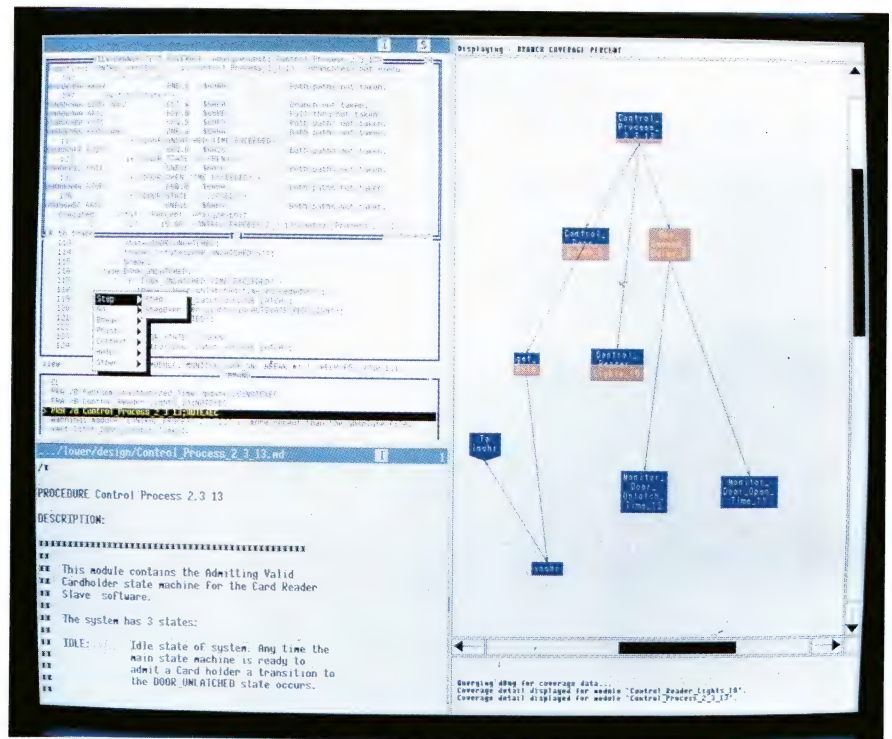

By converting your C source code to object code, Codelink allows you to check your software on Mentor's QuickSim hardware simulator before you build any hardware.

hardware and software constructs will be likely to meet your overall specifications.

Most of the focus in new CASE products for embedded systems is for the 32-bit processors and controllers. Yet the vast majority of embedded controllers are 8-bit. Archimedes Software has two CASE tools for the 8051 μ C—SimCASE and SimI/O, which cost \$995 and \$695, respectively.

SimCASE is an 8051 simulator that can run your compiled C program. It also contains an input stimulus generator that allows you to synthesize any possible input to the simulated μ C. The advantage of running your code through a simulator rather than through the target system via an emulator is that in a simulator you can run worst-case input conditions. For example, in most cases an input switch may debounce in 1 msec, but worst-case time is 5 msec. In the

target system the worst-case condition may never occur, but you can force the condition with a simulator. You'll need SimI/O to simulate all input and output responses at the 8051's I/O ports.

You can use SimCASE with one of the real-time kernels supplied by Intel for the 8051, but Archimedes Software anticipates that most of the work done with 8-bit systems won't require a kernel.


Automatic code generation

ISI's embedded systems CASE tool set, Matrix, includes a code generator. Automatic code generators are often derided for the exhaustive thoroughness their specifications require. By the time you've specified a software module to a code generator's satisfaction, you could have written the code yourself. ISI claims that because its code generation is only for narrowly defined embedded systems, the gen-

"Vroom!"

Turbocharge your memory for zero wait state design with Signetics fast 7.5ns PAL-type devices.

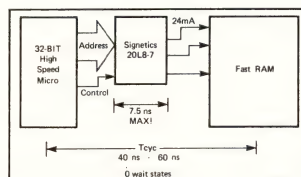Vroom! Now you can get the zero wait state performance that will allow memory to keep pace with the new ultra-fast microprocessors. And you won't have to pay top price for your memory to do it!



7.5ns PAL-type device improves system performance.

Vroom! Boost system speed, lower memory cost. Signetics offers the fastest (7.5ns) PAL-type devices for high-speed decoding. Now you can design with slower, less expensive, more available memory devices and still enhance system speed. And all Signetics PLDs are easily supported by ABEL, CUPL or our powerful AMAZE design software.

7.5ns 20-pin		7.5ns 24-pin	
PLUS16L8-7	PLUS16R6-7	PLUS20L8-7	PLUS20R6-7
PLUS16R4-7	PLUS16R8-7	PLUS20R4-7	PLUS20R8-7

Vroom! We've got the guts! That's right, we have those essential PLDs you need to improve total system performance. Programmable Macro Logic, Logic Arrays, Logic Sequencers and our PAL-type products that cut system cost while boosting system speed.

Turbocharge your memory now! Call Signetics at (800) 227-1817, ext. 985D, for a free High-Speed Decoder Handbook. For surface mount and military product availability, contact your local Signetics sales office.

PAL is a trademark of AMD/MMI. ©1988 NAPC

Signetics

Philips Components



SUNRISE ELECTRONICS, INC.**A WHOLE NEW WAY TO
PROGRAM EPROMs,
PLDs, and MCUs**

In-circuit Programming lets you program your EPROMs after they have been installed in your circuit card. It is the most efficient and most reliable way to program. It simplifies your manufacturing process and reduces your documentation. It also eliminates sockets, labeling and insertion related failures.

Our programmers can program multiple data files into different cards simultaneously. In addition we test the cards automatically after they are programmed.

Best of all, we do all the work for you. Sunrise in-circuit programmers can be delivered as complete turnkey systems, or you can develop your own interface using the built-in self guided menu driven software.

**T-8000 HIGH VOLUME
IN-CIRCUIT PROGRAMMER**

- Program 48 or more cards at a time
- 40 MB hard disk, dual floppy drives
- 660 Watts of programming power
- MS-DOS compatible

**T-6000
BRIEF CASE
PORTABLE
IN-CIRCUIT
PROGRAM-
MER**

- Optional lift out UV board size eraser
- Program several boards in one pass
- 3.5 inch, 1.2 MB floppy
- Rugged, shock mounted case, water tight

**T-5000 TRANSPORTABLE
MS-DOS BASED IN-CIRCUIT
PROGRAMMER**

- Program several boards in one pass
- 20 MB hard disk, 3.5 inch floppy
- Rugged, shock mounted construction

**T-4000 LOW COST
IN-CIRCUIT PROGRAMMER**

- Customer supplies IBM AT or compatible
- Program whole circuit cards in one pass
- Supplied turnkey or develop your own interface using built-in self guided, menu driven software

See our complete line of Universal and Gang programmers

SUNRISE ELECTRONICS, INC.

524 S. Vermont Ave., Glendora, CA 91740

(818) 914-1926

FAX (818) 914-1583

TECHNOLOGY UPDATE

CASE for embedded systems

erator can make many assumptions that simplify your code definition. According to Naren Gupta, president of ISI, most of the company's customers are system designers rather than programmers, and systems designers like to try several designs before selecting the final one. "Our users typically throw away a million lines of code before anyone else can write 10,000," she said.

The price for the package is comparatively steep: a practical implementation can cost about \$120,000, although portions of the tools are available starting from \$20,000. As you might expect, current customers are large companies in the aerospace and automotive industries. But if you need to be able to quickly generate, test, and discard different designs, then you may save many times the initial price over the life of the tools.

It's clear that CASE tools for embedded systems will give them more capability. Perhaps the biggest area to watch for new product introductions over the next year

will be from companies like Micro-Case and Hewlett-Packard, who, unlike the companies covered in this article, closely integrate hardware emulation with the software-development tools. Development tools for the embedded systems of the future will probably integrate software- and hardware-based tools like nothing presently available.

EDN

References

1. Small, Charles H, "Logic analyzers evolve in response to high-level languages," *EDN*, Feb 6, 1986, pg 61.
2. Strassberg, Dan, "ICs and tools tame tough technology," *EDN*, Oct 26, 1989, pg 73.

Article Interest Quotient
(Circle One)

High 518 Medium 519 Low 520

For more information . . .

For more information on the embedded systems CASE tools discussed in this article, circle the appropriate numbers on the Information Retrieval Service card or use EDN's Express Request service. When you contact any of the following manufacturers directly, please let them know you saw their products in EDN.

Archimedes Software, Inc
2159 Union St
San Francisco, CA 94123
(415) 567-4010
FAX 415-567-1318
Circle No. 720

Mentor Graphics Corp
8500 SW Creekside Pl
Beaverton, OR 97005
(503) 626-7000
TLX 160577
Circle No. 722


Integrated Systems, Inc
2500 Mission College Blvd
Santa Clara, CA 95054
(408) 980-1500
FAX 408-980-0400
Circle No. 721

Ready Systems
470 Potrero Ave
Sunnyvale, CA 94086
(408) 736-2600
FAX 408-736-3400
Circle No. 723

"Clak!"

IF-THEN-ELSE. Programmable Sequencers for advanced state machine design. From Signetics—who else!

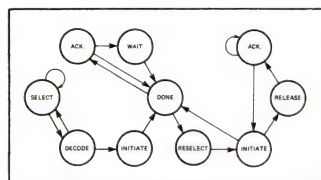Clak! At last, advanced state machine design is easy. Signetics Programmable Logic Sequencers (PLSs), including the new 50MHz PLUS405, have a unique architecture that employs buried registers to store intermediate values. The result—greater silicon and pin utilization with increased system functionality.



Advanced state machine designs become easy with Signetics sequencers.

Clak! IF-THEN-ELSE functionality. Signetics unique architecture makes complex IF-THEN-ELSE states possible. Connecting any AND term to any OR term (product term sharing) eliminates redundant state transition terms. And JK or SR type registers optimize the logic used in generating state transitions.

In addition, all our PLDs are supported by ABEL, CUPL or our powerful AMAZE software with auto test vector generation to make your job easier.

Clak! We've got the guts! That's right, we have those essential PLDs you need to improve total system performance. PAL[®]-type devices, Programmable Macro Logic, Logic Arrays and our high-speed PLSs with buried registers that make advanced state machine design easier.


Make your state machines state-of-the-art! Call Signetics at (800) 227-1817, ext. 987D, for a PLD Data Manual. For surface mount and military product availability, contact your local Signetics sales office.

© 1988 NAPC

Signetics

Philips Components



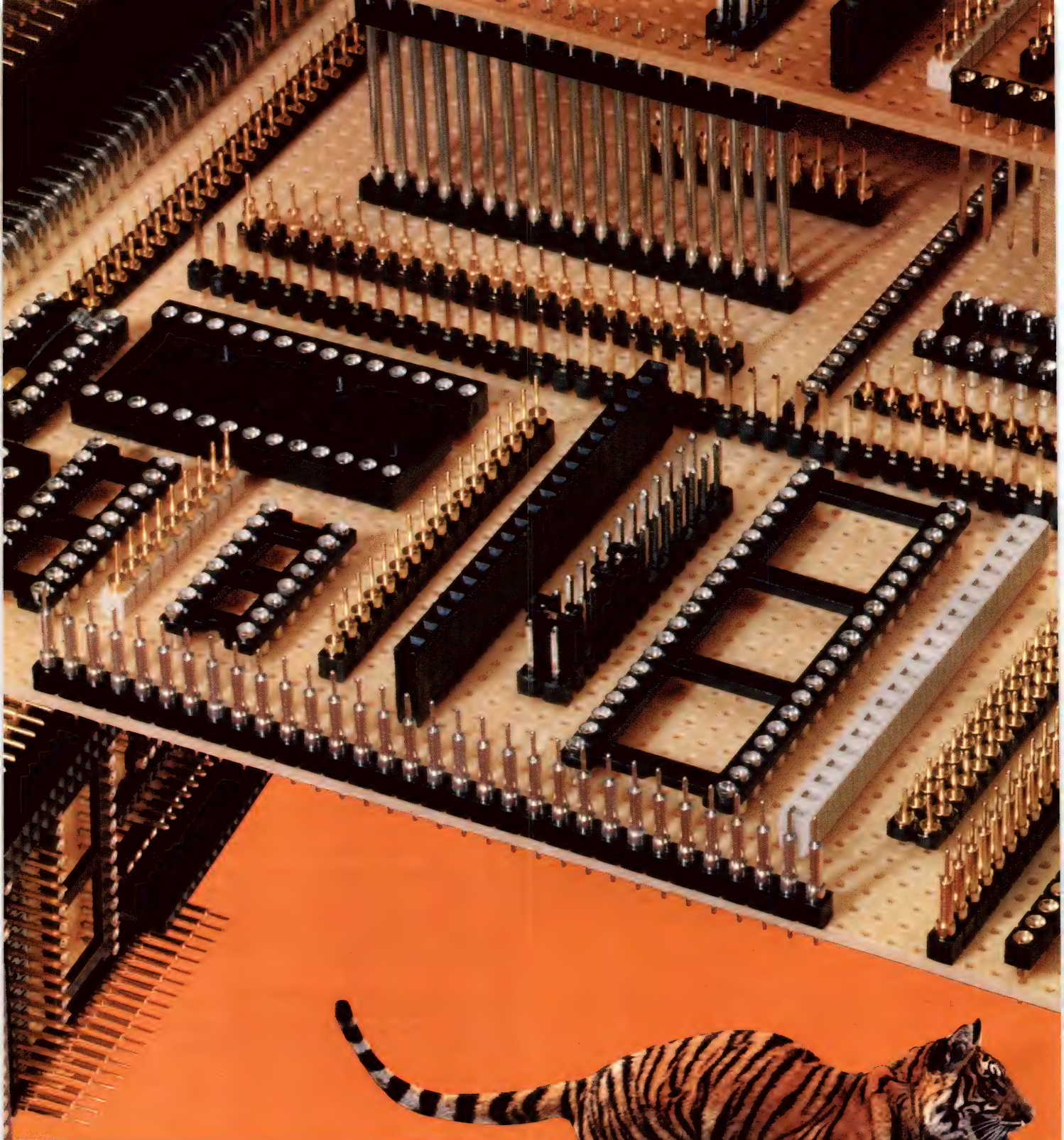

samtec

IS

New Albany, Indiana USA • Sacramento, California USA • Cumbernauld, Scotland UK • Singapore

SAMTEC, INC. • P.O. Box 1147 • 810 Progress Boulevard • New Albany, IN 47150 USA • Tel 812-944-6733 • Fax 812-948-5047 • Twx 810-540-4095 • Tlx 333-918



IN STOCK

Samtec guarantees shipment of over a thousand commonly specified connectors.

Shipped within 1 day... Samples are shipped by air within one day of request.


Shipped within 2 days... Up to 500 of any connector in our current In-Stock Catalog shipped within 2 days of your order, or you don't pay the freight.*

Shipped within 3 days ... If your order for up to 500 connectors from our current In-Stock Catalog isn't shipped within three days, you get them free.* Your account will be credited for the full amount of the connectors, plus freight!

Samtec "Sudden Service" is *guaranteed* service. Don't delay. Call Samtec today for our new In-Stock Catalog.


812-944-6733

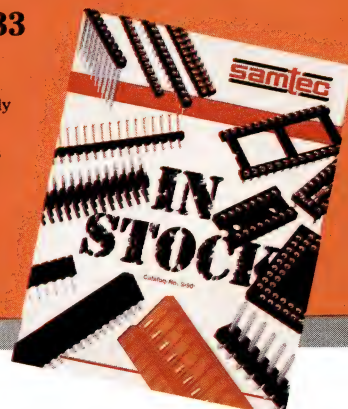*Subject to approved credit. Guarantees apply to full work days from receipt of order; weekends and holidays are excluded. Products shown in the In-Stock catalog may vary by market and are subject to change.



SUDDEN SERVICE

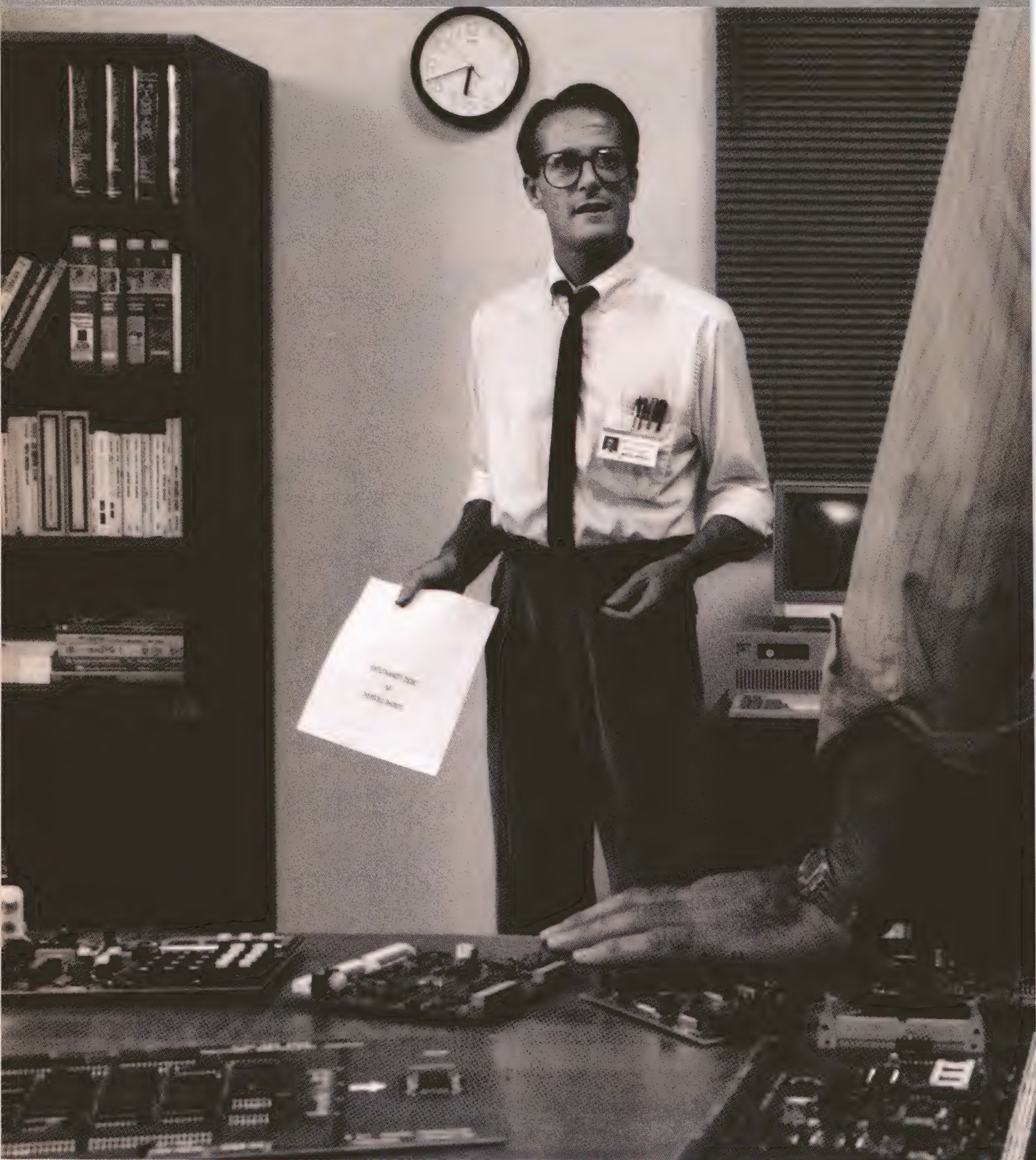"Have you heard? Toshiba has a full line of high spe



ALABAMA, Marshall Electronics Group, (205) 881-9235, Migray Electronics, Inc., (404) 393-9666, Repron Electronics, (404) 446-1300; ARKANSAS, Marshall Electronics Group, (214) 233-5200, Migray Electronics, Inc., (214) 248-1603, Sterling Electronics-Dallas, (214) 243-1600; ARIZONA, Marshall Electronics Group, (602) 496-0290, Sterling Electronics-Phoenix, (602) 286-2121; CALIFORNIA, Sterling/Imaging Electronics, (619) 271-6555, (714) 259-0900, (818) 407-8850, Marshall Electronics Group, (818) 407-0101, (714) 458-5395, (408) 942-4600, (916) 635-9700, (919) 578-9600, Merit Electronics, Inc., (408) 434-0800, Western Microtechnology, (919) 453-8430, (714) 637-0200, (408) 725-1660, (818) 707-0377; COLORADO, Marshall Electronics Group, (303) 451-8383, Sterling Electronics-Denver, (303) 792-3939; CONNECTICUT, Cronin Electronics, Inc., (203) 265-3134, Marshall Electronics Group, (203) 265-3822, Migray/Milford (203) 878-5538, Sterling Electronics-Wallingford, (203) 265-9535; DELAWARE, General Components, Inc., (609) 768-6767, Marshall Electronics Group, (301) 840-9450, Migray/Delaware Valley, Inc., (609) 983-5010, (800) 257-7808, (800) 257-7111, Sterling Electronics-Sterling, (703) 450-2373; DISTRICT OF COLUMBIA, Marshall Electronics Group, (301) 840-9450, Migray/Washington, Inc., (301) 521-8669, (800) 638-6658, Sterling Electronics-Sterling, (703) 450-2373; FLORIDA, Marshall Electronics Group, (813) 573-1399, (305) 977-4880, (305) 767-8585, Repron Electronics-Tampa, (813) 855-4656, (305) 735-1112; GEORGIA, Marshall Electronics Group, (404) 923-5750, Migray Electronics, Inc., (404) 446-9777, Repron, (404) 446-1300; IDAHO, Marshall Electronics Group, (801) 485-1551, Western Microtechnology, (503) 629-2082, Migray Electronics, Inc., (801) 272-4899; ILLINOIS, Good Electronics, (312) 860-7171, Marshall Electronics Group, (312) 490-0155, (314) 291-8554, Migray Electronics, Inc., (913) 236-8800, (312) 350-0490; INDIANA, Good Electronics, (312) 593-3220, Marshall Electronics Group, (317) 297-0483, Migray-Chicago, Inc., (312) 350-0490; IOWA, Marshall Electronics Group, (612) 559-2211, Migray Electronics, Inc., (913) 236-8800; KANSAS, Marshall Electronics Group, (913) 492-3121, Migray Electronics, Inc., (913) 236-8800, Sterling Electronics-Kansas, (913) 492-3121, Migray Electronics, Inc., (913) 236-8800, Sterling Electronics-Dallas, (214) 243-1600; MAINE, Cronin Electronics, Inc., (617) 449-5000, Marshall Electronics Group, (617) 658-0810, Sterling Electronics-Boston, (617) 938-6200, Western Microtechnology, (617) 273-2800; MARYLAND, Marshall Electronics Group, (301) 622-1118, Sterling Electronics-Sterling, (703) 450-2373; MASSACHUSETTS, Cronin Electronics, Inc., (617) 449-5000, Marshall Electronics Group, (617) 658-0810, Sterling Electronics-Boston, (617) 938-6200, Western Microtechnology, (617) 273-2800; MICHIGAN, Marshall Electronics Group, (313) 525-5850, Repron Electronics, Inc., (313) 525-2700; MINNESOTA, Marshall Electronics Group, (612) 559-2211, Repron Electronics, (612) 938-0000, Sterling Electronics, (612) 831-2666; MISSISSIPPI, Marshall Electronics Group, (205) 881-9235, Migray Electronics, Inc., (404) 393-9666; MISSOURI, Marshall Electronics Group, (913) 492-3121, (314) 291-8554, Migray Electronics, Inc., (913) 236-8800, Sterling Electronics-Kansas, (913) 236-5589; NEBRASKA, Marshall Electronics Group, (913) 492-3121, Migray Electronics, Inc., (913) 236-8800, Sterling Electronics-Kansas, (913) 236-5589;

RAMs."

"How many? How fast?"

"256K for starters. Plus 144K and 64K. And the 144K at 20ns, is the fastest application specific Cache Data RAM available anywhere."

"Great! When can we get our hands on them?"

"They're available immediately. In quantity. Right now."

The addition of these state-of-the-art 256K SRAMs and 144K Cache Data RAM gives Toshiba the broadest line in the industry. More densities. More configurations. More speeds. More choices to fit your design needs.

Toshiba high speed CMOS SRAMs are not only fast, they're reliable. And Toshiba has more than 20 years of CMOS experience.

You can cut qualification costs with Toshiba SRAMs, too. All the devices employ the same 1.0 μ CMOS process and aluminum master slice that's common to all configurations within each density. So you can qualify by family.

The 20ns Cache Data RAM is the fastest on the market. (25ns and 30ns versions are also available.) The devices are user configurable to either 4K \times 18 \times 2, or 8K \times 18. The \times 18 organization gives you two extra bits to support

the parity check required in specific applications like Intel's 80486™. Both devices are provided with byte control, and on-chip address latches are designed to interface directly with the Intel 82385™ cache controller. Pin-out is compatible with other suppliers.

Toshiba high speed SRAMs are ideal for high-end system designs. Anywhere you need top speed and fully static operation, Toshiba has a high performance solution.

They offer a wide range of packaging options, too. Why not call today for a complete set of data sheets? Call 1-800-888-0848, ext. 517. *Service is our key component.*

Toshiba High-Speed SRAMs						
Configuration	Density	Speed (ns)			Availability	
64K \times 1	64K	35	45	55	Now	
16K \times 4	64K	15	20	25	Now	
16K \times 4 (OE)	64K	15	20	25	Now	
8K \times 8	64K	15	20	25	Now	
8K \times 9	72K	15	20	25	Now	
4K \times 18 \times 2	144K	20	25	30	Now	
8K \times 18	144K	20	25	30	Now	
64K \times 4	256K	17	20	25	Now	
64K \times 4 (OE)	256K	17	20	25	Now	
32K \times 8	256K	17	20	25	Now	
32K \times 9	288K	17	20	25	Now	
16K \times 12	192K module	25	35		Now	
16K \times 16	256K module	25	35		Now	
PART	CE	A12	t _{acc}	t _{OE}	V _{cc}	PACKAGE
TC55187	unlatched	unlatched	20/25/30	10/10/12	$\pm 10\%$	PLCC
TC55188	latched	latched	20/25/30	10/10/12	$\pm 10\%$	PLCC

In Touch with Tomorrow

TOSHIBA

TOSHIBA AMERICA ELECTRONIC COMPONENTS, INC.


© Toshiba America Electronic Components, Inc. TM Intel, 80486 and 82385 are trademarks of Intel Corporation. MST-012-88-1



High Speed. Low Power. Low Cost.

Impossible? Not anymore. Today, you can get high-speed operational amplifiers so advanced, they don't rob your system of power. And, better yet, PMI brings you this outstanding performance without holding you up on cost! For example, PMI's dual OP-260 in an 8-pin mini-DIP package offers a slew rate of $1000\text{V}/\mu\text{s}$ at the low cost of \$7.95.

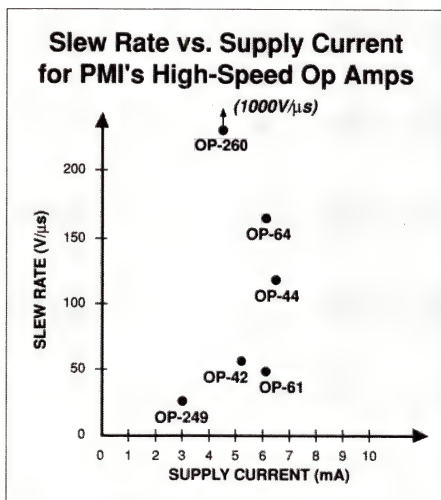Plus, we make it easy for you to design with our high-speed op amps.



Precision Monolithics Inc.
1500 Space Park Drive
Santa Clara, California 95054-3434

PMI has developed "PMISpice," advanced SPICE models including J-FET, Bipolar, even current feedback devices. At last, accurate AC modelling!

At PMI we've beat the trade-off between high speed and low power – at affordable prices! Circle the reader service number below to receive complete information on PMI's extensive family of high-speed op amps and advanced SPICE models. In a hurry?

Call us at 800-843-1515.
Or, FAX us at (408) 727-1550.

CIRCLE NO. 70

AD8



tandards are made to be broken. And bettered. And built upon. At Brooktree, we've created a feature-laden, pin-compatible family of RAMDACs that enable graphics systems designers to do just that.

Brooktree is synonymous with high resolution color graphics. Now we've got the whizziest graphics chips alive for laptops, multi-window color, 8514A clones, true color and image capture.

So get creative. Deviate. Get Brooktree. Because random selection may work fine for humans. But it's designer deviation that paces PC evolution.

**You can't control color
in multiple windows
unless you DV 8**

Oops! In the headlong rush toward windows environments, graphic-based applications and multitasking, color palette technology got left behind—almost.



Each window in a multi-tasking environment can control its own color palette—if you design in the Bt479.


Simply stated, each new application brought to your system's display will rewrite the RAMDAC with its own application-specific color palette, recoloring underlying applications in the process.

Naturally there are some red faces over this.

Voila! Introducing the Bt479, the first and only VGA-compatible RAMDAC that does windows right. It includes our proprietary WindowVu™ architecture to provide four separate color palettes, each storing 256 different colors and supporting up to 16 windows at a time.

To manage all that color we gave the Bt479 a window priority encoder that keeps track of each window's physical location on the screen, its priority in the stack and which palette it prefers.

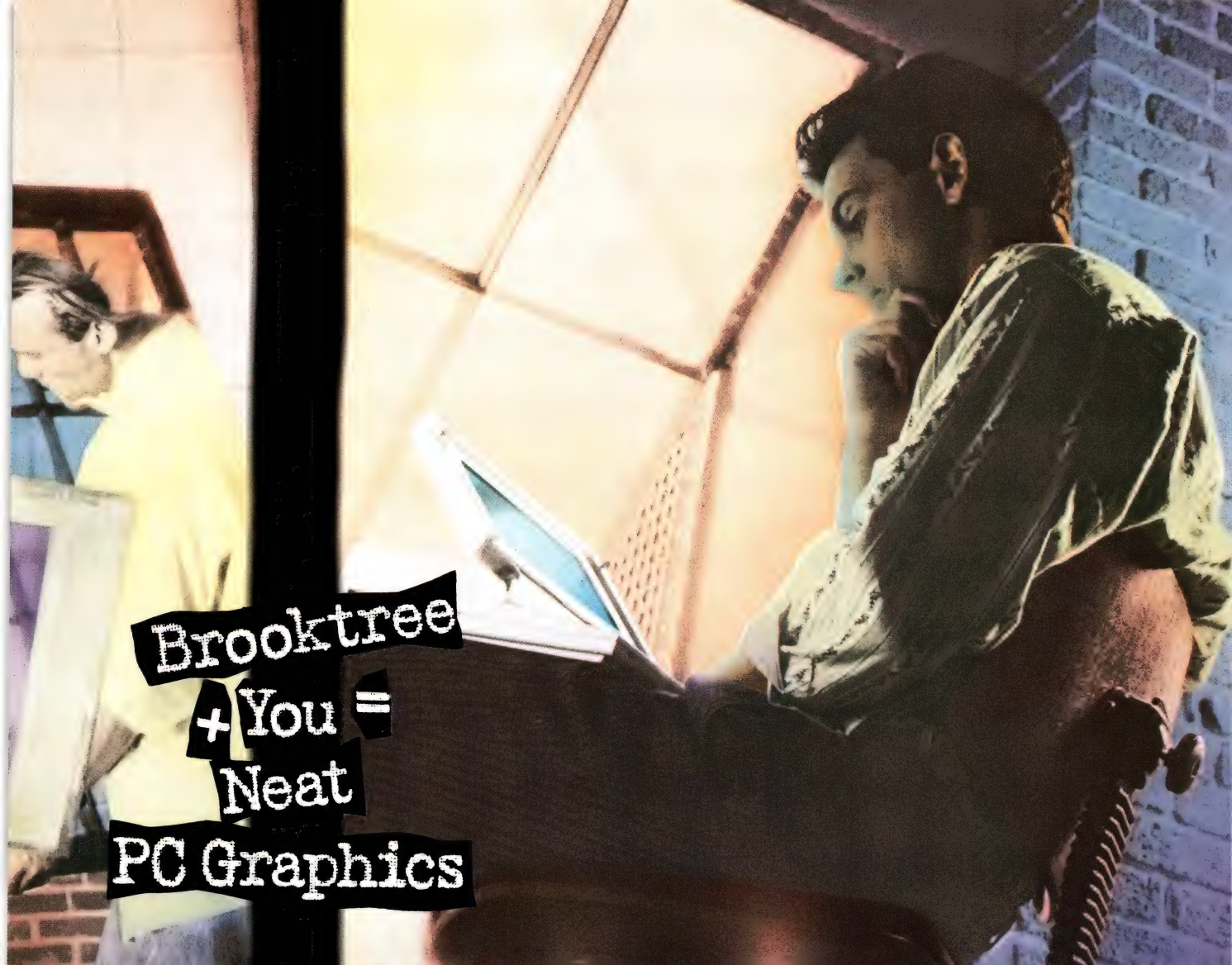For basic 640x480x4 VGA resolution, the Bt479 offers 16 separate 16x24 color palettes. For enhanced VGA at



Brooktree + You = Neat PC Graphics

800x600x8 or 8514A clones, each of the 16 windows may choose one of four 256x24 palettes.

And because the Bt479 is pin-compatible with Bt471, Bt476 and Bt478, it's easy to upgrade your system designs for multiple windows in color.

So show your true colors. Convert to Brooktree.

You can't do
power miser portables
unless you DV8

In the laptop/portable game, every ounce, every milli-amp counts. So we created two highly integrated color palette RAMDACs that go to sleep whenever an external VGA monitor isn't connected. Result: Power consumption plunges to under 5mW.

The Bt475 is an 80 MHz 256x18 PS/2-compatible RAMDAC. The Bt477, also 80 MHz and PS/2-compatible, is a 256x24

RAMDAC that is selectable for both 6-bit and 8-bit color.

Both devices feature automatic power down capability when their analog outputs are not required, keeping the palette alive for instant access.

There's no snow in the forecast with the Bt475/477. We've included anti-sparkle circuitry to eliminate the scattered palette conflicts that can occur when reading or writing to a RAMDAC during active video.

The on-chip voltage reference simplifies your design cycle, requiring just one external resistor to set the full-scale output current of the triple 8-bit DACs. And on-chip comparators verify proper connection of the CRT.

So don't just plagiarize desktop VGA circuitry for your laptop design. Innovate with Brooktree.



DV₈ to the future

lithic CMOS solution to programmable video timing, with programmable sync noise gating. And it's designed specifically for image capture

And if you think that's all pretty neat, wait until you see our color space conversion chips and other image manipulation breakthroughs. Or maybe you would like to see a family of CCIR601 RGB/YCr/Cb image transmission solutions? Stay tuned.

i DV. do u
8

Life's too short to not design the Brooktree way. So call 1-800-VIDEO IC for complete product details on our innovative graphics and imaging ICs. Just use the secret phrase: *IDV8. Do U?* Brooktree Corporation, 9950 Barnes Canyon Rd., San Diego, CA 92121. 619-452-7580. TLX 383 596. FAX 619-452-1249.

Brooktree®

Cut-and-paste technique lowers cost and cuts design cycle for custom microcontrollers

As the price of microcontrollers continues to drop, the available selection is becoming increasingly homogenized. Although commodity-type pricing is attractive, to differentiate your product from your competition's you should have a controller that suits the particular needs of your circuit.

If you can order millions at a time, custom-designed controllers provide the best price/performance ratio. But for new projects or smaller production runs, the tens of thousands of dollars required for nonrecurring engineering (NRE) charges alone make custom ICs impractical.

However, you can now order customer-specific integrated circuits, or CSICs (pronounced "sea-six"). By mixing and matching standard functional subsystems from the manufacturer's library, you can reduce or eliminate NRE charges and reduce the development cycle from years to approximately six months (from specification to working silicon circuits).

One significant difference between CSICs and ASICs lies in the performance and density of the chips. CSICs are built from hand-packed, highly optimized and field-tested circuits that are based on existing Motorola products. In contrast, ASIC development tools use automated short cuts that compromise performance for the sake of expediency.


Any alterations to the functional subsystems or microcontroller core and any rerouting of interconnections are executed manually to ensure high performance and quality. Peripheral functions include an assortment of memory modules, I/O ports, counters, timers, PWM outputs, real-time clocks, A/D and D/A converters, comparators, display drivers, and DTMF generators. The resulting CSIC chips can cost less than \$1 apiece, and you can order low-cost development tools for your CSIC that will help you create and debug your system software.

Motorola makes each CSIC a permanent part of its standard line of

products; therefore, if you want to be sure that none of your competitors will have access to the CSIC you've conceived, you can pay some NRE charge in exchange for a temporary permit of exclusivity.

In addition, if Motorola considers the quantity of microcontrollers you want to order too small to be practical for CSIC development, it will provide you with an interactive computer disk that lets you specify the chip functions, cost targets, expected volume, and turnaround time you require. The company then adds your information to a database, and—whenever possible—will combine similar requests to achieve sufficient volume to justify initiation of the CSIC's design. The company also screens requests to determine technical feasibility, profitability, and potential for becoming a successful standard product.—*J D Mosley*

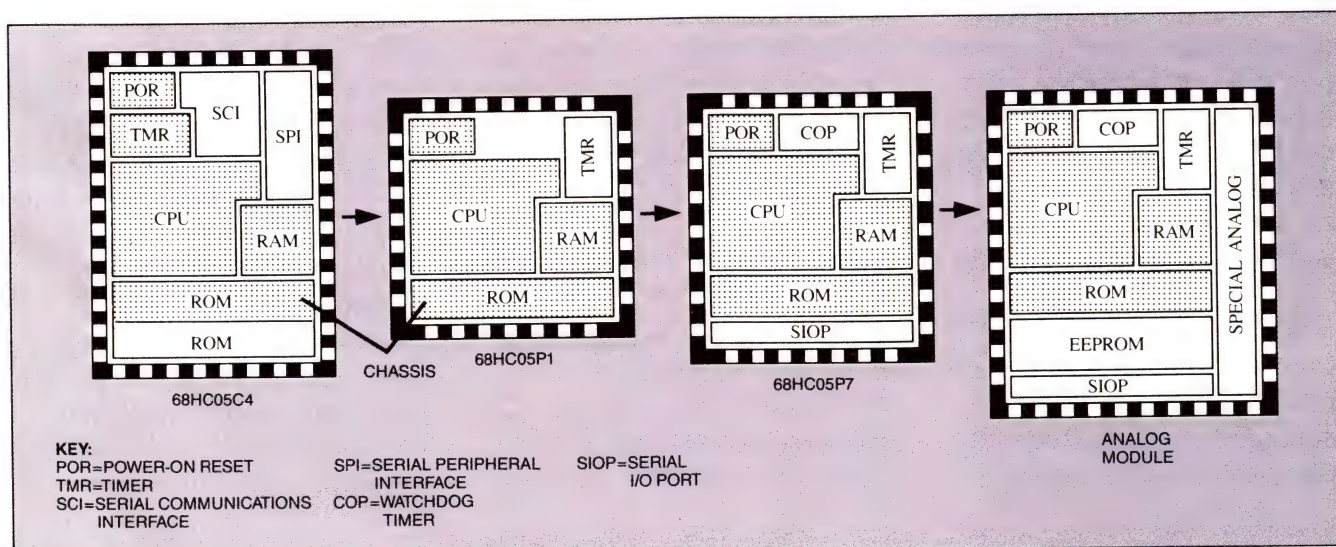Motorola Inc, 6501 Wm Cannon Dr W, Austin, TX 78735. Phone (512) 891-3260. Circle No. 730



By treating Motorola's microcontroller subsystems as building blocks, you can design customer-specific ICs that combine the high-performance characteristics of custom, hand-packed circuits with the low cost of ASIC development.

*The biggest little pellet
in the universe.*



*New pellet technology creates tantalum caps with
built-in fuse or smaller case.*

NEC is using innovative techniques to pack more capacitance power into each micron of its tantalum pellets. Therefore you can have a built-in fuse without any increase in case size, or a smaller case without any decrease in capacitance value.

Built-in fuse enhances safety.

Our SVE-Series tantalums incorporate a fuse to minimize damage from reverse current. Compatible with our R-Series,

the SVE capacitors are ideal for noise absorption in computers, terminals or measuring equipment. Choose from 21 types with ratings from 1.0 to 33 μ F and from 10 to 50 V DC.

**10 μ F power in
the industry's smallest case.**

R-Series extended-capacitance chips offer ratings up to 10 μ F in the A case measuring 1.6 x 3.2 x 1.6 mm. The extended R-Series consists of 46 device types with

ratings from 0.47 to 100 μ F and from 4 to 35 V DC.

NEC not only produces more tantalum caps than anyone in the industry, we also invest more of our resources in intensive R&D programs dedicated to giving you the best device for your design. To find out how our tantalums give you maximum performance per micron, call NEC today. Ask about the SVE-Series with the built-in fuse or R-Series extended-capacitance chips.

For fast answers, call us at:

USA Tel: 1-800-632-3531. TWX: 910-379-6985. W. Germany Tel: 0211-650302. Telex: 8589960. The Netherlands Tel: 040-445-845. Telex: 51923. Sweden Tel: 08-753-6020. Telex: 13839. France Tel: 1-3946-9617. Telex: 699499. Italy Tel: 02-6709108. Telex: 315355. UK Tel: 0908-691133. Telex: 826791. Hong Kong Tel: 3-755-9008. Telex: 54561. Taiwan Tel: 02-719-2377. Telex: 22372. Korea Tel: 02-551-0450. Fax: 02-551-0451. Singapore Tel: 4819881. Telex: 39726. Australia Tel: 03-267-6355. Telex: 38343.

Data Acquisition
Graphics, Analysis,
Communications and
Vision Applications

KEITHLEY

METRAYTE/ASYST/DAC

BECOMING
THE FIRST NAME
IN PC-BASED
DATA ACQUISITION
AND CONTROL
SYSTEMS IS EASY
WHEN YOU
HAVE A GOOD
LAST NAME.

You've known Keithley for years as the first name in sensitive test and measurement instrumentation. Now we're the first name in PC-based data acquisition and control hardware and software, too.

Introducing Keithley MetraByte/Asyst/DAC. The one company with the strength of three.

By bringing together three of the leaders in the PC-based data acquisition and control industry, Keithley now offers you a single source for hardware and software with the expertise to put it all together.

Keithley MetraByte and Keithley DAC manufacture the broadest range of high quality hardware in the data acquisition industry. Keithley Asyst supplies the acquisition and analysis software that works with the hardware from many manufacturers, as well as our own.

All together, Keithley MetraByte/Asyst/DAC has the answers...to hardware questions, to software questions, to application questions. And it's only one phone call away. You can reach the industry's most versatile technical support group at 508-880-3000.


And if you'd like to meet the people that can answer the questions, we offer seminars in cities nationwide. It's your chance to see how all the pieces fit together, discuss your application with an expert, and learn about the new products and support that could make your job a lot easier.

Keithley MetraByte/Asyst/DAC has it all. And, it's all in one catalog. Call 508-880-3000 and ask for your free copy.

When it comes to PC-based data acquisition and control hardware and software needs, it's all in a name. Keithley MetraByte/Asyst/DAC.

KEITHLEY METRAYTE/ASYST/DAC
PC Data Acquisition Hardware and Software

STD BUS 80C186

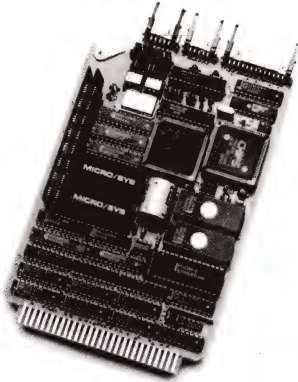

with
RUN.EXE™

THE CARD...

A high-performance computer on a single STD card. 10 MHz CPU, 512K 16-bit wide RAM, 384K EPROM, COM1, COM2, LPT1, clock/calendar, watchdog. Operates in both STD/MG standard transfer modes: 8-bit and 16-bit.

THE FIRMWARE...

Our popular RUN.EXE firmware lets you use your favorite PC language compiler and libraries. Then copy the .EXE file byte-for-byte into an EPROM and plug it in. Our "Implied AUTOEXEC.BAT" loads and runs your program on powerup.

THE SAVINGS...

At \$395 in OEM quantity, the SB8186 doesn't blow your budget. RUN.EXE saves memory and DOS royalty money, while its companion PC/XBUG debugger saves development time.

THE FAMILY...

Don't need 16-bits and 896K memory? V20RUN.EXE systems start at \$285 in quantity. Call today for details on the SB8186 and other RUN.EXE family members.



1011 Grand Central Ave.
Glendale, CA 91201
(818) 244-4600

RUN.EXE™ trademark MICRO/SYS, Inc.

CIRCLE NO. 11

PRODUCT UPDATE

Digital scope module extends logic analyzer


The 30DSM digital-storage-oscilloscope (DSO) module for Prism 3002 series logic analyzers isn't the first DSO to be paired with a logic analyzer. Both Hewlett-Packard (Palo Alto, CA) and Orion Instruments (Redwood City, CA) have offered DSOs combined with logic analyzers. The distinguishing features of the 30DSM are a 300-MHz bandwidth, a single-channel sample rate of 500M samples/sec (250M samples/sec dual channel), and 8-bit resolution. These specifications make it the highest performing DSO to be integrated with a logic analyzer.

One of the benefits of a combined logic analyzer and DSO is cross-triggering. The logic analyzer sends a trigger signal to the DSO when it detects a trigger event. A Prism 3002 series logic analyzer and a 30DSM combine to support a cross-triggering mode, in addition to other DSO triggering modes.

Another benefit of the combined logic analyzer and DSO is a time-correlated display of digital and analog waveforms. On the same instrument display, you can simultaneously check analog and digital waveforms and their timing relationships. This time-correlated display helps speed your operations when tracking down problems or verifying circuit operation.

Although the DSO module does not have as complete a set of automatic parameter measurements as you would find on a high-performance stand-alone DSO, it does offer frequency, time-interval, amplitude, and cursor measurements.

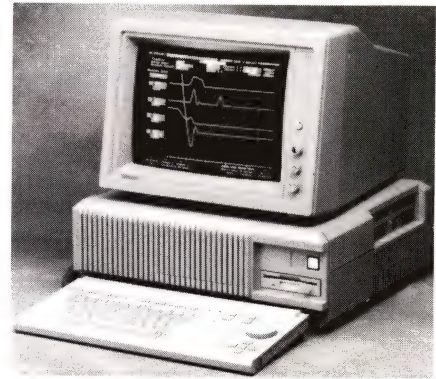Some other features of the 30DSM that are useful on repetitive waveforms are its averaging function to reduce noise and its envelope mode to capture waveform vari-



The 30DSM is a high-performance DSO module for the Prism 3002 logic analyzer. The module provides two 300-MHz bandwidth channels having 8-bit resolution. The DSO display is time correlated with logic analyzer data.

ation over time.

The digital-scope module stores data in a 32k-word record for single-channel acquisitions and in two 16k-word records for dual-channel acquisitions. Nonvolatile storage of waveforms and instrument setups are possible on the Prism 3002 series platform disk.

The 30DSM rounds out the capabilities of the Prism 3002 system, whose logic-analysis capabilities include state analysis, or synchronous clocking, to 300 MHz; timing analysis to 2 GHz; and dual-threshold margin analysis to 200 MHz. The Prism 3002 also has ROM-emulation capability to speed debug operations.

The Prism 3002 series accommodates any combination of logic analysis and DSO modules to a maximum of 10 modules. The 30DSM sells for \$6000.

—Doug Conner


Tektronix Inc, Logic Analyzer
Div, Box 12132, Portland, OR
97212. Phone (800) 245-2036.

Circle No. 731

Z I L O G

REAL SCC CHOICES

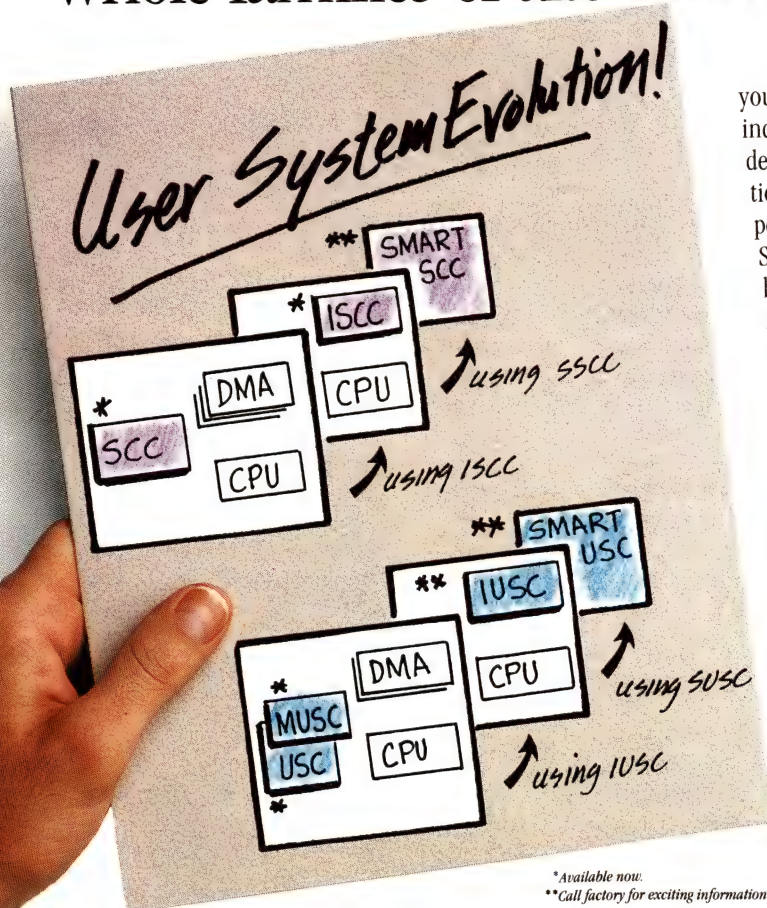When you need more than the basic SCC, we give you whole families of alternatives. *Done right!*



At Zilog, we develop products the way you develop systems. Starting with our industry standard SCC, for example, we've developed families of serial communications controllers that give you the system performance your applications call for. Smaller, more integrated systems are fast becoming true "systems on silicon." And Zilog's Superintegration™ technology helps make denser, faster, simpler systems a smooth, natural evolution. With products that are fully upwardly compatible, we solve your systems problems on silicon. As new applications dictate new requirements, you can be sure Zilog will provide the new versions and the new generations you'll need. When you need them. Off the shelf. At a cost that makes sense. Isn't that really the way things should be? Contact your local Zilog sales office or your authorized distributor today. Zilog, Inc., 210 Hacienda Ave., Campbell, CA 95008, (408) 370-8000.

*Available now.
**Call factory for exciting information.

Right product. Right price. Right away.



ZILOG SALES OFFICES: CA (408) 370-8120, (714) 838-7800, (818) 707-2160, CO (303) 494-2905, FL (813) 585-2533, GA (404) 448-9370, IL (312) 517-8080, NH (603) 888-8590, MN (612) 831-7611, NJ (201) 382-5700, OH (216) 447-1480, PA (215) 653-0230, TX (214) 987-9987, WA (206) 523-3591, CANADA Toronto (416) 673-0634, UNITED KINGDOM Maidenhead (44) (628) 39200, W. GERMANY Munich (49) (89) 672045, JAPAN Tokyo (81) (3) 587-0528, HONG KONG Kowloon (852) (3) 723-8979, KOREA (82) (2) 552-5401, TAIWAN (886) (2) 741-3125, SINGAPORE 65-235 7155, **DISTRIBUTORS:** U.S. Anthem Electronics, Hall-Mark Electronics, JAN Devices, Inc., Schweber Electronics, Vargas Electronics, Western Microtechnology, CANADA Future Electronics, SEMAD, LATIN AMERICA Argentina-Yel.-(1) 46-2211, Brazil-Digibyte (011) 581-1945, Semiconductores Profesionales (5) 536-1312.

SNA Systems from 20 Hz to 22 GHz

Why the communications industry quite obviously prefers our Spectrum and Network Analyzers.

The technical world associates Wandel & Goltermann with peak performance in electronic measurements. In five decades we have become a world leader in measuring-technology for analog and digital transmission systems. Our leadership in experience has been used to particular advantage in our Spectrum and Network Analyzers. You can always expect the best from Wandel & Goltermann. Our SNA Systems offer new dimensions in peak performance. User friendliness and ultrahigh product quality are our hallmarks. Let's take an example: in the realization of our Synthesizers we have made no compromises. The high spectral purity and exceptional stability allow, in conjunction with the 3 Hz bandwidth, measurements of the best quality reproduction and resolution. Return the reply card or write to the following address for full information about the entire SNA-family.



USA: Wandel & Goltermann,
Inc., 1030 Swabia Court, R. T.P., NC 27709,
Tel.: (919) 941-5730, Telex II: 810-621-0002,
FAX (919) 941-5751. **Canada:**
Wandel & Goltermann Inc., 21 Rolark
Drive, Scarborough, Ontario M1R3B1,
Tel.: (416) 291-7121. **Worldwide:**
Wandel & Goltermann,
VMW, Postfach 1262,
D-7412 Eningen,
Tel. + (49) 71 21-86-0,
Tlx. 7 29 833
Fax + (49) 71 21-884 04
CIRCLE NO. 131
Please Visit Us at CeBIT
Hanover, 21.-28.3.90
Hall 13, Stand A18/B17



We drive quality to heights!

SNA Systems from
Wandel & Goltermann
From 30 Hz to 22 GHz.
First class in all performance
categories.

USA: Wandel & Goltermann, Inc.,
1030 Swabia Court, R. T. P., NC 27709,
Tel.: (919) 941-5730, Telex #: 810-821-0005,
FAX (919) 941-5751

Canada: Wandel & Goltermann Inc.,
21 Rolark Drive Scarborough, Ontario M1R 3B1,
Tel.: (416) 291-7121

Worldwide: Wandel & Goltermann, VMW,
Postfach 12 62, D-7412 Eningen,
Tel. F (49) 71 21-86-0, Tlx. 7 29 833
Fax + (49) 71 21-8 84 04

Wandel & Goltermann

Electronic Measurement Technology

COUPON

Name

Company/Dept.

Street/P.O. Box

City/Postcode


Telephone

E 7.89/VMW/05/4C/NA
EDN011890
EM/2



EDN SPECIAL REPORT

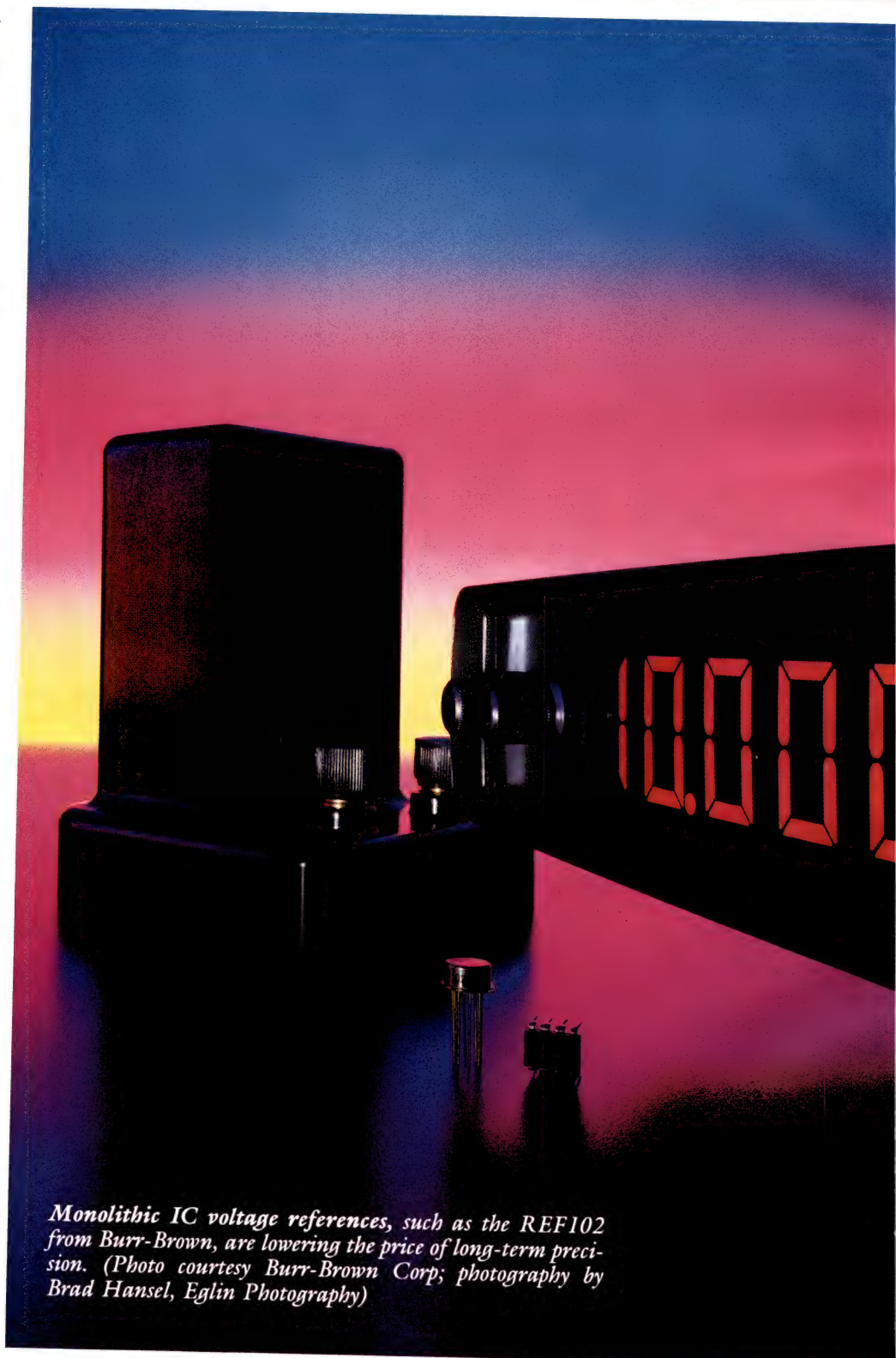Although seemingly mundane, voltage references play an important role in a wide range of applications. Manufacturers offer a variety of types from which to choose, but choose carefully and with an eye to what's important for your application.



Monolithic IC voltage references, such as the REF102 from Burr-Brown, are lowering the price of long-term precision. (Photo courtesy Burr-Brown Corp; photography by Brad Hansel, Eglin Photography)

Voltage references

Integrated-circuit voltage references are available in a variety of voltage ratings and package styles and with widely differing specifications. All, however, base their performance on the action of either a zener diode or a bandgap cell, each of which has its own peculiar set of characteristics. The most widely used reference is probably the temperature-compensated zener diode, particularly for voltages above 5V. Although bandgap cells are often scaled to provide voltages as high as 10V, the principal advantage of a bandgap reference lies in its ability to provide a stable low voltage such as 1.2, 2.5, or 5V. Before looking at the specifications of some of the available devices, consider how each of the two basic types works.

Although discrete zener diodes are available in voltage ratings as low as 1.8V to as high as 200V, they don't make very good references. The typical 10% tolerance and poor temperature characteristics of these devices preclude their use in applications requiring even a moderate degree of precision and stability. Moreover, zener diodes rated at less than about 6V suffer from high output impedance. For these reasons, discrete zener-diode-based references include temperature compensation and, in the case of IC types, the additional circuitry needed to obtain specific performance objectives.

A zener diode has two distinctly different reverse-bias characteristics: zener breakdown and avalanche break-

down, both of which are evident in the 4- to 6V range. The zener breakdown voltage (**Fig 1**) *decreases* as the temperature increases (negative TC); the avalanche breakdown voltage *increases* as the temperature increases (positive TC). At low current values, the zener effect dominates; at higher values, the avalanche effect dominates. Because these current-dependent effects oppose each other, you can, at least theoretically, cancel them by adjusting the operating point, thus obtaining a TC of zero.

Practical temperature compensation

Another way to provide temperature compensation is by connecting a conventional forward-biased diode in series with a zener diode operating in the avalanche mode. In this case, the negative TC ($-2 \text{ mV}/^\circ\text{C}$) of the conventional diode cancels the positive TC of the zener diode. Manufacturers use this method in most zener-based references.

If you're primarily concerned with temperature stability and the exact reference voltage is unimportant, a good combination might be a 5.6V zener diode in series with a single forward-biased diode. **Fig 2** illustrates this simple circuit. The 0.7V typically developed across forward-biased diode D_1 adds to the 5.6V of zener diode D_2 to provide a temperature-compensated reference of about 6.3V. Resistor R_1 sets the current level through the diodes. Although you can buy such a diode combination in discrete form (the 6.2V 1N821 series is

Dave Pryce,
Associate Editor

Although they are available in a wide range of voltages, the typical 10% tolerance and poor TC of a conventional zener diode preclude its use as a reference.

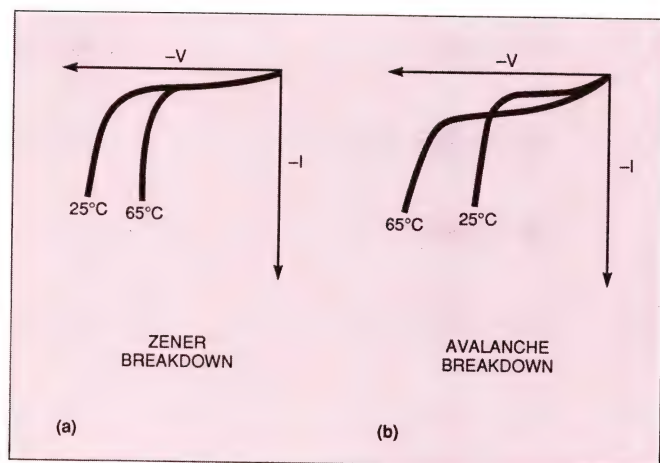


Fig 1—A zener diode has two different breakdown characteristics. In the zener mode (a), the breakdown voltage decreases with increasing temperature. In the avalanche mode (b), the breakdown voltage increases with increasing temperature.

similar), most voltage references come in IC form, which offers advantages over discrete versions.

In its most basic form, the circuit for a zener-based IC reference is similar to that of Fig 3. The IC can be either a hybrid or monolithic type; the choice depends on the manufacturer's objectives and processing capabilities. In this circuit, R_4 provides the startup current for the diode combination, thus setting the positive input of the op amp at V_Z . R_3 sets the desired bias current for the diode combination. The current through R_3 equals $(V_{OUT} - V_Z)/R_3$ and remains at that value, independent of the supply voltage and amplifier loading.

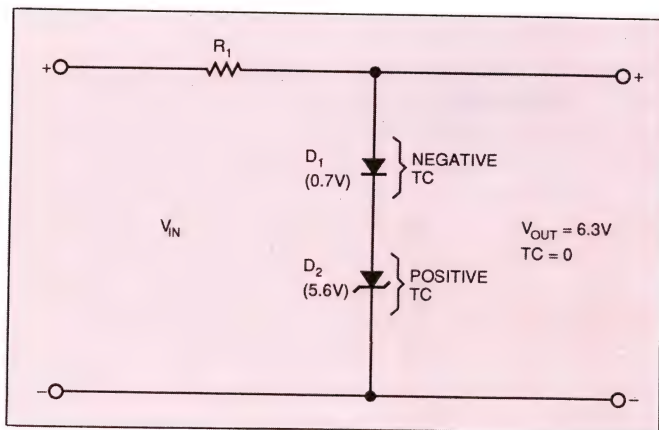


Fig 2—In this simple voltage reference, the voltage across forward-biased diode D_1 adds to the zener voltage of D_2 to provide an output of 6.3V. The negative TC of D_1 cancels the positive TC of D_2 to provide temperature compensation.

A zener-based IC reference has several advantages over a simple discrete reference. Manufacturers can scale the output voltage to a value different from that of the zener voltage and, by trimming the ratio of R_1 to R_2 , set the output voltage to the desired accuracy. It's also possible to trim R_3 to optimize the bias current of the zener diode, thus decreasing its output temperature coefficient.

Many of today's monolithic zener-based references have ion-implanted buried zeners, which exhibit superior TC characteristics and better stability over time than do surface-based zeners. TC specifications as low as 1 ppm/°C are possible for a buried-zener reference. Compared with a bandgap reference, a zener-based reference also has less output noise because the zener voltage needs less amplification than does a 1.2V bandgap cell. Although frequency dependent, a typical 10V bandgap reference might have two to three times more noise than an equivalent zener-based reference.

Consider the bandgap reference

Bandgap references are available with output-voltage ratings of about 1.2 to 10V. The 1.2, 2.5, and 5V types can operate from lower supply voltages than can zener-based references, a distinct advantage in some applications. Although bandgap cells typically have a lower output impedance than low-voltage zeners, the additional circuitry used in both bandgap and zener-based references usually masks any difference.

Because the bandgap voltage of about 1.2V is often scaled to a higher voltage by an internal amplifier, bandgap references of 5 and 10V tend to have more

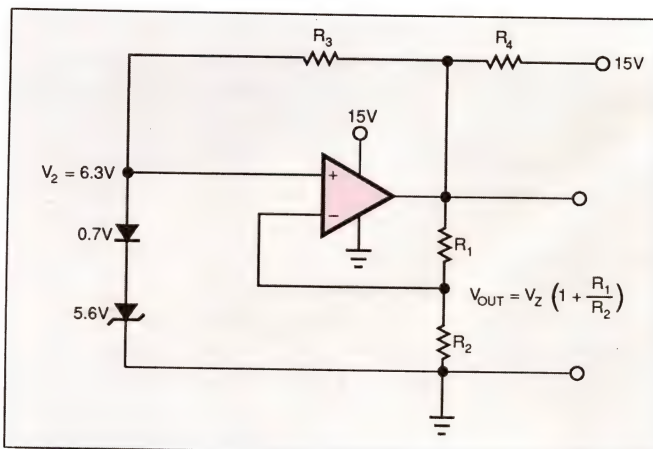


Fig 3—This basic IC reference uses a temperature-compensated zener diode, an op amp, and voltage divider R_1 and R_2 to scale the zener voltage to a higher output voltage.

noise than equivalent zener-based references, which need much less amplification. Moreover, the TC of a well-designed bandgap reference, although very good, is not quite as good as that of the best buried-zener references. Typically, the TCs of bandgap references range from about 5 to 50 ppm/°C.

The operation of a bandgap reference is based on the difference between the forward base-emitter voltage (V_{BE}) of two similar transistors operating at the same current but at different current densities. Extrapolated to absolute zero, V_{BE} is equal to 1.205V, the bandgap voltage of silicon. By adding a voltage to V_{BE} that increases proportionally with temperature at the same rate that V_{BE} decreases, a bandgap reference can, theoretically, generate a constant 1.205V at any temperature. Practically, however, designers can only approach that ideal.

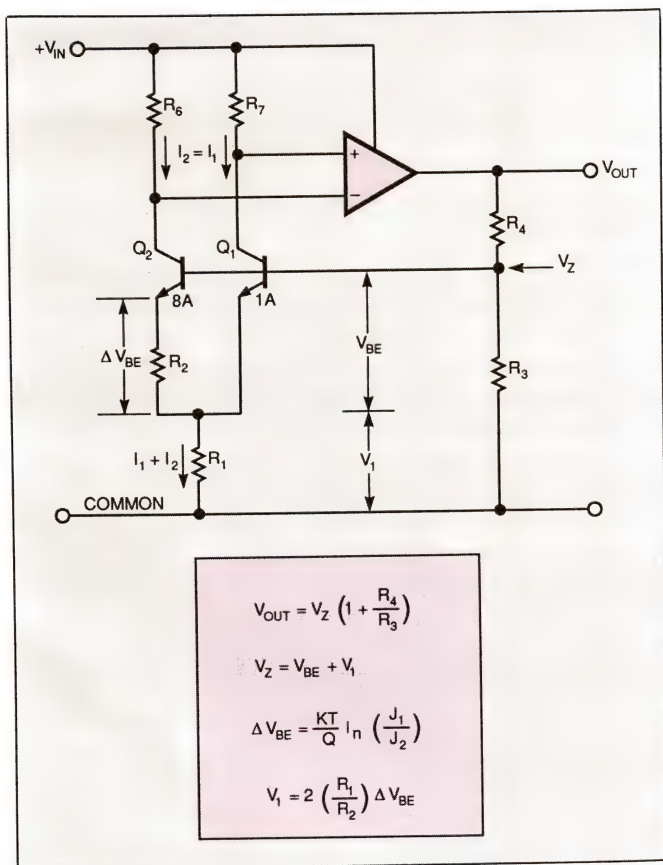


Fig 4—The operation of bandgap reference depends on the difference between the base-emitter voltage of two similar transistors operating at different current densities. In this basic circuit, the emitter area of Q_2 is eight times that of Q_1 . And although both transistors operate at the same current, their current densities are vastly different.

Fig 4 illustrates the basic operation of a bandgap circuit. In this circuit, the emitter area of Q_2 is eight times that of Q_1 . Calculations show that this ratio provides a near-zero TC by generating an optimum difference in current densities (J_1 and J_2) between Q_1 and Q_2 . **Ref 1** and **Ref 2** provide a rigorous analysis of these calculations. V_{BE} is the base-emitter voltage of Q_1 , and ΔV_{BE} , which appears across R_2 , is scaled by the R_1/R_2 ratio to V_1 . This voltage has a TC that cancels that of V_{BE} . The op amp raises the V_Z bandgap voltage, which is the sum of V_1 and V_{BE} , to a higher voltage at the output of the reference. This voltage, V_{OUT} , is determined by $(R_4/R_3) + 1$ and is usually in the range of 2.5 to 10V, although it can be the bandgap voltage itself.

Designers of IC bandgap references often incorporate additional features to make the devices more flexible. For example, some circuits have terminals brought out from an internal voltage divider, which lets you program a variety of fixed, calibrated voltages, such as 2.5, 5, 7.5, and 10V. You can also use these terminals with external resistors to set arbitrary voltages. Although special-purpose hybrid types are available, most bandgap references are fabricated in the less expensive monolithic form.

Look at the specifications

An ideal voltage reference would have no errors at all. Its output voltage would be initially exact and not vary with time, temperature, input voltage, or load conditions. In the real world, an ideal reference is not possible, and manufacturers provide specifications to let the user know what the expected variations are for a number of key parameters. Of prime importance are the specifications for output voltage error, temperature coefficient, line regulation, load regulation, and long-term stability. You should look at these specifications both individually and collectively to obtain a true picture of a reference's expected performance.

The *output voltage error* is the initial, untrimmed accuracy of the reference at 25°C at a specified input voltage. Specified in millivolts or a percentage, the measurement is normally made using a device that is traceable to a voltage standard. Some references provide pin connections for trimming their initial accuracy with an external potentiometer.

The *temperature coefficient* of a reference is its average change in output voltage as a function of temperature compared with its value at 25°C. Specified in ppm/°C or mV/°C, the TC is independent of variations in other operating conditions.

Zener-based IC references use temperature-compensating diodes and op-amp circuitry to obtain voltage-reference performance.

Line regulation is the change in output voltage for a specified change in input voltage. Usually specified in %/V or $\mu\text{V}/\text{V}$ of input change, line regulation is a measure of a reference's ability to handle variations in supply voltage.

Load regulation is the change in output voltage for a specified change in load current. Specified in $\mu\text{V}/\text{mA}$, %/mA, or ohms of dc output resistance, load regulation includes any self-heating effects due to increased power dissipation at high values of load current.

Long-term stability is the change in the output voltage of a reference as a function of time. Specified in ppm/1000 hours at a specific temperature, long-term stability is difficult to verify. As a result, manufacturers usually provide only typical specifications based on device data collected during the characterization process.

Although these specifications are the most important, others, such as *dynamic impedance* and *noise*, may also be of concern. In particular, noise is an important consideration when using a reference with a high-resolution A/D or D/A converter. For example, a 12-bit A/D converter has an LSB weight of about 0.0244% of its full-scale range. For a full-scale range of 10V, the value of the LSB weight would be about 2.44 mV. The noise from the reference should be less than 10% of that value, or less than 244 μV . For a 16-bit converter, the requirement gets even tougher—the LSB weight is about 0.0015% and the reference noise should be less than 15 μV . You need to look carefully at the data sheet to make sure that the specifications you're interested in are well defined. Data sheets for some low-cost references don't always provide information on all possible parameters.

The level of sophistication and pricing for voltage references runs the gamut from simple and inexpensive to complex and costly. Devices are available for, literally, almost any conceivable application.

Typical of the lower-cost, general-purpose references is the LM136 series, which is available from companies such as National Semiconductor, SGS-Thomson, and Texas Instruments. Categorized for operation over the military, industrial, and commercial temperature ranges, respectively, the LM136, -236, and -336 are bandgap references with an output voltage of 2.5V and an accuracy of 1 or 2%. These references find application in digital voltmeters, power supplies, and op amp circuitry. They're particularly useful in obtaining a stable reference from a 5V logic supply.

Because the LM136, -236, and -336 operate as shunt




Many precision references have a 10V output. The nominal 10.000V output of the REF102 from Burr-Brown features an initial accuracy of ± 2.5 mV and a drift of 2.5 ppm/ $^{\circ}\text{C}$ over the -25 to $+85^{\circ}\text{C}$ temperature range.

regulators, you can use them as either positive or negative references. Characterized for operation at 1 mA, these references have a typical TC of 3.5 mV from -25 to $+85^{\circ}\text{C}$ and 12 mV from -55 to $+125^{\circ}\text{C}$. A pin connection lets you trim the devices externally for minimum temperature drift. At 25°C , the typical dynamic impedance is 0.2Ω , and long-term stability is ± 20 ppm. Available in TO-92, TO-46, and SO-8 packages, commercial and industrial versions range in price from about \$0.70 to \$1.30 (1000).

Although better known for its power-supply and motion-control circuits, Silicon General also has a modest line of bandgap references. Its SG103 series—equivalent to National Semiconductor's discontinued LM103 series—is available in 13 voltage ratings ranging from 1.8 to 5.6V. Packaged in a low-profile TO-46 metal can, the \$12.75 (100) SG103 complies with MIL-STD-883B and is specified for operation over the military temperature range of -55 to $+125^{\circ}\text{C}$. Primarily used in low-voltage power supplies, the 2-terminal device features a typical TC of -1 mV/ $^{\circ}\text{C}$ and a dynamic impedance of 5Ω .

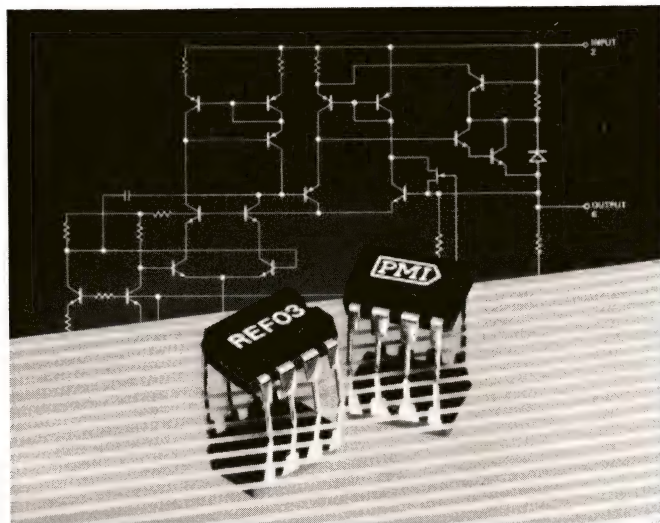Other manufacturers of bandgap voltage references include Analog Devices, Linear Technology, Maxim Integrated Products, Motorola Semiconductor, Precision Monolithics (PMI), and Teledyne Semiconductor. Many of these companies' references are interchangeable



Low-cost references, such as this 2.5V bandgap device from PMI, often come in 8-pin plastic DIPs.

with devices from other manufacturers, and some offer improved performance compared with the original versions. For example, the LT1019 from Linear Technology is a direct and, in many cases, improved replacement for many bandgap references, including the AD580, AD581, REF-01, REF-02, MC1400, MC1401, and LM168.

Available in voltage ratings of 2.5, 4.5, 5, and 10V, the LT1019 is a third-generation device utilizing thin-film technology and wafer-level trimming of both the reference voltage and the output voltage. Typical specifications for the LT1019 include an output voltage error of 0.02%, a TC of 5 ppm/°C, line regulation of 0.5 ppm/V, and load regulation of 0.1 mV/mA. For low-drift applications, you can achieve a TC of less than 2 ppm/°C by operating the LT1019 in a heated mode using its internal resistor and an external amplifier. Available in either an 8-pin metal can or plastic DIP, the LT1019's prices start at \$3.90 (100). Applications for this device include A/D and D/A converters, V/F converters, precision regulators, and strain-gauge bridge excitation.

Maxim Integrated Products offers improved replacements for the 10V REF-01 and the 5V REF-02 bandgap references, two standards introduced by PMI. Maxim's 10V MAX674 and 5V MAX675 have a pretrimmed output voltage that is accurate to $\pm 0.15\%$, compared with $\pm 0.3\%$ for the REF-01 and REF-02. In addition, the load regulation of 0.002%/mA for the MAX674 and MAX675 is somewhat better than that specified for the REF-01 and REF-02. The MAX674

and MAX675 are available in 8-pin metal cans, plastic DIPs, and SO packages; prices start at \$4.25 (100).

Designed for large-volume customers who need a precision reference but can't justify a high cost, the REF-03 from Precision Monolithics 2.5V bandgap reference offers good performance at a unit cost of only \$1.75 (100). The REF-03 features a typical output voltage tolerance of $\pm 0.2\%$ ($\pm 0.6\%$ max) and a typical TC of 10 ppm/°C (50 ppm/°C max). Typical line and load regulation are 0.002%/V and 0.006%/mA, respectively. The REF-03 is available in 8-pin DIPs and 8-pin SO packages.

A companion to the REF-03, the REF-43 operates at a lower supply current (450 μ A max vs 1.4 mA max) and offers better performance, albeit at the higher starting price of \$3.75 (100). The 2.5V REF-43 features a maximum output voltage tolerance of $\pm 0.05\%$ and a maximum TC of 20 ppm/°C. The REF-43 is available in a variety of package styles, including 8-pin TO-99s, 8-pin DIPs, and 20-pin LCCs.

For very low-cost applications, Teledyne Semiconductor offers its 1.25V TSC04 and 2.5V TSC05 bandgap references. Although these devices provide only moderate performance, they can satisfy many applications and—at \$0.70 (100) in a TO-92 plastic package (\$0.95 in TO-52 metal)—are cost effective. The TSC04 and TSC05, which can operate over a range of 20 μ A to 20 mA, have an output tolerance of 2% and a maximum TC of 50 ppm/°C. By not using thin-film resistors in these devices, Teledyne is able to reduce manufacturing complexity—and cost. Teledyne also offers bandgap references rated at 5 and 10V, which offer tighter specifications at higher costs.

An unusual device, the micropower LT1034 from Linear Technology, combines a 1.2 or 2.5V bandgap reference with a 7V zener-based auxiliary reference in a single package. Operating at 100 μ A, the bandgap reference features a 1% initial tolerance, a TC of 20 ppm/°C typ, and a dynamic impedance of 0.5 Ω typ. Useful for less demanding applications, the 7V reference has a 5% initial tolerance and a typical TC of 40 ppm/°C. The LT1034 comes in 3-pin TO-46 or TO-92 packages; prices start at \$2.15 (100).

Zener-based references

Although bandgap references that can operate from 5V supplies are widely available, zener-based references, which are usually used with analog circuits that operate from 12 to 15V supplies, are just as plentiful. In addition, compared with bandgap references, many

Bandgap references can provide good performance and, because of their low-voltage capabilities, are particularly useful in circuits operating from 5V logic supplies.

zener-based references have superior performance characteristics. Major suppliers of zener-based references include Analog Devices, Burr-Brown, Linear Technology, National Semiconductor, and Precision Monolithics.

Typical of the high-performance possible with zener-based references is the 10V REF102 from Burr-Brown. Available in a range of temperature grades and degrees of precision, the REF102's best incarnation features a maximum initial error of only ± 2.5 mV, a TC of 2.5 ppm/ $^{\circ}$ C, line regulation of 1 ppm/V, load regulation of 10 ppm/mA, and noise of only 5 μ V p-p from 0.1 to 10 Hz. Moreover, the REF102 achieves its performance without the use of a heater, which results in a quiescent current of only 1.4 mA. The REF102's combination of specifications make this device well suited for use with high-resolution A/D and D/A converters or as an accurate comparator threshold reference.

Available in industrial and military temperature grades and in three grades of precision, prices for the REF102 range from \$2.75 to \$14 (100).

Analog Devices offers a wide range of both bandgap and zener-based precision references as part of its line of data conversion products. Unique among its offerings is the AD689, an 8.192V zener-based reference that bridges the gap between 5 and 10V references. Many data-conversion and analog circuits operate from ± 12 V supplies, which can vary over a 10% range. However, using a 10V reference when the supply drops to ± 10.8 V is a marginal situation at best. Before the availability of the AD689, designers were forced to choose between a 5V bandgap reference or a less complete zener reference between 5 and about 7V. The 8.192V AD689 lets designers maximize a circuit's signal swing when operating from 12V supplies.

The AD689 uses an ion-implanted zener diode and

Manufacturers of voltage references

For more information on voltage references such as those discussed in this article, circle the appropriate numbers on the Information Retrieval Service card or use EDN's Express Request service. When you contact any of the following manufacturers directly, please let them know you saw their products in EDN.

Analog Devices
1 Technology Way
Norwood, MA 02062
(617) 329-4700
Circle No. 650

Burr-Brown Corp
Box 11400
Tucson, AZ 85734
(602) 746-1111
Circle No. 651

Cherry Semiconductor Corp
2000 S County Trail
East Greenwich, RI 02818
(401) 885-3600
Circle No. 652

Linear Technology Corp
1630 McCarthy Blvd
Milpitas, CA 95035
(408) 432-1900
Circle No. 653

Maxim Integrated Products
120 San Gabriel Dr
Sunnyvale, CA 94086
(408) 737-7600
Circle No. 654

Motorola Inc
Linear IC Div
7402 S Price Rd, MD-PR340
Tempe, AZ 85283
(602) 897-3840
Circle No. 655

National Semiconductor Corp
Box 58090
Santa Clara, CA 95052
(408) 721-5000
Circle No. 656

Precision Monolithics Inc
Box 58020
Santa Clara, CA 95052
(408) 727-9222
Circle No. 657

SGS-Thomson Microelectronics
1000 E Bell Rd
Phoenix, AZ 85022
(602) 867-6100
Circle No. 658

Silicon General
11861 Western Ave
Garden Grove, CA 92641
(714) 898-8121
Circle No. 659

Teledyne Semiconductor
1300 Terra Bella Ave
Mountain View, CA 94039
(415) 968-9241
Circle No. 660

Texas Instruments
Box 809066
Dallas, TX 75380
(800) 232-3200, ext 700
Circle No. 661

VOTE...

Please also use the Information Retrieval Service card to rate this article (circle one):


High Interest 488

Medium Interest 489

Low Interest 490


Type TN Lab Grade Low TC Precision Resistors

New

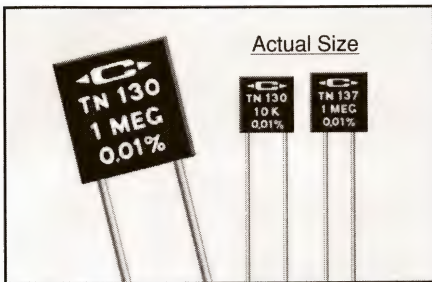


1 K to 1 Meg, Tolerance to $\pm 0.01\%$
Low TC to 5 ppm/ $^{\circ}\text{C}$, 0°C to 70°C
• **Non-Inductive Design**
• Tolerance of $\pm 0.01\%$, $\pm 0.025\%$, $\pm 0.05\%$, $\pm 0.1\%$, $\pm 0.25\%$, $\pm 0.50\%$ or $\pm 1\%$
• Low TC of 5, 10 or 20 ppm/ $^{\circ}\text{C}$, 0 to 70°C
• Space Efficient Radial-Lead Design
For Type TN data, circle number 101

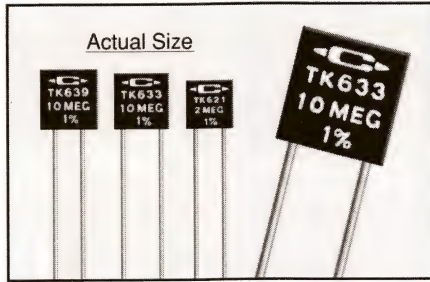Type TK Low TC Precision Radial-Lead Film Resistors



Low TC to 5 ppm/ $^{\circ}\text{C}$, -55°C to 125°C
• **Non-Inductive Design**
• Resistance Range 1 Kohm to 10 Meg
• TC of 5, 10 or 20 ppm/ $^{\circ}\text{C}$, -55 to 125°C
• Tolerance of $\pm 1\%$ (available to $\pm 0.05\%$)
• Space Efficient Radial-Lead Design
For Type TK data, circle number 102

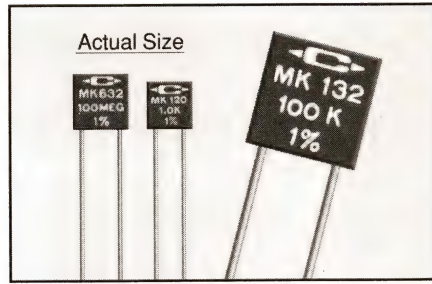Type MK Precision Power Radial-Lead Film Resistors




0.50 Watt (CK05), 0.75 Watt (CK06)
• **Non-Inductive Design**
• Resistance Range 1 Ω to 100 Meg
• TC as low as 50 ppm/ $^{\circ}\text{C}$, -15°C to 105°C
• Tolerance of $\pm 1\%$ (available to $\pm 0.1\%$)
• Space Efficient Radial-Lead Design
For Type MK data, circle number 103

CADDOCK® Resistor Technology

Precision and Ultra Precision Resistors and Resistor Networks
with a 25 year record for solving problems across the board!

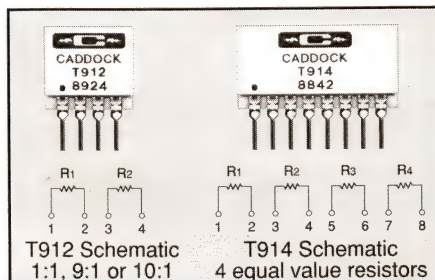Type T912 and Type T914 Precision Resistor Networks




Ultra Precise Ratios to 0.01%

- 14 Standard Resistance Values from 1 Kohm to 1 Meg (Custom to 2 Meg)
- Ratio Tolerance from 0.01% to 0.1%
- Ratio TC of 2, 5 or 10 ppm/ $^{\circ}\text{C}$, 0 to 70°C
- Custom ratios available, 1:1 to 250:1

For Type T912/T914 data, circle number 104

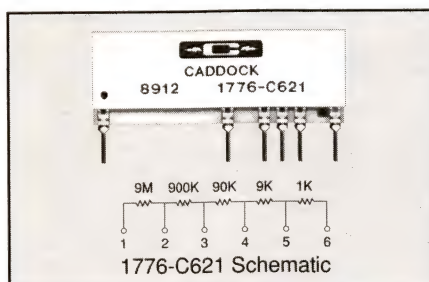Type 1776 Precision Decade Voltage Dividers




Voltage Division 10:1 to 10,000:1

- Ratio Tolerance 0.02%, 0.05%, 0.1%, 0.25% or 0.5%
- Ratio TC of 5, 10, 25 or 50 ppm/ $^{\circ}\text{C}$, from 0°C to 70°C
- Select from 39 Different Models
- Voltage Rating to 1,200 Volts

For Type 1776 data, circle number 105

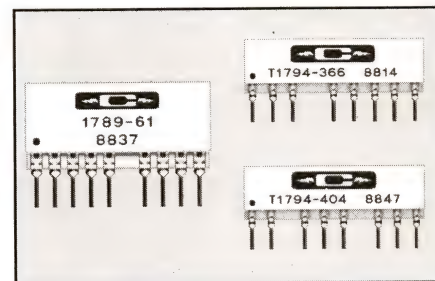Custom Precision and Ultra-Precision SIP Networks



Ratio Tolerance to 0.01%

- Resistance Range 0.5 ohm to 50 Meg
- Abs. Tolerance from $\pm 0.025\%$ to $\pm 1\%$
- Ratio Tolerance from 0.01% to 1%
- Abs. TC of 15 ppm, 25 ppm, 50 ppm or 80 ppm/ $^{\circ}\text{C}$, from 0°C to 70°C
- Ratio TC of 5 ppm, 10 ppm, 25 ppm or 50 ppm/ $^{\circ}\text{C}$, from 0°C to 70°C

For Custom data, circle number 106


More high
performance
resistor products
from

CADDOCK
ELECTRONICS, INCORPORATED


These products are manufactured with Caddock's exclusive Micronox® or Tetrinox® Resistance Film Technologies. For your copy of the Caddock General Catalog call or write:

Applications Engineering
Caddock Electronics, Inc.
1717 Chicago Avenue
Riverside, California 92507
(714) 788-1700

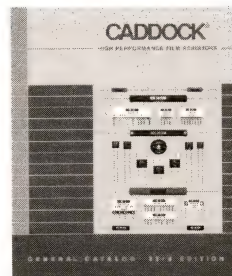The Caddock General Catalog includes specifications on over 200 models of high performance resistor products.



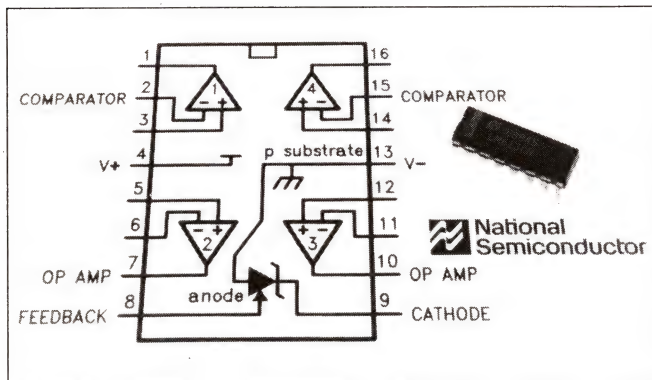For applications requiring very low drift, you can use some references in a heated mode.



Exemplifying a trend to higher integration, this IC from National Semiconductor contains an adjustable 1.2 to 6.3V reference in addition to dual op amps and dual comparators.

laser-trimmed thin-film resistors to obtain its high precision. The part features an initial accuracy of ± 4 mV and a TC of 5 ppm/ $^{\circ}$ C, and its 8.192V rating provides a convenient 2-mV/LSB scaling for 12-bit converters. Other specifications include a line regulation of ± 200 μ V/V max, load regulation of 100 μ V/mA max, and noise of 2 μ V p-p typ from 0.1 to 10 Hz. Long-term stability is typically 15 ppm/1000 hours. For applications requiring higher initial accuracy, the AD689 provides connections for fine trimming the output to 8.000V. In addition, force and sense connections allow remote sensing of load and ground variations. Available in 8-pin ceramic DIPs, prices range from \$2.95 to \$25 (100), depending on accuracy and temperature range.

If your application requires maximum performance and cost is no object, you may want to check out the LTZ1000, a 7.2V zener-based reference from Linear Technology. The LTZ1000, which requires external circuitry to set the operating currents, incorporates a subsurface zener, a heater resistor for temperature stabilization, and a temperature-sensing transistor. Designed for use in standard cells, calibrators, and precision voltmeters, the LTZ1000 features a thermal drift of 0.05 ppm/ $^{\circ}$ C, about 1.2 μ V p-p of noise, and long-term stability of 2 μ V per month. Packaged in an 8-pin metal can, the LTZ1000 operates over the temperature range of -55 to $+125$ $^{\circ}$ C and costs \$35.50 (100).

Stand-alone IC references will continue to dominate many applications, but there's a gradual, definite trend toward incorporating voltage references in other cir-

cuits—notably A/D and D/A converters. In addition, at least one company has incorporated adjustable references in monolithic building blocks containing op amps and comparators.

For example, over the course of the past year, Maxim Integrated Products has introduced a family of 12-bit A/D converters that include either bandgap or zener references. Analog Devices, among others, offers a wide range of A/D and D/A converters with on-chip references. And National Semiconductor recently introduced several monolithic chips containing single, dual, or quad op amps and a voltage reference.

The main advantage of this higher level of integration is convenience. The designer is freed from the task of matching a specific reference to a particular converter or op amp. In addition, there are advantages in cost and board space. Manufacturers can often include an on-chip reference with little penalty in chip real estate and no change in packaging. For many applications in which a reference is needed, this approach offers a cost-effective alternative.

EDN

References

1. *Analog-Digital Conversion Handbook*, edited by Daniel H Sheingold, Analog Devices Inc, Prentice-Hall, Englewood Cliffs, NJ, 1986.
2. Knapp, Ron, "Selection criteria assist in choice of optimum reference," *EDN*, February 18, 1988, pg 183.

Article Interest Quotient (Circle One)
High 488 Medium 489 Low 490

WHAT'S COMING IN EDN

EDN Magazine's February 1, 1990, issue will feature a staff-written Special Report about add-on buses. Part 3 of the designer's guide to flash-ADC testing concludes this design series with a discussion of the measurements you'll need to fully characterize flash A/D converters. Also, Contributing Editor Bill Travis looks at analog comparators that address TTL and ECL ICs. Be sure to look for our regular departments.

IT HAS TO BE GOOD. OUR NAME IS ON IT.



At Xilinx, quality is more than just an abstract concept.

It's a day to day commitment to providing our customers with the best products and services humanly possible.

It's a commitment to providing our employees with a working environment that enhances creativity and fosters

creative risk taking.

It's standing behind everything we do.

One hundred percent. Every day.

You have our word on it.



The Programmable Gate Array CompanySM

A-to-D performance that stands the test of time... and temperature.

THE ADC1241 12-BIT PLUS SIGN SELF-CALIBRATING A/D CONVERTER FROM NATIONAL.

The ADC1241 guarantees improved A-to-D performance over the long haul, covering the full industrial and military temperature ranges. That means no missing codes, not at 125°C in the shade or 55°C below zero. It means no parametric drifts, not today, tomorrow or ten years down the line. It means the ADC1241 is designed to last in your high-performance, microprocessor-based design.

MORE CODES, MORE RESOLUTION, MORE SPEED.

With 12 bits plus sign, the ADC1241 offers twice the number of codes (8192) and twice the resolution (1.22 mV) of standard 12-bit devices. And it's fast: conversion (13.8 μ s) and acquisition (3.5 μ s) times are guaranteed over the complete industrial and military temperature ranges.

WITH SELF-CALIBRATION.

Self-calibration prevents parametric drifts due to time and temperature, thereby improving overall system performance. It also minimizes non-linearity and zero errors over temperature. This eliminates the need for external



adjustments, saving you precious board space and reducing your manufacturing costs.

The ADC1241 goes through a self-correction cycle during every conversion to adjust non-linearity errors to less than $\pm 1/2$ LSB and zero error to less than ± 1 LSB. On request, the device also performs offset and/or non-linearity calibration.

AND ON-BOARD SAMPLE-AND-HOLD.

By integrating a high-speed sample-and-hold, the ADC1241 will track and hold the analog signal without the cost of additional components, testing or board space.

ALL ON A MINIMUM OF POWER.

The ADC1241 operates on a scant 70 mW (maximum) of power, making it ideal for portable or remote applications. And it can accommodate a unipolar analog input voltage range (0V to +5V) or a bipolar range of (-5V to +5V) with ± 5 V supplies and a single +5V reference.


FILLING OUT THE FAMILY.


The ADC1241 is the newest member of National's growing family of high-performance data conversion products, joining a full array of A/Ds, D/A's, analog switches, filters, sample-and-hold devices, multiplexers, voltage references, and temperature sensors.

ADC1241	AD7572-12	CS5012-12	
12-Bit + Sign	12-Bit	12-Bit	Resolution
13.8 μ s	12.5 μ s	12.25 μ s	Max Conversion Time
Yes	No	Yes	On-Board Sample/Hold
Yes	No	Yes	Self-Calibrating
70mW, +5/-5V	215mW, +5/-15V	250mW, +5/-5V	Max Power Consumption
\$15.90	\$35.00	\$37.40	Price, 100pc

TIME TO ACT.

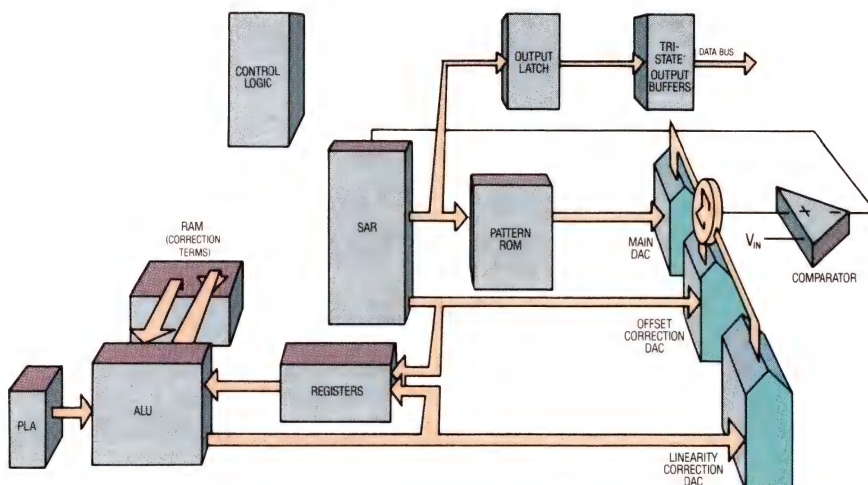For information on the ADC1241—or any data conversion product, take the time to call us toll-free at **1-800-624-9613, Ext. 89**, or write to: **National Semiconductor Corporation, P.O. Box 7643, Mount Prospect, IL 60056-7643**. In just a few minutes, we'll show you an A-to-D converter to last the ages. Regardless of the temperature.



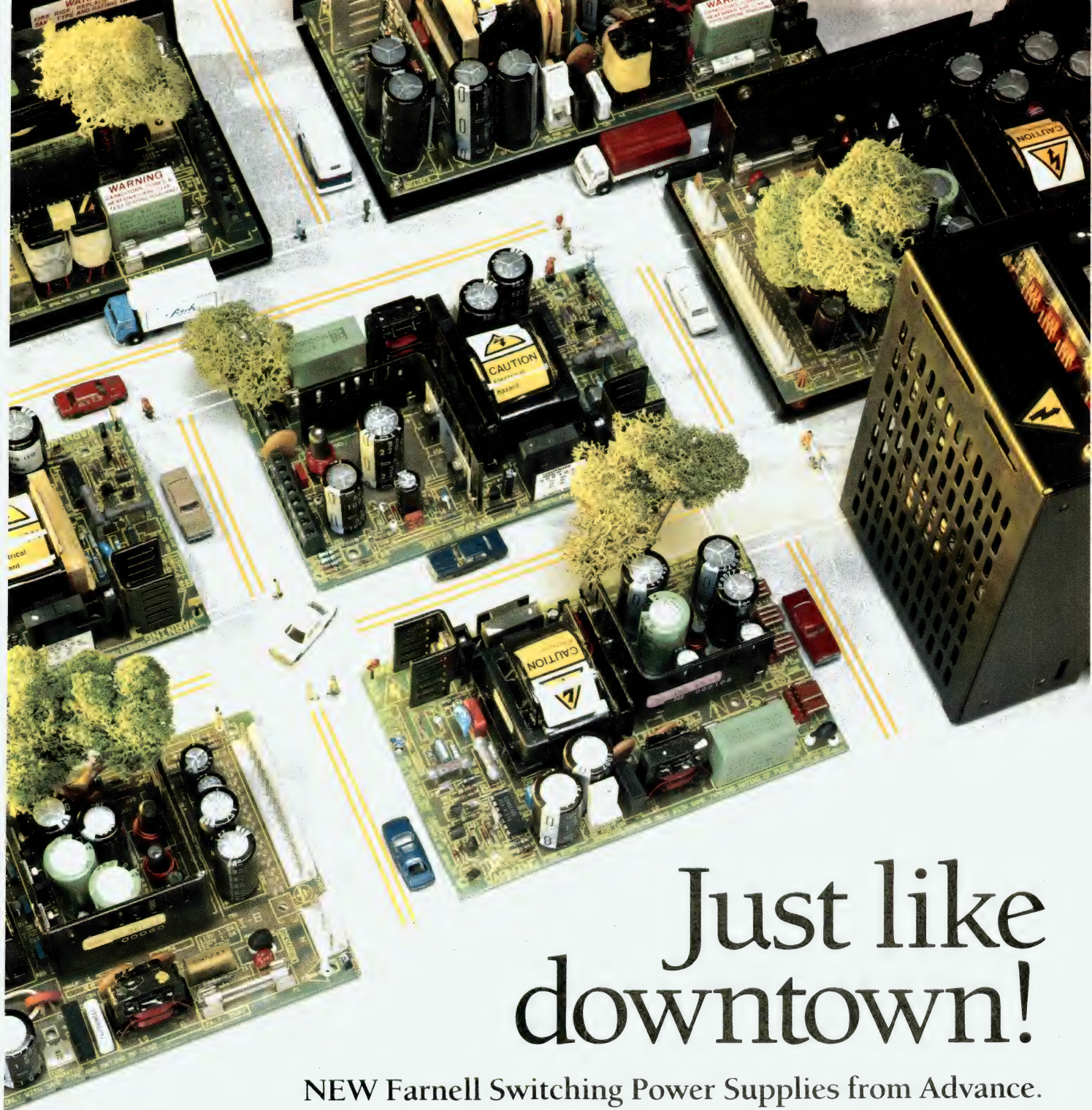

Just like downtown!

NEW Farnell Switching Power Supplies from Advance.

Now it's easier than ever to do your switch mode power supply shopping by going to Advance. Advance now offers two new quality lines of open frame and enclosed switching power supplies from Farnell Instruments in addition to the already-broad Advance line.

The "N" Range open-frame units include models from 50 to 500 watts, provide one to five outputs, meet international standards, incorporate the latest advances in

power supply technologies, and are competitively priced.

The "G" Range enclosed, convection-cooled units include models from 60 to 600 watts in a wide choice of voltage and current outputs. They are compact, high-efficiency units designed to meet strict RFI standards.

When you need a precise dependable switching power supply up to 1500 watts for a well-designed instrument, computer or control,

call your Advance representative or call 1-216-349-0755 and take advantage of our one-stop shopping. FAX 1-216-349-0142.

Advance Power Supplies
32111 Aurora Road
Solon, OH 44139

 **ADVANCE
POWER SUPPLIES**



DEECO SEALTOUCH® DISPLAY SYSTEM. SEALS IN PERFORMANCE. SEALS OUT DIRT AND MOISTURE.

If there's one thing you don't need, it's dirt and moisture seeping into your display system and disrupting its performance. The Deeco SealTouch display system is the best solution for your most demanding industrial applications.

Designed especially for harsh environments, SealTouch delivers consistently reliable performance under the most threatening conditions.

The SealTouch display system is a 3-part module consisting of flat-panel display and sealed I-R Touch panel, mounted on a controller card with VT100 text emulation and extensive drawing graphics. All within an absolute minimum footprint.

Easy-to-use touch software, pop-up menus and convenient button draw routines make SealTouch easy to design-in and simple to use. The system's programmable touch sensitivity allows you to easily implement protection against annoying false triggers. What's more, the SealTouch infra-red beam diagnostics continuously monitor system performance, assuring you of consistent reliability.

Don't take chances with any other display system. Call or write for full product information. Let SealTouch seal in performance for your design. And seal out dirt and moisture.

DEECO

Digital Electronics Corporation, 31047 Genstar Road, Hayward, CA 94544-7831 (415) 471-4700

SealTouch and Deeco are registered trademarks of Digital Electronics Corporation.

DSP test techniques keep flash ADCs in check

By testing your flash A/D converter, you can ensure that it's faithful to all the specifications listed on its data sheet. Part 2 of this 3-part series presents a number of methods, including sine-wave curve fitting and the FFT, that you can use to test flash converters. Readily available benchtop instruments or personal computers are the only equipment that you'll need to use these methods.

Walt Kester, Computer Labs Div,
Analog Devices

It's important to know how your flash A/D converter will perform in real-world applications. Therefore, you may want to perform any one of a variety of tests on your converter to determine its deviation from ideal performance. As Part 1 of this series discussed, flash ADCs exhibit errors due to static and dynamic nonlinearities, and these errors increase as the input signal's slew rate increases. Thus, the actual S/N ratio will fall short of the converter's theoretical value. Even if you don't apply these tests yourself, becoming familiar with them will help you evaluate data-sheet specifications more accurately, because many manufacturers use these same methods.

Another reason you may want to test your flash converter is to gain information that the manufacturer doesn't provide. Specifications such as S/N ratio and

its related effective number of bits are key in all applications and are normally specified, but other specifications that are more important for your particular application may not be included on the data sheet. For example, video designs typically require that you know a converter's differential phase and gain (Ref 1). Communications systems may even depend on esoteric specifications such as the spurious-free dynamic range, which isn't available on many data sheets.

For a full-scale sine-wave input, the theoretical rms-signal to rms-quantization noise ratio is

$$\text{S/N RATIO} = 6.02N + 1.76 \text{ dB},$$

where N equals the number of bits (Ref 2). The rms quantization-noise voltage for an ideal ADC within the Nyquist bandwidth is $q/\sqrt{12}$, where q is the weight of the LSB expressed in volts.

The most popular method for extracting a flash converter's S/N ratio and effective number of bits is through discrete Fourier transforms (DFTs). Today, you can perform sophisticated DSP tests with PC-based test systems and standard software packages. The test system in Fig 1, for example, can execute a 1024-point FFT in less than one second. Most of the hardware you'll need is available as plug-in boards for the PC. However, you'll have to do a fair amount of work before you can begin to use a PC-based test system. First, you'll need to design a high-speed buffer-memory board to capture the data from the flash

DSP test techniques determine your converter's deviation from ideal performance, and they even tell you certain specifications that the ADC's data sheet doesn't.

ADC. Typically, you'll need to use high-speed static CMOS or ECL RAMs. Second, plan to design an appropriate logic interface to connect this buffer memory to the digital I/O card of the PC.

Another hardware feature you might consider is an evaluation board, which certain manufacturers of video-speed ADCs supply to ease design testing. Many evaluation boards contain reference voltages, power-supply decoupling, timing circuits, output registers, and connectors. The evaluation boards usually have a matching reconstruction DAC. In most cases, the manufacturer has optimized the design of these boards so that your ADC test won't be corrupted by faulty or poorly designed support circuits.

Your software must include a program to capture the data and then load it into the memory of the PC. If you plan to use FFT analysis, you must link a standard FFT software package to your test program. You may also have to generate a look-up table to store any special weighting functions required by your particular sampling scheme. Also, adding a coprocessor card will speed up the thousands of multiplications that FFT-based analysis requires.


If you don't have the time or the energy to build your own test system, consider one of the benchtop instruments available from a number of instrumentation manufacturers. These turnkey systems typically utilize a high-speed logic analyzer to capture data. Because menu-driven software allows you to select from

a variety of tests, you incur practically no hardware or software development time.

To test a flash ADC using Fourier analysis, you must apply a spectrally pure sine wave to the converter and store a number of contiguous output data samples. Then, using DFT techniques, your test program calculates the rms-signal and rms-noise content and determines the ratio of the two. Noise calculations using DFT techniques include not only the converter's quantization noise but also the harmonics of the input sine wave. In addition, harmonics that fall outside the Nyquist bandwidth are aliased back into the Nyquist bandwidth because of the sampling process. Thus, to achieve accurate and repeatable results, the purity of the sampling clock and the input sine wave is critical.

You can use either coherent or noncoherent sampling to evaluate the ADC performance. Coherent sampling simply means that your record of samples contains an integer number of sine-wave input cycles. Alternatively, noncoherent sampling produces a record that contains noninteger multiples of the input. You must choose between these sampling schemes based on the type of input data you expect. Coherent testing is more suited to a laboratory environment when you know the precise frequency content of an input signal, and it requires careful attention in the selection of the input and sampling frequencies. Noncoherent testing yields a better representation of ADC performance in a real-world application such as spectral analysis, because

Fig 1—This DSP test system for a flash ADC can execute a 1024-point FFT in less than one second, but the system requires a significant design effort. Hardware requirements include a high-speed buffer memory and logic interface between this memory and your PC. Software requirements include a program to capture the data and load it into the memory of the PC, as well as a link between your test program and a standard FFT software package.

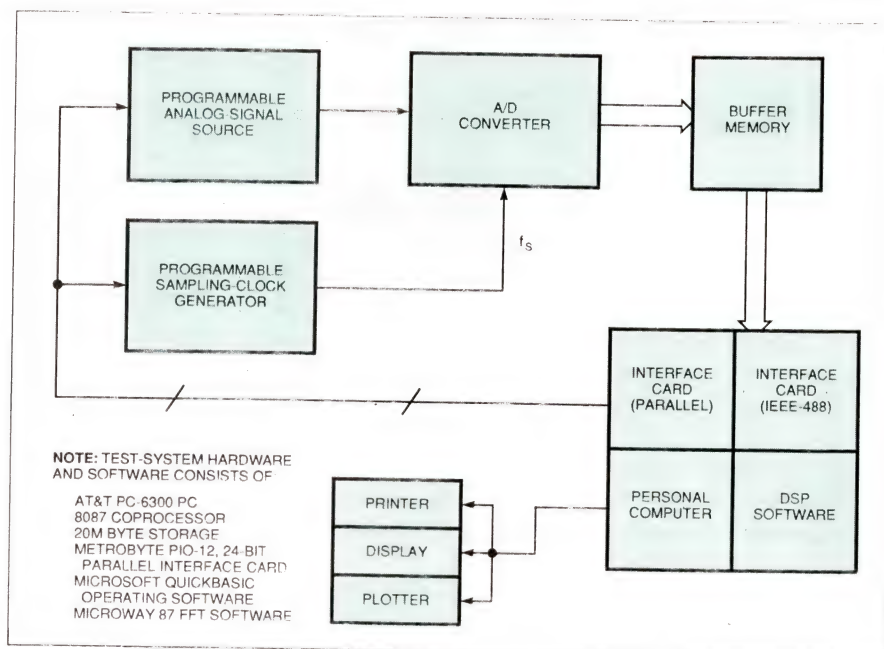

the precise frequency content of the signal being digitized is a mystery.

However, whenever the number of time samples doesn't contain an integer number of input cycles (noncoherent testing), you'll have to time-weight the samples to reduce frequency side lobes. Without weighting, discontinuities will cause the main lobe's energy—the fundamental—to leak into many other frequency bins. The term "bins" refers to the spaces between spectral lines or spectral peaks. The number of bins for a particular spectrum equals the sampling frequency divided by the record length, or f_s/M . The leakage of the signal from the central bin to side-lobe bins makes accurate spectral measurements impossible—you simply can't distinguish the frequency bins that contain actual signal information from those that contain noise. Another reason to time-weight the samples is that the end user of your A/D-conversion system

may be interested in the performance of the ADC using an identical or similar window.

Noncoherent sampling involves fewer input- and sampling-frequency restrictions than coherent sampling does, but it requires careful attention in the selection and use of the weighting function. Also, to prevent masking out harmonics of the fundamental, avoid using inputs that are integer submultiples of the sampling frequency. If your input frequency is an integer submultiple of the sampling frequency, the quantization noise, $q/\sqrt{12}$, will be concentrated in the harmonics of the input frequency rather than uniformly distributed across the Nyquist bandwidth. Ultimately, this condition leads to incorrect harmonic-distortion test results.

One popular weighting function is the Hanning window (Ref 3), which is described by the equation

$$W_n = 0.5 - 0.5 \cos \left(\frac{2\pi n}{M} \right),$$

where W_n is the weighting coefficient for the n th data sample, and M is the total number of samples. Fig 2 graphically depicts the Hanning window in both the time and the frequency domains.

To calculate the S/N ratio, you have to decide the number of frequency bins to include in the fundamental and the number of bins to consider as noise. As Fig 2 shows, you can correlate the amount of side-lobe attenuation with the lobe's distance, in terms of bins, from the fundamental bin. Fig 2b includes a table that lists some of these values. You'll have to make your decision based on the theoretical S/N ratio of the converter you're testing.

For example, an 8-bit converter has a theoretical, maximum S/N ratio of approximately 50 dB. In order to ensure that the side-lobe energy doesn't cause an artificially high noise measurement (and hence an artificially low S/N-ratio measurement), you should include at least 10 frequency bins on either side of the fundamental when calculating the signal level. (Simply take the square root of the sum of the squares of all 21 bins as your signal level.) Now, any side-lobe energy outside this region will be at least 68 dB below the fundamental signal level (18 dB below the theoretical, 8-bit quantization noise floor of 50 dB), and side-lobe leakage won't significantly affect the accuracy of your S/N-ratio measurement.

Other weighting functions may better suit your application. For example, Fig 3 compares the popular

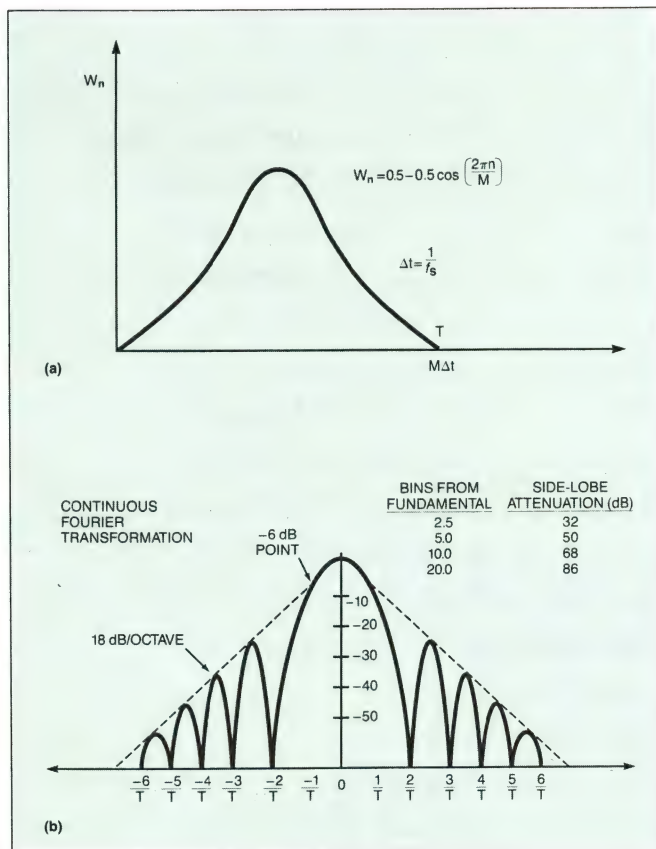


Fig 2—When the record of samples doesn't contain an integer number of input cycles—that is, when you're using noncoherent sampling—you must precondition the data with a weighting function. The Hanning window shown here in the time domain (a) and the sampled-frequency domain (b) is a popular weighting function.

Today, you can perform sophisticated DSP tests with PC-based test systems and standard software packages.

Hanning window's spectral representation with the more sophisticated, minimum 4-term, Blackman-Harris type. For the same record length, the Blackman-Harris window provides better spectral resolution than the Hanning window, making it more suitable for critical spectral analysis, such as measuring 2-tone, third-order intermodulation-distortion products. The extra computations for the Blackman-Harris window don't lengthen processing time, because you calculate them only once and store them in a look-up table.

As previously stated, you can use coherent sampling if you know the characteristics of your input signal and if you choose the sampling rate accordingly. Coherent sampling eliminates leakage and the need for windowing (Ref 4); the spectral result of a coherently sampled signal is simply a single-frequency peak. Certain restrictions apply to the choice of the sampling rate and

the sine-wave frequency, however. First, you must observe the following ratio:

$$\frac{f_{in}}{f_s} = \frac{M_C}{M}$$

M_C equals the number of integer cycles of the sine wave during the record period. For a whole number of cycles, M_C must be an integer. To ensure that you don't take repetitive data, M_C should also be a prime number: 1, 3, 5, 7, 11, 13, 17, etc. By using prime numbers, you ensure that all samples during the record period are unique. When using coherent sampling, it's mandatory that the ratio M_C/M be constant. This requirement implies that you derive f_s and f_{in} from two locked frequency synthesizers.

Calculate the DFT

After selecting the record length and determining the weighting function (for noncoherent sampling), you must write your DFT test program. Your program must find the DFT of the sequence of weighted data samples for $M/2$ frequencies (the Nyquist frequency). Thus, the program should solve the following two equations for the k th frequency:

$$A_k = \frac{1}{M} \sum_{n=1}^M W_n D_n \cos \left[\frac{2\pi k(n-1)}{M} \right]$$

$$B_k = \frac{1}{M} \sum_{n=1}^M W_n D_n \sin \left[\frac{2\pi k(n-1)}{M} \right]$$

In these equations, A_k and B_k represent the magnitudes of the cosine and sine parts of the k th spectral line; n is the number of time samples; W_n is the weighting function; D_n is the amplitude of the time-function data point; and k is the number of a spectral line. The total magnitude of the k th spectral line is

$$\text{MAGNITUDE}_K = \sqrt{A_k^2 + B_k^2}$$

The program's results yield $M/2$ components, which are the frequency-domain representation of the M time samples. The resolution or spacing between the spectral lines, Δf , equals f_s/M and is the bin size or bin width.

Typically, you should select the number of time samples (M) to be between 256 and 4096, depending on

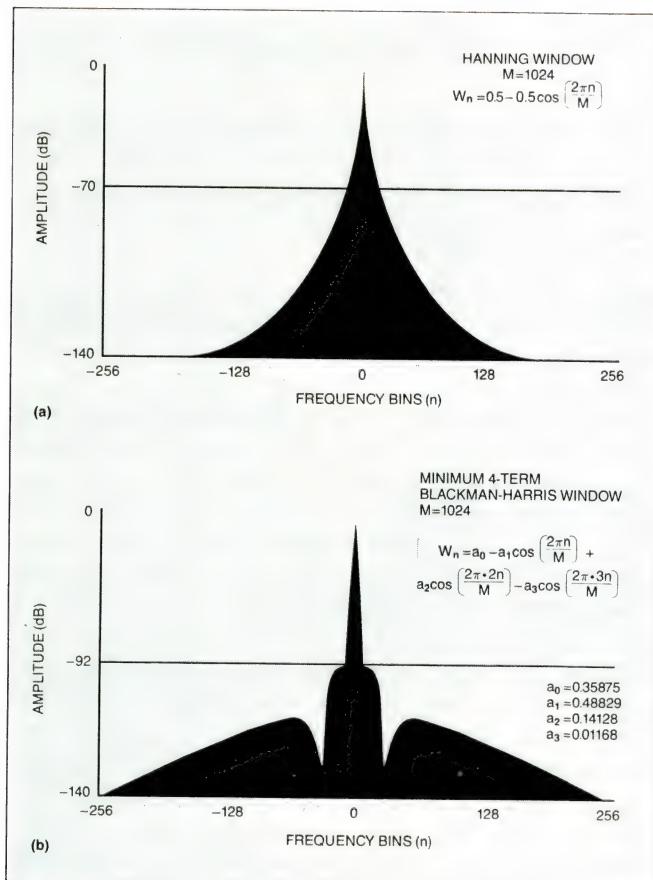


Fig 3—The Blackman-Harris windowing function (b) resolves closer peaks in a frequency spectrum than does the Hanning window (a). The mathematical expression for the Blackman-Harris window is more complex, but you only need to calculate the terms once and then store them in a look-up table.

THE CONFIDENCE IT GIVES YOU IS PRICELESS.


When you can't afford to miss a thing, get the new 2232 digital storage oscilloscope from Tek.

The 2232 is a 100 MHz, 100 MS/s digital-plus-analog scope that can detect glitches down to 10 nanoseconds at any sweep speed. As a result, it exposes random events and transient phenomena that elude comparable instruments.

And it's at home in applications ranging from digital-system design to medical equipment service.

You also get features like trigger-level readout, automatic time and voltage measurement, and storage of up to 52 waveform sets—plus a three-year warranty on all parts and labor.

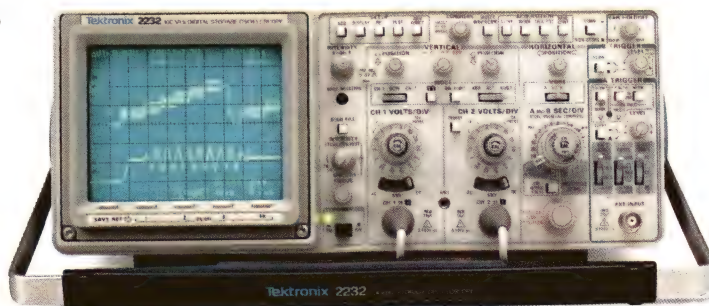Priceless confidence for only \$5495. The new 2232 from Tek.



Confidence at an even lower price.

For outstanding waveform confidence under \$2500, look into the new 50 MHz 2211 digital storage oscilloscope.

It combines 20 MS/s digital sampling and analog measurement in one portable, easy-to-use package. And comes with waveform cursors, a 4K record length, horizontal magnification

of X10 and X50, a hardcopy interface and much more—all for only \$2495.

The free offer is worth up to \$340.



Order a Tek 2232 or 2211 DSO between January 15 and May 1, 1990 and you'll receive one of these great items *free!*

☐ **CFG250 2 MHz Function Generator** Produces sine, square and triangle waves plus TTL signals.

A \$340 value.

☐ **P6062B 1X/10X Switchable Probe** A 100 MHz, 6 ft. probe, list price \$190.

To take advantage of our special offer, complete and return this coupon to your local Tek representative or distributor (be sure to check one of the boxes above). Or, order from Tek direct at **1-800-426-2200, ext. 200** and mention this ad.

Name _____

Title _____

Company _____

Address _____

City _____

State _____

Zip + 4 _____

Phone _____

Ext. _____

Application _____

Offer good in U.S. ONLY

EDN011890

Confidence is only a call away.

To order your 2232 or 2211, or for more information, contact your local Tek representative or distributor. Or call us direct at

**1-800-426-2200
ext. 200.**



Tektronix
COMMITTED TO EXCELLENCE

CIRCLE NO. 77



The discrete Fourier transform is the most popular method for determining a converter's true S/N ratio and effective number of bits.

the desired resolution and the size of the buffer memory. M must be equal to an integer that's a power of two. If you're using noncoherent sampling, you can compress leakage around the main lobe by using a larger record length, thereby leaving a larger percentage of the Nyquist spectrum uncontaminated. For example, the Hanning weighting leakage is ± 10 bins from the fundamental for 68-dB side-lobe suppression. If the record length is 256, then the leaky fundamental occupies 20 bins out of 128 spectral components, or 16% of the digital spectrum. When M equals 1024, the percentage reduces to 20/512, or 4%.

In practice, you can use one of the many FFT algorithms to simplify and speed the DFT calculations (Ref 5). An FFT algorithm will produce the same results as the DFT equations above, and the computation time is much faster.

Verify the FFT

Consider the noise floor when verifying the FFT. Assuming that the round-off error contributed by the DSP-noise calculation (the error caused by using a finite number of bits in the FFT multiplications and additions) is negligible, the rms-signal to rms-noise level in a single frequency bin of width Δf is

$$\text{S/N RATIO}_{\text{FFT}} = 6.02N + 1.76 \text{ dB} + 10 \text{ LOG}_{10} \left(\frac{M}{2} \right).$$

This equation represents the FFT noise floor. You should choose M so that any spurious components you want to resolve lie at least 10 dB above this floor.

Basic software can easily generate an ideal N -bit sine wave by using the Integer (INT) function to truncate the value to the proper resolution. For instance, an input signal of frequency f_{in} is equal to

$$V_q = V_o \sin \left(\frac{2\pi n f_{\text{in}}}{f_s} \right),$$

where n is the n th time sample for an ADC that has infinite resolution. You can calculate the corresponding quantized value using

$$V_q(n) = \text{INT} \left(\frac{V_o \sin \left(\frac{2\pi f_{\text{in}}}{f_s} \right)}{q} \right),$$

where $q = 2V_o/2^N$. Substituting this expression for q in the above equation yields

$$V_q(n) = \text{INT} \left[2^{N-1} \sin \left(\frac{2\pi n f_{\text{in}}}{f_s} \right) \right].$$

The INT function simply truncates the fractional portion of $V_q(n)$.

To check the dynamic range of the FFT, calculate the S/N ratio by using $6.02N + 1.76$ dB for increasing values of N and observing the point at which the S/N ratio no longer increases by 6.02 dB/bit. The sine-wave input to the weighting function and the FFT are more ideal as N approaches infinity. By making N arbitrarily large, you can greatly reduce quantization-error effects and analyze the true noise floor of the FFT. You can also examine the characteristics of the weighting function.

Match the sine wave to a curve

Another test method to use with flash ADCs is sine-wave curve fitting. You perform this test after the ADC digitizes the sine wave and after your test system stores the data in its memory. A record length of 1024 samples is usually sufficient. The software then calculates the best-fit, ideal N -bit sine wave to match the data points, based on the sine wave's amplitude, offset, frequency, and phase required to minimize the rms error between the actual and the ideal sine wave (Refs 6 and 7). This method also requires that the input sine-wave frequency contains no subharmonics of the sampling rate. If you know the precise sine-wave frequency, the curve-fit algorithm is much simpler than the FFT method, and the probability that the algorithm will converge is higher.

After the software computes the rms error, Q_A , between the ideal sine wave and the actual sine wave, you can calculate the effective number of bits by using

$$\text{EFFECTIVE NUMBER OF BITS} = N - \text{LOG}_2 \left(\frac{Q_A}{Q_T} \right),$$

where Q_T is the theoretical rms quantization error, $q/\sqrt{12}$. This measurement includes errors due to differential nonlinearity, integral nonlinearity, missing codes, aperture jitter, and noise, in addition to the quantization noise.

At last, an entirely new approach to clock speed

Get five times faster throughput from NEC K-Series™ microcomputers.

As a developer of real-time control systems, you know that designing in a faster CPU is not enough. You also need intelligent I/O management for the best possible system throughput.

NEC's K-Series™ microcomputers are perfect for real-time control designs requiring multi-tasking, such as automotive control, ISDN and computer peripheral controllers.

Peripheral Management Unit™

The K-Series' unique architecture includes a revolutionary Peripheral Management Unit™ macro service for nonstop instruction execution while processing up to 16 I/O requests at the same time. By designing in the K-Series microcomputer, you can improve your system throughput by as much as 5X.

The K-Series 8-bit and 16-bit microcomputers give you a real-time output port; an advanced counter/timer system; a high-speed, high-resolution A/D converter; and many other on-chip intelligent peripherals.



Not since the invention of the hourglass has anyone come up with a more ingenious way to speed up silicon.

The K-Series provides you a worry-free upgrade path from the 8-bit K2 microcontroller family to the 16-bit K3 devices. And your future designs will exploit the power of the lightning-fast 125-ns K6, with real-time operating system in microcode, and complete K3 software compatibility.


Free Knowledge Kit™

To learn more about the K-Series microcomputers with up to 1K bytes of on-board RAM, 32K bytes of ROM/EPROM, and Peripheral Management Unit coprocessing power, call now.

1-800-632-3531

A free 81-page Knowledge Kit™ will be rushed to you along with complete information on the K-Series with the Peripheral Management Unit. Development tools and samples are available now.

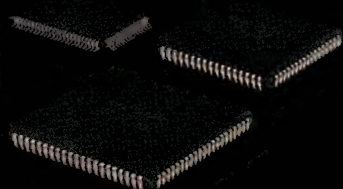NEC Electronics Inc.
401 Ellis Street
Mountain View, CA 94039-7201
1-800-632-3531/415-965-6158



Coherent testing is more suited to a laboratory environment; noncoherent testing more closely represents ADC performance in the real world.

The effective number of bits that you calculate using the sine-wave curve-fitting method correlates with the value of the full-scale, FFT S/N-ratio measurement obtained using the equation

$$\text{EFFECTIVE NUMBER OF BITS} = \frac{\text{S/N RATIO}_{\text{ACTUAL}} - 1.76 \text{ dB}}{6.02}$$

However, if you measure the effective bits of a sine-wave input signal whose amplitude is less than full scale, you must include the following correction factor in the above equation to achieve correlation between the two methods:

$$\text{EFFECTIVE NUMBER OF BITS} = \frac{\text{S/N RATIO}_{\text{ACTUAL}} - 1.76 \text{ dB}}{6.02}$$

$$+ \frac{\text{LEVEL OF SIGNAL BELOW FULL SCALE (dB)}}{6.02}$$

One useful method for reducing the effects of the D/A converter in making gross back-to-back measurements on an ADC is the beat-frequency method. **Fig 4** illustrates a basic test setup. This test method stresses the converter with a near-Nyquist signal and drives the converter at its maximum sampling rate. Thus, the analog-input sine wave should be slightly lower in frequency than half the sampling frequency. The test system updates the registers that drive the DAC at an even submultiple of the sampling rate, f_s/N , where N is a power of 2. (N is not the ADC's resolution.) The resulting signal from the DAC is a low-frequency sine wave whose exact frequency equals the


difference between half the sampling rate and the analog-input frequency. As **Fig 4** shows, you should clock the DAC at a much lower rate, f_s/N —known as the decimation rate—thereby reducing the effects of glitches and other dynamic errors.

You can use the beat-frequency method to make signal-to-noise measurements over the Nyquist bandwidth, $f_s/2N$. You also can examine the low-frequency beat on an oscilloscope for missing codes and other nonlinearities. To measure the harmonic content of the beat frequency, you can use a low-frequency spectrum analyzer. The harmonics of the low-frequency beat are directly related to the harmonics of the analog-input frequency. A beat frequency of a few hundred kilohertz works well. To prevent jitter on the low-frequency beat signal, you must derive both the analog-input sine wave and the sampling frequency from frequency synthesizers or crystal oscillators.

This beat-frequency test is also effective in measuring the flash converter's performance for input signals near the sampling frequency. The performance under these conditions is useful for radar in-phase and quadrature-phase systems and in IF-to-digital conversion. To perform this test, set the ADC's analog-input frequency to slightly less than the sampling rate. The circuit generates a low-frequency beat even if the DAC updates at the sampling rate. However, updating the DAC at f_s/N reduces the effects of DAC dynamic errors on the measurements.

You can use DSP techniques and FFTs to analyze **Fig 4's** decimated data for a wide range of input frequencies. You do have to remember the rules of aliasing, however, to know where to expect the funda-

Fig 4—The beat-frequency test stresses the converter with a near-Nyquist input signal, and it drives the converter at its maximum sampling rate. You can then examine the low-frequency beat on an oscilloscope and search for missing codes and other nonlinearities.

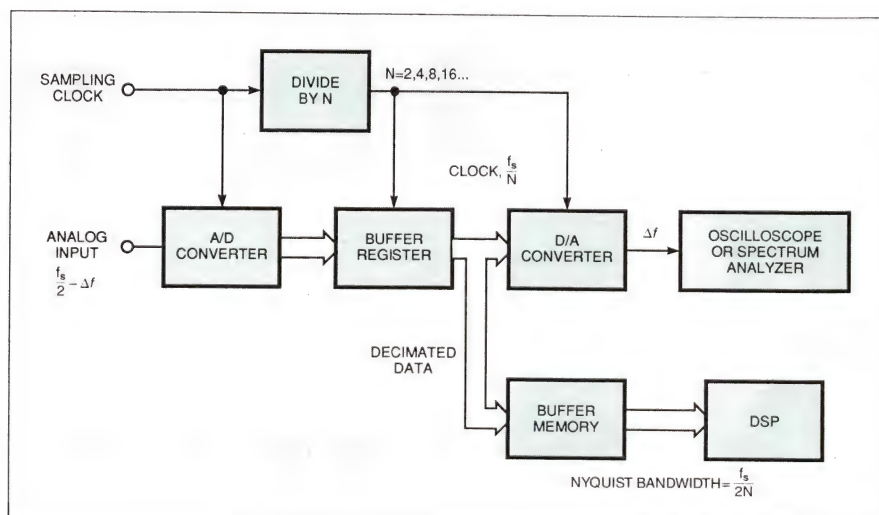

Here's what we're up to.

Ontario, Canada, is a place of achievement. We pioneered telecommunications. Hydro electric power. Satellite transmission. Space robotics.

The result—a well-established infrastructure of skilled suppliers to the North American electronics industry. If you haven't explored this alternative source for quality components, it's time you took a look at what's here.

We give you quality, at a competitive price, without the inevitable problems caused by distance and language differences. We're your neighbours, and we think and talk like neighbours.

When you source in Ontario, it's as easy as dealing with a domestic supplier. You may find us easier to deal with. Ontario is close to major manufacturing centres of the U.S., and our excellent transportation links make us a prime partner for JIT

and similar time-sensitive supply arrangements.

One phone call will bring you information about Ontario suppliers of the quality components you need.

Contact the International Electronics Marketing Consultant for the Government of Ontario, Canada at this number (416) 965-5436. Or write to the Ministry of Industry, Trade and Technology at 900 Bay Street, Hearst Block, Toronto, Ontario, Canada M7A 2E1. Fax: (416) 965-7791.

Ontario, Canada: the best-kept secret of the North American electronics industry.



**ONTARIO'S
BUSINESS**
More than Competitive!

Ministry of Industry,
Trade and Technology



Ontario, Canada

CIRCLE NO. 79

POWER

When your products depend on reliable power, depend on DATEL. With 20 years experience in the design and manufacture of power products, DATEL's complete line offers

- 1W to 30W DC/DC Converters
- Single, dual, triple and high voltage outputs
- PC or chassis mounting
- Wide range inputs
- Outstanding regulation, accuracy and low noise
- Line operated supplies, Switching supplies
- Miniature packages

Call or write for DATEL's new brochure detailing more than 140 power products.



DATEL

INNOVATION AND EXCELLENCE IN PRECISION DATA ACQUISITION
DATEL, Inc., 11 Cabot Boulevard, Mansfield, MA 02048 (508) 339-3000

CIRCLE NO. 12

MAXIMUM PERFORMANCE

WITH MINIMAL HEAT



- IERC military packaging products include ZIF circuit board retainers, custom coldwalls and enclosures and SEM card cages.
- Superior thermal conductivity increases reliability and provides higher density packaging of electronics
- Unique 1/2 turn positive LOCK/UNLOCK simplifies board replacement and meets MIL-STD-883C for vibration and shock
- When the action's hot . . . IERC comes to the rescue!

IERC International Electronic Research Corporation
a subsidiary of Dynamics Corporation of America
135 W. Magnolia Blvd., Burbank, CA 91502
(213) 849-2481 • (818) 842-7277 • FAX: (818) 848-8872

CIRCLE NO. 13

mental signal to show up in the FFT output spectrum. You may think your FFT is sampling your signal at a rate of f_s/N , but the converter is actually sampling at a rate of f_s .


Once you understand how to use these various techniques, you can start to probe your particular converter to measure its real performance. Part 3 will discuss how you apply these techniques to actually test an ADC in your system and determine a number of static and dynamic specifications. **EDN**

References

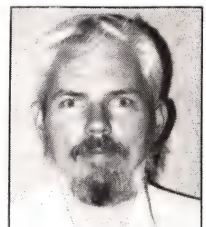1. Kester, W A, "PCM Signal Codecs for Video Applications," *SMPTE Journal*, No. 88, November 1979, pg 770.
2. Bennett, W R, "Spectra of Quantized Signals," *Bell System Technical Journal*, No. 27, July 1948, pg 446.
3. Harris, Frederic J, "On the use of windows for harmonic analysis with the discrete Fourier transform," *IEEE Proceedings*, Vol 66, No. 1, January 1978, pg 51.
4. Coleman, Brendan, Pat Meehan, John Reidy, and Pat Weeks, "Coherent sampling helps when specifying DSP A/D converters," *EDN*, October 15, 1987, pg 145.
5. Ramirez, Robert W, *The FFT: Fundamentals and Concepts*, Prentice Hall, Englewood Cliffs, NJ, 1985.
6. Peetz, B E, A S Muto, and J M Neil, "Measuring Waveform Recorder Performance," *HP Journal*, Vol 33, No. 11, November 1982, pg 21.
7. Frohring, B J, B E Peetz, M A Unkrich, and S C Bird, "Waveform Recorder Design for Dynamic Performance," *HP Journal*, Vol 39, February 1988, pg 39.
8. "Dynamic performance testing of A to D converters," HP Product Note 5180A-2, 1982.

Author's biography

Walt Kester is a technical-support manager for the Computer Labs division at Analog Devices. Walt has been with the company for 20 years and supports the development of high-speed ADCs, DACs, S/H amplifiers, and op amps. He has a BSEE from North Carolina State University and an MSEE from Duke University. In his spare time, Walt enjoys carpentry and travel.



Article Interest Quotient (Circle One)
High 497 Medium 498 Low 499

At Mizar, peripheral boards aren't just a sideline.

Whatever your application need, Mizar has VMEbus peripherals to match.

The right interfaces and controllers are key to the performance of your microcomputer system. Choosing those peripherals involves finding not only a supplier of reliable products, but a company that understands systems.

Mizar and its single- or double-height VMEbus boards are the perfect solution: memory cards; serial, parallel, and analog/digital boards; SCSI, SASI, and GPIB interfaces; and floppy disk, hard disk, tape, and Ethernet controllers.

When you choose Mizar, you're backed by one of the most respected names in VME. A leader in high performance boards and integrated Unix and real-time systems, Mizar is your ideal "one-stop shop".

Above all, Mizar provides the systems support you need, including leading software solutions and timely technical service.

To find out more about Mizar's VMEbus boards and systems, or to receive a free catalog, call today. **1-800-635-0200**



MIZAR

Mizar/Integrated Solutions


1419 Dunn Drive • Carrollton, TX 75006
(214) 446-2664 • 1-800-635-0200

CIRCLE NO. 80

Why 8,000 of the world's leading companies design PCBs with P-CAD:

A Supercharged Product

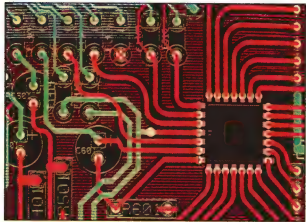If you're like most PCB designers and engineering managers, you want PCB CAD software that'll help



With Master Designer you have it all: full analog support, including filled polygons, curved traces, trace hugging and trace plowing.


you do your job, not dictate how you're going to do it. That's why nearly half the world's PC-based PCB design is done with P-CAD.[®] No other software can get your product to market faster with more reliable, more manufacturable boards. And it's incredibly flexible, too.

The P-CAD Master Designer[™] lets you design huge boards of up to 2,500 components, 4,000 nets, and 800 component definitions. Zip through our library of over 6,000 parts, point and click — no need to type in part numbers. Layout information is incorporated right into the schematic, improving your design speed and accuracy. Managing ECOs is a snap, with complete forward and back annotation.

Powerful add-on modules like Digital Design Lab,[™]

Analog and Digital Simulators help you perfect your design before you build it.

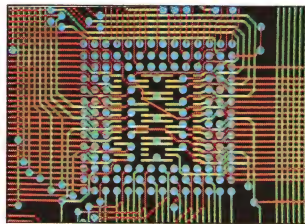For flexibility, nothing matches P-CAD's Master Router[™] automatic routing system. It's fully re-entrant with features like unlimited net classes plus route-by-window to give you the control you need to select the best routing strategy for your design. Routing priorities can be specified up-front to ensure that critical signals are routed efficiently. Clean routing with fewer vias




Use all the current technologies: SMT, high-speed circuits, fine-line, ultrafine-line and more.

reduces your manufacturing costs. For the really tough designs, our 100%-completion Rip-n-Route[™] option lets you fine-tune routing on-the-fly and create manufacturable boards without manual clean-up.

Everything about P-CAD is fully integrated. You go from schematic capture to simulation, verification, and routing, right up to manufacture, from a single database with a single user interface. Programmable function keys and macros allow you to customize your system for the way you work best.

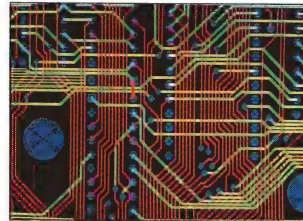Virtually all popular hardware configurations are supported, including hardware pan and zoom for lightning-fast redraws. An open architecture combined with the famous P-CAD




With the flexible P-CAD autorouting system, you're never locked into preset design strategies.

Database Interchange Format (PDIF) database translator makes it easy to integrate with MICRO CADAM[™] mechanical design, drafting systems like AutoCAD[®] and documentation software like Ventura[®] and Interleaf[®], complete with PostScript[®] support.

From A Dedicated Company

P-CAD Master Designer comes with a lot more than terrific software and superb documentation. P-CAD

users enjoy the comfort of knowing they're never alone. They also get outstanding support from technical field representatives in over 100 locations with over 19 training centers. But that's not all. P-CAD maintains a technical support center and hot line, user groups and a 24-hour electronic bulletin board. All from the company that is the acknowledged leader in PCB design and analysis software. That's why over 14,000 P-CAD installations are slashing PCB design

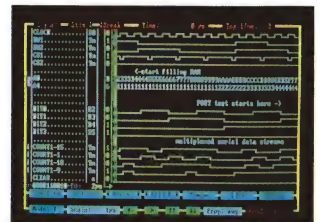

Let Digital Design Lab run, test, and debug your circuit before you even build a prototype.

times and boosting profits around the world.

When you combine a powerful product with a dedicated successful company it all adds up to the highest-performance PCB design system available on any platform.

**Call P-CAD today, toll-free:
800-523-5207**

(in CA 800-628-8748)

Find out how to put Master Designer to work for you now!

P-CAD, 1290 Parkmoor Avenue
San Jose, California 95126 USA
(408) 971-1300 Fax (408) 279-3752

p-cad[®]
A CADAM COMPANY

P-CAD is a registered trademark and Master Designer, Master Router, Digital Design Lab, Rip-n-Route are trademarks of Personal CAD Systems. MICRO CADAM is a trademark of CADAM Inc. Ventura is a registered trademark of Xerox Corporation. Interleaf is a registered trademark of Eastman Kodak Co. AutoCAD is a registered trademark of Autodesk, Inc. PostScript is a registered trademark of Adobe. All product specifications are hardware and design dependent and are subject to change without notice. © Copyright P-CAD 1989



Available

Today, Multibus II is supported by a wide range of products. Including important recent announcements that open new avenues of opportunity for engineering teams designing for the next decade, and beyond. ■ The Multibus Manufacturers Group (MMG) members who sponsored this ad invite you to send for their all-new 1990 *Multibus II Product Data Book*. It's full of information on their complete lines of Multibus II boards, systems, software and bus interface chips. And it's available free to qualified engineers and managers. ■ To request your copy just send your business card to the MMG. Or call our special toll free number today:

800 448 9602. (U.S. and Canada)

Discover a world of design freedom made possible by the Architectural Discipline of Multibus II. For large, complex applications. And small, simple ones. Just about anywhere a PC is not enough. ■



MULTIBUS MANUFACTURERS GROUP

P.O. Box 6208, Aloha, Oregon 97007 503-696-7155

■ CENTRAL DATA

800-482-0315 FAX 217-359-6904

Contact: Mark Decker

Family of high performance intelligent boards including single- and dual-channel SCSI host adapters, 80386 SBC, communications/terminal controller, and SBX motherboard.

■ CONCURRENT TECHNOLOGIES

217-356-7004 FAX 217-356-6238

Contact: Jerry Hoffman

Full line of high performance 386 and 186 CPU boards, analog and digital I/O, communications, Ethernet, Cheapernet, and 16-channel terminal controllers.

■ DIGITAL RESEARCH INC.

408-982-0700 FAX 408-982-0715

Contact: Director of OEM Sales

Full-featured systems software OEM products including 186, 286 and 386 FlexOS operating systems, Token Ring and TCP/IP network software, and new X/GEM graphics user interface.

■ HEURIKON CORP.

800-356-9602 FAX 608-831-4249

Contact: Jeremy Wright

Range of quality CPU boards and systems.

The most recent introduction is a 68030-based SBC with on-card Ethernet.

■ INTEL

800-548-4725


Comprehensive Multibus II solutions: UNIX/iRMX based System 520, new i486 CPU, new 80386-based modular I/O, and new low cost MPI-based I/O.

■ MICRO INDUSTRIES

614-895-0404 FAX 614-882-6357

Contact: Susan Lawton

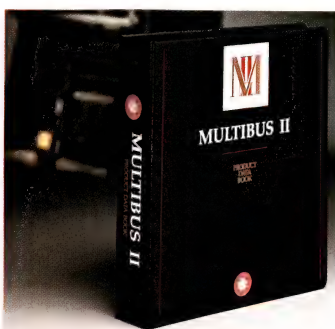Complete line of Multibus I and II products for industrial control, office automation, telecommunications, military and aerospace.



■ MICRO MEMORY INC.

818-998-0070 FAX 818-998-4459

Contact: Mosé Jadon

Full line of high density memory modules up to 128M bytes in a single card slot. Single and dual ports (IPSB/LBX), Dynamic and non-volatile CMOS RAM memories.

■ MICROBAR SYSTEMS

408-720-9300 FAX 408-773-9475

Contact: Alex London

Reduces board development cycles to 12 weeks while meeting your application-specific requirements through our design library based on 80X86 or 680X0 processors.

■ PLX TECHNOLOGY, INC.

800-759-3753 FAX 415-960-0479

Contact: Gaylord Galihier

Low-cost, high drive current, bus interface specialists. Programmable and off-the-shelf interface chips for Multibus II and all other high performance buses.

■ SIEMENS AG

Advertising Dept., 333 State Bridge Road

Alpharetta, GA 30201

A complete range of CPU, memory and I/O cards, including local buses as OME, AMS, SMP, and AT, from the leading European board supplier for industrial automation.

■ THE WOLLONGONG GROUP

415-962-7200 FAX 415-969-5547

Contact: Douglas Ambort

TCP/IP and NFS protocol suites on Multibus computers running the UNIX System V Release 3.2 operating system supported on the 186/530 and 186/622A.

■ XYLOGICS, INC.

617-272-8140 FAX 617-273-5392

Contact: Dave Padley

Full line of very high performance, multichannel peripheral controllers under development, supporting such interfaces as ESDI, IPI and SCSI.

Legend:

- Boards
- Systems
- Software
- Bus Interface Silicon

Discipline

specification, orderly design approach, and host of new products make any application requiring more than a PC.

4

INTEROPERABLE

Nowhere is the virtue of Architectural Discipline more apparent than in the superior interoperability of Multibus II.

■ *All* Multibus II boards from *all* manufacturers work together. Right out of the box. ■ Problematic issues like interrupt line assignments, dual-port memory allocations and slot dependence simply don't exist. ■ You can even mix message passing and shared memory communications methods. Or migrate from one to the other with ease. ■ This makes uniprocessor systems simpler to integrate, and multiprocessor systems a practical reality. And restores the original idea behind open bus architectures—"mix-and-match" computing. ■

5

RELIABLE

Multibus II's unique advanced features make your application more reliable and easier to maintain. ■ Like synchronous operation with full parity error detection/correction. Built-in self test and diagnostic capabilities. The freedom to plug any board into any slot. And the system's ability to automatically configure each board without jumpers or DIP switches. ■ And, naturally, Multibus II uses only DIN connectors for all backplane and I/O connections. ■ All these features are designed into the architecture itself, as well as all Multibus II boards, backplanes, chassis and other products. ■ Multibus II's Architectural Discipline means reliability you can depend on. ■

6

SCALABLE

Only Multibus II provides a virtually linear increase in performance as the number of boards grows. For scalable performance across your complete systems architecture. ■ Multibus II supports simple applications with low-cost "dumb" I/O boards, and shared memory communications. At the high end, Multibus II's cohesive structure for multiprocessing operates like a 40 Mb/sec. Local Area Network. With backplane protocols that can extend to Ethernet or fiber-based LANs. ■ Of all the buses available today, only Multibus II is capable of efficiently handling the full range of applications—from simple single-processor systems, to very complex multiple-CPU applications. Just about anywhere a PC is not enough. ■



ARCHITECTURAL

Discipline

Multibus® II's Architectural Discipline is your design freedom. A solid
Multibus II the clear choice for virtually

1

SIMPLE

Multibus II brings more than just power to your application. It brings simplicity that speeds development and eliminates risk. Without compromising performance or economy. ■ The spec itself (IEEE 1296) is clean, complete, disciplined. It defines a bus that is synchronous and highly deterministic. ■ Multibus II is supported by the Multibus II Systems Architecture (MSA)—an extensive *system-level* open standard. MSA implements advanced functions so you don't have to. And supports standard transport protocol to simplify complex systems. MSA even includes firmware for system configuration and self-test. ■ Choosing Multibus II can cut months off your development cycle. And zeros off your budget. ■

2

COST EFFECTIVE

Multibus II helps you reduce costs in all the places you'd expect. Plus quite a few you wouldn't. ■ Initially, Multibus II speeds development by increasing on-board functionality, and simplifying system integration. Which doesn't just reduce costs, it helps you recover them faster by getting to market sooner. ■ A range of bus interface silicon economically meets the needs of high-end multiprocessor systems, low-cost single-CPU applications, and everything in between. ■ Assembly, test and maintenance costs are reduced by features like jumperless board configuration, and built-in self test and diagnostics. For the life of your system. ■

3

FLEXIBLE

Architectural Discipline increases your choices. Of applications you can solve. And ways to solve them. ■ The Message Passing Coprocessor (MPC) and two new lower cost slave interface chips let you build systems ranging from high bandwidth to low-speed I/O. Economically. With full compatibility. ■ You have complete freedom of processors and software. 80x86s, 680x0s and 88000s. Running iRMX*, DOS, OS/2*, UNIX*, FlexOS* and VRTX*. In the same box. At the same time. ■ iSBX*, iLBX* II, MIX and OME allow vast memory expansion and custom I/O. ■ And, Multibus II's unused P2 connector opens a world of possibilities. Like AT Bus on P2 that's available now. And other buses on P2 that are planned. ■



MULTIBUS® II

RESTORES

A

GREAT

VIRTUE:

NEW

MARK 10-1 Thermal Array

Has All The Features You've
Been Waiting For.



- Firmware based
- Screen dumps
- Printer/plotter
- User friendly software
- Best specs on the market
- Flexible, easy to customize/upgrade
- Expandable/overlapped analog traces
- Variety of preamps, including programmable
- 2 year warranty

Call today for more information or to upgrade your existing Mark 10.
Inside California **800-624-8396**, outside California **800-854-8385**.

 **GRAPHTEC**
WESTERN GRAPHTEC, INC.

Switch on the future with solid state.

AT&T's Solid-State Relays are tomorrow's components ready for use today—with new dimensions in speed, reliability, size and efficiency.

AT&T's Solid-State Relays (SSRs) outdistance low-current electromechanical relays (EMRs) in several key match-ups.

Only AT&T's SSRs offer a current limiting feature to protect your existing circuitry.

SSRs provide faster switching speeds than EMRs and do not require on/off settling times.

Because they don't have contacts, SSRs will not fail due to contact wear—a problem inherent in EMRs.

SSRs are more compact than EMRs and may be automatically inserted during the manufacturing process.

And, SSRs have low overall system power requirements.



Designed by Bell Laboratories, AT&T's SSRs are manufactured in state-of-the-art facilities.

Assuring they'll meet the highest quality standards possible, as well as meet a variety of solid-state specifications.

And by offering the widest variety of catalog SSRs, we provide you with access to existing AT&T solutions—easily obtainable through our distributors, Hamilton-Avnet and Schweber.

For more on how AT&T's Solid-State Relays fit into today's circuits and tomorrow's designs, call us at **1 800 372-2447**.

**The
components
of success.**

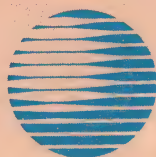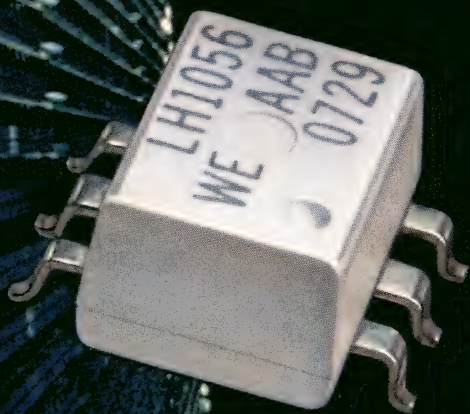

AT&T

The right choice.

Basic principles and ingenious circuits yield stout switchers

A substantial percentage of power supplies are step-down regulators. Although the theory of step-down, "buck" switching regulators is well established, myriad practical details, if mishandled, can spoil the theory's pristine beauty. Luckily, convenient, easily applied switching-regulator ICs have recently become available.

Jim Williams, *Linear Technology Corp*

To design a step-down switching regulator, you can't just copy a circuit from a data sheet or use a theoretical method from a book. Designing step-down switching regulators means solving a nettlesome host of problems and properly following some basic principles.

By far, the toughest nuts to crack are the magnetic components. Magnetic components account for probably 90% of the problems in switching-regulator design. Because of the overwhelming level of difficulty associated with magnetic components, you must choose them judiciously.

The most common magnetic-component problem is saturation. An inductor saturates when it cannot support any more magnetic flux. As an inductor saturates, it begins to look more resistive and less inductive. When it's saturated, only the inductor's dc copper resis-

tance and the source's capacity limit current flow. Thus, saturation often results in destruction.

Although you could apply electromagnetic theory (Ref 1), practically speaking, an empirical approach is often the best way for you to select inductors. A practical approach involves real-time analyses using the ultimate simulator—a breadboard. If you desire, you can use inductor-design theory to augment or confirm your experimental results.

Fig 1 shows a typical step-down switching regulator. The #845 inductor kit from Pulse Engineering (San Diego, CA) proves useful at the breadboard stage. Fig 2a shows the results of installing a 450- μ H, high-capacity-core inductor in Fig 1's circuit and the circuit running at its intended voltage and current levels. Trace A is the regulator-IC V_{SW} pin's voltage; trace B shows its current. When V_{SW} is high, inductor current flows. This particular inductor's high value results in the current rising relatively slowly. The circuit's behavior is linear, indicating that no saturating is occurring.

Fig 2b shows the results of installing a lower-value unit. Although the current rises at a steeper rate, the inductor does not saturate. Fig 2c shows a still lower inductance. Here the current ramp is quite pronounced, but still well controlled. Fig 2d brings some informative surprises. This high-value unit, wound on a low-capacity core, starts out well but saturates rapidly; it is clearly unsuitable.

Trying out different inductors this way quickly narrows your choice to a range of devices. Several may produce acceptable results. You could further select

Magnetic components account for probably 90% of the problems in switching-regulator design.

the optimal unit on the basis of other parameters, such as cost, size, and operating temperature. A standard device may suffice, or the inductor manufacturer can supply a customized version.

The invasion of the drawer dwellers

An alternate inductor-selection method exists—one favored by those who have no inductor kit, time, or adequate instruments. You can use this alternate method when faced with an immediate deadline and a drawer full of inductors of unknown or questionable lineage. Confronting these challenges, engineers often simply insert one of these drawer dwellers into an unsuspecting circuit.

Although this method's theoretical underpinning is perhaps questionable, its seemingly limitless popularity compels coverage. At Linear Technology, we've developed a 2-step procedure for screening inductors of unknown characteristics. Inductors passing both stages of the test have an excellent chance (75%—based on a sample of randomly selected inductors) of performing adequately in a prototype circuit. The only instruments required are an ohmmeter and a scale.

The first test consists of weighing the candidate inductor. Acceptable limits range between 0.01 and 0.25 lbs. The second test involves measuring the inductor's dc resistance. Acceptable limits are usually between 0.01 and 0.25 Ω .

When using an inductor selected by this method, by all means try low power first, then gradually increase loading. As you increase loading, observe the inductor's and regulator chip's heating, making sure that their dissipation is no more than warm to the touch. Disproportionate heat increases as you increase the load probably indicate that the inductor is saturating. Either reduce the load or go back to the drawer and try again.

Capacitors require consideration

Think carefully about your capacitors' requirements, as you must account for all operating conditions. Though voltage rating is the most obvious consideration, remember to also plan for the effects of the capacitors' equivalent series resistance (ESR) and inductance. These specifications can have significant impact on your circuit's performance. In particular, an output capacitor with high ESR can make compensating the loop difficult or decrease efficiency. Other considerations are layout, diode breakdown, and switching requirements.

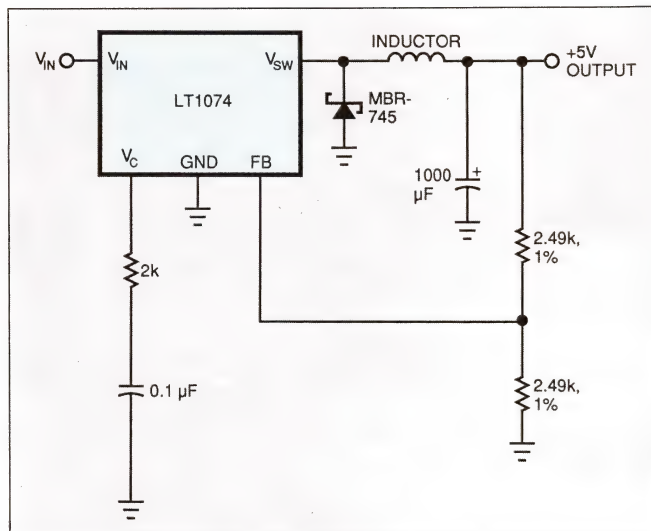


Fig 1—You can use a typical switching-regulator circuit to sample candidate inductors.

Layout is vital. Don't mix signal, frequency-compensation, and feedback returns with high-current returns. Arrange the grounding scheme for the best compromise between ac and dc performance. In many cases, a ground plane may help. Account for possible effects of stray flux from the inductor or other components and plan your layout accordingly.

You must think through diodes' breakdown and switching ratings and account for all operating conditions. Transients usually cause the most trouble for diodes, introducing stresses that are often hard to predict. Study the datasheet's breakdown, current capacity, and switching-speed ratings carefully. Ask yourself if these specifications were determined under the same conditions as those in your circuit. If in doubt, consult the manufacturer.

Switching diodes have two important transient characteristics: reverse-recovery time and forward turn-on time. Reverse-recovery time occurs because the diode stores charge during its forward-conduction cycle. This stored charge causes the diode to act as a low-impedance conductive element for a short period of time after reverse drive is applied.

Hard turn-off diodes switch abruptly from one state to the other following reverse-recovery time. They therefore dissipate very little power, even with moderate reverse-recovery times. Soft turn-off diodes have a gradual turn-off characteristic that can dissipate considerable power during the turn-off interval.

Even fast diodes can be useless if stray inductance

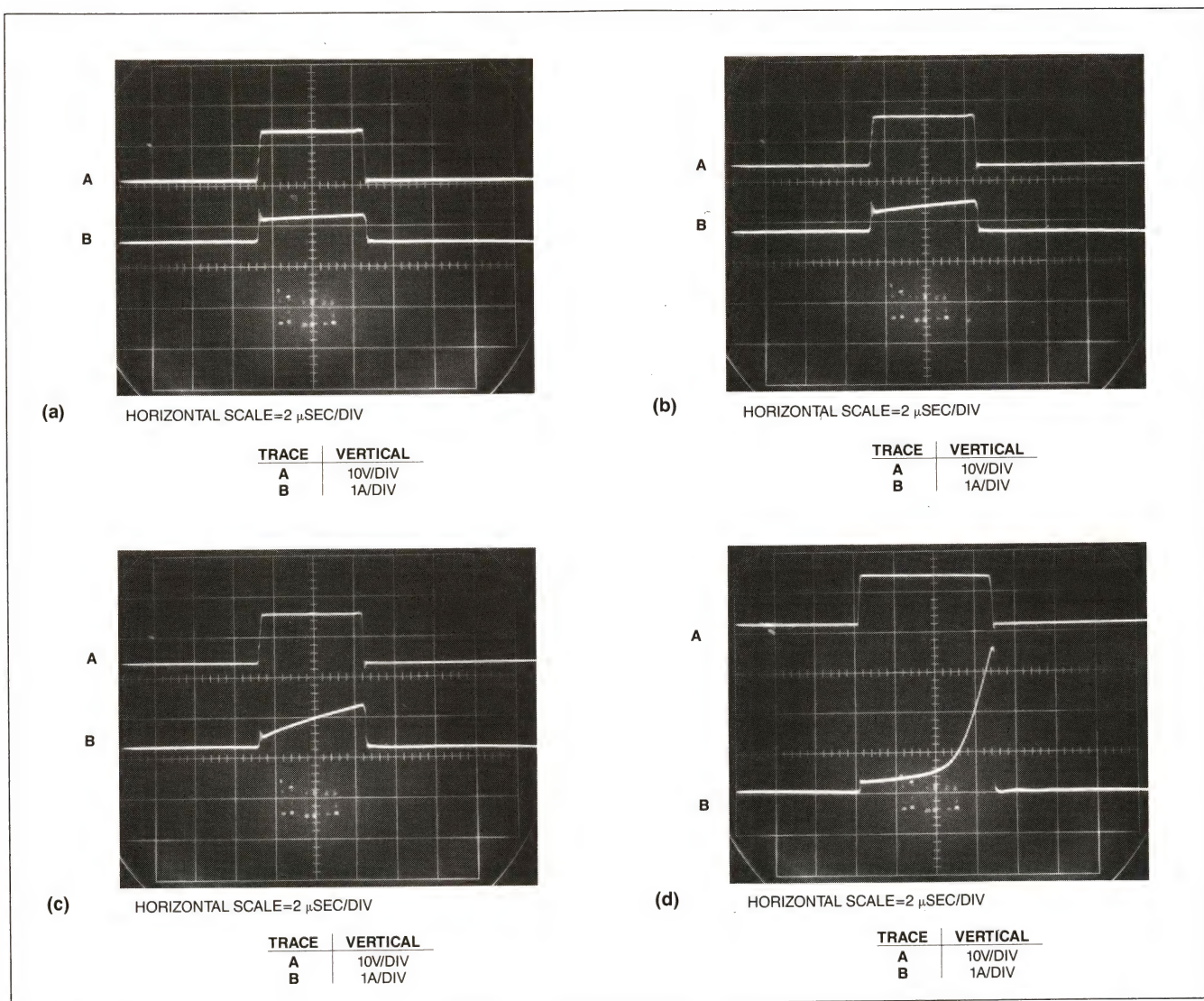


Fig 2—After installing a 450- μ H, high-capacity-core inductor in the test circuit the waveforms in (a) result: Trace A is the regulator-IC V_{SW} pin's voltage; trace B is its current waveform. A lower-value, 170- μ H inductor produces these waveforms (b). After installing an even lower-value, 55- μ H inductor, the current ramp becomes quite pronounced (c). In (d), a 500- μ H, low-capacity-core inductor plainly has too low a value because the current waveform shows that the inductor has quickly saturated.

in the diode, output capacitor, or control loop is high. Remember that 20-gauge hook-up wire has 30 nH/in. of inductance. Currents switching on the order of 10 A/sec are typical in regulator circuits. These fast-changing currents can easily generate several volts/in. across the wiring's stray inductance. Keep the diode, capacitor, and regulator-chip-lead lengths short.

The basic step-down configuration of Fig 1 is relatively free of frequency-compensation difficulties. A simple RC damper network from the V_C pin to ground will usually suffice. Things become more complex when

you add gain- and phase-contributing elements to the regulator's control loop. In these cases, you should view the regulator IC as a low-bandwidth power stage. The stage's delays arise from the sampled-data nature of its power delivery (100-kHz switching frequency) and its output LC filter. In general, limiting the regulator's gain-bandwidth product below that of the added loop elements will stabilize such a complex loop. This principle accords with established feedback theory.

Squeezing the utmost efficiency out of a switching regulator is a complex, demanding design task. Effi-

The most common magnetic-component problem is saturation.

ciency exceeding 80 to 85% requires some combination of finesse, witchcraft, and just plain luck. Interacting electrical and magnetic terms produce subtle effects that influence efficiency. A detailed, generalized method for obtaining maximum converter efficiency isn't possible, but some guidelines do exist.

Losses fall into several loose categories including drive, junction, ohmic, switching, and magnetic. Semi-

conductor junctions produce losses. Diode drops increase with operating current and can be quite costly in low-output-voltage switchers. For example, a 700-mV drop in a 5V-output switcher introduces more than a 10% loss. Though Schottky devices will cut the loss nearly in half, it is still appreciable. The ohmic losses in germanium diodes (now rarely used) are lower still, but switching losses negate the low dc drop of germa-

Techniques and equipment measure changing current

Accurately measuring rapidly changing current flow is essential to switching-regulator design. In many cases, current waveforms contain more valuable information than do voltage measurements.

The most powerful and convenient current-measuring tool is the clip-on current probe. The Tektronix P-6042 (bottom left in Fig A) is a Hall-effect, stabilized current transformer that responds from dc to 50 MHz.

These clip-on probes contain a current transformer and a Hall-effect transducer. The transducer senses current at dc and low frequencies; the transformer simultaneously processes the signal's high-frequency content. Their dc response allows you to determine the dc content of high-speed current waveforms. Sensitivities

range from fractions of a milliamperere to amperes.

The combination of convenience, broad bandwidth, and dc response make Hall-effect, stabilized current probes the instruments of choice for converter designers.

Transformer-based clip-on current probes are also available. Though they lack the dc response of their Hall-effect cousins, they're still quite useful. The Tektronix type 131 (upper left, Fig A), and the more modern 134, respond from hundreds of hertz to about 40 MHz.

AC current probes are also available with a simple termination (left foreground Fig A). These devices are more difficult

to use than the actively terminated models because of their complex gain switching. Their low-frequency response is also poorer, although their high-frequency response exceeds 100 MHz.

The simple transformer (Fig A's foreground) is a final form of ac current probe. These transformers are not clip-on devices, and they usually have significant performance limits compared with the clip-on instruments. However, they are inexpensive and can provide meaningful measurements when used according to manufacturers' recommendations. In practice, you thread the conductor through the opening provided and monitor the signal at the transformer's output pins.

Fig A also shows a wide-ranging dc clip-on current probe. The Hewlett-Packard 428B (upper right) responds from dc to only 400 Hz but features 3% accuracy over a 100- μ A to 10A range. The instrument obviously cannot distinguish high-speed events, but it is invaluable for determining overall efficiency and quiescent current.

A great strength of these probes is that they take a fully floating measurement. Extract-



Fig A—A host of devices can help you make current measurements.

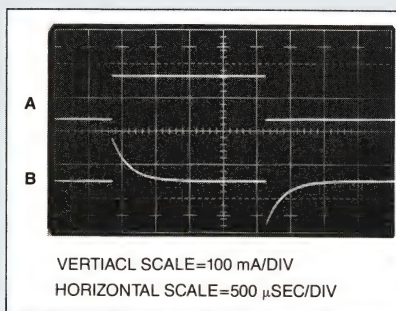


Fig B—Trace A is the output of a stabilized Hall-effect current probe, and trace B is the same signal measured with a transformer-based probe; clearly, the transformer-based probe is useless at low frequencies.

nium at high switching speeds. In very low-power switchers, germanium's reverse leakage may be equally oppressive. Synchronously switched rectifiers are more complex, but can sometimes simulate a more efficient diode.

When evaluating rectifying and switching schemes, remember to include both ac and dc drive losses in your efficiency estimates. DC losses include base or

gate current in addition to dc consumption in any driver stage. AC losses might include the effects of base or gate capacitance, transition-region dissipation (the switch spends some time in its linear region), and power lost because of timing skew between drive signals and actual switch action.

The LT1074 regulator IC's output switch, for example, comprises a PNP transistor driving a power NPN

ing current information via magnetic coupling eliminates common-mode voltage considerations. As good as they are, however, current probes have limits and characteristics that you must remember in order to avoid unpleasant surprises. At high currents, for example, the probe may saturate. The saturation will corrupt the resulting CRT waveforms, rendering the measurement useless and confusing the unwary.

Further, for Hall-effect types, noise interferes with measurements below a few hundred microamperes. Luckily, this noise is obvious on the display.

Keep in mind that signal-transit delays vary from current probe to current probe and all are different from voltage probes. At

high-sweep speeds these effects show up in multitrace displays as time skewing between individual channels. You can mentally factor in the current probes' transit-time delay to reduce error when interpreting the display. Note that active probes have the longest signal transit, on the order of 25 nsec.

When interpreting CRT displays, you must also keep in mind the low-frequency bandwidth restrictions of ac current probes.

Fig B clearly demonstrates this principle by showing the ac probe's inability to follow low frequency. Similarly, remember that the probe's stated bandpass is -3 dB, meaning that signal information is not entirely present in the display at this frequency. When working at, or approaching, either end of the probe's bandpass consider that displayed information may be distorted or incomplete.

There are other ways to measure wideband current signals, although they're less convenient and desirable than clip-on current probes. Current shunts (**Fig C**, foreground) are low-value resistors with 4-terminal connections for accurate measurement. In theory, measuring voltage across a current shunt should yield accu-

rate information. In practice, common-mode voltages introduce measurement difficulties, particularly at speed. Making such measurements requires an isolated probe or high-speed differential oscilloscope plug-in. The isolation amplifier in **Fig C** from Signal Acquisition Technologies (Minden, NV), has a 10-MHz bandwidth, a galvanically floating input, and 600V common-mode capability. The instrument allows any oscilloscope to take a floating measurement across a shunt.

Differential oscilloscope plug-ins, while not galvanically floating, can measure the voltage across a shunt. Tektronix types W, 1A5, and 7A13 have 1-mV sensitivity with a bandwidth as high as 100 MHz and excellent common-mode rejection. Types 1A7 and 7A22 have 10- μ V sensitivity, although their bandwidth is limited to 1 MHz. All differential plug-ins have bandwidth or common-mode-voltage restrictions that vary with sensitivity. You must review these tradeoffs when you select the optimal shunt value for a particular measurement. In general, the smallest practical shunt value is preferable. This small value minimizes the inserted resistance's parasitic effects on the circuit's operation.



Fig C—Current shunts are low-value resistors having 4-terminal connections for accurate current measurements.

An empirical approach, using the ultimate simulator—a breadboard—is often the best way for you to select inductors.

transistor. The switch's drop can reach 2V at high currents. This drop will usually be the major loss in the circuit. You can mitigate the drop's effect on efficiency by using the highest possible input voltage. Higher output voltages will further minimize losses.

Actual losses from switch-saturation effects and diode drops are sometimes difficult to precisely ascertain. Changing duty cycles and time-varying currents make determining losses tricky. One simple way to judge relative losses is to measure various devices' temperature rises. Appropriate tools here include thermal probes and, at low voltages, the perhaps more readily available human finger. At lower power, even though the percentage of loss may be as great, the latter "digital" technique is less effective. Sometimes deliberately adding a known loss to the component in question and noting changes in efficiency allows you to determine actual losses.

Ohmic losses in conductors are usually only significant at higher currents. Hidden ohmic losses include socket and connector-contact resistance and ESR in capacitors. ESR generally drops with capacitor value and rises with operating frequency. Consider the copper resistance of inductive components. You must often evaluate tradeoffs of an inductor's copper resistance versus its magnetic characteristics.

Switching losses occur when the switching device

spends significant amounts of time in its linear region relative to operating frequency. At higher switching frequencies, transition times can engender substantial losses.

The design of the magnetic components also influences efficiency. Inductive-component design is well beyond the scope of this article, but some of the trade-offs and specifications include core-material selection, wire type, winding techniques, size, operating frequency, current levels, temperature, and others. No substitute exists for access to a skilled magnetic-components specialist. Fortunately, the nonmagnetic losses previously mentioned usually dominate, allowing you to obtain good efficiencies with standard magnetic components. Thus, you usually need to employ custom magnetic components only after you have reduced other circuit losses to their lowest practical level.

Practical circuits

To illuminate practical circuits, first reconsider the simple example of a voltage step-down regulator in Fig 1 with a 150- μ H inductor installed. Conceptually, you can think of the regulator IC as having a switch between its V_{IN} and V_{SW} pins. When this "switch" closes, the input voltage appears at the inductor. Current flowing through the inductor-capacitor combination builds over time. When the switch opens, current flow

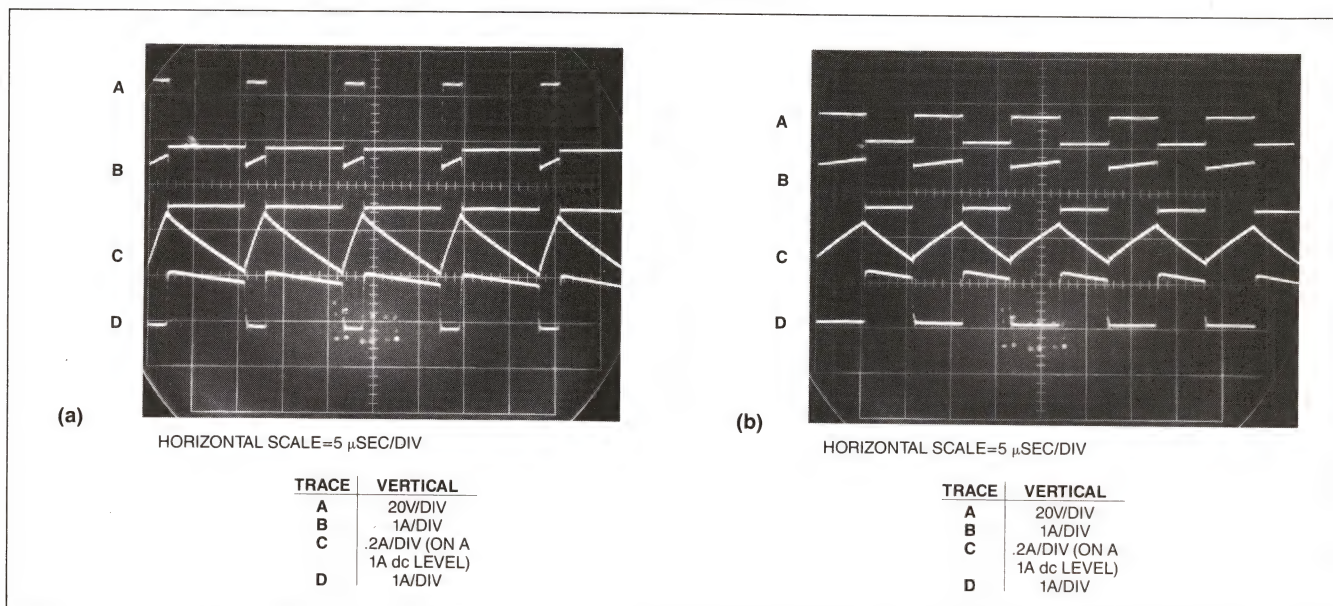


Fig 3—In these operating waveforms for Fig 1's circuit with a 150- μ H inductor installed and $V_{IN}=28$ V, trace A is the V_{SW} pin's voltage and trace B is its current. Inductor current appears in trace C and diode current in trace D. The waveforms in (a) correspond to a 5V, 1-k Ω load while the waveforms in (b) show significant duty-cycle changes when the input voltage drops to 12V.

ceases and the magnetic field around the inductor collapses.

As Faraday demonstrated, the voltage that the collapsing magnetic field induces is opposite in polarity to the originally applied voltage. As such, the inductor's left side becomes negative and the diode clamps it to ground. The capacitor's accumulated charge has no discharge path and a dc potential appears at the output; the dc potential is lower than the input voltage because the inductor limits current during the switch's on time. In this basic circuit, feedback-controlled switching action regulates the output voltage. Switch on time, and thus inductor charge time, vary to maintain the output-voltage level against changes in input voltage or output loading.

Ideally, no dissipative elements exist in this voltage step-down conversion. Thus, although the output voltage is lower than the input voltage, no energy-conversion losses occur. In practice, the circuit elements *do* have losses, of course, but step-down regulator efficiency is still higher than with inherently dissipative, voltage-divider approaches.

Components at the regulator IC's V_C compensation pin control the IC's frequency compensation, stabilizing the feedback loop. You select the feedback resistors to force the voltage at the FB feedback pin to match the device's internal 2.5V reference value.

Fig 3a shows operating waveforms for the regulator

at $V_{IN}=28V$ with a 5V, 1-k Ω load. Trace A is the V_{SW} pin's voltage; trace B is its current. Inductor current appears in trace C; diode current appears in trace D. Examining the current waveforms allows you to determine the V_{SW} 's and diode path's contributions to the inductor's current. Note that the inductor current's waveform occurs on top of a 1A dc level. **Fig 3b** shows significant duty-cycle changes when V_{IN} drops to 12V. This lower input voltage requires longer inductor-charge times to maintain the required output level.

Dual-output step-down regulator

Fig 4, a logical extension of the basic step-down switching regulator, provides positive and negative outputs. The circuit is essentially identical to **Fig 1**'s basic switcher, except that it has a winding coupled to L_1 . This floating winding's output gets rectified, filtered, and regulated to a -5V output. The negative output can use a positive voltage regulator because its floating bias allows you to assign the regulator's output terminal to ground. You can also reference its output to any voltage within the breakdown capability of the device. Hence, the secondary output *could* be +5V or, if stacked on the +15V output, +20V.

Flux pickup from L_1 's driven winding sets the limit for negative output power. With a 2A load at the +15V output, the -5V output can supply more than 500 mA.

You can also obtain negative outputs with a simple,

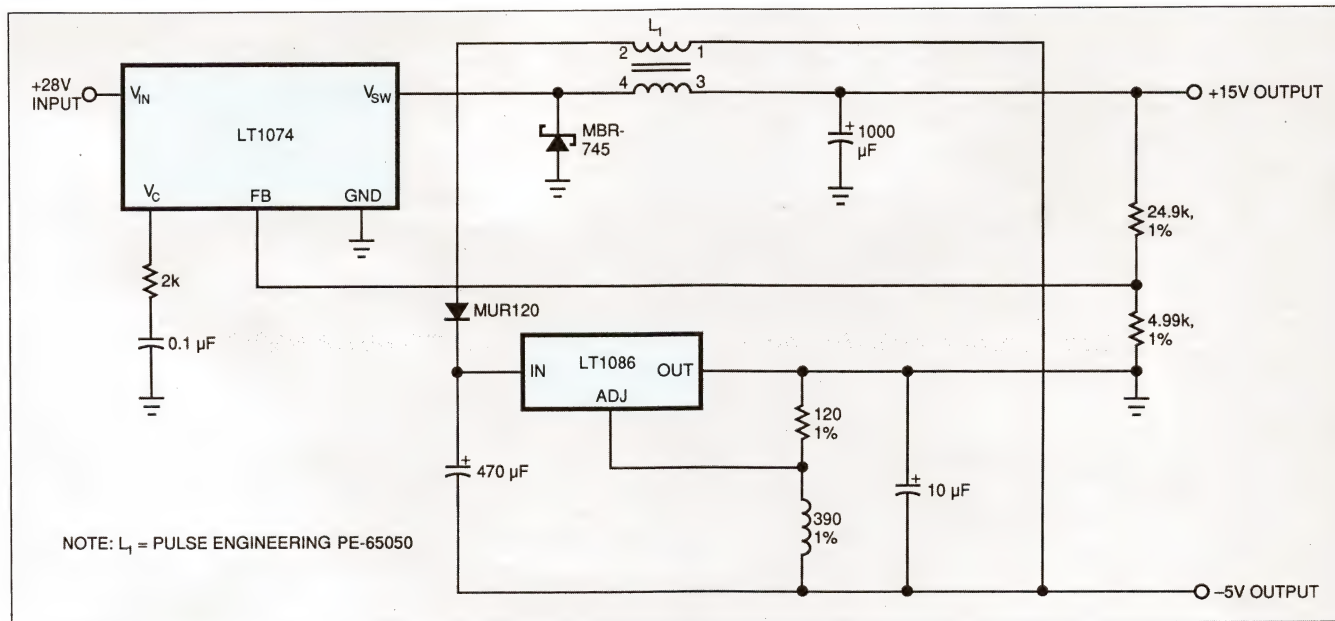


Fig 4—Adding a coupled winding to the basic circuit's inductor allows you to tap off a floating auxiliary output.

Confronting the challenge of selecting the proper inductor, engineers often simply insert an anonymous drawer dweller into an unsuspecting circuit.

2-terminal inductor instead of a multiwinding inductor (Fig 5). You essentially ground the inductor and steer the catch diode's negative current to the output. IC₂ closes the loop by inverting and scaling the negative output to the regulator IC's feedback pin. The 1% resistors' scale factor sets output voltage; the RC network around IC₂ gives frequency compensation. Waveforms for this circuit are reminiscent of Fig 1's, with the exception that diode current is negative.

Fig 6, which we call "Nelson's circuit," provides the same function as the previous circuit, but eliminates the level-shifting op amp. Circuit ground is common to input and output. Connecting the regulator IC's ground pin to the negative output accomplishes the design's level shift. The regulator IC senses feedback relative to the circuit's ground, and it drives its output so as to force its feedback pin to be 2.5V above its ground pin. The previous negative-output circuit has

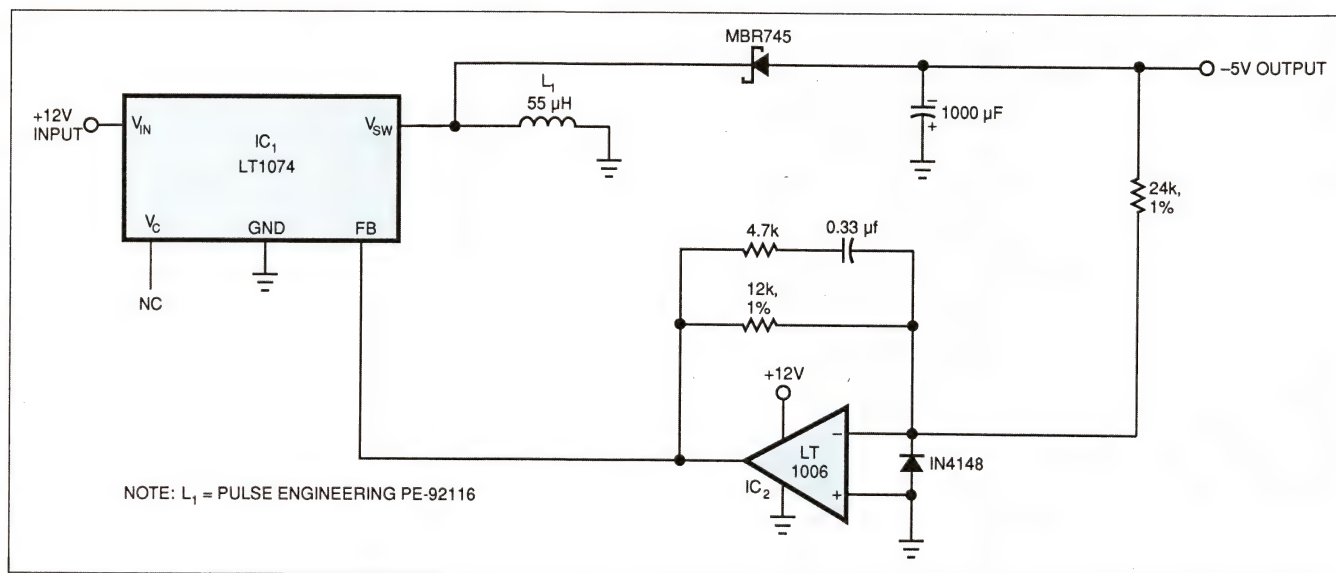


Fig 5—You can obtain negative outputs using a simple 2-terminal inductor—if you ground one end and properly orient the catch diode.

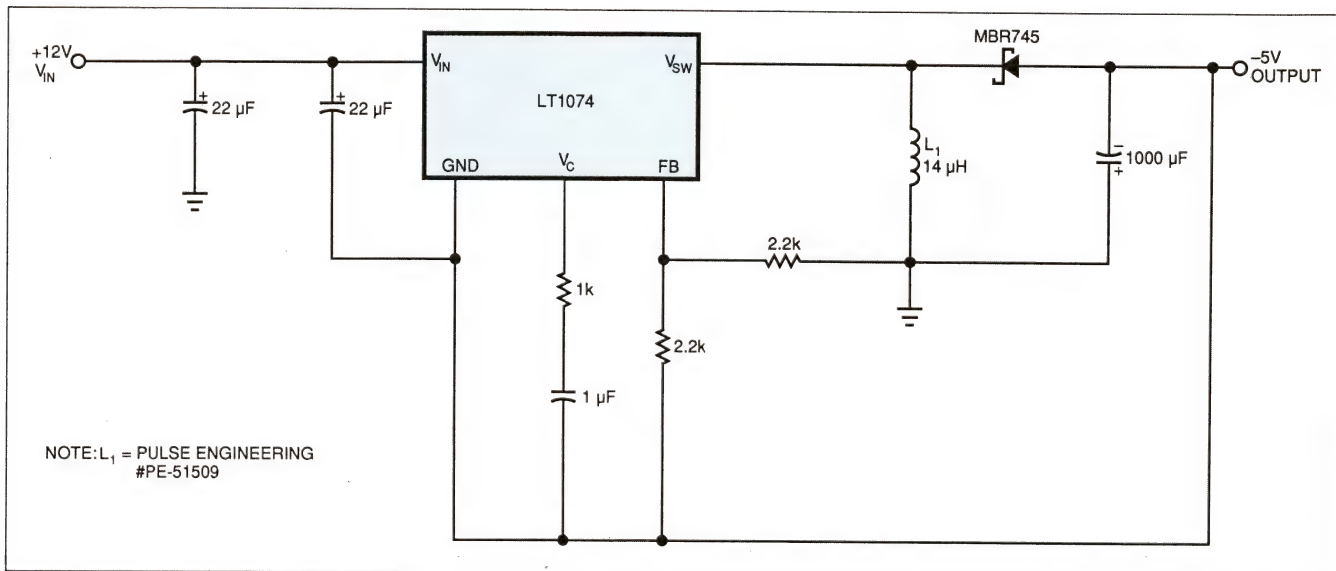


Fig 6—This negative-output circuit eliminates the level-shifting op amp. Connecting the regulator IC's ground pin to the negative output accomplishes this design's level shift.

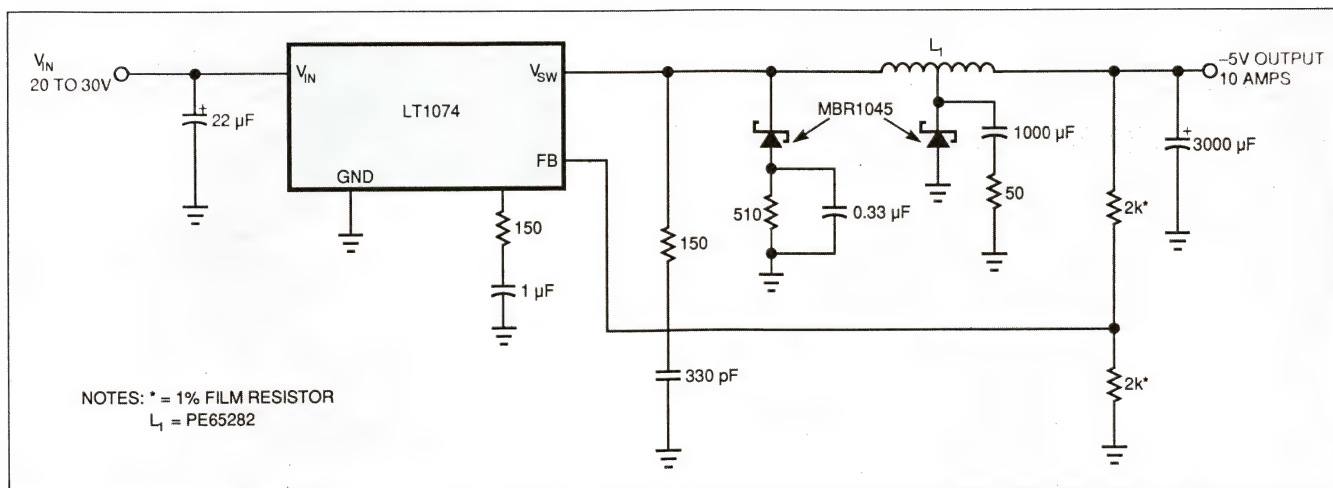


Fig 7—Don't be fooled. D_1 is not a catch diode; it's part of a snubber circuit. D_2 is the catch diode. When D_2 conducts, it switches out a portion of the inductor's turns, forcing the inductor's magnetic field to deliver its stored energy through an effectively smaller inductance and thereby increasing the circuit's output-current capability.

two advantages, compared with Nelson's. First, the package can directly contact a grounded heat sink. Second, the IC's control pins are ground referred.

Note that the inductor values in both negative-output designs are notably lower than in the positive-output designs. The reduced loop-phase margin of these circuits demands the lower-value inductors. Higher inductance values, while preferable for limiting peak current, will make the loop unstable or even cause it to oscillate.

Current-boosted step-down regulator

Fig 7 shows a novel way to obtain significantly higher output currents—by utilizing efficient energy storage in the regulator IC's output inductor. The technique prolongs current flow from the inductor and thereby effectively increases the inductor's duty cycle, compared with the standard step-down switching regulator's, allowing more energy storage in the inductor. But beware, the increased output current comes at the cost of higher output-voltage ripple.

The key to the design is its tapped inductor. With it, the circuit has current gain. If N is the ratio of switch-side turns to output-side turns, current delivered to the output will be $N + 1$ times higher during the V_{SW} 's off time as compared to the current flowing during its on time.

Fig 8 shows the circuit's operating waveforms. Its operating characteristics are initially similar to that of the step-down switching regulator in Fig 1. During V_{SW} 's on time (trace A), the regulator IC applies the

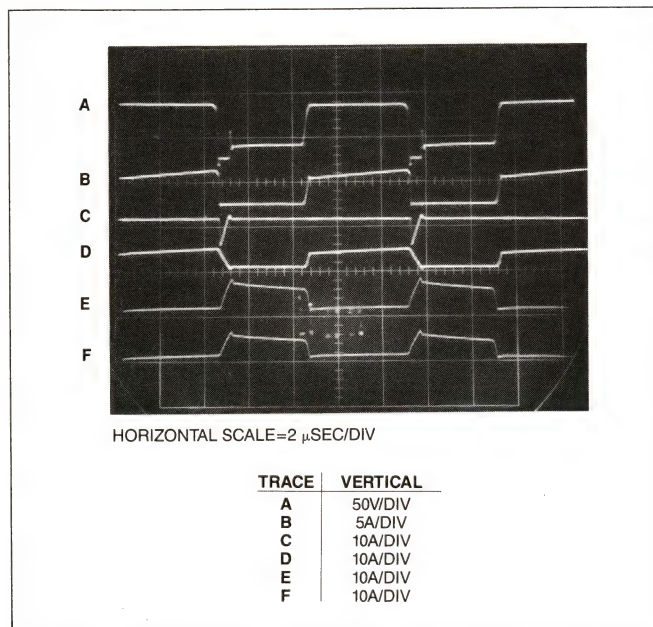


Fig 8—In these operating waveforms for Fig 12's circuit, trace A is V_{SW} 's voltage, trace B is its output current, trace C is the snubber circuit's D_1 current, trace D is the inductor's input current (minus the snubber circuit's contribution), trace E is the current through D_2 , and trace F is the output current.

input voltage to one end of the tapped inductor. Because inductor current (trace F) is still present, current from the V_{SW} pin (trace B) ramps up almost instantaneously, then slows as the core stores energy. The current proceeds into the inductor (trace D) and finally to the load.

Think carefully about your capacitors' requirements; you must account for all operating conditions.

When the V_{SW} pin is off, current is no longer available to charge the inductor. The magnetic field therefore collapses, causing the V_{SW} pin's voltage to go negative, ending the similarity to the basic regulator. In the modified version the output current (trace F) receives a boost as the magnetic field collapses. The boost results when the energy stored in the tapped inductor transfers to the output. This current step circulates through C1 and D2 (trace E) and increases the output-voltage ripple.

Not all the energy, however, transfers to the output-side turns. Current (trace C) will continue to flow in the switch-side winding because of leakage inductance, whose effects are suppressed by a snubber network. To minimize snubber losses, the tapped inductor is bifilar wound for maximum coupling.

In most instances the switching regulator's output will go directly to the load. However, those applications requiring faster transient response or reduced noise will benefit from linear post regulation. To incur minimal efficiency losses, you must set the switching-regulator IC's output to provide just enough voltage to the linear regulator to maintain regulation. In such applications, a low-dropout linear regulator works best.

Post regulation, variable case

Some applications require variable linear post regulation (Fig 9a). The circuit operates with little efficiency sacrifice. The linear regulator operates in normal fashion, supplying a variable 1.2 to 28V output. The remainder of the circuit forms a switched-mode preregulator that maintains a small, fixed voltage



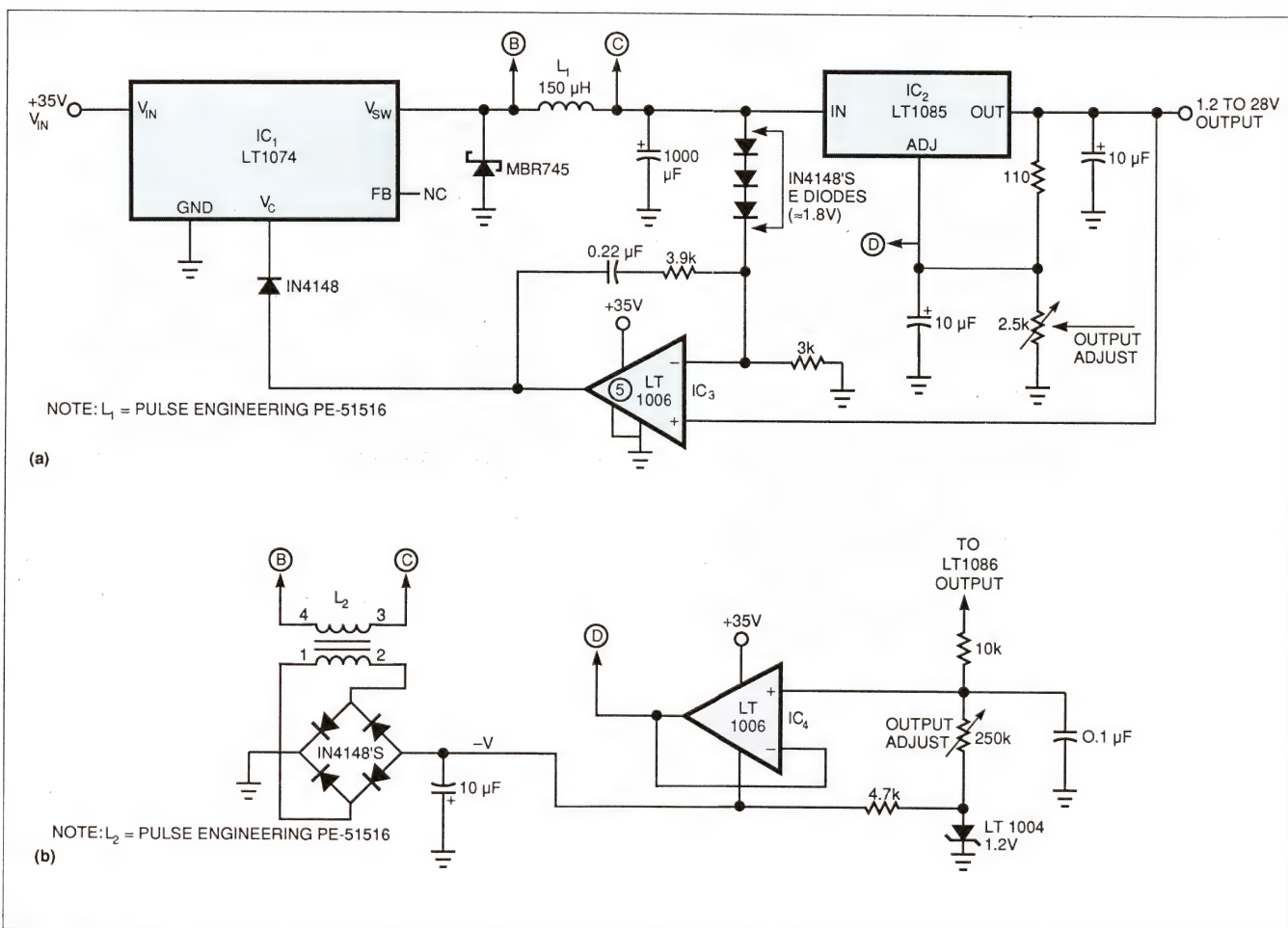


Fig 9—The feedback loop of this variable-output regulator, (a), ensures that the voltage impressed across the linear postregulator, set by the "E" diode string, is always just the minimum voltage it needs to operate. The optional circuit in (b) permits output voltages down to 0V.

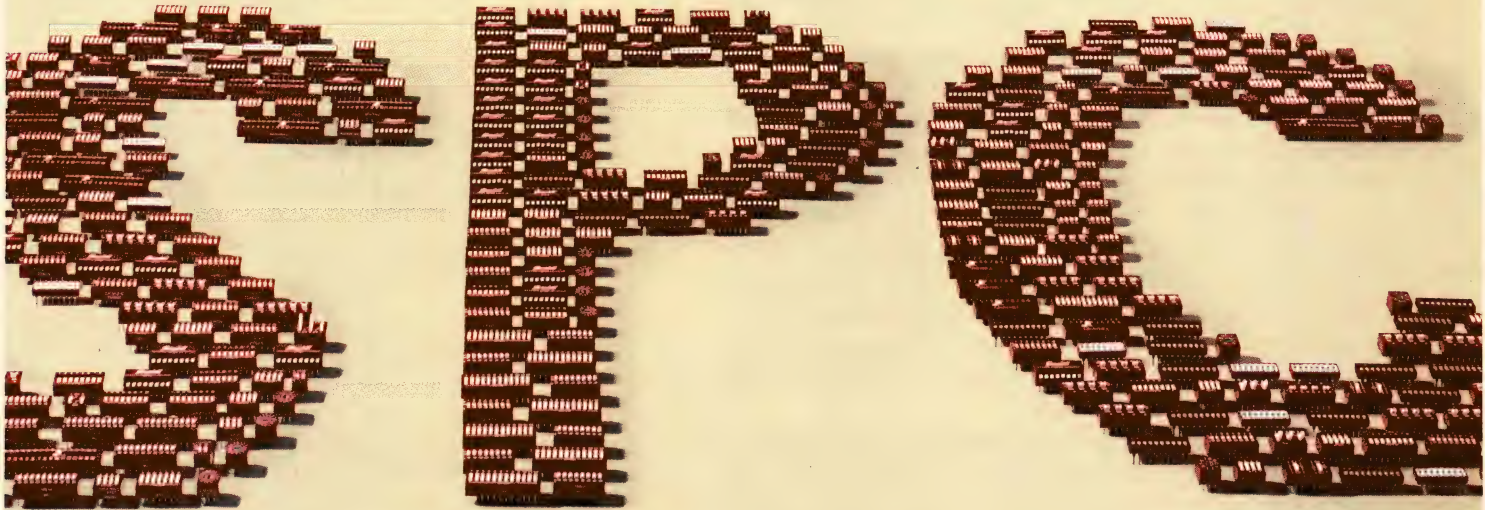
Grayhill Statistical Process Control makes DIP switch quality a reality, not a slogan



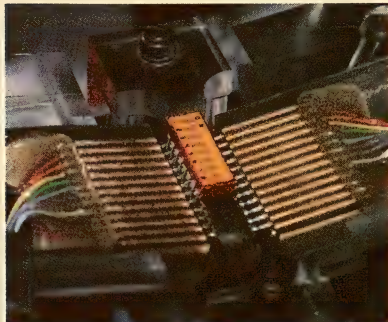Is your DIP switch supplier being measured by SPC?



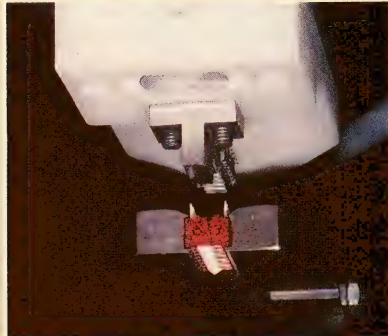Grayhill DIP Switches are tested every step of the way in the manufacturing process. If initial contact resistance varies from control limits, the problem is immediately diagnosed and cured.



This machine automatically tests every DIP switch for actuation force. We get reliable ppm data and you get reliable DIP Switches.


The industry's reliance on Grayhill leadership has received another boost with the implementation of SPC manufacturing techniques to our DIP switch lines. (Note: SPC data not yet available for all configurations.)

In-line measurements are control-charted. Variations are identified to maintain processes within controlled limits. Only acceptable product comes off the Grayhill line and onto yours!

If your DIP switch supplier can't give you parts per million data, you should be talking to Grayhill. We offer you the widest choice of DIP switch actuators, stations, and circuitries, including MIDIP™ machine-insertable switches. Prices are competitive, but we offer features as standard that are extras elsewhere.

Grayhill DIP switches, as well as rotary and pushbutton switches, keyboards, solid state relays and I/O modules, are available from authorized distributors world-wide and are described in detail in EEM.

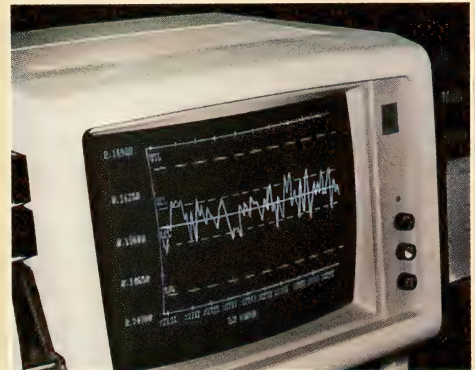Ask us for your FREE copy of Engineering Catalog #1 with detailed DIP switch specifications... and call now for full details on SPC DIP switches.



Variable data is entered electronically at production sites and transmitted to the Grayhill mainframe to track performance and compile reports.

Grayhill
INC.

561 Hillgrove Avenue, P.O. Box 10373
LaGrange, Illinois 60525-0373 USA
Phone: (312) 354-1040 FAX: (312) 354-2820
TLX or TWX: 190254 GRAYHILL LAGE

Layout is vital; don't mix signal, frequency-compensation, and feedback returns with high-current returns.

across the linear regulator regardless of its output.

IC₃ biases the step-down switching regulator to produce whatever voltage is necessary to maintain the “E diodes” potential across the linear regulator. You can adjust the number of diodes in the “E diode” string to achieve different voltages across the linear regulator. IC₃’s inputs are balanced when the linear regulator’s output is “E diodes” below its input. IC₃ maintains this condition regardless of line, load, or output-voltage conditions. Thus, the circuit maintains good efficiency over the full range of output voltages. The RC network at IC₃ compensates the loop.

Deliberately introducing a positive offset to IC₃ ensures loop startup. Grounding IC₃'s appropriate balance (in this case pin 5), induces the offset, resulting in a positive 6-mV offset, which, normally considered poor practice because it increases amplifier drift, causes no measurable error in this application. As shown, the circuit cannot produce outputs below the regulator IC's 1.2V internal reference. Applications requiring outputs adjustable down to 0V will benefit from the option in **Fig 9b**, which replaces L₁ with L₂. L₂'s primary winding performs the same function as L₁'s, while its coupled secondary winding produces a negative-bias output, $-V$. The negative bias allows regulated outputs down to 0V.

The $-V$ potential derived from L_2 's secondary winding varies considerably with operating conditions; wildly varying duty cycles necessitate the optional circuit's full-wave bridge rectifier. The high feedback string values and IC_4 's buffering ensure that the circuit will be stable for "starved" values of $-V$. IC_4 and its attendant circuitry replace all components associated with the linear regulator's ADJ pin.

Low quiescent-current regulators

Many applications require currents in the ampere range under normal conditions, but only microamperes while in standby or “sleep” mode. A typical laptop computer, for example, may draw 1 to 2A running, but need only a few hundred microamperes for its memory when turned off. In theory, any regulator, with a loop properly designed to be stable under no load, will work. In practice, a switcher having relatively large quiescent current may be unacceptable because of excessive battery drain during low current-output periods—even if it operates serenely.

Fig 10's simple loop effectively reduces circuit quiescent current from 6 mA to only 250 μ A. The circuit uses the regulator IC's shutdown pin. When the circuit

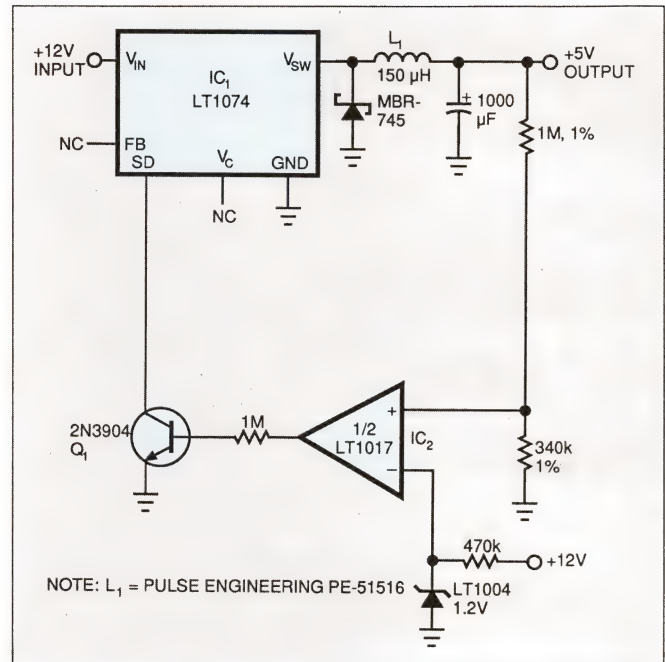


Fig 10—This circuit's simple loop reduces its quiescent current from 6 to only 250 mA by switching the regulator off at low loadings.

pulls this pin to within 350 mV of ground, the IC shuts down and draws only 1200 μ A. Short on times keep the duty cycle low, resulting in the small, effective quiescent current. Comparator IC₂ combines with the regulator IC's reference and Q₁ to form a "bang-bang" control loop around the regulator IC, which bypasses the regulator IC's internal feedback amplifier and reference.

When the circuit's output falls slightly below 5V, IC₂'s output switches low, turning off Q₁ and enabling the regulator IC. The V_{sw} pin then pulses at full duty cycle, forcing the output back above 5V. IC₂ then biases Q₁ on again, the regulator IC goes into shutdown, and the external loop's action repeats. The frequency of this on-off control action is directly load dependent, with typical repetition rates of 0.2 Hz at no load. The on-off operation combines with the LC filtering action in the regulator's V_{sw} line to generate an output hysteresis of about 50 mV.

The external loop performs well but has two potential drawbacks. At higher output currents the loop oscillates in the 1 to 10-kHz range, causing audible noise, which users may object to. Also, the control loop's operation forces about 50 mV of ripple on the output. Ripple frequency ranges from 0.2 Hz to 10 kHz depending on input voltage and output current.

All-Star Performers

Dynamic FET Op Amps Give Designers More Speed, Fewer Errors.

Our new OPA627 and OPA637 op amps minimize speed vs precision trade-offs for a very broad range of instrumentation, data acquisition, and audio applications. No other amps on the market come close to matching the all-around AC and DC performance of these uncompromising new devices:

- ★ Ultra-low noise: $4.5\text{nV}/\sqrt{\text{Hz}}$ (10kHz)
- ★ Fast settling to 0.01%: 550ns (OPA627), 450ns (OPA637)
- ★ Low V_{os} : 100 μV max
- ★ Low drift: 0.8 $\mu\text{V}/^\circ\text{C}$ max
- ★ Low THD+N: 0.0005% OPA627, (G = +1, 1kHz)
- ★ Low I_B : 5pA max
- ★ GBW: 16MHz (OPA627), 80MHz (OPA637)
- ★ Supplies: $\pm 4.5\text{V}$ to $\pm 18\text{V}$
- ★ Output: 45mA at $\pm 10\text{V}$



Complementary Bipolar *Difet*® Design

These new, monolithic op amps are fabricated on our high speed,


dielectrically-isolated, complementary bipolar process and laser trimmed for exceptional accuracy, stability, and dynamic performance.

OPA627 is unity-gain stable, and OPA637 is stable in gains of five and above. They are available in 8-pin plastic DIPs and metal TO-99 packages and in industrial and military specified temp ranges. (Available Q1 '90 in SOIC and die.)

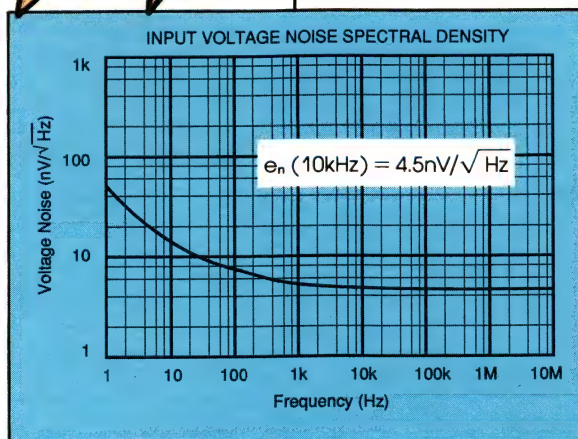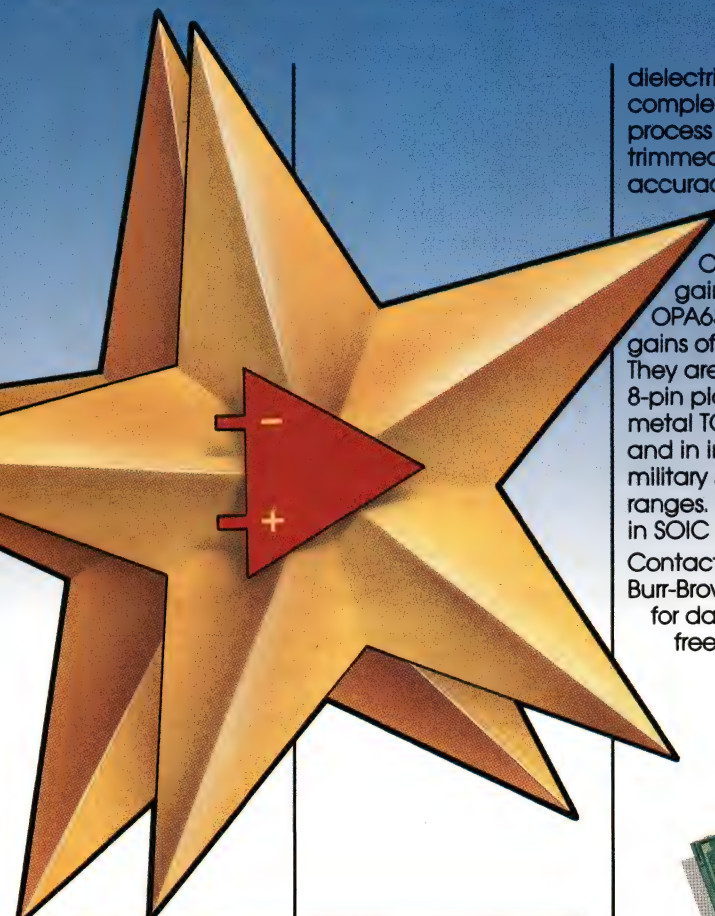Contact your local Burr-Brown sales office for data sheets and free samples.



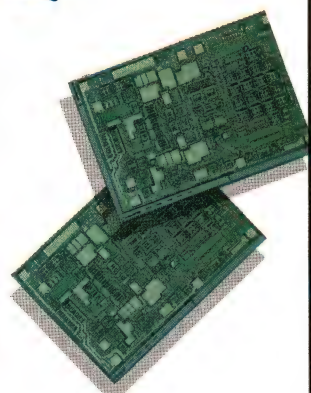OPA627/637 exhibit low noise over a wide frequency spectrum. They are the industry's lowest noise FET op amps.



Burr-Brown Corp.
P.O. Box 11400
Tucson, AZ 85734
U.S.A.

FAX (602) 741-3895

Difet® - Burr-Brown Corp.


*U.S. OEM prices, in 100s.

BURR-BROWN®
BB

Fig 11's signal flow is similar to **Fig 10's**, but additional circuitry appears between the feedback divider and the regulator IC. The circuit does not use the regulator IC's internal feedback amplifier and voltage reference. Under no load, the output voltage will slowly ramp down over a period of seconds, during which the comparator IC₁'s output is low, as are the outputs of the paralleled 74C04 inverters. The inverters, in turn, pull the regulator IC's V_C pin low, forcing the IC to a zero duty cycle. Simultaneously, IC₂'s output is low, putting the regulator in shutdown mode. Therefore, the V_{sw} pin is off and no inductor current flows.

This “bang-bang” control loop keeps the 5V output’s level within the loop’s 60-mV hysteresis window. Note that compared with the loop’s oscillation period of seconds, the R_1 - C_2 time constant at V_C is not significant. Because the regulator spends almost all of its time in shutdown mode, the circuit draws very little quiescent current—150 μ A.

As the load increases, the loop's oscillation frequency increases to keep up with the load's demand; R_1 - C_1 begins to filter the waveform at the V_C pin. If the load continues to increase, the loop's oscillation frequency will also increase. The R_1 - C_1 time constant, however, is fixed. Beyond some frequency, R_1 - C_1 must average loop oscillations to dc. Here, the V_C waveform becomes heavily filtered at loads of 7 mA and above. At 1A

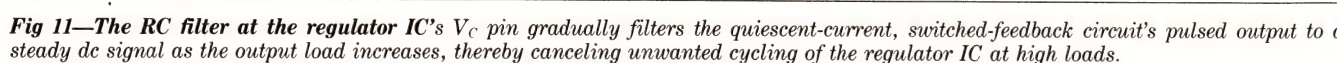

"The final design has the
circuit board in the back,
but the LEDs must be
in the front.

Now what?!"



All indications are Dialight.

Call it a problem that could have led to considerable expense. The customer thought he'd have to add several steps to his assembly process. Instead he called Dialight.

As the leader with over half a century of experience in every type of indicator light, for Dialight solving problems is standard operating procedure. Applying our engineering expertise in optoelectronics and utilizing state of the art CAD equipment, we rapidly proceeded to custom design the ideal solution – a totally integrated, remote LED indicator. Not only did it fit the unit perfectly, but it also saved the expense and effort of cumbersome wiring, soldering, and testing. Plus it added the reliability of a push-on connector for easy assembly. All while being low cost. And, thanks to our extensive in-house tool fabrication

and molding facilities, we delivered it virtually overnight.

Saving costs while solving problems is something we've long done with our panel mount and circuit board LEDs. Over the years customers have asked us to pair, gang, piggyback, right angle mount, recess, bicolor, tricolor, slant, standoff, snap-mount, bin, do whatever you can imagine to them and we haven't been stumped yet!

So, the next time you think there's a remote chance of finding the right solution to an indicator design issue, remember that no one has more solutions than Dialight.

DIALIGHT CORPORATION

A Cambridge Electronic Industries Co.

1913 Atlantic Avenue, Manasquan, NJ 08736 201-223-9400

In theory, any regulator, with a loop properly designed to be stable under no load, will work.

loads, the regulator IC's V_C pin will see pure dc; the regulator IC will be running at its full 100-kHz clock rate.

With the V_C pin at dc, you can conveniently think of IC₁ and the inverters as a linear error amplifier with a closed-loop gain set by the R_2 - R_3 feedback divider. In fact, IC₁ is *still* trying to modulate the duty cycle at the V_C pin, but at a rate far above R_1 - C_1 's break frequency. R_1 - C_1 's roll-off and the phase lead of C_3 into IC₁ dominate C_2 's phase error (C_2 was, after all, selected for low loop frequency at low output currents).

The loop is stable and responds linearly for all loads beyond 10 mA. In its high-current region, the regulator IC is desirably fooled into behaving like a conventional step-down regulator.

Formal analysis difficult

A formal stability analysis for this circuit is quite complex; simplifying it somewhat lends insight into the loop's operation. At 250 μ A, C_2 and the 20-k Ω load form a decay-time constant exceeding 30 sec. This delay is orders of magnitude larger than R_2 - C_2 , R_1 - C_1 , or the regulator IC's 100-kHz commutation rate. As a result, C_2 dominates the loop. Wideband comparator IC₁ sees phase-shifted feedback, and very low-frequency oscillations occur. Although C_2 's decay time constant is long, its charge time constant is short because the circuit has low sourcing impedance. This difference accounts for the ramp nature of the oscillations.

Increased loading reduces the C_2 -load decay time constant. As loading increases, the loop oscillates at a higher frequency because of C_2 's decreased decay time. When the load impedance becomes low enough, C_2 's decay time constant ceases to dominate the loop. R_1 and IC₂ almost entirely determine this point. Once R_1 and IC₂ reign as the dominant time constant, the loop begins to behave like a linear system. Now, C_3 becomes significant, performing as a simple feedback lead to smooth output response ("zero compensation" for all you technosnobs out there).

A fundamental tradeoff exists for C_3 's phase lead. When the switcher is running in its linear region, C_3 's phase lead must dominate the loop's time-lag-generated hysteretic characteristic. As such, select C_3 to be the best compromise between output ripple at high load and loop-transient response.

Despite the circuit's complex dynamics, its transient response is quite good. Further, its high-power efficiency is similar to standard switchers; low-power effi-

ciency is somewhat better—although poor in the lowest ranges. The poor efficiency is not particularly bothersome, because power loss is very small.

The loop provides a controlled, conditional instability instead of the usually more desirable (and often elusive) unconditional stability. This deliberately introduced instability dramatically lowers switcher quiescent current without sacrificing high-power performance.

EDN

References

1. Williams, J, "Switching Regulators for Poets," Linear Technology Corp, AN-25.
2. Williams, J, and B Huffman, "Some Thoughts on DC-DC Converters," Linear Technology Corp, AN-29.
3. Williams, J, "High Efficiency Linear Regulators," Linear Technology Corp, AN-32.
4. Williams, J, "Applications of New Precision Op Amps," Linear Technology Corp, AN-6.
5. Williams, J, "Power Conditioning for Batteries," Linear Technology Corp, AN-8.
6. Pressman, A I, *Switching and Linear Power Supply, Power Converter Design*, Hayden Book, Co, Hasbrouck Heights, NJ, 1977.
7. Chryssis, G, *High Frequency Switching Power Supplies, Theory and Design*, McGraw-Hill, New York, NY, 1984.

Author's biography

Jim Williams, staff scientist at Linear Technology Corp (Milpitas, CA), specializes in analog-circuit and instrumentation design. He has served in similar capacities at National Semiconductor, Arthur D Little, and the Instrumentation Development Lab at the Massachusetts Institute of Technology. A former student of psychology at Wayne State University (Detroit, MI), Jim enjoys art, collecting antique scientific instruments, and restoring old Tektronix oscilloscopes.



Article Interest Quotient (Circle One)
High 491 Medium 492 Low 493

Now that we've been properly introduced,

Intel To Show 2-Mb, 4-Mb EPROMs

By David Roman

TOKYO — Intel Corp. chairman Gordon Moore will introduce his company's highest-density EPROMs at a press conference here tomorrow.

Intel executives are flying to Tokyo to take the wraps off two 2-megabit EPROMs and one 4-Mbit EPROM to demonstrate the company's commitment to the Japanese market.

Though Intel is the world's leading producer of EPROMs, the company owns less than 5% of Japan's EPROM market, said Tom Price, marketing manager of Intel's Programmable Memory Operation.

Intel owned 18% of the world's \$1.8 billion EPROM market in 1988, according to Dataquest Inc.

The Japanese market has been quick to pick up high-density EPROMs, Price said, and Intel is hoping to enter some market at its 128-Kbit, which is

× 8 (2-Mbit) part; and a 4-Mbit EPROM organized as 256-K × 16, which will be in production in August.

Moore said these chips could reduce the number of memory chips in a system up to 75% while facilitating the design of more-compact systems.

Fujitsu Ltd., NEC Corp. and Toshiba Corp. are the only manufacturers shipping either 2- or 4-Mbit EPROMs, according to Dataquest industry analyst Mary Olsson.

Though Japanese suppliers made their public announcements of 2- and 4-Mbit EPROMs before Intel did, Price said Intel is determined to ramp very quickly to volume production.

Intel's swift ramp-up of its 2- and 4-Mbit EPROMs will bring selling prices down quickly in terms of cost per bit. Parts will



Intel's Moore: In Japan to show off his company's densest EPROMs.

The Intel parts are all produced with the same 1-micron CHMOS process Intel uses to build its 80386 microprocessors.

ration costs \$55 apiece; the 256-K × 8 configuration costs \$55 apiece in 10,000-piece quantities. Faster, 150-ns versions of all the new EPROMs will be for about 25% more.

The byte-wide (256-K) part comes in a 32-pin package while the 16-bit (256-K) comes in 40-pin and 32-pin and 40-pin packages. The same ones as the 1-Mbit EPROMs, but with word widths of 16 bits for future EPROMs.

Intel's surf-

NEWS JAPAN

BIOS ソフトをストアするパソコンのシステムに最適したメモリだ。

もう 1 種類の 2 M EPROM (256K × 8) 27C020 は、高性能超

み込み制御システムなどに最適に、複雑なプログラムや大量の

コード記憶に多数の EPROM を使用するシステムでの利用が

考えられる。いずれもサンプル

出荷は始まっているが、量産に

入るのは今年 9 月から。

インテルでは今後、メモリビ

ジネスとして EPROM とフ

ラッシュメモリを中心にビジ

ネスを展開していくという。最

まで DRAM に注

Intel erweitert EPROM-Spektrum nach oben

2- und 4-Mbit-EPROMs in 1,0-µm-CMOS-Technologie


Ein 4-Megabit-Typus und zwei Architektur-Varianten des 2-Megabit-Typs hat Intel vorgestellt. Die neuen Speicherbauelemente werden in 1-µm-CHMOS-III-E Technologie gefertigt und haben Zugriffszeiten zwischen 150 und 200 ns. Die bereits in Mustern verfügbaren Bausteine, deren Massenproduktion im August anläuft, sind auch im PLCC-Gehäuse erhältlich.

Das EPROM 27C240 ist ein nichtflüchtiger Speicher mit einer Kapazität von 4 Mbit, organisiert zu 256K × 16 bit, und mit 150 oder 200 ns Zugriffszeit verfügbar. Es hat ein 40-poliges Keramik-DIP-Gehäuse nach JEDEC-Standard und ist aufwärtskompatibel zu Intels 1-Megabit-EPROM 27C210 im 40-poligen DIP. Um den unterschiedlichen Systemanforderungen entgegenzukommen, bietet Intel auf der 2-Megabit-Ebene zwei Architekturen an. Das EPROM 27C220 ist zu 128K × 16 bit organisiert und bietet mit seinem 40-poligen Keramik-DIP ebenfalls eine direkte Nachrüstmöglichkeit vom 1-Mbit-Typ 27C210.

Diese Architektur ermöglicht den wirtschaftlichsten und kompaktesten Platinenentwurf für Systeme wie etwa Personalcomputer, die lediglich ein oder zwei EPROMs zum Speichern von Boot-Code oder BIOS Software benötigen.

Das 2-Mbit-EPROM 27C020 ist organisiert zu 256K × 8 bit und untergebracht im 32-poligen DIP, eignet sich optimal für leistungsstarke Mikroprozessor-Schaltungen mit zahlreichen Speicherbanken angeordneten EPROMs, die komplexe Datenprogramme oder grosse Datenmengen speichern. Typische

take me home.

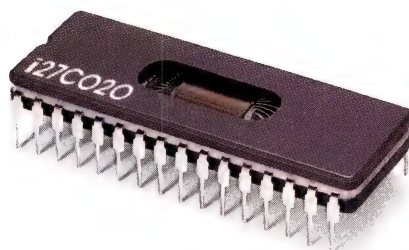

Recently, we announced our commitment to 2- and 4-Mbit EPROMs. And now, we're shipping our 2-Mbit EPROMs in volume. With our 4-Mbit EPROMs right behind them.

But, this high-speed ramp should hardly come as a surprise. After all, we invented the EPROM and have always been the volume leader.

And we've produced this latest generation with the same proven 1-micron CHMOS* III process as our 1-Mbit EPROMs. So we can deliver 2-Mbit production quantities in no time at all.

As you can see from the chart, we're the EPROM source you've been looking for. Only Intel gives you the widest range of densities, from 16K to 4-Mbit. And that's just the beginning. We also let you choose byte-wide or word-wide architectures. PLCC or Cerdip packaging. And a range of speeds, from 120 ns to 200 ns.

But whichever Intel EPROM you choose, the benefits are obvious. Using one 2-Mbit instead of eight 256K EPROMs, for example, results in reduced board space, increased system reliability and

*CHMOS is a patented process of Intel Corp.

overall lower system cost.

Our 1- and 2-Mbit EPROMs are available today in whatever quantity you need. More importantly, our 1-Mbits are your most cost-effective solution now, fol-

lowed by our 2-Mbits in 1990. Or you can design in our 4-Mbit EPROMs today. They'll be available in full volume and

Available in Volume	Product	Organization	Pins	Package
1-Mbit	27C010	128K \times 8	32	CERDIP
	27C010	128K \times 8	32	PLCC
	27C210	64K \times 16	40	CERDIP
	27C210	64K \times 16	44	PLCC
2-Mbit	27C020	256K \times 8	32	CERDIP
	27C220	128K \times 16	40	CERDIP
4-Mbit	27C240	256K \times 16	40	CERAMIC

in a full range of configurations for your next generation of products.

For technical and product line details call (800)548-4725, Lit. Dept. #GA18. But please call soon. Because


we've already been introduced. And now we're ready for a serious relationship.

intel[®]

AUGAT VME...



Any slot... Any

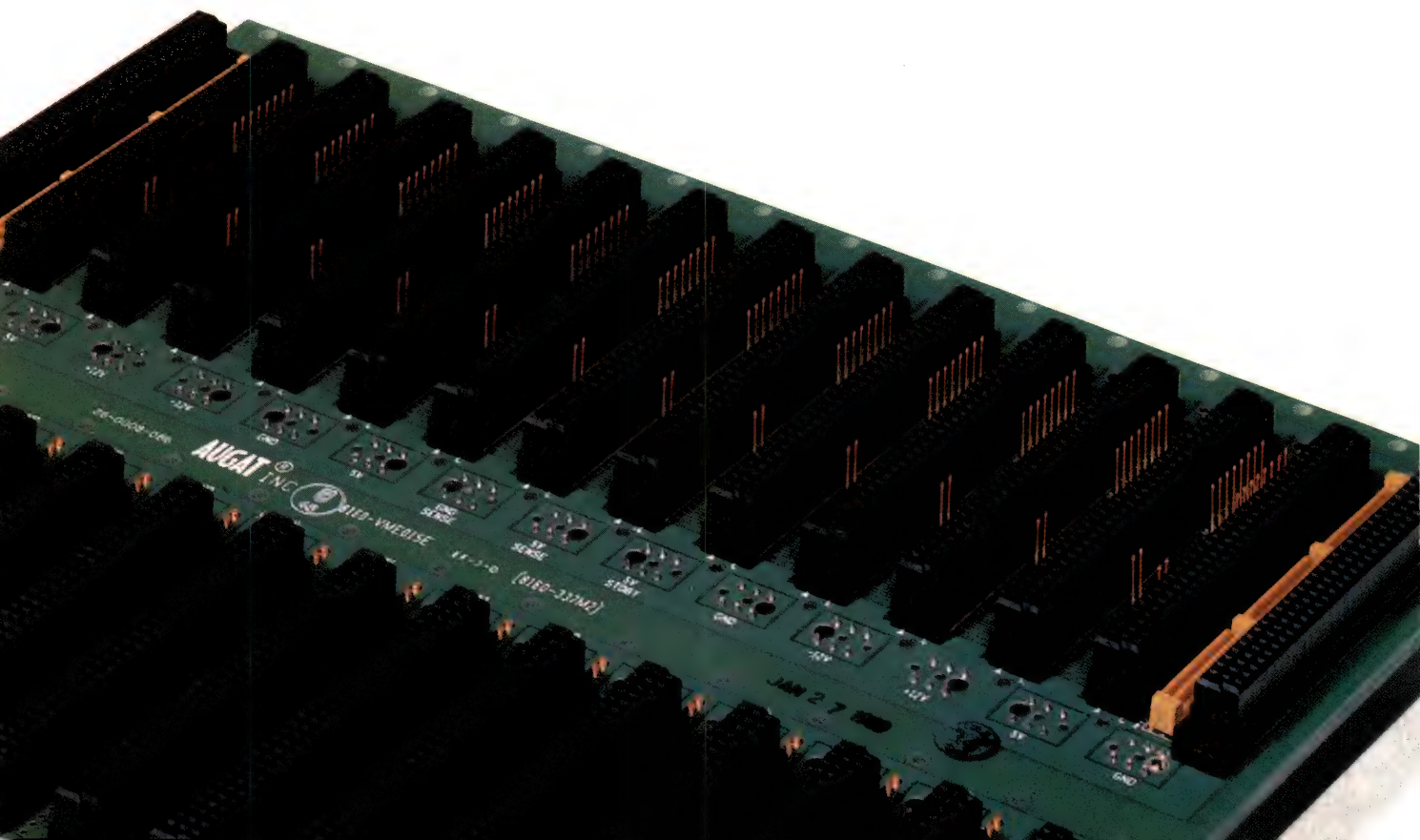



size... 7 days*

Now, within just 7 working days, AUGAT will ship you a backplane or card cage in any size you need, from 3 through 21 slots. This isn't simply a promise — it's AUGAT's GUARANTEE*...

Or you pay 20% less!

Our no-nonsense 7-Day VME Program includes both J1 and J2 backplanes. It even includes our new high-performance monolithic backplanes, too. Only AUGAT has the production capability to guarantee 7-day shipment on such a broad selection of backplanes. Now you can plan on the arrival of your VME packaging hardware with no fear of delaying your critical development schedule.

In addition, AUGAT has greatly expanded its entire VME line to include more

standard products ... including new VME power chassis complete with backplane, fully harnessed power supply, cooling, card cage and optional enclosure. AUGAT also has the engineering talent and experience to handle your customized VME packaging needs.

Send for a copy of our new VME catalog today ... because when time is of the essence in locating quality VME products with full engineering support, your surest source is AUGAT!

* AUGAT GUARANTEES to ship backplanes and/or card cage kits in any size (from 3 through 21 slots) in 7 working days from date of approved credit — or you pay 20% less! (limit: 3 pieces per part number)

***PLUS
An Expanded
VME
Product Line***

***NEW
Power Chassis***

***More
Power
Supplies***

***More
Extender
Boards***

***More
Wire-Wrap†
Panels***

***More
Cage Dividers***

***More
Support Data***

For answers or orders


1-800-999-9VME




AUGAT INC., INTERCONNECTION PRODUCTS GROUP

†Wire-Wrap is a registered trademark of Gardner-Denver


It's not just the way we It's the way we

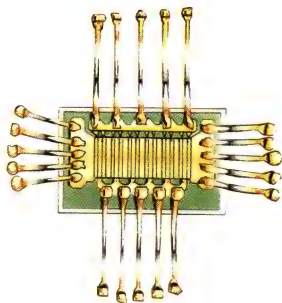

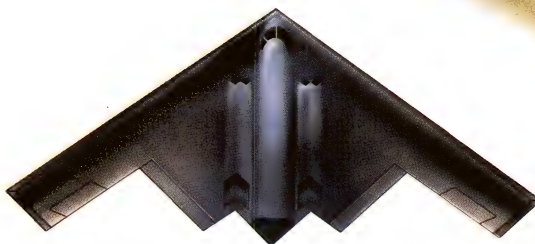The Harris Military and Aerospace Division is dedicated to bringing the military the highest in high technology. From submicron CMOS to GaAs, from digital to analog ASICs. And we bring high technology down to earth by making your visions of the future become reality. Fast.



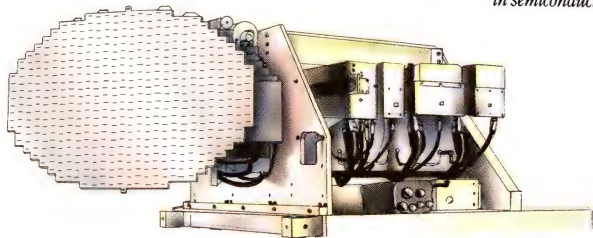
While VHSIC performance is still just a vision at some companies, the Harris Research Triangle Park facility (RTP) has already shipped over 150,000 Class B and Class S processed VHSIC-class devices. No wonder Harris is first in semiconductors for military and aerospace.



Harris products from RTP were right on target for the F-16 Fire Control Radar project. And that's just one of the 30 military and aerospace projects in which products from RTP are already at work.



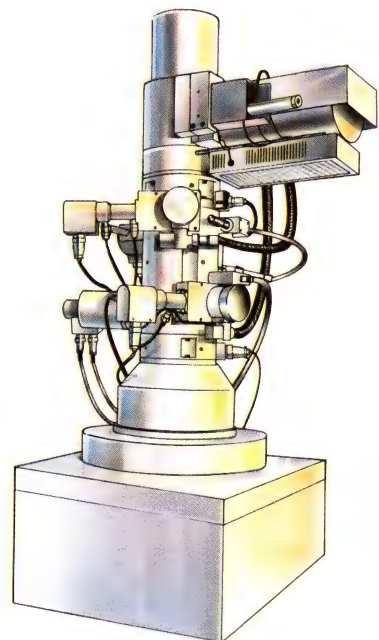
The Q stands for quality. Harris RTP facility participated in the government's QML alpha site program, helping define the way ICs will be qualified in the future. We have been selected to be a beta site, and building on this, we're now qualifying for QML approval status.



With gate arrays, standard cells and compiled designs—in your choice of CMOS/bulk, CMOS/SOS and SOI—the range of Harris' radiation-hardened ASIC capabilities is unparalleled. We even offer E-beam direct write technology. No wonder Harris is the #1 supplier of ASICs to the U.S. military.



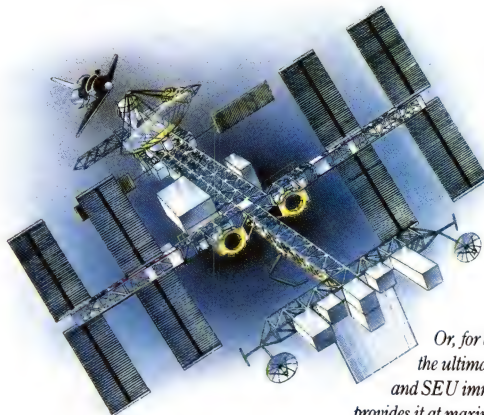Take your pick. Harris has a process technology designed to give you the price/performance your design demands. Select our VHSIC-class CMOS process for high-speed performance, or a radiation-hardened version for upgraded tactical military applications.




Or, for applications requiring the ultimate in total dose radiation hardness and SEU immunity, our CMOS/SOS process provides it at maximum performance.

From submicron CMOS to GaAs, smart power to digital and analog ASICs, Harris brings you the highest in high technology. And we bring it down to earth through a complete division dedicated to turning the visions of military and aerospace designers into realities.

*Gensil and GDT are trademarks of Silicon Compiler Systems. DAZIX is a trademark of Daisy/Cadnetix, Inc. Mentor Graphics is a registered trademark of Mentor Graphics Corporation.


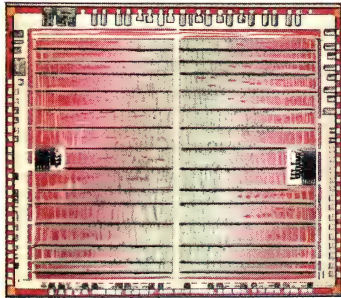
Bring you high technology. Bring it down to earth.



*Fast.
Fast.
Fast.
Harris gate
arrays give you
cost-effective
performance*

with fast design cycles. CMOS/SOS and CMOS/bulk arrays are available now. 100,000 gates are on the way. And standard cells to 25,000 gates, including the RTX microcontroller, are also available.

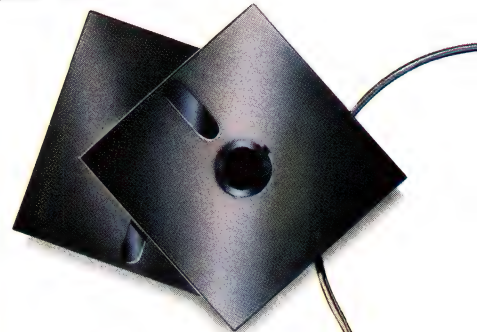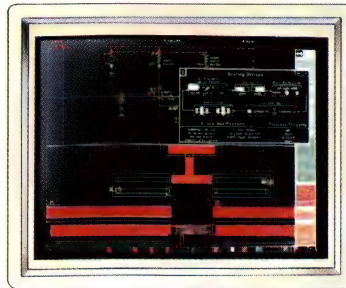
*Visions of the future
quickly become reality with Harris'
comprehensive design libraries.
We support all the popular workstations, including
DAZIX*, Mentor Graphics* and Harris' own
FASTRACK™ integrated workstation.*





*Harris' support
of Silicon Compiler System's Gensil*
and GDT* programs let you create
the most complex IC designs simply
and easily. And we're a qualified lab for
Silicon Compiler Systems.*

*Whatever ASIC technology you select, Harris can deliver on time and
on budget. We're fully approved to design, manufacture and
test to MIL-STD-883C and Class S.*

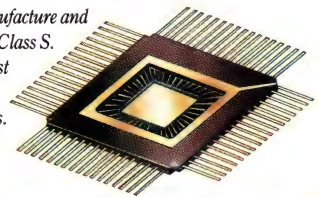
*With assembly and test
capabilities for up
to 288 pins.*



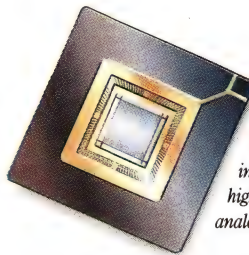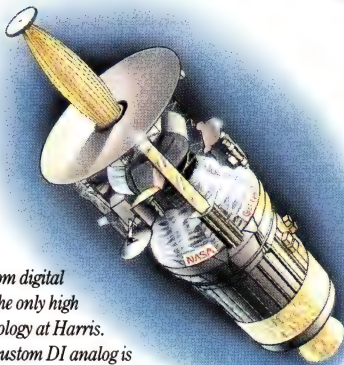
*Custom digital
isn't the only high
technology at Harris.
Our custom DI analog is
the ultimate in high performance
for analog design, including high-speed
op amps with slew rates to 1000 μ V/sec.*



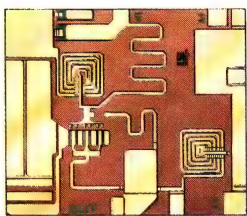*Harris smart power is
the perfect synthesis of power and
intelligence. Combining high voltage and
high power with dense logic and precision
analog on a single chip.*



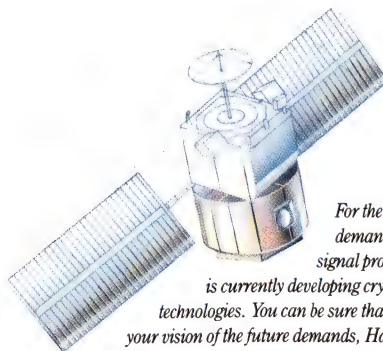*That dream technology,
GaAs, is more than a dream at Harris.
We're already in production with 0.5 and 1.0 micron
processes, with 0.25 micron on the way. And
we're a MIMIC program participant.*



*For the extreme
demands of focal plane
signal processing, Harris
is currently developing cryogenic rad-hard
technologies. You can be sure that whatever
your vision of the future demands, Harris is
probably working on it today.*



*For more information
on the latest in high technology at Harris,
call 1-800-4-HARRIS, ext. 1003
(in Canada, 1-800-344-2444, ext. 1003).*

It's the kind of dedication to your unique needs that has made Harris the #1 supplier of semiconductors in military and aerospace. Harris Semiconductor. What your vision of the future demands. Today.

 **HARRIS**
SEMICONDUCTOR
HARRIS • RCA • GE • INTERSIL

Now, One Name Gets You Thousands Of Choices In Components And Materials.

Philips Components Discrete Products Division

The products of Amperex, Mepco/Centralab, and Ferroxcube are now available from one source — Philips Components.

The names have changed, but the industry leadership hasn't.

We still offer superior product quality and performance. On time delivery. Professional service. And competitive prices.

But now it's all backed by one of the world's largest electronic components manufacturers, N.V. Philips. With worldwide resources.

You'll benefit from our leadership across all our product groups. And you'll move ahead because of our innovations in surface mount technology.

In Passives: aluminum electrolytic, ceramic, film, variable, and tantalum capacitors. Resistor products include: fixed resistors, varistors, thermistors, sensors, and cermet trimmers. And we're the only tantalum capacitor manufacturer to be certified a Class "A" MRP II user.

In Discrete Semiconductors: vast

Philips Components



selections of
small signal prod-
ucts, power devices,
and optoelectronic products.

In Professional Components:
camera tubes, CCD image sensors, UHF
Klystrons, and much more.

In Materials: a broad range of ferrite cores
for power supply and telecommunications
equipment (pots, U E and I cores, and toroids).
Plus beads, chokes and rods for EMI/RFI

suppression.

For all this and more, call
or write to the broad range
product source for solutions: Philips
Components Discrete Products Division.


Philips Components
Discrete Products Division **1-800-447-3762**
A North American Philips Company Fax: 407-881-3300
2001 W. Blue Heron Boulevard
P.O. Box 10330
Riviera Beach, FL 33404

More Products. More Solutions.



PHILIPS

NEW GENERATION OF LOGIC CAPTURE SOFTWARE

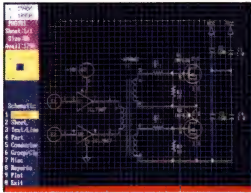


A New Generation of Logic Capture, PADS-LOGIC, is now available from CAD Software, Inc. PADS-LOGIC has a true multi-sheet, design oriented database which provides a very

high level of performance for Electronic Engineers. Some of the systems features include: Automatic Reference Designations, Automatic Gating, powerful Macro Commands, interfaces to Logic Simulation, Circuit Analysis, and most CAD systems. Large circuit (250 sheets), and 100 layer level Hierarchical capability, enables the Logic Capturing of any size design. An Engineering Change Order (ECO) feature forwards changes made to the schematic to automatically update the PCB design; changes in the board layout, including Automatic Gate and Pin Swapping, and Component Renaming, are automatically backward incorporated to the original schematic.

A security key is not required. The software cost is \$450.00.

Contact CAD Software, Inc., Littleton, MA
Inside MA: (508) 486-8929 or Outside MA: (800) 255-7814

PC-BASED ELECTRONIC DESIGN VERIFICATION

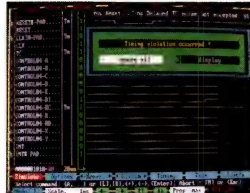


Engineers can verify their designs, and reduce Hardware breadboarding, through the use of CAD Software, Inc.'s, Logic Simulation and Circuit Analysis Programs.

PADS-SUSIE, is a Digital Simulator with Timing, Functional & Glitch Mode verification modes. Simulation passes can be made at either this Board Level, or the Hierarchical Level.

PADS CIRCUIT ANALYSIS, for Analog Circuit Analysis, is based upon Microsim Corporation's highly successful version P-Spice, and includes a tightly coupled Analog and Digital Mixed Mode Simulator.

Contact CAD Software, Inc., Littleton, MA
Inside MA: (508) 486-8929 or Outside MA: (800) 255-7814

PADS-PCB VERSION 3.13 NOW SHIPPING

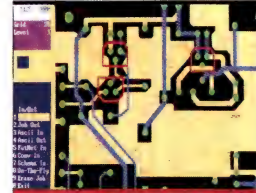


Version 3.13 of PADS-PCB, the highly popular PCB CAD System, is now being shipped. The Personal Computer-Based PADS-PCB System has a Very Large Board, (450 Equivalent per ICs) Capability, with up to 30 layers. All technologies, including Digital, Analog, Multilayer and SMT, are supported. Both Automatic & Interactive Placement and Routing Algorithms are available. Automatic Design Rules Checking is included. (\$975.00)

Contact CAD Software, Inc., Littleton, MA
Inside MA: (508) 486-8929 or Outside MA: (800) 255-7814

30 Day Money Back Guarantee on all software!

PADS-THERMAL SOFTWARE

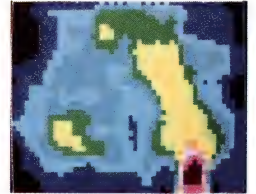

A Printed Circuit Board Thermal Analysis software package is available from CAD Software of Littleton, MA. This software, (PADS-THERMAL), is used to evaluate the Thermal effects on a board, while operating in various packaging environments, including closed containers with variable airflows, open containers, components on top and bottom layer of boards, and other constraints.

A unique feature allows the relocation of the Parts on the board, in order that different locations of heat generating parts can be evaluated.

Contact CAD Software, Inc., Littleton, MA, Inside MA: (508) 486-8929 or
Outside MA: (800) 255-7814

POWERFUL SUITE OF AUTOROUTES NOW AVAILABLE

An extremely Powerful suite of autorouters that addresses every conceivable Design Technology, is now available from CAD Software, Inc..

The PADS-SUPERROUTER, an intelligent Ripup and Reroute Autorouter, is available for those Digital Circuit Designers wanting autorouter performance that is equal, or better than the currently available autorouters on workstations, yet at a very modest price. PADS-SUPERROUTER is a costed Lee's Maze Search Algorithm, that operates in Ripup and Reroute Batch operations, ripping up blocking tracks and rerouting until the board is 100% complete. (\$4,500.00)

PADS-PUSH N' SHOVE (New), has been configured for those Engineers and Designers that have critical circuits on their boards, such as high speed circuits, ECL, Bus lines, or Analog Boards, where the designer wants precise control over the track position, yet wants the power of an autorouter to quickly route the connections. (\$1,495.00)

CAD SOFTWARE LEASING

CAD Software, Inc., brings the leasing of SOFTWARE ONLY, to its customers. Traditionally, leasing firms do not lease software only, but require a minimum of 50%-60% of the lease value to be made up of the hardware component. CAD Software, Inc.'s, software ONLY leasing plan, changes this requirement.

With CAD Software, Inc.'s Leasing Plan, a firm can have a high-performance PADS CAE & CAD System for only \$400 - \$500 per month, on an Annual Lease Basis.

Contact CAD Software, Inc., Littleton, MA, Inside MA: (508) 486-8929 or
Outside MA: (800) 255-7814

Finally . . . “An Affordable, Integrated, Single Source CAE/CAD System For Every Electronic Engineer”

CAD
Software, Inc.

SEE US AT WESCON BOOTH #1344

CIRCLE NO. 91

the developers of PADS-PCB

119 Russell Street, Suite #6, Littleton, MA 01460
Inside MA: (508) 486-8929 or Outside MA: (800) 255-7814

DESIGN IDEAS

EDITED BY CHARLES H SMALL

Program plots transformer response

Hugh M Adams, PE
Rtronics Inc, Pensacola, FL

The HP Basic program in **Listing 1** plots the leading edge of the step response of a high-voltage transformer after you input all of its known, or measurable, parameters. **Fig 1** shows a high-voltage transformer's equivalent circuit with all elements referred to the secondary side. This program helps you quickly evaluate the effects that the many different, specialized winding techniques employed in high-voltage transformers will have on your design.

EDN

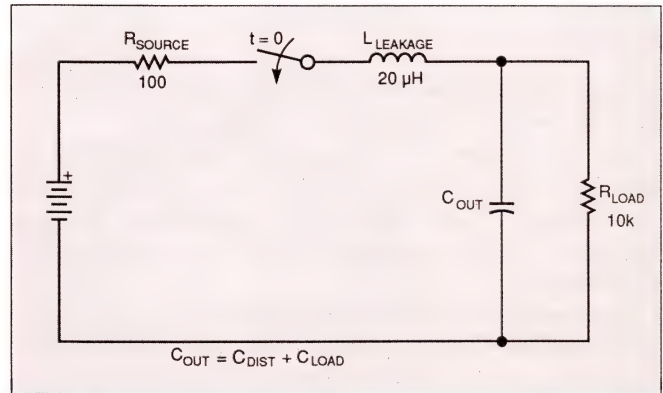


Fig 1—This simple model, embodied in the program in **Listing 1**, incorporates the known and measurable parameters of a high-voltage transformer.

To Vote For This Design, Circle No. 746

Listing 1—HP Basic, high-voltage-transformer step-response program

```
10 GCLEAR
20 CLEAR
30 DISP "PLOT OF STEP RESPONSE OF HV TRANSFORMER"
40 DISP "ENTER R1,R2,L(UH),C(PF)";
50 INPUT R1,R2,L,C
60 L=L*.000001 @ C=C*.0000000000001
70 D=(C*R1+L/R2)*(L*C)^-.5*(1+R1/R2)^-1.5
80 D=D/2 @ D=INT (1000*D)/1000
90 DISP "DELTA =" ;D
100 RAD
110 P=0
120 W1=(L*C)^-.5*(1+R1/R2)^-.5
130 DISP "RING FREQUENCY=" ;INT (W1/2*PI ); " HZ"
140 DISP @ DISP @ DISP "PRESS 'CONT' TO SEE PLOT"
150 PAUSE
160 LOCATE 25,150,25,80
170 SCALE 0,.00001,0,2
180 FXD 1,1
190 LAXES .000001,.5,0,0,1,.5
200 FOR T=0 TO .00001 STEP .00000005
210 V=(1+(1-D^2)^-.5*EXP (- (D*W1*T))*SIN (W1*(1-D^2)^.5*T-P))*(R2/(R1+R2))
220 PLOT T,V
230 NEXT T
240 MOVE .0000005,2.3
250 LABEL "R1/R2=" ;R1/R2 ; "R1=" ;R1 ; "L/C=" ;L/C ; "C=" ;C*1.E12 ; "PF"
260 MOVE .0000005,2.1
270 LABEL "DELTA=" ;D ; "FREQ=" ;INT (W1/2*PI ); " HZ"
280 MOVE .000004,-.85
290 LABEL "TIME"
300 END
```


PLD expands arbiter chip

Ted Burton and Charlie Dike
Signetics, Orem, UT

If you expand the 74F786 high-speed, 4-input bus arbiter using the chip's built-in, independent, 4-input AND gate (Fig 1a), the resulting solution will be seriously flawed. Any activity on bus-request lines A through D can block bus requests on lines E through G. The circuit in Fig 1b overcomes this deficiency.

You can generalize Fig 1b's scheme to accommodate any number of inputs if your expanded circuit follows two rules. First, any two bus-request lines must connect to at least one arbiter chip. Second, the PLD must assert the proper bus-grant line for any possible combination of valid inputs from the arbiter chips.

The PLD must recognize two possible classes of valid inputs. Obviously, if a given input to the arbiter chips wins *all* of its arbitration contests taking place in all the chips to which it's applied, the PLD must grant that input's bus request (the $\overline{A_1A_2}$ term in Listing 1 for $\overline{BG_A}$'s equation, for example). In addition, you must program the PLD to grant only one bus request

arbitrarily when two or more bus-request lines win some—but not all—of their respective arbitration contests (for example, the remaining minterms in the $\overline{BG_A}$ equation). **EDN**

To Vote For This Design, Circle No. 747

Listing 1—Arbitration-PLD equations

$$\begin{aligned}\overline{BGA} &= \overline{A_1A_2} + \overline{A_1B_2} + \overline{C_1A_2E_3} + \overline{C_1A_2F_3} \\ \overline{BGB} &= \overline{B_1B_2} + \overline{B_1A_2} + \overline{C_1B_2E_3} + \overline{C_1B_2F_3} + \overline{D_1B_2E_3} + \overline{D_1B_2F_3} \\ \overline{BGC} &= \overline{C_1C_3} + \overline{C_1D_3} + \overline{B_1E_2C_3} + \overline{B_1F_2C_3} \\ \overline{BGD} &= \overline{D_1D_3} + \overline{D_1C_3} + \overline{D_1A_2E_3} + \overline{D_1A_2F_3} + \overline{B_1E_2D_3} + \overline{B_1F_2D_3} \\ \overline{BGE} &= \overline{E_2E_3} + \overline{E_2F_3} + \overline{A_1E_2C_3} + \overline{A_1E_2D_3} \\ \overline{BGF} &= \overline{F_2F_3} + \overline{F_2E_3} + \overline{A_1F_2C_3} + \overline{A_1F_2D_3}\end{aligned}$$

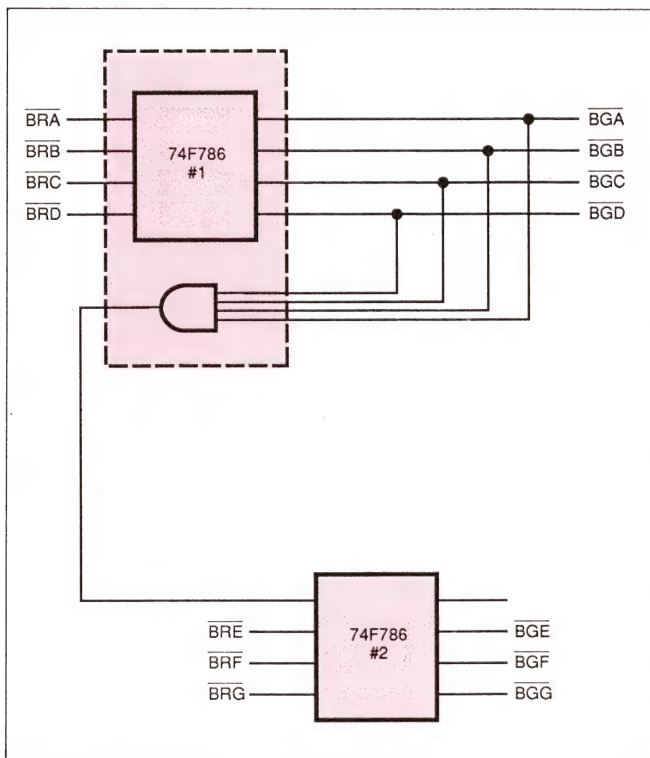


Fig 1a—Using the 74F786's built-in AND gate to expand the number of bus-request lines beyond four isn't a perfect solution.

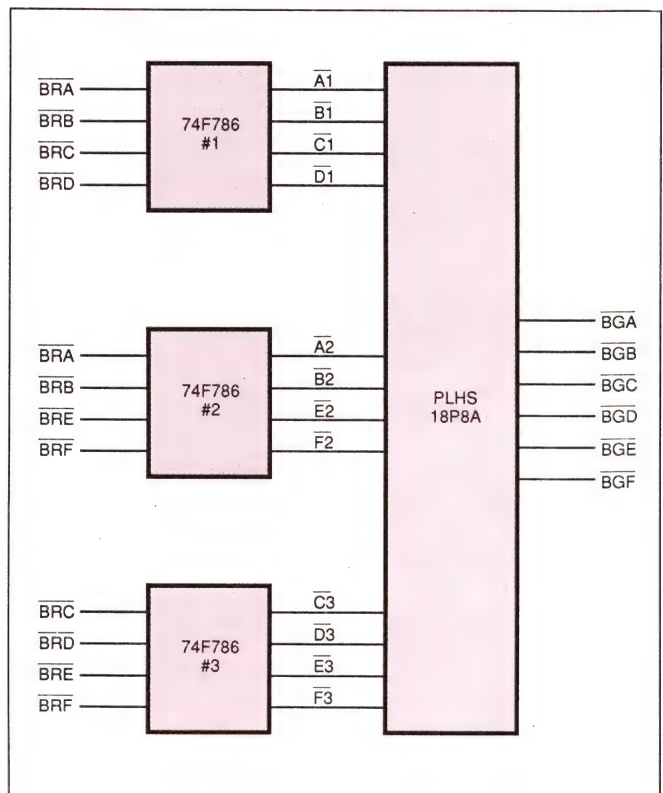


Fig 1b—By skillfully grouping the bus-request lines at a parallel array of bus-arbitration chips and using a PLD to perform a secondary arbitration, you can retain the 74F786's excellent metastability characteristics and still serve all inputs in order of arrival.

SURFACE MOUNT MIXERS



\$3.30
(1,000 qty)

The opportunity for automated, low-cost assembly is a key benefit of surface-mount technology, but is often wiped out by the high price of surface-mount components. Now, Mini-Circuits offers a new series of mixers to meet the pricing demands of SMT...only \$3.30 in 1,000 quantity (\$3.95 ea. in quantity of 10)...at a cost even lower than most conventionally-packaged mixers.

The SCM-1 spans 1 to 500MHz and the SCM-2 covers 10 to 1,000MHz. Housed in a rugged, non-hermetic 0.4 by 0.8 by 0.3 in. high (maximum dimensions) plastic/ceramic package. Spacing between connections is 0.2 in. The mixer is offered with leads (SCM-L) or without leads (SCM-NL) to meet a wide range of pc board mounting configurations.

Each SCM is built to meet severe environmental stresses including mechanical shock/vibration as well as temperature shock. The operating and temperature storage range is -55°C to +100°C. Each SCM, designed and built to meet today's demanding reliability requirements, carries Mini-Circuits' exclusive 0.1% AQL guarantee of no rejects on every order shipped (up to 1,000 pieces).

When you think SMT for low-cost production, think of Mini-Circuits' low-cost SCM mixers.

finding new ways...
setting higher standards

Mini-Circuits

A Division of Scientific Components Corporation
P.O. Box 350166, Brooklyn, New York 11235-0003 (718) 934-4500
Fax (718) 332-4661 Domestic and International Telexes: 6852844 or 620156

SPECIFICATIONS (typical)	SCM-1L SCM-1NL (L=with leads)	SCM-2L SCM-2NL (NL=no leads)
FREQ. RANGE (MHz)		
LO,RF	1-500	10-1000
IF	DC-500	5-500
CONVERSION LOSS (dB)		
Midband	6.3 dB	6.5 dB
Total Range	7.5 dB	8.0 dB
ISOLATION (dB)	(L-R)(L-I)	(L-R)(L-I)
Low-Band	60 45	45 35
Mid-Band	45 40	35 30
High-Band	40 35	25 20
PRICE	\$3.30 (1000 qty) \$4.25 (1-9)	\$4.15 (1000 qty) \$5.45 (1-9)

Units are shipped in anti-static plastic "tubes" or "sticks" for automatic insertion.

*NOTE: L & NL suffix for ordering only
Not marked on units

Routines give Quick Basic huge arrays

Steven B Leeland

Fairchild Data Corp, Scottsdale, AZ

The Quick Basic subroutine and function in **Listing 1** lets your programs read and write to a large array. Normally, Quick Basic's dynamic arrays can be no larger than 16k, 4-byte elements. The subroutine WriteLarge writes array elements; LargeArray reads

them. You refer to elements as if they were normal subscripted variables. The main program is a simple test that verifies the unique existence of every array element. **EDN**

To Vote For This Design, Circle No. 748

Listing 1—Quick Basic large-array routines

```
DECLARE SUB WriteLarge (address, value)
DECLARE FUNCTION LargeArray (address)

MaxLength = 16383           'Maximal Length Dynamic Arrays
DIM LargeArray1(MaxLength)  '(Outside DGroup)
DIM LargeArray2(MaxLength)
DIM LargeArray3(MaxLength)
DIM LargeArray4(MaxLength)

CLS

FOR address = 0 TO 65535     'Large Array Convergence Test
    WriteLarge address, address 'Fill Array with Addresses
    LOCATE 8, 20
    PRINT "Filling array element: "; address;
NEXT

FOR address = 0 TO 65535     'Test Results
    IF address = LargeArray(address) THEN
        LOCATE 16, 20
        PRINT "Testing array element: "; address;
    ELSE
        LOCATE 23, 20
        PRINT "Error at "; address; " = "; LargeArray(address);
    END IF
NEXT

END

FUNCTION LargeArray (address)
    SHARED LargeArray1(), LargeArray2(), LargeArray3(), LargeArray4()
    IF address < 16384 THEN
        LargeArray = LargeArray1(address)
    ELSEIF address < 32768 THEN
        LargeArray = LargeArray2(address - 16384)
    ELSEIF address < 49152 THEN
        LargeArray = LargeArray3(address - 32768)
    ELSE
        LargeArray = LargeArray4(address - 49152)
    END IF
END FUNCTION

SUB WriteLarge (address, value)
    SHARED LargeArray1(), LargeArray2(), LargeArray3(), LargeArray4()
    IF address < 16384 THEN
        LargeArray1(address) = value
    ELSEIF address < 32768 THEN
        LargeArray2(address - 16384) = value
    ELSEIF address < 49152 THEN
        LargeArray3(address - 32768) = value
    ELSE
        LargeArray4(address - 49152) = value
    END IF
END SUB
```


RS232 Transceiver with Automatic Power Shutdown Control


Sean Gold

The LT1180/81 RS232 transceivers with on-chip charge pumps offer some unique features that greatly enhance serial interface performance. Like the LT1080 and LT1130 series transceivers, the LT1180 is fully compliant with all RS232 specifications. The LT1180 is unique since it utilizes a charge pump which oscillates at 150kHz to 200kHz — about twice the frequency of the standard transceivers. In addition to providing excellent current delivery capability, the high speed charge pump can operate with storage capacitors as small as 0.1μF.

Reducing storage capacitor size to 0.1μF shrinks board space, thereby lowering production costs. Small capacitors also shorten the transceiver turn-on time to less than 200μs, which makes the LT1180 ideal for applications which must address the RS232 transceiver quickly. The interface de-

scribed here takes advantage of fast turn-on to reduce power dissipation.

The circuit shown in Figure 1 automatically shuts down when there is no data flow through the interface. A data stream on either the RS232 or logic inputs activates the transceiver. The data must begin with a logic 1 preamble, and the data stream must contain a sufficient number of 1's to keep the transceiver active. The preamble may be as short as 50μs. Alternatively, the input to the Automatic SHUTDOWN circuit could be an RS232 handshake signal, such as Data Set Ready (DSR) or Clear to Send (CTS), which remain high during the data transfer. The LT1180's 200μs turn-on delay does not limit the data rate in the transceiver. Once the LT1180 is active, it can process data at the maximum 100k baud data rate.

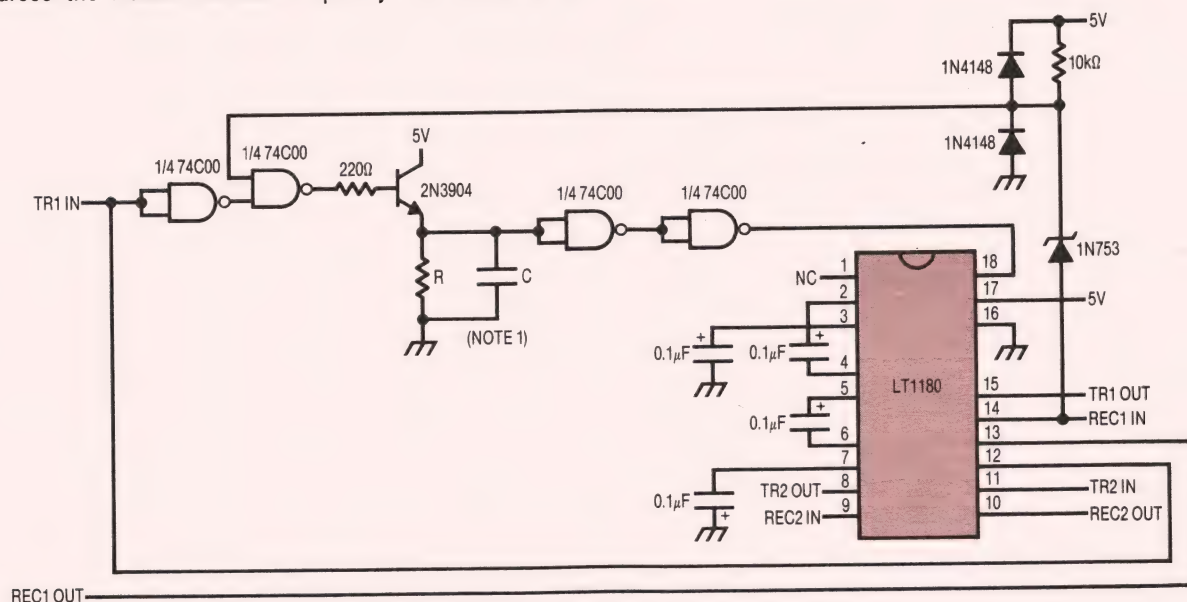

NOTE 1: SELECT RC BASED ON CLOCK SPEED AND REQUIRED DROP OUT TIME.
 $T = RC \approx 2 \cdot T_{\text{DROP OUT}}$. FOR THIS EXAMPLE, $R = 100k\Omega$ AND $C = 1\mu F$.
 C SHOULD NOT EXCEED 1μF UNLESS THE 2N3904 CURRENT LIMITED
 WITH A COLLECTOR RESISTOR.

Figure 1. Fast Turn-On Transceiver with Automatic SHUTDOWN Control

A peak detector senses data flow. The extra CMOS gates are buffers which ensure the time constant is relatively independent of input signal level. The drop out time, i.e. the duration of inactivity prior to SHUTDOWN, is approximately $0.5RC$. More specifically, drop out occurs when the voltage on the peak detector decays from $V_{CC} - 0.7V$ to the logic switch point of $V_{CC}/2$. The RS232 input to the control circuit is clamped to protect the logic inputs. The zener diode, D3, forces the turn-on threshold on the RS232 side to $-3.5V$, which prevents the transceiver from turning on when the cable is grounded.

Figures 2 through 4 demonstrate the automatic SHUTDOWN control's response to logic and RS232 signals, as well as zero data flow. The minimum pulse width is $50\mu s$ and the drop out time is set to 50ms. The power supply outputs — the lower two traces in Figures 2 and 3 — become active in less than $200\mu s$. When active, the circuit consumes 16mA of quiescent current. In SHUTDOWN state, the Q-current drops to $50\mu A$.

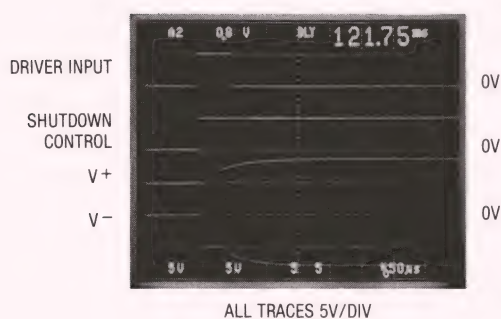


Figure 2. Transceiver Turn-On Via Logic Input

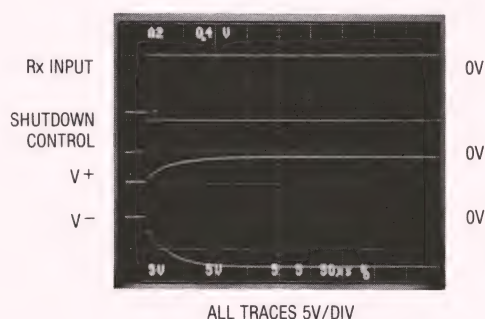


Figure 3. Transceiver Turn-On Via Receiver Input

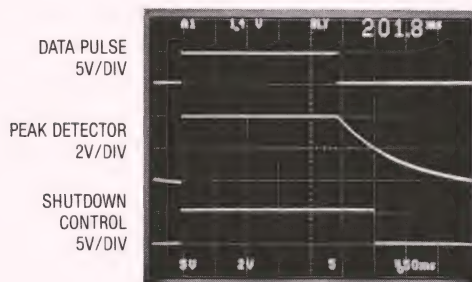


Figure 4. SHUTDOWN After 50ms Without Data Transmission

For literature on our interface products, call (800) 637-5545. For help with an application, call (408) 432-1900, Ext. 445.

EMI SHIELDING AT A FAST CLIP

Meeting FCC/VDE requirements is quick and simple with Chomerics' low-cost clip-on EMI gaskets. Each combines Chomerics quality and technology with labor-saving attachment mechanisms. All are available off-the-shelf.

Five configurations feature our new CHO-SEAL® 1000 series conductive elastomers, priced at a fraction of their military counterparts. They deliver up to 60dB of shielding from 30MHz to 1GHz, even when deflected only 25% under low closure force.

Our METALKLIP™ gaskets offer a choice of wire mesh-over-elastomer, or hollow carbon-filled silicone.

CLIP THIS FOR FREE CLIP SAMPLES.

Clip this to your letterhead. We'll send you samples for evaluation. We make choosing EMI shielding a snap.

FREE: SELECT UP TO THREE

CHO-SEAL® 1000
Gaskets

- ☐ Plastic Clip, Black
- ☐ Plastic Clip, White
- ☐ Steel Clip
- ☐ Stick-On Shield & Seal

☐ Aluminum Frame
Mount

METALKLIP™
Gaskets

- ☐ Mesh-Over-
Elastomer
- ☐ Carbon-Filled
Silicone

Name _____

Job Function _____

Company _____

Dept. _____

Address _____

City _____

State _____ Zip _____

Tel: () _____

Chomerics, Inc.

77 Dragon Court • Woburn, MA 01888-4014

EDN011890

CHO-SEAL® 1000 GASKETS

1&2. Plastic Clip. Streamlined, rigid PVC clip is UL94V-0 rated. Tan or blue elastomer with choice of white or black clip and two grip ranges. Closure force as low as 1 lb/in.

3. Stainless Steel Clip. Series 302/304 SS clip has sharp tines which bite through paint or oxide for electrical contact. Closure force as low as 1 lb/in. Available mitered.


4. Stick-On Shield & Seal. Co-extruded conductive/nonconductive elastomers provide best environmental seal. Permanently mounts with pressure-sensitive adhesive. Closure force as low as 3 lb/in.

5. Aluminum Frame Mount. Positive mechanical mount with screws or pop rivets. Built-in compression stop. Metal-to-metal contact. Ultra low closure force—0.8 lb/in. Available pre-drilled, mitered, and painted.

METALKLIP™ GASKETS

6. Mesh-Over-Elastomer. Choice of monel or Ferrex® wire mesh over sponge or hollow elastomer core. Up to 90dB shielding from 10MHz to 1GHz. Sharp tines in SS clip bite through paint or oxide.

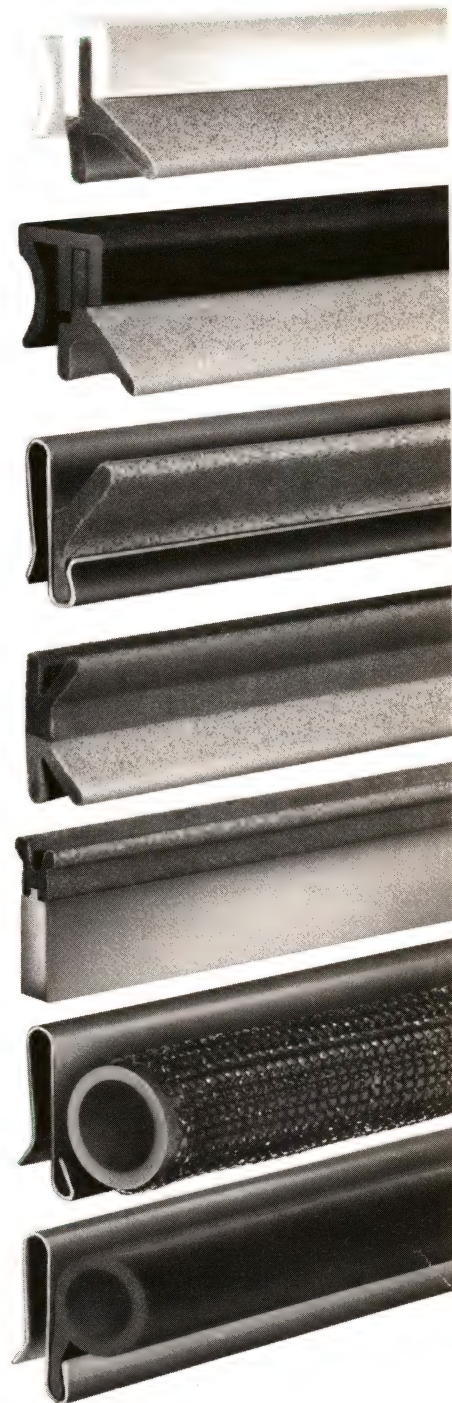7. Carbon-Filled Silicone. UL94V-0 rated hollow gasket in the same series 302/304 SS clip. Lowest cost, for lower shielding requirements with low closure force.



CHOMERICS
a GRACE company

Chomerics, Inc.
77 Dragon Court
Woburn, MA 01888-4014
TEL: 800-225-1936
(In MA: 617-935-4850)
TWX: 710-393-0173

Chomerics (UK) Ltd.
Unit 8, First Avenue
Globe Park Industrial Estate
Marlow, Bucks., SL7 1YA
ENGLAND
Tel: (06284) 6030
Telex: 849817 CHOMER G

Chomerics GmbH
Postfach 320208
Moltkestrasse 32
4000 Dusseldorf 30,
WEST GERMANY
Tel: 0211/488001
Telex: 8589743 CHOM D

Chomerics S.A.
Rue Jacques Brel
Zone Industrielle Les Bellevues
95610 Eragny-sur-Oise
FRANCE
Tel: (1) 30.37.63.30
Telex: 608255F CHOMESA

Resistor isolates grounds

John Dunn

Bertan Associates, Hicksville, NY

System-design mavens insist that you should keep your analog and digital grounds completely separate except for one common point. However, if you're trying to lay out an IEEE-488 device, standard device-interconnection cables can foil your best intentions when their metal shells connect digital ground to your device's chassis; in effect, you'll have a ground loop as soon as you plug a cable into your device (Fig 1).

In this case, your best bet is to use a resistor to connect the two grounds within your device. That way, any appreciable digital-ground currents will flow through the external path in the cable shell. It isn't a good idea to eliminate the 1Ω resistor and use the cable shell as the only ground path. Such a configuration causes a problem if you ever have to operate your device without the cable plugged in.

EDN

To Vote For This Design, Circle No. 749

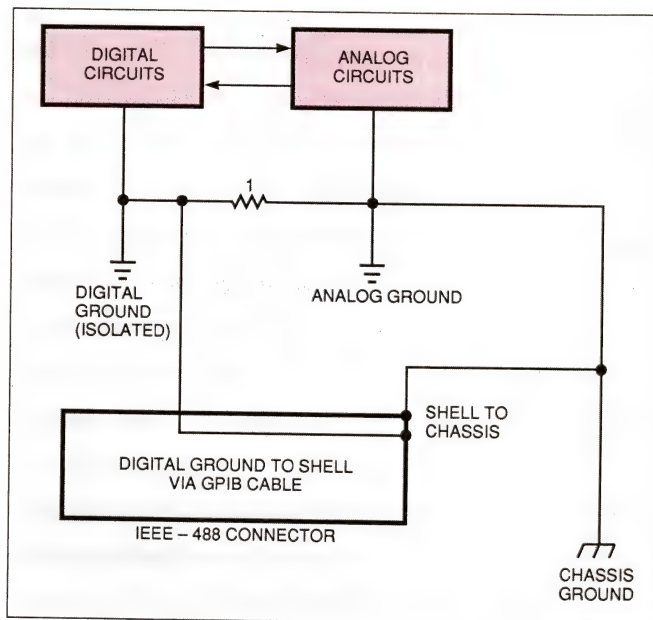


Fig 1—Connecting analog and digital grounds with a 1Ω resistor kills a possible ground loop in IEEE-488 systems whose cables have metal connector shells that connect digital ground to your chassis.

Op amp increases output impedance

Jimmy D Slife

XEL Communications Inc, Aurora, CO

Conventional op-amp circuits provide very low output impedances, but occasionally you may need a higher output impedance. One easy way to get your desired output impedance is simply putting that value resistor in series with the output of the op amp. Unfortunately, this scheme limits the op amp's output range.

For example, putting a 600Ω resistor in series with an op amp's output to achieve a 600Ω impedance would mean that for a 1V rms output, the op amp could deliver only about $420\mu\text{W}$ to the load. The circuit in Fig 1, on the other hand, can use a much smaller output resistor and still have the 600Ω output impedance. For example, it would supply approximately 1.24 mW at the 1V output level using a 90Ω output resistor. This design is valid only for $\sim 600\Omega$ and $\sim 90\Omega$.

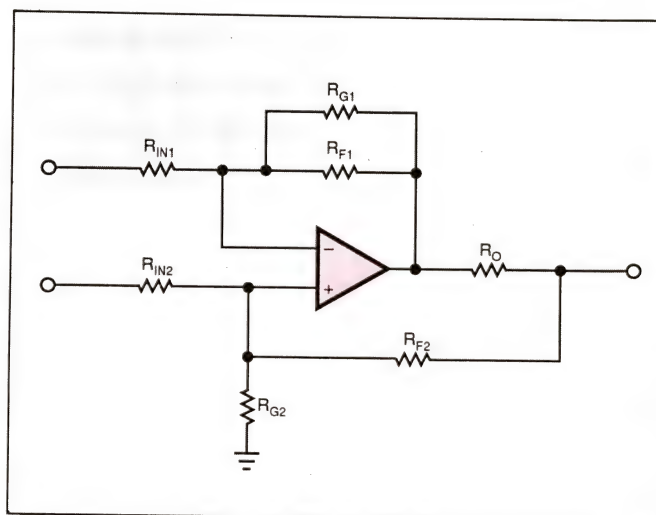


Fig 1—This op-amp circuit presents a high-impedance output without dissipating excessive power in its series-output resistor.

Commitment to Technology

Magazine Edition

The electronics industry's leading design publication

News Edition

The electronics industry's only technical newspaper



EDN Magazine
Edition
News
Edition

A Partnership in Power and Prestige Worldwide

DESIGN IDEAS

Design Entry Blank

\$100 Cash Award for all entries selected by editors. An additional \$100 Cash Award for the winning design of each issue, determined by vote of readers. Additional \$1500 Cash Award for annual Grand Prize Design, selected among biweekly winners by vote of editors.

To: Design Ideas Editor, EDN Magazine
Cahners Publishing Co
275 Washington St, Newton, MA 02158

I hereby submit by Design Ideas entry.

Name _____

Title _____ Phone _____

Company _____

Division (if any) _____

Street _____

City _____ State _____ Zip _____

Design Title _____

Home Address _____

Social Security Number _____
(Must accompany all Design Ideas submitted by US authors)

Entry blank must accompany all entries. Design entered must be submitted exclusively to EDN, must not be patented, and must have no patent pending. Design must be original with author(s), must not have been previously published (limited-distribution house organs excepted), and must have been constructed and tested.

Exclusive publishing rights remain with Cahners Publishing Co unless entry is returned to author or editor gives written permission for publication elsewhere.

In submitting my entry, I agree to abide by the rules of the Design Ideas Program.

Signed _____

Date _____

ISSUE WINNER

The winning Design Idea for the October 26, 1989, issue is entitled "C program rotates vectors," submitted by Branko Zebec of PEL Electronics (Varazdin, Yugoslavia).

Your vote determines this issue's winner. All designs published win \$100 cash. All issue winners receive an additional \$100 and become eligible for the annual \$1500 Grand Prize. **Vote now**, by circling the appropriate number on the reader inquiry card.

The circuit's design equations are

$$\frac{V_o}{V_i} = \frac{R_G}{R_{IN}}$$

$$Z_o = R_o \left(\frac{R_G}{R_F} + 1 \right),$$

$$R_G = R_F \left(\frac{Z_o}{R_o} - 1 \right),$$

$$R_F = \frac{R_G}{\left(\frac{Z_o}{R_o} \right) - 1}, \text{ and}$$

$$Z_o = \frac{V_o}{I_o} = \frac{R_G R_o (R_F + R_G)}{R_F R_G}.$$

The circuit can be inverting or noninverting. If you use the inverting configuration, combine R_{IN2} and R_{G2} into a single resistor. Also, you can usually combine R_{F1} and R_{G1} into a single resistor.

EDN

To Vote For This Design, Circle No. 750


Sampling A/Ds

DATEL's video speed sampling A/D converters give superior dynamic performance, to bring both harmonic distortion and signal-to-noise ratios to new lows.

For complete information call (508) 339-3000

Model	Sampling Rate	Effective Bits at Nyquist Frequency	THD* at Nyquist Frequency	Power Dissipation	Package
ADS-112	1MHz	11.0	-73 dB	1.3 watts	24-pin DDIP
ADS-132	2MHz	11.0	-73 dB	2.9 watts	32-pin TDIP
ADS-131	5MHz	10.6	-69 dB	4.2 watts	40-pin TDIP
ADS-130	10MHz	10.6	-69 dB	4.5 watts	40-pin TDIP

*THD (Total Harmonic Distortion)

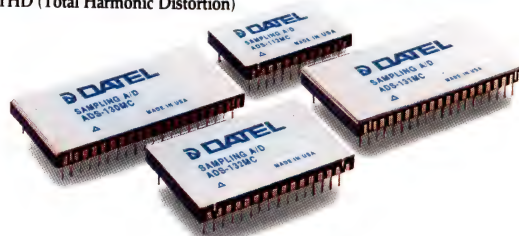

DATEL

INNOVATION AND EXCELLENCE IN PRECISION DATA ACQUISITION
DATEL, Inc., 11 Cabot Boulevard, Mansfield, MA 02048 (508) 339-3000

CIRCLE NO. 16


NEW PRODUCTS

COMPUTERS & PERIPHERALS

Handheld Scanners For Macintosh Computers

- 400-dpi resolution on black-and-white documents
- 3-color single-pass scanning for 4000 colors on color model

The Model 400A and Model 270A are handheld scanners for Macintosh computers. The Model 400A provides 400-dpi resolution when scanning black-and-white documents. This model uses variable scanning methods, which create bayer, mesh, or spiral dithering patterns for monochrome line art. The unit has a scanning speed of 3.1 in./sec and a scan width of 4.1 in. A window on the scanner permits visual scan alignment. The Model 270A provides 3-color single-pass scanning for documents with as many as 4000 colors. The unit provides a resolution of 4 bits/color for each color. Its scanning speed

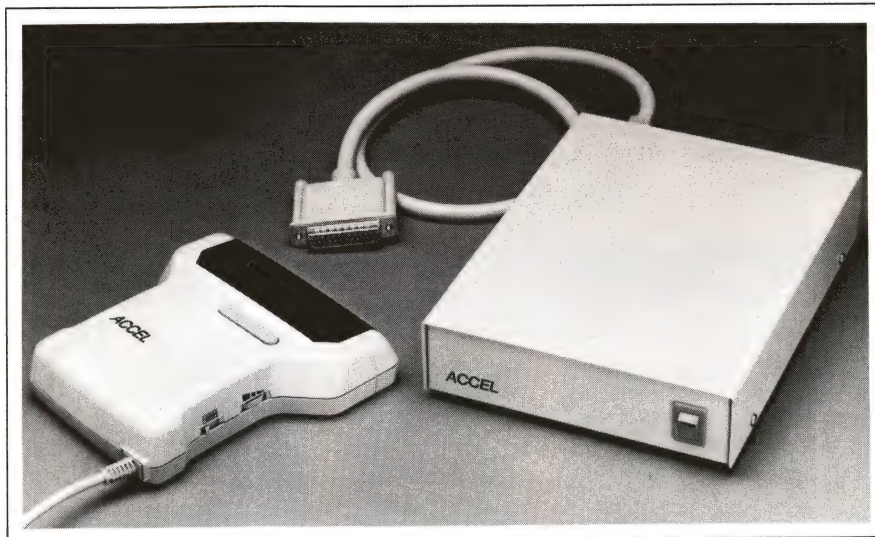

is 1 in./sec, and it can scan color images that are 2.53 in. wide in a single pass. Both models have a switch to start scanning and variable intensity controls. They come with an external SCSI unit and connectors for interfacing with the

Mac. Model 400A, \$500; Model 270A, \$800.

Accel Computer Corp., Von Karman Commerce Center, Suite 110, 17145 Von Karman Ave, Irvine, CA 92714. Phone (714) 757-1212. FAX 714-757-1288. **Circle No. 375**



Expansion Station For Laptop Computers

- Three to five IBM PC, PC/XT, and PC/AT expansion slots
- Multiple bays house 3 1/2- and 5 1/4-in. storage devices

The LapStation expansion unit provides laptop computers with the features of a desktop computer. The unit provides from three to five 8-or 16-bit IBM PC, PC/XT, or PC/AT expansion slots and multiple bays that can house 3 1/2- and 5 1/4-in. storage devices such as hard-disk drives, streaming-tape drives, and floppy-disk drives. The unit comes

with a Personality Adapter Kit that adapts the unit for operation with laptops from Sharp, Toshiba, Datavue, NEC, Epson, Hitachi, Compaq, Sanyo, Zenith, and Mitsubishi. The LapStation comes in two models and has a 3-ft interface cable that permits the unit to be placed behind a desk. \$795.


Axionix Corp., 2257 S 1100 East, Suite 2C, Salt Lake City, UT 84106. Phone (800) 866-9797; in UT, (801) 866-9797. FAX 801-485-6204.

Circle No. 376

Arcnet Adapter Board For DEC Computers

- 2k-byte RAM provides four 512k-byte packet buffers
- Acts as slave on 16-, 18-, and 22-bit versions of Q Bus

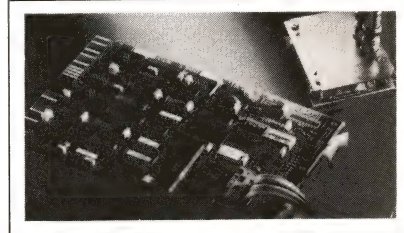The Q-ARC-01X Arcnet adapter board for MicroVAX, VAX II, PDP-11, and LSI-11 computers functions as an intelligent slave for



16-, 18-, and 22-bit versions of the Q Bus. The board uses a Standard Microsystems 9026 LAN controller IC and 2k bytes of RAM, which provide four 512-byte packet buffers. The packet buffers can send and receive in any combination. The buffer base address can be located on any 2048-byte boundary within the Q Bus address range, including the I/O space. The control and status-word base can be located on any 4M-byte boundary within the I/O page-address space. Drivers are available for the RSX-11M/M+ and VMS operating systems. A NetBIOS, endorsed by the Arcnet Trade Association, is also available

and permits the interconnection of VAX and ISA bus computers that use high-level software. The board also operates with Fast File Transfer software. \$1995.

C&C Technology Inc., Bldg 9, Unit 60, 245 W Roosevelt Rd, West Chicago, IL 60185. Phone (312) 231-0015.

Circle No. 377

Board For IBM PC, PC/XT, and PC/AT computers


- Has 4-user interface using a single expansion slot
- Dedicated CPU and as much as 4M bytes of RAM/user

The K-Slave/4 is a modular multi-user plug-in system for IBM PC, PC/XT, PC/AT, and compatible

computers. A single-slot plug-in board accepts daughter modules to provide 4-user access to the computer's resources. The modules provide each user with a dedicated 8-MHz NEC V20 CPU and either 512k, 768k, or 1M byte of RAM. Of the 1M-byte memory, you can use 704k bytes for application software. In addition, the board provides features that push network overhead over the 704k-byte boundary. These features enable the implementation of memory-hungry software applications that typically require an extended or expanded memory board. You can also connect a display terminal through an RS-232C port. Base board with one daughter module, \$400; additional daughter modules, \$300 each.

Kimtron Corp., 1709 Junction Ct, Bldg 380, San Jose, CA 95112. Phone (408) 436-6550. FAX 408-436-1380. TLX 6975590.

Circle No. 378

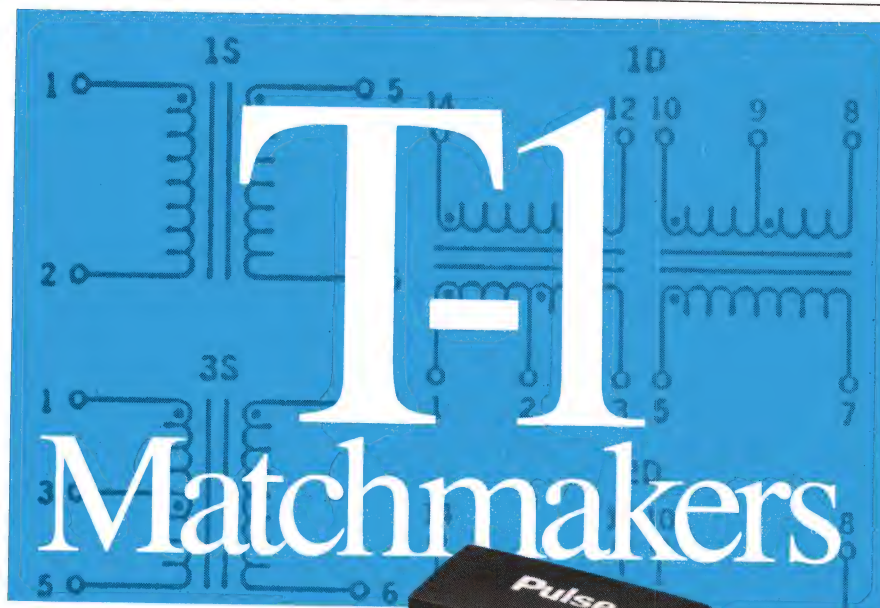

A broad line of interface transformers for use in T-1/CEPT line interfaces.

Each transformer is designed to **MATCH** a specific transceiver chip. Our transformers allow your equipment to **MATCH** standards such as CCITT G.703, FCC and others. Just as important, they **MATCH** what you need.

- Tested by major chip manufacturers
- 1500 V isolation voltage
- Optimized for balance and pulse waveform
- Passed surge voltage tests
- Low profile encapsulated packages
- Space saving dual packages include both transmit and receive functions

Pulse's transformers make a perfect MATCH.

For the entire list of transformers with corresponding transceiver chips and an application note on how to incorporate them in your T-1/CEPT circuit designs, please contact:



Pulse Engineering, Inc.

P.O. Box 12235, San Diego, CA 92112
(619) 268-2400, FAX: 619-268-2515


CIRCLE NO. 17



X Window Terminal With MC68010 μ P

- Applications for Unix, VMS, and Xenix
- Has an X server in EPROM based on the MIT X standard

The QXT 10 X Windows terminal provides simultaneous access to networked computers that can be running X Windows applications using Unix, VMS, Xenix, and other operating systems. The terminal employs an MC68010 μ P, and it has an X server in EPROM that's based on the MIT X, V11, release 3 stan-



"I'm not a writer who writes about engineering; I'm an engineer who writes."

Anne Swager, EDN Magazine Edition Associate Editor

Anne's been reading EDN since she became an electrical engineer. And as an engineer, she has always counted on EDN to keep her up to date on new products and technology in the electronic markets. "As an engineer, I found myself always focusing on one project. I read EDN to find out what was going on in other areas of electronic engineering. Becoming a technical editor gave me greater exposure to the entire spectrum of electronics."

Not too long ago, Anne saw an ad like this one and answered it. "When I saw EDN's ad, I sent in my resume. I never even considered working for another publication."

Anne doesn't see working at EDN as a career change. "As an engineer, I liked problem solving, hands-on work, and circuit design. As an EDN editor, I still keep in touch with all three engineering activities. . . I just approach them from different angles. This position lets me investigate trends and new technologies and then write about them. So, I'm not limiting my capabilities as an engineer; I'm expanding them. Before you can explain a concept to someone else, you must understand it yourself."

You too can be an engineer who writes for EDN. All you need are a BS in electrical engineering, at least two years of design experience and the ability to write clearly. Salaries are competitive with those paid to engineers.

If you're interested in a career with the world's most prestigious electronics publication, send your resume to Kathy Leonard, EDN Magazine Edition, 275 Washington Street, Newton, MA 02158-1630. Or reach EDN by phone at 617/558-4405.

EDN Magazine Edition
News Edition

dard. The QXT 10 comes with a flat-screen monitor and an enhanced PC/AT keyboard. The terminal's low-profile box, which contains the logic board and interconnects, fits directly under the monitor. Its logic board has an Ethernet interface, which supports TCP/IP (Transmission Control Protocol/Internet Pro-

ocol) and Telnet data-transfer network protocols. In addition, it provides VT 220 terminal emulation through an RS-232C interface. The terminal also has additional ports that interface with a local printer and an optional 3-button mouse. 1M-byte version with network interfaces, software, monitor, key-

board, and mouse, \$1495.

Qume Corp., 500 Yosemite Dr., Milpitas, CA 95035. Phone (408) 942-4000. FAX 408-942-4052.

Circle No. 379




VACTEC

OPTOELECTRONICS

With EG&G Vactec LDR's there has never been a lead interconnect failure reported. The reason: superbly designed IBM lead pinners.

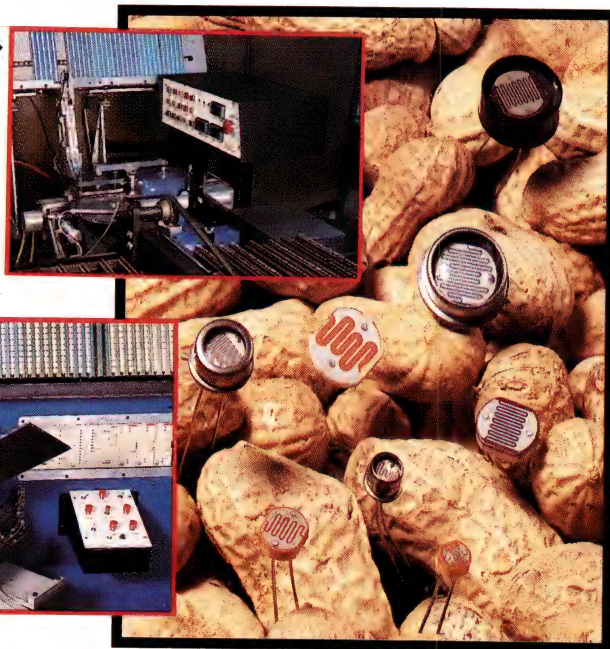Automatic testers 100% test and characterize each unit (twice) to provide the precise performance you specify.



LIGHT DEPENDENT RESISTORS

(Photoconductive Cells)


World-class high-speed automation provides superb quality at very competitive prices. (You might say the cost is peanuts.) Over 1/3-billion already shipped to EG&G Vactec customers worldwide—a testimonial to their dependability.

APPLICATIONS:

- Use like any variable resistor—LDR resistance is inversely proportional to illumination.
- ON-OFF controls for day/night operation—general lighting, street lighting, controls, signs, safety equipment.
- Automatic adjustment of brightness of displays in automotive accessories, instruments, clocks, appliances, and TV sets.

Call or write for more information:

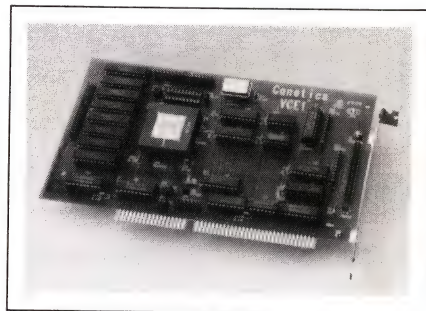EG&G Vactec, Inc. • 10900 Page Blvd. • St. Louis, MO 63132
(314) 423-4900 • TWX 910-764-0811 • FAX 314-423-3956



Vector-Processor Board For ISA Bus

- *Parallel addition and multiplication operations*
- *Delivers 12.5 MIPS and performs 32-bit floating-point math*

The VCE1 vector-processor board for the ISA bus uses an AT&T DSP32C DSP chip, which executes parallel multiplication and addition at 12.5 MIPS. The card performs 32-bit floating-point math, according to the IEEE format, as fast as 25M flops. Other features include 256k bytes of zero-wait-state RAM for program and data; daughter cards for as much as 16M bytes of memory expansion; DMA transfer rates between the host and the card at 2M to 4M bytes/sec; a 20M-byte data transfer to an external interface; and an option for an analog I/O port. Benchmark results include a 1024-point complex FFT calculation in 3 msec and an FIR filter implementation with as many as 12M taps/sec. Fortran and C subroutine libraries are also available. 20M-flops version with 256k bytes of RAM, \$1675; 25M-flops version with 256k bytes of RAM, \$1995; C or Fortran libraries, \$485; software development kit, \$1500.

Canetics Inc., Box 70549, Pasadena, CA 91107. Phone (818) 584-0438. FAX 818-584-0439.

Circle No. 380

How many more reasons do you need to add IEC shock-safe protection?

No one can completely eliminate every possibility of electrical shock. But *you* can eliminate the possibility of electrical shock as defined in IEC Standards 65 and 257, when you ask for Littelfuse Shock-safe Fuseholders.

They meet the widest range of international standards to help bring your designs to market across the country and around the world.

With a choice of styles that meet your assembly needs and reduce fuseholder body inventories.

Just select the terminal style you want—including $\frac{1}{4}$ " Q.C. Then add your choice of color-coded, interchangeable finger grip or screwdriver slot knob to match the standard 3AG, European 5 x 20 mm or miniature 2AG fuse you've selected.

To put your hands on some free samples, call your Littelfuse representative today. And remember, it's better to be shock-safe than sorry.

Littelfuse Inc.

800 E. Northwest Highway
Des Plaines, IL 60016
FAX (708) 824-3024
(708) 824-0400

CIRCLE NO. 95

Ask for Littelfuse.

Call for your free copy of the Littelfuse Shock-safe Fuseholder Product Bulletin #1031.

© Littelfuse Inc.



BROADEN YOUR DEVELOPMENT HORIZONS...

68000

C, PL/M, ASM

68020

XRAY

68030

XDB

80186

C-SPY

80286

80386

SOFTVIEW

8052



... with the ultra-extensive MICE (Micro In-Circuit Emulator) line from Microtek, supporting practically all the popular 8,16, and 32 bit microprocessors. A range of emulators so powerful and complete that none of your development needs are overlooked.

When you need speed, MICE are fast! Swiftly debug high-speed targets without accumulating wait state and with no distortion whatsoever.

Full software support is readily available for the MICE series, which can be used in conjunction with such popular hosts as the *IBM-PC, *NEC-PC, *Sun Workstation, *VAX, *MicroVAX and *Apollo.

Add all these factors to the streamlined design and affordability of the MICE and you get a valuable investment for all your microprocessor projects.

MICROTEK

Microtek Lab, Inc.

680 Knox Street
Torrance, CA 90502
U.S.A.

Tel: (213)321-2121
Telex: 797880 MICRO
Fax: (213)538-1193

*Registered Trademarks: PC/XT/AT, PS/2: International Business Machines. VAX, μ VAX: Digital Equipment Corporation; Apollo: Apollo Computer Inc.; Sun: Sun Microsystems, Inc.; NEC: NEC Corporation.

CIRCLE NO. 96


NEW PRODUCTS

INTEGRATED CIRCUITS

ISDN Echo Canceller

- Includes layer-2 functions
- Optimized for PABX extension lines

According to the company, the PCB2391 is the first single-chip ISDN (Integrated Services Digital Network) echo canceller to incorporate on-chip layer-2 functions. Optimized for PABX extension lines, the circuit also supports remote multiplexers and can operate in public exchange lines that serve nearby subscribers. The canceller is line-polarity independent and needs no active external components for sending on the line. Like most ISDN echo cancellers, the IC provides full-duplex transmission of 2B + D channels via normal twisted-pair wires. A 1B + D mode allows for time-slot saving on the exchange side. The PCB2391 provides a 2.048M-bps highway interface,

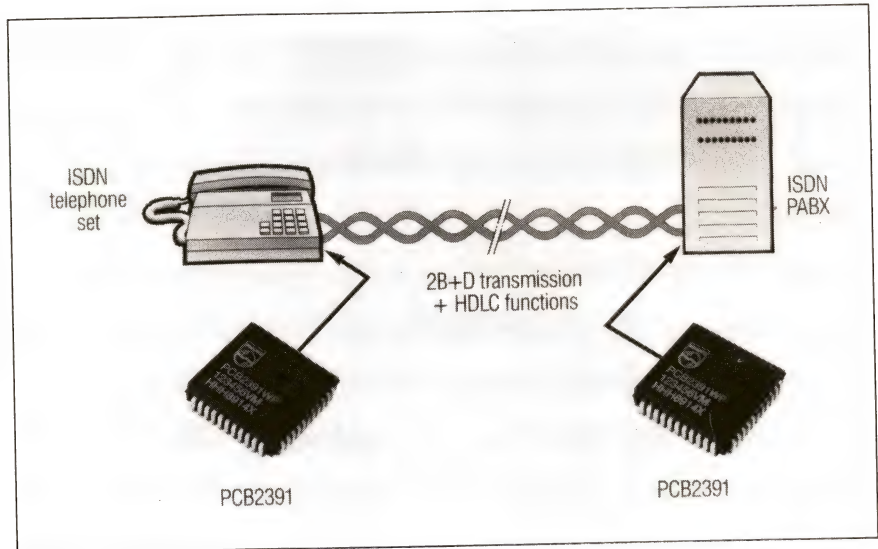

which is compatible with standard codecs, using both long- and short-frame sync timing modes. On the line side, the IC uses a Manchester biphasic code at a line rate of 152k bps. In a 44-pin PLCC (plastic leaded-chip carrier), \$43 (1000).

Philips Components, Box 218, 5600 MD Eindhoven, The Netherlands. Phone (040) 724324. TLX 51573. **Circle No. 368**

Signetics Corp., 811 E Arques Ave, Sunnyvale, CA 94088. Phone (408) 991-4535. **Circle No. 369**

Switching Regulator

- Has 3.5A output capability
- Operates over a 15-to-50V input range

Featuring a high-efficiency DMOS power stage, the L4974 switching regulator has a 3.5A output capability. Housed in a 20-pin DIP that needs no heat sink, the device can deliver as much as 120W to the load. Heat is dissipated via a few square centimeters of printed-circuit copper. The regulated output voltage from the L4974 stepdown dc/dc converter is variable from 5.1 to 40V; the input range is 15 to 50V. Included in the switching regulator's circuitry are a 2% reference, current limiting, thermal protection, soft start, voltage feed-forward control, and reset and power-fail functions. \$2.90 (5000).

SGS-Thomson Microelectronics, 1000 E Bell Rd, Phoenix, AZ 85022. Phone (602) 867-6100. FAX 602-867-6290. **Circle No. 370**

Preregulator IC That Controls Power Factor

- Offers power factors to 0.99
- Accepts line voltages of 75 to 275V

Offering a power factor as high as 0.99, the UC3854 family of preregulator ICs uses average-current control to accomplish fixed-frequency current control with stability and low distortion. Unlike peak-current control, average-current control accurately maintains sinusoidal line current without slope compensation. The UC3854's high reference voltage and high oscillator amplitude minimize noise sensitivity, and fast pulse-width-modulation elements permit chopping frequencies above 200 kHz. The UC3854 operates from line voltages of 75 to 275V and from line frequencies of 50 to 400 Hz. Other features include fast feed-forward line regulation, a low-offset analog multiplier/divider, and a 0.5A totem-pole

driver. In 16-pin plastic and ceramic DIPs, from \$5.90 (100).

Unitrode Integrated Circuits Corp., 7 Continental Blvd, Merrimack, NH 03054. Phone (603) 424-2410. **Circle No. 371**

34-Channel Driver

- Features push-pull output
- Has 250V rating

Manufactured using the company's HVCMOS II process, the HV70 combines high-speed, low-power CMOS logic with 34 250V push-pull CMOS outputs on a single monolithic chip. The driver is a pin-compatible replacement for the Siliconix SI9560 and can also replace TI's SN75563 and SN75564 pair. The cascable serial-to-parallel converter accepts 12V CMOS serial data and outputs it at 250V and 70 mA max at data rates in excess of 4 MHz. A direction pin allows data to flow either clockwise or counter-

clockwise, which makes the HV70 particularly useful in display applications. Standby current is less than 50 nA. In plastic or ceramic J-lead packages, from \$8.80 (1000).


Supertex Inc., 1225 Bordeaux Dr, Sunnyvale, CA 94088. Phone (408) 744-0100. FAX 408-734-5247.

Circle No. 372

Space-Saving Memory Modules

- Feature 4M-bit dynamic RAMs
- Have single in-line construction

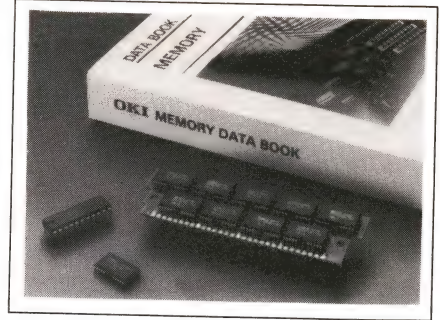Using 4M-bit dynamic RAMs mounted on a small pc board, these single in-line memory modules (SIMMs) save space and reduce assembly costs. The SIMMs allow the



user to plug large arrays of memories into the computer's main circuit board or a plug-in card. Existing 1M-bit modules can be replaced by the 4M-bit modules, reducing power consumption/bit by 75%, according to the company. The modules are organized as 4M × 8 bits or 4M × 9 bits. 4M × 9-bit SIMM, \$700 (1000); individual DRAMs in SOJ and DIP packages, from \$75 (10,000).

Oki Semiconductor, 685 N Mary Ave, Sunnyvale, CA 94086. Phone (408) 720-1900. Circle No. 373

U S E R R A T E D  E X C E L L E N C E

Feed this to your PC and it'll think it's an HPBASIC workstation.



Finally, there's a way for serious technical computer users to get the power and features of HP BASIC on a PC. The answer is HTBasic, a real engineering BASIC that turns your PC into an HP 9000 series 200/300 BASIC workstation—at a fraction of the cost.

Like HP's Rocky Mountain BASIC, HTBasic from TransEra is a state-of-the-art BASIC that gives you all the capabilities you need for complex engineering applications. Plus, you get important advanced features you won't find with any other PC BASIC. Like the complete set of HP graphic commands. Integrated HP-IB (GPIB) syntax for intelligent instrument control. The advanced I/O Path system. And built-in matrix math. In fact, all the optional HP binaries are built in. There's nothing else to load. You even get the full screen program editing and debugging environment.

Discover the new solution for cost-effective technical workstations. HTBasic from TransEra.

HTBasic
High Tech Basic

HP, HP BASIC and HP-IB are registered trademarks of Hewlett-Packard.

DISCOVER HTBASIC FOR YOURSELF

Call today at
(801) 224-6550
or FAX us at
(801) 224-0355

TransEra 3707 North Canyon Road, Provo, Utah 84604 • TEL: 801-224-6550 • FAX: 801-224-0355

Dual BiFET Op Amp With Fast Settling Time

- Settles to 0.01% in 500 nsec
- Has 13-MHz gain-bandwidth product

A dual version of the popular AD744 precision op amp, the AD746 settles to 0.01% in 500 nsec for a 10V step, a speed that is three times faster than existing dual BiFET op amps, according to the company. Other dynamic specifications include a 13-MHz gain-bandwidth product, a 75V/μsec slew rate, and only 0.0001% total harmonic distortion. For dc performance, the op amp features a typical offset voltage of 0.3 mV (1.5 mV max) and input offset drift of 12 μV/°C. Open-loop gain is a minimum of 150V/mV and is typically 300V/mV. In 8-pin miniDIP, hermetically sealed ceramic-DIP, and surface-mount packages, from \$4.25 (100).

Analog Devices, Literature Center, 70 Shawmut Rd, Canton, MA 02021. Phone (508) 658-9400. TWX 710-394-6577. Circle No. 374

CIRCLE NO. 19

CLOCK IN AT

Super Fast SRAM Modules

Clock in at some of the highest speeds in the industry with Micron's family of super high quality, super Fast SRAM modules.

Our SRAM modules feature low-power, CMOS-design memories that produce record-breaking speeds from 15 through 45ns. They're the only modules that offer our unique protection circuitry which enhances performance. And the 128K X 8 modules are fully compatible with next-generation monolithic SRAMs.

We offer a variety of SRAM and DRAM modules manufactured to industry-standard and custom specifications. So, no matter what your application, Micron can help you design and develop a solution.

For more information about Micron SRAM and DRAM modules, call us today at 1-208-386-3900. And discover how we can help you beat the clock.

Micron. Working to improve your memory.

ORGANIZATION	PACKAGES	SPEED
SRAM MODULES		
128K X 8	32-PIN DIP	30, 35, 45
64K X 16	40-PIN DIP	30, 35, 45
32K X 16	40-PIN DIP	30, 35, 45
64K X 32	64-PIN ZIP	25, 30, 35, 45
16K X 32	64-PIN ZIP	15, 20, 25, 30, 35, 45
DRAM MODULES*		
512K X 36	SIMM/ZIP	80, 100, 120
256K X 36	SIMM/ZIP	80, 100, 120
1MEG X 8/9	SIMM/SIP	80, 100, 120
256K X 8/9	SIMM/SIP	80, 100, 120, 150
64K X 8/9	SIMM/SIP	80, 100, 120, 150
64K X 4/5	SIMM/SIP	80, 100, 120, 150

* Micron offers a variety of packages configured in both standard and low profile versions. Access Cycles offered are Fast Page Mode, Page Mode, Static Column and Nibble Mode.

MICRON


TECHNOLOGY, INC.

2805 E. Columbia Road, Boise, Idaho 83706 208-386-3900


WHEN YOUR REPUTATION'S ON THE LINE.

RAYOVAC

**Computer
Clock
Battery**

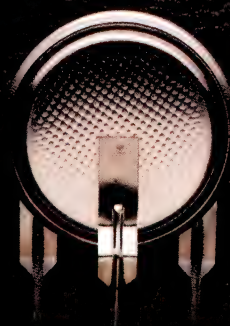

RAYOVAC
FB 2325 H2

MADE IN U.S.A. 

For superior battery performance, reliable enough to risk your reputation on, specify Rayovac.

For quality in the long run, consider our 844 Computer Clock Battery. Its unique architecture delivers economical long life and safe, reliable operation.

Our Lifex Lithium Coin Cells offer a shelf life ten times longer than conventional crimp seal batteries. With greater capacity retention and superior performance. They're available in a variety of tab and pin configurations.

For reliability in harsh environments, consider our Lifex

FB batteries. Encapsulated cell technology allows them to withstand humidity, thermal shock and temperatures from -40°C to +100°C.

To set your ideas into motion, call your distributor. And tap into the power of innovation at Rayovac.

RAYOVAC

The power of innovation.

Newark Electronics
Locations Worldwide


Sager
1 617 749-6700

Hammond/EMSCO
1 407 849-6060

Cypress Electronics
1 408 980-2500
1 800 538-5112 outside CA

Marsh Electronics
1 414 475-6000

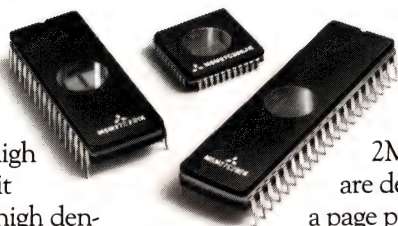2 Megabit, 100 Nanosecond EPROMs. Available Now. From Mitsubishi.



Now, with Mitsubishi's 2Mb CMOS EPROMs, high performance 16- and 32-bit MPU systems can access high density memory as fast as 100ns. Plus, system current drain and EPROM programming through-put time can be significantly reduced.

Mitsubishi's sub-micron CMOS process technology makes fast, 100ns, 2Mb EPROM production feasible. And, it results in a low, 30mA active (100 μ A standby) current drain.

The 100ns, 2Mb EPROMs are designed with a page programming algorithm that writes two words (32 bits) simultaneously. That means all bits can be written in about 28 seconds—four times faster than conventional byte mode.

The 100ns, 2Mb EPROMs are the latest in Mitsubishi's expanding EPROM line which also includes 2Mb OTP ROM options in DIP, flat pack and PLCC packaging.

Soon, a ceramic leaded chip carrier (CLCC) will be available that combines the advantages of high memory density, fast access time and erasability/reprogrammability for surface mount applications.

For more information on fast, 2Mb Mitsubishi EPROM's, call now. (408) 730-5900 Ext., 2106. 1050 E. Arques Avenue, Sunnyvale, CA 94086.





“Meets spec. But can we do it in budget?”

Your design is like a baby. First, it's conceived. Then you nurture it. And prepare it for the real world.

To your design, however, the real world is a manufacturing plant. And if your design can't be manufactured cost-effectively, it will never get past the infancy stage.

Fortunately, there's National Design. Where the nation's premier OEM specialists will help you create designs that combine the best of your creative skills with producibility.

At National Design, you'll see innovative systems and technologies from over 800 OEM exhibitors. Plus leading CAD/CAM/CAE exhibits to help you create more freely. And the full spectrum of OEM components and materials for every stage of your design's development.

There's also a complete Conference program sponsored by the ASME. With sessions and workshops that deal specifically with Design for Manufacturability.

These days, creating a design to be manufactured is an awesome responsibility. But you don't have to do it alone. Come to National Design. And discover how to prepare your design for the real world.

***We help designs make it
in the real world.***



**National
Design
Engineering
Show & Conference™**

**February 26 - March 1, 1990
McCormick Place North •
Chicago, IL**

SPECIAL DISCOUNT OFFER!
Save \$15
**Bring this ad to the show for
discount admission of only \$10.**

For more information, call 203-964-8287 today.



**Cahners
Exposition
Group**

A member of the Reed Exhibition Companies.

© Reed Publishing (USA) Inc., 1989


NEW PRODUCTS

COMPONENTS & POWER SUPPLIES

DC/DC Converters

- Radiation hardened
- Available with single, dual, or triple outputs


MRH Series dc/dc converters will function through exposure to 10^{13} neutrons/cm², a 10^{11} rads/sec radiation dose rate, and a 10^5 rads total radiation dose. These 15W converters accept inputs of 16 to 36V and output 5, ± 12 , or ± 15 V in single-, dual-, and triple-output versions. Conversion efficiency equals 72%. Typical main output load regulation is 0.1%, and line regulation equals 0.05%. The multiple output models offer a flexible division of output power—the main output can handle from 2 to 10W, and each auxiliary will output from 0 to 6W. Worst-case start-up time measures 3 msec, and input-to-output ripple rejection equals -50 dB over the audio

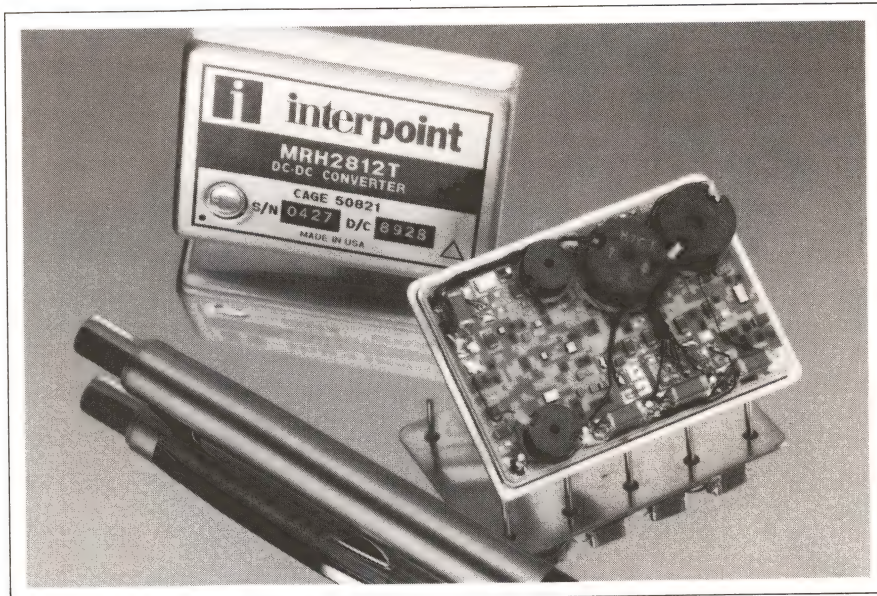

range. The units are housed in a hermetically sealed metal package that has a volume of just over 1 in³. \$667 (100).

Interpoint, Box 97005, Redmond, WA 98073. Phone (206) 882-3100. FAX 206-882-1990.

Circle No. 354

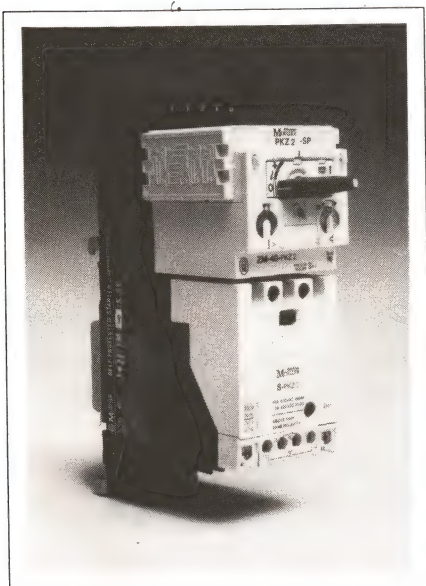

Self-Protecting Motor Controller


- Has an interrupt rating of 65 kA at 480V ac
- Measures only 8 x 2.625 in.

The PKZ 2-SP provides a number of functions—motor disconnect; motor branch-circuit protection; pro-

tection against short circuits, overloads, and ground faults; motor control; and self-protection under fault conditions. The basic unit, which measures 8 x 2.625 in., comprises disconnect, contactor, and trip modules. The controller has two sets of current-limiting main contacts: One single-break set provides disconnect and isolating functions; the other contact set provides the motor-switching capability. These contacts are functionally coordinated to minimize current and energy levels in the event of faults or short circuits. The plug-in trip modules, which come in 11 versions with ratings of 0.6 to 40A, take care of overloads and overcurrents and can handle motors rated for 30 hp at 460V. The PKZ 2-SP has an interrupt rating of 65 kA rms at 480V ac or 100 kA at 240V ac. From \$446.

Klockner Moeller, 25 Forge Pkwy, Franklin, MA 02038. Phone (508) 520-7080. FAX 508-520-7084.

Circle No. 355

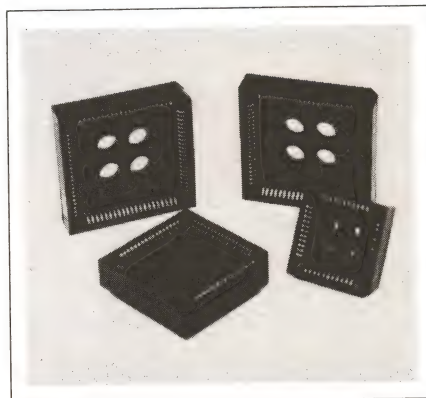


Chip-Carrier Sockets

- Available in surface-mount versions
- Meet requirements of MIL-STD-202 and MIL-STD-1344

These PLCC (plastic leaded chip carrier) sockets are available in standard- (-55 to +110°C) and high-temperature (-55 to +220°C) versions. In models with 20 to 100 positions, the sockets come in both through-hole and surface-mount types. Both types meet MIL-STD-202 and MIL-STD-1344 require-

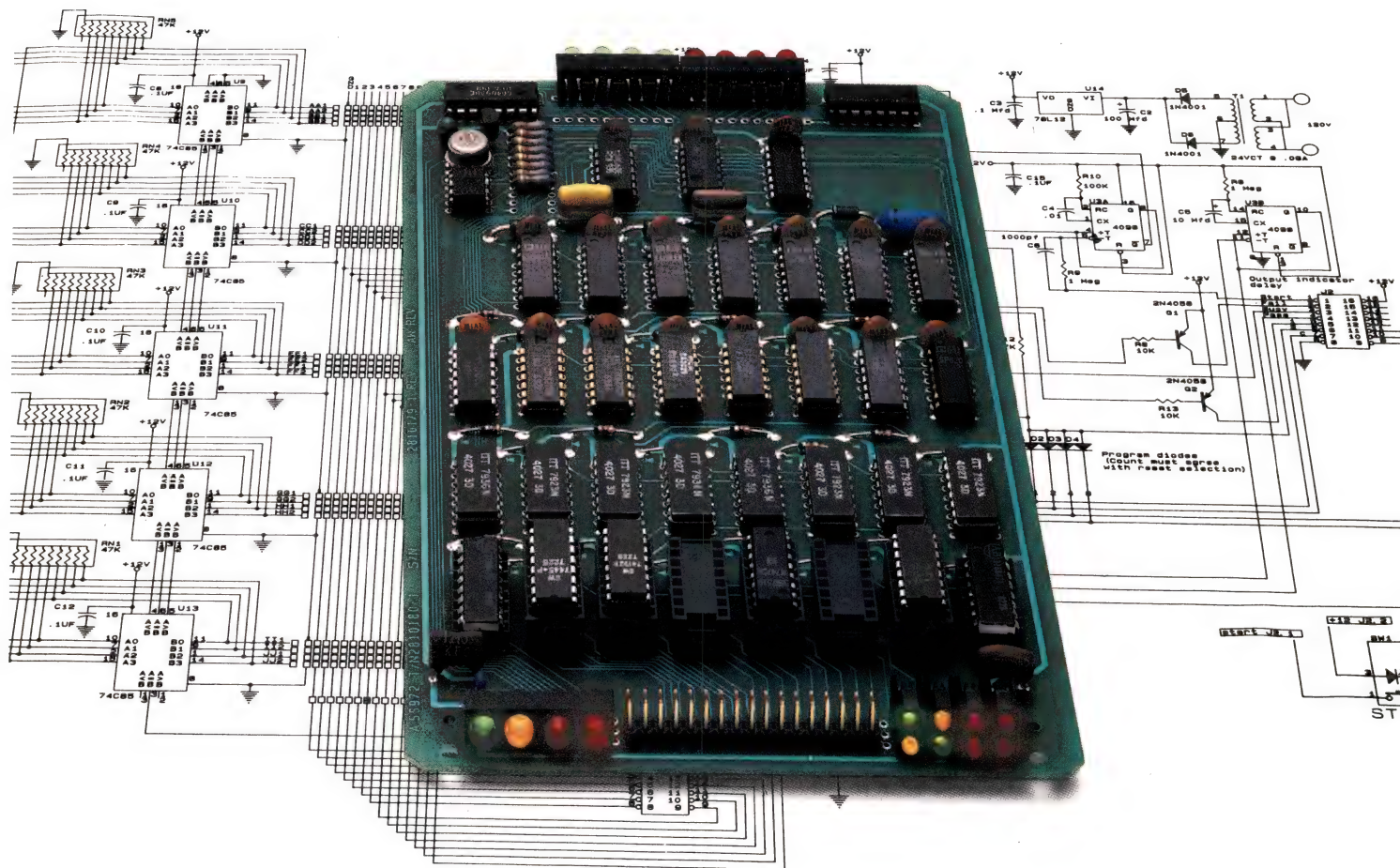IDI Packaged LEDs bring your design to light.



When it comes to designing in LEDs, you're concerned with more than performance specifications. You're also responsible for packaging considerations ... compatibility ... time and money. So are we.

IDI is your source for all kinds of indicator solutions. From a simple LED or lens to a ready-to-mount packaged LED assembly, IDI means competitive costs and fast supply. Select from our in-stock inventory with thousands of indicators and assemblies, or explore the possibilities of our custom-engineered packages.

IDI turns ideas into innovative solutions.

No one knows how to bring your needs to light better than IDI. We have years of experience and know-how in designing indicator lights. For special needs,



our engineers will work closely to design and manufacture the best product possible at the lowest cost.

Turn to the source.

From the smallest in-stock order to the most complex custom application, IDI is the home of indicator solutions. Write or call us direct and we'll send you the latest copy of "IDI" – The Source Data Book. It's packed with the largest selection of indicators ... standard variations ... money-saving packages ... customizing services and much more.

Only from IDI. Taking you from design to solution – fast. Call for your free IDI Data Book today!




Industrial Devices, Inc. 260 Railroad Avenue, Hackensack, NJ 07601 (201) 489-8989 (201) 489-6911 (FAX)

ments. The sockets have terminations on a 0.1-in.-square grid. They are rated to carry 1A and have a withstanding voltage rating of 500V rms. From \$1.50 (1000) for a 68-pin unit.

Arco Electronics Corp., 9016 Fullbright Ave, Chatsworth, CA 91311. Phone (818) 882-8707.

Circle No. 356

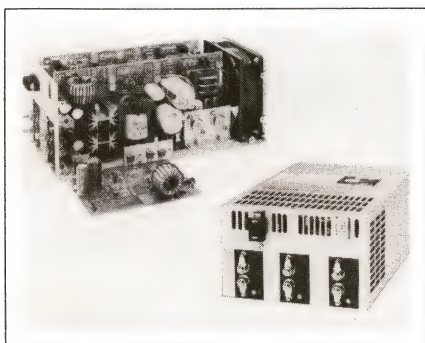

Triple-Output Power Supplies

- Output to 1600W
- Have 82% efficiency

Additions to the VF Series switching-power-supply family, these three models offer 5V at 120A on the main output and 12V ratings on auxiliaries to provide total output powers of 850, 1100, and 1600W. All three feature 82% typical efficiency, isolated regulated outputs, and VDE-, IEC-, UL-, and CSA-approved internal modules. An optional filter enables the supplies to meet FCC 20780 Part 15 Class A and VDE 0871/6 Class A for conducted emissions. \$860 to \$1260. Delivery, four to eight weeks ARO.

Deltron Inc., Box 1369, North Wales, PA 19454. Phone (215) 699-9261. TWX 510-661-8061.

Circle No. 357

Transmission Adapters

- Let you mix serial and parallel devices
- Increase transmission distance to 4000 ft

The Distance Extender family includes a series of parallel and serial

adapters that extend the transmission distance between computers and peripherals using standard wire cable. Parallel models operate to 4000 ft at 56k bps/port over 2-pair wires; serial models provide the same distance gains at 115k bps over 4-pair wire cables. You can mix parallel and serial units in the

same application. Models with Centronics 36-in. connectors and DB25 male plugs are available. From \$110.

Digital Products Inc., 108 Water St, Watertown, MA 02172. Phone (800) 243-3333; in MA, (617) 924-1680. FAX 617-924-7814.

Circle No. 358

Turn Good Ideas Into Good Articles


With EDN's FREE Writer's Guide!

Would you like to get paid for sharing your clever engineering ideas and methods with your professional colleagues? If so, then send for EDN's new FREE writer's guide and learn how.

You don't need the skills and experience of a professional writer. And you don't need to know publishing jargon. All you *do* need are a little perseverance, your engineering skills, and the ability to communicate your ideas clearly.

Our new writer's guide takes the mystery and intimidation out of writing for a publication. It shows you how to write for EDN using skills you already have. Plus, it takes you step-by-step through the editorial procedures necessary to turn your ideas into polished, professional articles.

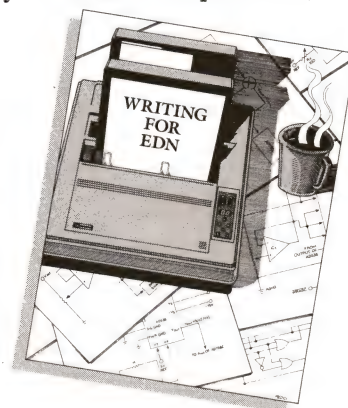Get your FREE copy of EDN's writer's guide by circling number 800 on the Information Retrieval Service Card or by calling (617) 964-3030.



"WE DEPEND ON **EDN'S MAGAZINE** AND **NEWS EDITIONS** TO DELIVER THE SPECIFICS ON MAXIM PRODUCTS TO POTENTIAL CUSTOMERS."


Mike Dikas
Director of Communications
Maxim Integrated Products

Maxim Integrated Products is one of today's fastest growing international suppliers of quality analog ICs. In the past five years they have introduced more than two hundred proprietary and improved second source devices.

Director of Communications, Mike Dikas has piloted Maxim's advertising program since its inception. "EDN's magazine and news editions have played a significant role in introducing many of our new products. In the past two years, over 25,000 EDN Magazine and News Edition readers have responded to Maxim ads, product releases and articles," says Mike. "Our ads consistently fall in the top 10% in reader response in both editions of EDN. What's even more amazing is that we typically get less than 5% duplication of responses to the same ad in both the Magazine and News Editions."

What's that mean for Maxim? "Since both editions deliver the same circulation, it's apparent to us that the same engineers read both the Magazine and News Editions for different reasons. Given Maxim's charter of product proliferation, EDN's in-depth coverage of technical issues and timely coverage of new products are both of the utmost importance to Maxim."

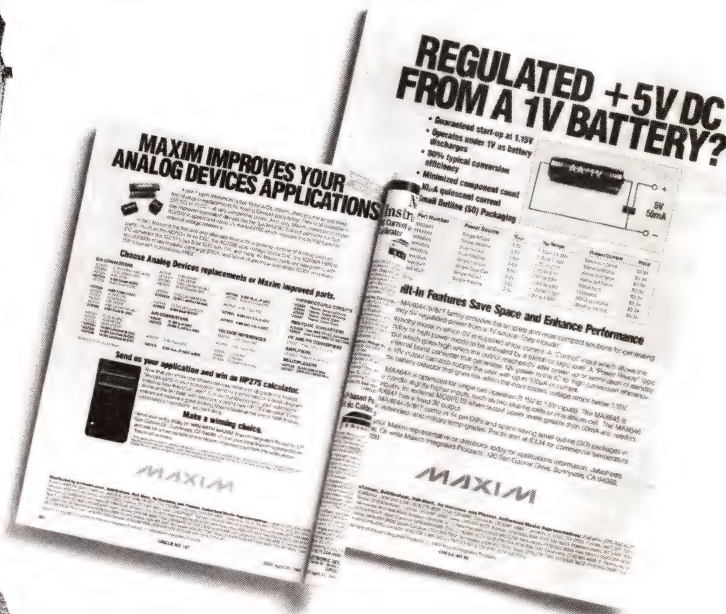Mike Dikas believes in the complementary roles of EDN Magazine and EDN News Editions.



EDN Magazine and News Editions work for
Maxim Integrated Products.
They can work for you.

EDN

A Partnership in Power and Prestige Worldwide.

Pushbutton Switches

- Available with silver- or gold-plated terminals
- Feature a 100,000-cycle life

Measuring 0.156 in. deep by 0.36 in. in diameter, TL-360 pushbutton switches are well suited for pc-board-mount applications. They have a life of 100,000 cycles and feature oxygen-free copper terminals, which are available with silver or gold plating. Actuating force measures 25 oz max, and switch-travel figures range from 0.015 to 0.025 in. Maximum switch bounce equals 5 μ sec. The switches are environmentally sealed against contamination during board-fluxing and -soldering operations. \$0.49 (1000). Delivery, four to six weeks ARO.

Standard Grigsby Inc., 920 Rathbone Ave, Aurora, IL 60507. Phone (312) 844-4300. FAX 312-844-4286.

Circle No. 359

mV and 0.01 to 0.0001V are featured for dc measurements. A miniature DIP switch, accessible from the front panel, allows you to change between C and F measurements. Alarms, BCD output, and analog output are some of the plug-in options available. From \$339.


Beckman Industrial Corp., 3883 Ruffin Rd, San Diego, CA 92123. Phone (619) 495-3200. FAX 619-268-0172.

Circle No. 360

Flat-Package Power Supplies

- Offer tunable outputs
- Feature EMI/RFI filter

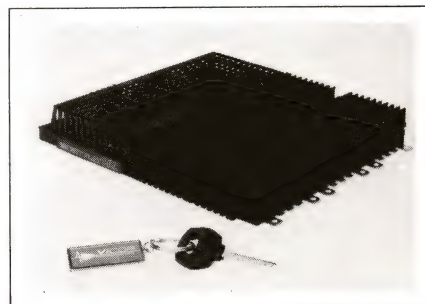The FlatPac family of user-definable off-line switching power supplies combines standard dc/dc converters with a set of modular-package and front-end subassemblies. Standard outputs are 5, 12, 15, 24, and 48V. All outputs are trimmable



by +10 and -100%. The supplies feature EMI/RFI filtering to VDE/FCC class A requirements and have safety-agency approvals pending. Sharing a common flat-package profile measuring 1.37 x 8.6 in., FlatPacs come in widths of 2.5, 4.9, and 7.4 in. and can supply as much as 200, 400, and 600W, respectively. From \$0.85/W.

Vicor Corp., 23 Frontage Rd, Andover, MA 01810. Phone (508) 470-2900. FAX 508-475-6715.

Circle No. 361



Panel Indicators

- Feature a large LED display
- Offer 1-count repeatability

Units in the 400A Series of digital panel indicators have LED displays that feature 0.8-in.-high characters, which are readable from across a room. The indicators offer 3500- and 35,000-count resolution with 1-count repeatability. The units have temperature resolutions of 1, 0.1, and 0.01°; resolutions of 0.1 to 0.001

**In February,
we'll introduce a
90 Watt per Cubic Inch*,
3-Terminal,
Integrated Switching
Regulator.**

*@ +12 VDC output

*If you can't
wait that long,
call Power Trends
at 708-231-5505
for the details.*



POWER TRENDS

1020 Carolina Drive, West Chicago, IL 60185
Telephone: 708-231-5505
Fax: 708-231-5577

CIRCLE NO. 21



In the Battle Against Interference, TDK Is Your Best Defense.

TDK EMC Technology Provides Dependable Suppression of EMI/RFI.

As the activities of today's electronics industry advance further into the realms of digitalization and high frequency, EMI and RFI become more crucial than ever.


TDK has developed a full line of components to help your products overcome EMI and RFI. This can be

accomplished only through extensive research into magnetic and dielectric materials using the most advanced electronic technology. And each one of these components demonstrates TDK quality and reliability.


No matter what your product, look to TDK for the solution to all your EMI and RFI troubles.




EMI/RFI Suppression Filters

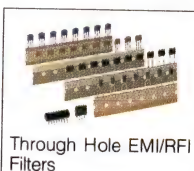


Through Hole EMI/RFI Filters

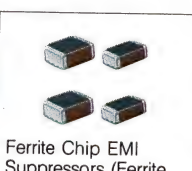

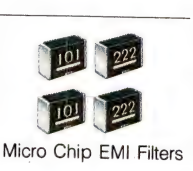
Ferrite Chip EMI Suppressors (Ferrite Chip Beads)



Micro Chip EMI Filters

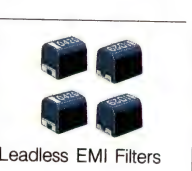


Leadless EMI Filters

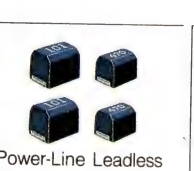

Power-Line Leadless Inductors




Leadless Line Choke SF Coils

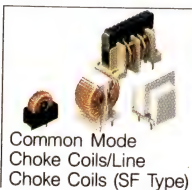

Common Mode Choke Coils/Line Choke Coils (SF Type)



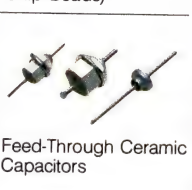UL Recognized (CSA, VDE, SEV, SEMKO, BS) Ceramic Capacitors



Feed-Through Ceramic Capacitors




EMI/RFI Suppression Ferrites



Ferrite Bead Cores



Varistors

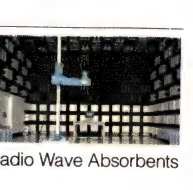

Radio Wave Absorbents

TDK Electromagnetic Compatibility Technology—At Your Service!



CEL, TDK's Component Engineering Laboratory in Torrance, CA, can custom design and test manufacture TDK EMI/RFI suppression components to meet your specific requirements. For more information, call (213) 530-9397.

TDK CORPORATION OF AMERICA HEAD OFFICE 1600 Feehanville Drive, Mount Prospect, IL 60056, U.S.A. Phone: (708) 803-6100 **CHICAGO REGIONAL OFFICE** Phone: (708) 803-6100 **INDIANAPOLIS REGIONAL OFFICE** Phone: (317) 872-0370 **NEW YORK REGIONAL OFFICE** Phone: (516) 625-0151 **LOS ANGELES REGIONAL OFFICE** Phone: (213) 539-6631 **DETROIT DISTRICT OFFICE** Phone: (313) 353-9393 **NEW JERSEY DISTRICT OFFICE** Phone: (201) 736-0023 **BOSTON DISTRICT OFFICE** Phone: (508) 624-4262 **HUNTSVILLE DISTRICT OFFICE** Phone: (205) 464-0222 **GREENSBORO DISTRICT OFFICE** Phone: (919) 292-0012 **DALLAS DISTRICT OFFICE** Phone: (214) 506-9800 **SAN FRANCISCO DISTRICT OFFICE** Phone: (408) 487-9585 **TDK CORPORATION** TOKYO, JAPAN.

NEW PRODUCTS

CAE & SOFTWARE DEVELOPMENT TOOLS

Ada For DOS 386

- *Runs on 80386-based computers under PC-DOS*
- *Shell displays Ada programs in tree form to show dependencies*

The TeleGen2 Ada program-development system runs on 80386-based computers under PC-DOS. The compiler generates native 32-bit 80386 code and comes with a source-level debugger; a global optimizer; a set of language tools that includes a cross-referencer, a source-dependency lister, and a source formatter; and TeleShell. TeleShell, a screen-oriented user interface, gives you window, menu, and text-icon access to all programming operations. It can display Ada programs in spreadsheet form or in a tree form that shows module dependencies and lets you move rapidly between multiple screen levels. The source-dependency lister produces a valid compilation-order list from programs that contain many source-code packages. \$2995.

TeleSoft, 5959 Cornerstone Ct W, San Diego, CA 92121. Phone (619) 457-2700. **Circle No. 362**

C Compiler For RISC

- *Works with Motorola 88000 RISC processor*
- *Conforms to ANSI X3J11 draft standard*

The D-CC/88K is a globally optimizing C cross-compiler for the Motorola 88100 RISC processor. The optimizations include automatic register allocations, reordering code scheduling, and global common-subexpression elimination. The compiler is compliant with 88-Open's Binary Compatibility Standard (BCS), and binary programs have successfully run on five different 88000-based computers. The compiler conforms to the proposed ANSI X3J11 C standard and accepts the standard Unix System V command-line options. It runs on a variety of host computers, including


Sun workstations under Sun OS, DEC workstations under VAX/VMS or Ultrix, and Macintosh II under MPW. From \$3500.

Diab Data Inc, 323 Vintage Park Dr, Foster City, CA 94404. Phone (415) 571-1700. **Circle No. 363**

Array-Design Tool

- *Helps you design high-density, multilevel circuits*
- *Allows Boolean-equation or state-machine data entry*

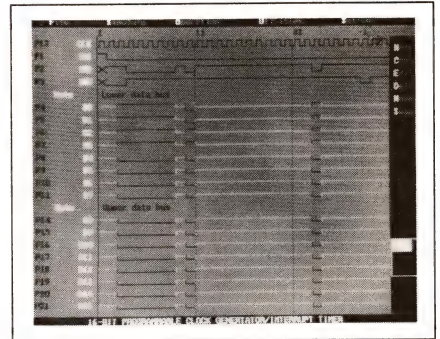The PACE (PEEL Architectural Compiler/Editor) software package lets you design high-density, multilevel, I/O logic circuits for implementation in the vendor's line of PEEL (Programmable Electrically Erasable Logic) arrays. A mouse-driven graphics editor illustrates and controls the architecture of the particular chip you are using and



makes the overall design easy to understand. It also allows you to define the logic by Boolean equations, state-machine terms, or a mixture of both. The built-in compiler transforms your logic and performs any one of five user-selectable levels of logic reduction. A simulator allows you to simulate both internal and external signals, and it generates a waveform-timing display for analysis. The package includes a direct interface to the vendor's PDS-1


In February, we'll introduce a 3-Terminal, Integrated Switching Regulator with an Efficiency that exceeds 90%, and an MTBF that exceeds 100 years.

If you can't wait that long, call Power Trends at 708-231-5505 for the details.



POWER TRENDS

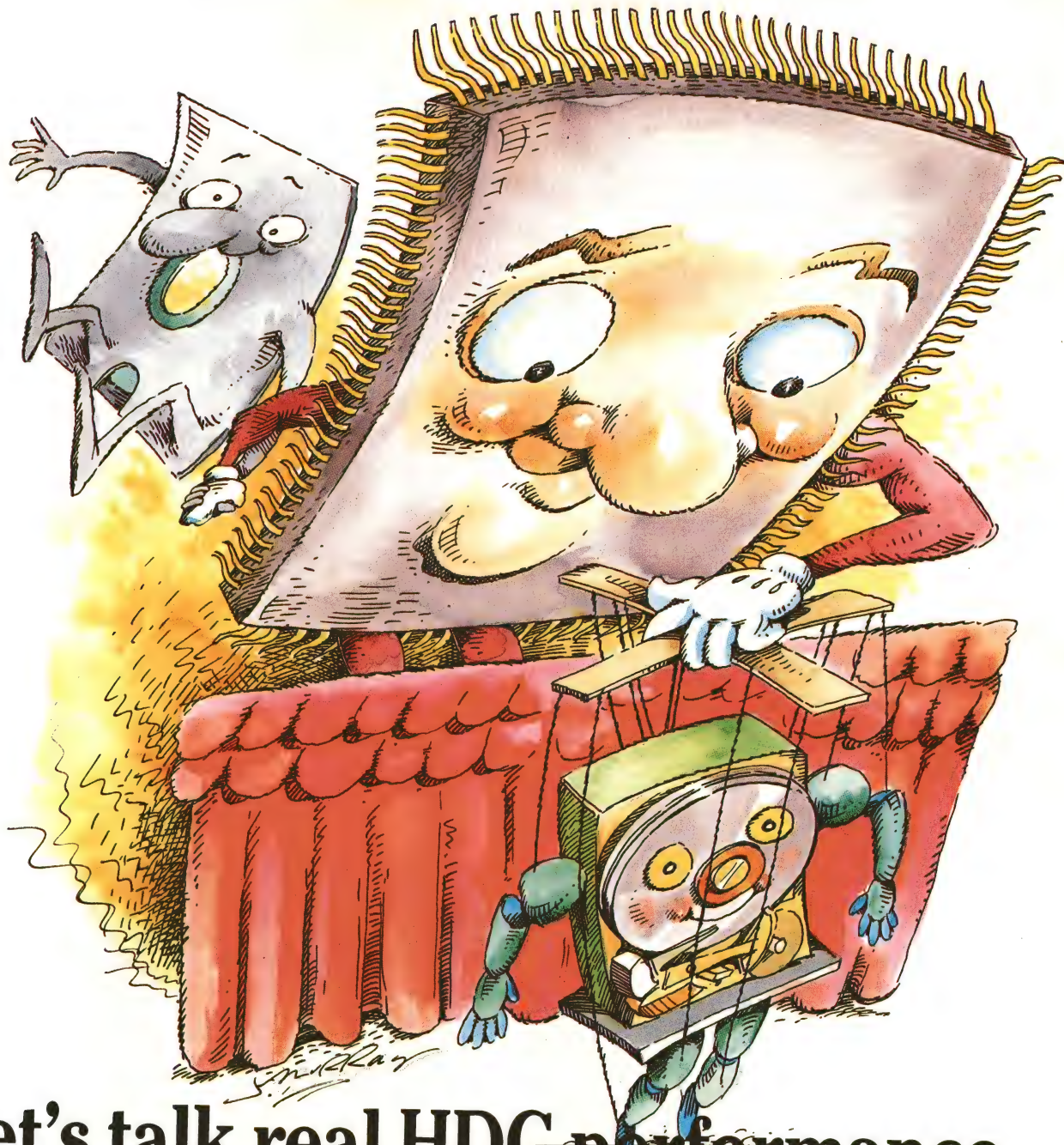1020 Carolina Drive, West Chicago, IL 60185
Telephone: 708-231-5505
Fax: 708-231-5577



Let's talk real HDC performance... That delivers 24 Mbits/sec with no wait states.

To compete today, you need all the extra performance and reliability to make your hard drive out-perform the others.

Blistering Speed

The LD1111 is 150% faster than anyone else. That means you get a full 24 Mbits/sec data transfer rate. Enough to set you ahead of the pack.

Dual Format

The LD1111 supports both ST506/412 and ESDI formats. It's also fully compatible with existing controllers and support chips.

Design Flexibility

The LD1111 is the only controller designed for embedded or surface mounting applications. It has a variable buffer size of from $2K \times 8$ to $64K \times 8$, and gives you no wait state 1 to 1 interleave. It's fully AT bus compatible, and can drive up to a 1 Gbyte hard drive.

Build Kits Available

Everything you need to design for MFM, RLL and ESDI controllers.

24-Hour Samples

We mean business. We'll turn your sample request around within 24 hours. And the call's on us.

Call Toll Free

1-800-272-8866

The Enhancement IC Specialists



550 E. Brokaw Road
San Jose, CA 95161-9048
Tel: 408-441-1615
Fax: 408-954-0727

array programmer, as well as the ability to download data to Data I/O and other popular programmers. To run the design tool you need an IBM PC/XT, PC/AT, or compatible computer that has 640k bytes of memory, IBM EGA/VGA or compatible graphics, and a mouse. \$695.

International CMOS Technology Inc., 2125 Lundy Ave, San Jose, CA 95131. Phone (408) 434-0678. **Circle No. 364**

Ada Development System For Transputers

- *Cross-compiler runs on DEC VAX computers*
- *Self-hosted compiler runs on Transputer board in IBM PC*

The company's Ada development system comes in two Transputer versions, both of which have been validated by the Ada Joint Program Office (AJPO). The cross-compiler runs on DEC VAX computers and generates code for the T8 Transputer; you can use the standard Occam tool set to download the executable code to the target processor. The self-hosted compiler runs on an auxiliary-processor board, which plugs into an IBM PC or compatible and is populated with T2, T4, or T8 transputers. You can run the executable code generated by the compiler on the auxiliary-processor board, using the I/O facilities of the PC; alternatively, you can download the code to a stand-alone Transputer system. Both compilers use standard optimization techniques, but in addition provide some Ada-specific optimizations, such as the elimination of redundant type-checking and the analysis of the call graph to eliminate uncalled code within a package. Self-hosted version, \$22,250; DEC VAX cross-compiler version, from \$30,000, depending on the host type and configuration.

Alslys Inc., 67 S Bedford St, Burlington, MA 01803. Phone (617) 270-0030. **Circle No. 365**

Telecomm Simulator

- *Simulates mixed analog and digital systems at block level*
- *Library has models of blocks for communications equipment*

TESS (Transient Electronic System Simulator) simulates mixed analog and digital systems at the block level. In particular, you can simulate microwave-radio and TV-transmission systems, codecs, PLLs, and most types of modulation. You can generate the free-format, Spice-like netlist with your text editor, which you can run from within TESS. For complex systems, you can use subcircuit models from the library of devices, including filters, mixers, and VCOs. You can also capture schematics created by CAE tools from OrCAD or P-CAD. To facilitate your use of these tools, the vendor can supply optional parts libraries of communication devices. The program can handle as many

as 800 blocks and 1000 nodes and can make use of a numeric coprocessor, if your computer has one. TESS performs simulation on all blocks concurrently, with no restrictions on feedback loops. For spectrum analysis, you have control over the resolution, span, and averaging; you can use FFTs with as many as 4096 points. In order to tweak the design without editing the circuit file, you can substitute your own parameter names for the model parameter values. TESS simulator, \$495; ModGen model generator, \$245; parts library for OrCAD SDT III, \$145; parts library for P-CAD MD-3, \$225. Educational institutions can obtain site licenses for 20 users at the price of two copies.

Tesoft, 205 Crossing Creek Ct, Roswell, GA 30076. Phone (404) 751-9785. FAX 404-664-5817.

Circle No. 366


In February, we'll introduce a 3-Terminal, Integrated Switching Regulator that will dramatically cut your design costs:

- no additional components
- no heat sinks
- surface mountable package
- 100% automated assembly

All in 1 Integrated Switching Regulator. Only from 1 company. And sampling in February.

If you can't wait that long, call Power Trends at 708-231-5505 for the details.

Shown actual size.

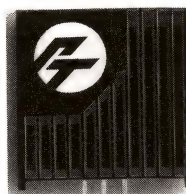

"Innovation in Power Technology."



POWER TRENDS

1020 Carolina Drive, West Chicago, IL 60185
Telephone: 708-231-5505
Fax: 708-231-5577

CIRCLE NO. 23

ASIC-Design Synthesizer


- Accepts input in VHDL or the Verilog language
- Produces a complete ASIC design you can fabricate in silicon

The ASIC Synthesizer will synthesize a complete ASIC design that you can fabricate in silicon. The package can accept input in either VHDL (VHSIC Hardware Description Language) or in Gateway's Verilog hardware-description language. Your design can be in the form of gate arrays, standard cells,


or optimized cell-based designs. The tool can evaluate the HDL description and determine the best solution for a particular set of constraints. By using product-specific compilers, the ASIC Synthesizer can implement a datapath, multiplier, and memory; by using the logic synthesizer, it can implement general-purpose logic. The tool will be released in three phases: Phase 1 (currently available) lets you synthesize complete chips, including I/O pad ring, logic, datapaths, and

memories, using a combination of behavioral and structural descriptions within the HDL; phase 2 (to be released in 1990) will recognize datapaths from the behavior within an HDL; and phase 3 (to be released in 1990) will recognize memory and other sequential elements, as well as datapaths. \$100,000.

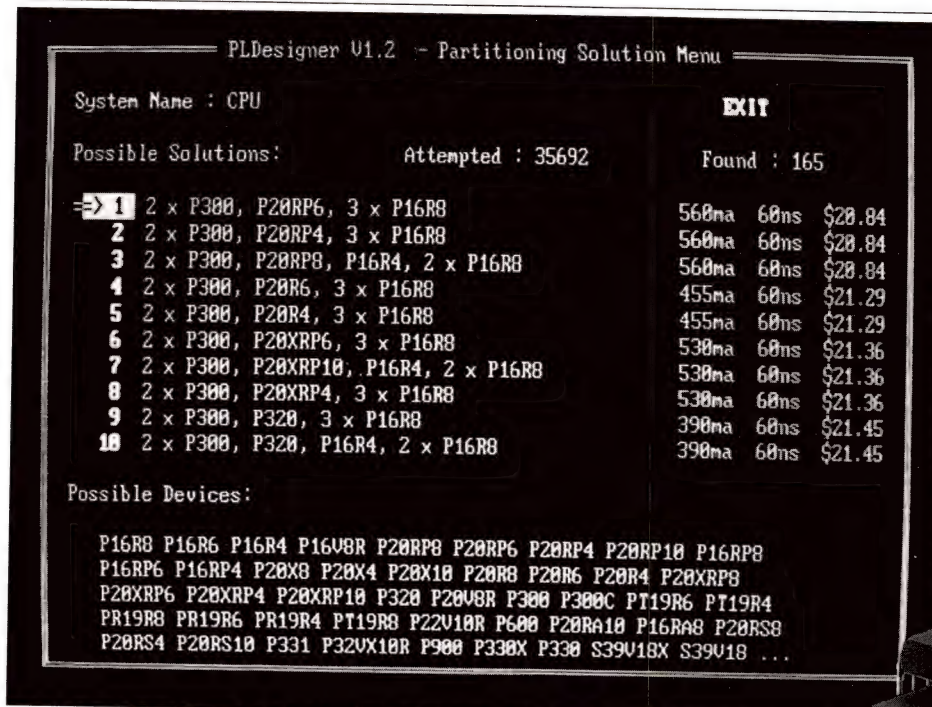VLSI Technology Inc., 1109 McKay Dr, San Jose, CA 95131. Phone (408) 434-3000. FAX 408-263-2511. **Circle No. 367**



PLDesigner uses your design philosophy when scanning its library of over 2500 different parts. Possible devices have architectures appropriate to implement the design. Attempted solutions are the combinations of possible devices. Of these combinations, 165 viable solutions were found. You can then choose from the top ten implementations displayed. Power consumption, propagation delay and estimated cost given for each solution ensure that the final implementation you select is the most rigorous solution for your design problem.

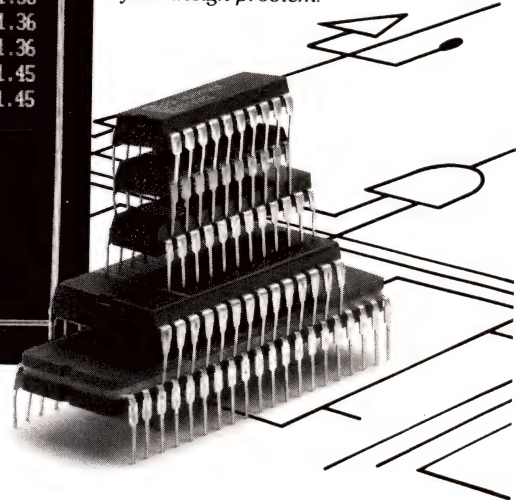

Synthesize and select your best PLD solution.

Only PLDesigner automatically generates multiple solutions for your design.


Whether you're new to PLD design or not, you'll benefit from PLDesigner's exclusive Architecture Mapping.

First enter, synthesize, and simulate your design using any combination of Minc's high-level language, schematic entry, or unique timing diagram entry. PLDesigner then automatically optimizes your design and selects the optimal device architectures, giving you solutions you may not have considered. Pick from the top ten solutions and PLDesigner will automatically

make pin assignments and, if required, automatically fit your design into multiple devices.

The intelligence of PLDesigner lets you concentrate on your design, without becoming an expert on hundreds of device architectures.

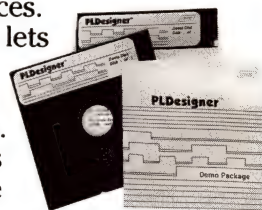To make PLD design as easy as multiple choice, call for your free PLDesigner demo disk now.



**6755 Earl Drive
Colorado Springs, CO 80918
719-590-1155 FAX 719-590-7330**


NEW PRODUCTS

TEST & MEASUREMENT INSTRUMENTS

10-kHz to 1.35- and 2.7-GHz Signal Generators

- Provide LCDs with fluorescent backlighting
- Step between frequencies in 1 msec

The 2030 signal generator covers frequencies from 10 kHz to 1.35 GHz; the 2031 extends the range to 2.7 GHz. Both units provide 0.1-Hz resolution. They incorporate a digitally controlled sweep capability and can step to a new frequency in 1 msec. You can adjust the RF output level of either instrument from -144 to +13 dBm with an accuracy of ± 1 dB. Optionally, the 2030's output extends to +19 dBm. The generators' user interface is based on menus that appear on a super-

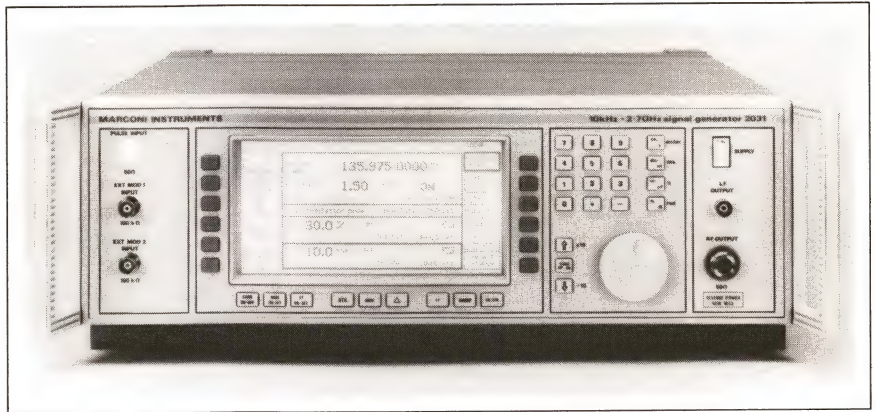


twist-LCD panel with fluorescent backlighting. The instruments allow modulation of their outputs with four simultaneous signals. Among the modulation modes are wideband FM, which on the 2031 allows 27-MHz deviation, and op-

tional pulse modulation with 15-nsec rise and fall times. From \$11,500. Delivery, six weeks ARO.

Marconi Instruments, 3 Pearl Ct, Allendale, NJ 07401. Phone (201) 934-9050. FAX 201-934-9229.

Circle No. 381

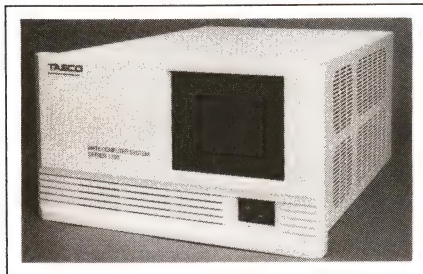


MATE-Compliant Computer System

- Includes hardware and software
- Expands by adding VME boards and 5 1/4-in. peripherals

The MCS-1700 computer system complies with the Air Force's MATE (Modular Automatic Test Equipment) standard. The hardware/software package is based on the MIL-STD-1750A instruction-set architecture. The CPU uses VME-bus boards and, therefore, expands in a modular fashion. The storage bays accommodate half-height 5 1/4-in. peripherals, making possible further modular expansion. The operating system, which is based on the MATE 5.0 operating system, supports four IEEE-488

buses and two SCSI disk drives. \$39,500.

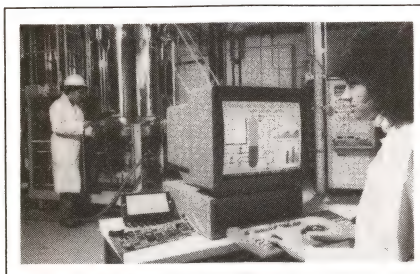Tasco Electronic Services Inc., 2121 W Crescent Ave, Anaheim, CA 92801. Phone (714) 635-0550. FAX 714-535-3458. **Circle No. 382**



Two Analog-I/O Cards

- One accepts 64 analog inputs
- Both provide 16 analog outputs

The RTI-220 analog-I/O board and the RTI-222 analog-output board plug into the IBM Micro Channel Architecture (MCA) bus. Each board provides 16 12-bit-resolution analog outputs derived from a single D/A converter; the RTI 220 also accepts 64 analog inputs and includes a 12-bit ADC capable of 21k conversions/sec. By use of external


signal-conditioning panels, the boards can provide either voltage or current outputs and can provide 1500V isolation between the computer-system ground and the loads. The vendor provides software drivers for several interpreted and compiled high-level languages, including Basic, Pascal, and C. RTI 220, \$650; RTI 222, \$450 (1 to 9).

Analog Devices Inc., 70 Shawmut Rd, Canton, MA 02121. Phone (800) 426-2564. **Circle No. 383**

50V Pulse Generator

- Provides 500-psec rise and fall times
- Produces pulses 20 nsec to 5 μ sec wide

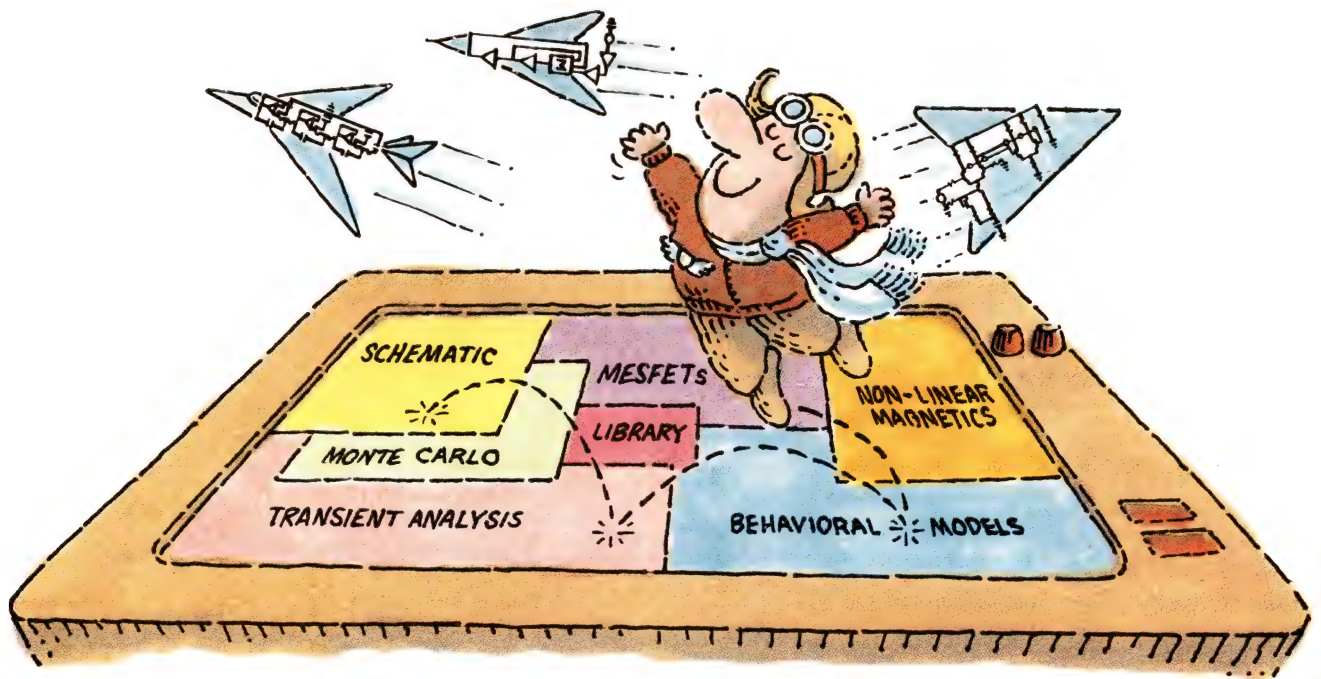The AVR-E2-C pulse generator produces 50V pulses with a rise and fall time of 500 psec and a width that you vary in two ranges from 20 nsec to 5 μ sec. The maximum pulse rate is 50 kHz. Companion models produce 20V pulses with 300-psec rise and fall times to 100 kHz and 100V pulses with 500-psec transitions to 20 kHz. The genera-




THE NEW MICRO-CAP III.™ SO YOU CAN TEST-FLY EVEN MORE MODELS.

It wasn't easy. But we did it. Made the long-time best-selling IBM® PC-based interactive CAE tool even better.

Take modeling power. We've significantly expanded math expression capabilities to permit comprehensive analog behavioral modeling. And, beyond Gummel Poon BJT and Level 3 MOS, you're now ready for nonlinear magnetics modeling. Even MESFET modeling.

Analysis and simulation is faster, too. Because the program's now in "C" and assembly language. That also means more capacity—for simulating even larger circuits.

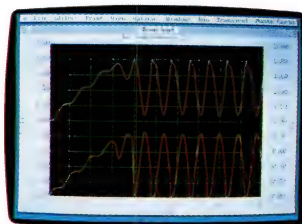
As always, count on fast circuit creation, thanks to window-based operation and a schematic editor. Rapid, right-from-schematics analysis—AC, DC, fourier and transient—via SPICE-like routines. The ability to combine digital/analog circuit simulations using integrated switch



Transient analysis



Schematic editor

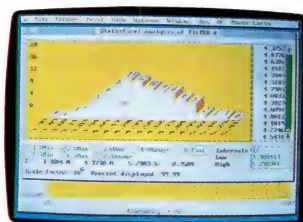

Monte Carlo analysis

models and parameterized macros. And stepped component values that streamline multiple-plot generation.

And don't forget MICRO-CAP III's extended routine list—from impedance, Nyquist diagrams and BH plots to Monte Carlo for statistical analysis of production yield. The algebraic formula parsers for plotting virtually any function. The support for Hercules, CGA, MCGA, EGA and VGA displays. Output for plotters and laser printers.

Cost? Still only \$1495. Evaluation versions still only \$150. Brochure and demo disk still free for the asking. Call or write for yours today. And see how easily you can get ideas up and flying.

spectrum

1021 S. Wolfe Road
Sunnyvale, CA 94086
(408) 738-4387

tors are available as ac-powered, stand-alone, benchtop units and as $1.7 \times 2.6 \times 4.2$ -in. modules that use 24V dc power and require an external TTL trigger. An optional terminal allows the insertion of dc offset voltages to ± 25 V. \$3552. Delivery, 60 days ARO.

Avtech Electrosystems Ltd, Box 265, Ogdensburg, NY 13669. Phone (315) 472-5270. **Circle No. 384**

der the same conditions, the ac-voltage accuracy is 0.02% of reading plus 0.01% of full scale from 40 Hz to 20 kHz. \$3695. Model 1362MT, compatible with the MATE (Modular Automatic Test Equipment) standard, \$3995. Delivery, six to eight weeks ARO.

Datron Instruments Ltd, Hurricane Way, Norwich Airport, Norwich NR6 6JB, UK. Phone (0603) 404824. **Circle No. 385**

Wavetek Corp, 9045 Balboa Ave, San Diego, CA 92123. Phone (619) 565-9234. FAX 619-565-9558.

Circle No. 386

VXIbus-Based Power-Supply Tester


- Includes ac and dc sources and electronic loads
- Has a multiplexer with 100-MHz bandwidth

The Powertest 8100I is a power-supply tester based on the VXIbus,

tem according to your requirements and keep it up to date as those requirements change. A frequency-selective voltmeter module measures peak and peak-to-peak voltages in seven frequency bands, and a peak detector/timer measures transient response with 100-nsec precision. From \$50,000. Delivery, 90 to 120 days ARO.

NH Research Inc, 16601 Hale Ave, Irvine, CA 92714. Phone (714) 474-3900. FAX 714-474-7062.

Circle No. 387

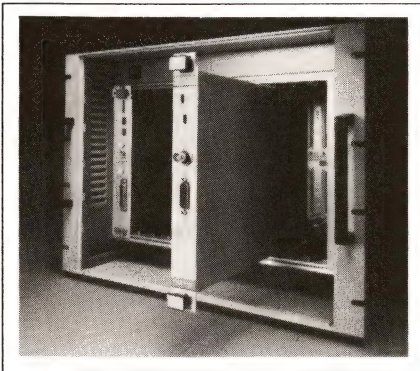


6½-Digit VXIbus DMM

- Fits in single-slot C-size module
- Incorporates isolated input to maximize noise rejection

The 1362 is a 6½-digit multimeter in a single-width, C-size VXIbus module. The unit enables systems based on the open-architecture instrumentation bus to make precise, accurate measurements of resistance and ac and dc voltage and current. To minimize the effects of noise originating in the digital portion of VXI systems, the meter has an isolated front end that makes possible a common-mode rejection ratio of 146 dB at dc, and when the integration period is synchronized with the ac line, the ratio is 134 dB at 50, 60, or 400 Hz. Normal-mode filtering can reduce line-frequency-related errors by an additional 20 dB. As a 6-digit dc instrument, the meter makes 5 readings/sec; with resolution reduced to four digits, the unit makes 1000 readings/sec. The dc-voltage accuracy is 5 ppm of reading plus 2 ppm of full scale on the 10V range at $23 \pm 1^\circ\text{C}$ for 24 hours after calibration. Un-



an open-architecture instrumentation bus derived from the VMEbus. The system can include single- and 3-phase ac sources, dc sources, and 500 and 2500W, high-current electronic loads. The loads, which you can connect in parallel for increased dissipation, operate in constant-current and -resistance modes and contain voltage- and current-metering circuits. Because of its open architecture, you can configure the sys-

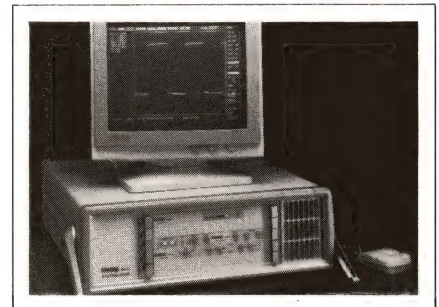

2G-Sample/Sec Waveform Digitizer


- Provides 63.5-dB (10.5-bit) dynamic range
- Can have 48 channels—12 at 2G samples/sec

The Series 2000 VMEbus-based waveform digitizer contains four 500M-sample/sec ADCs, each with a 330-MHz analog bandwidth; a 2k-word acquisition memory; and the ability to digitize with a signal-to-noise ratio of 63.5 dB (the equivalent of 10.5 bits). You can also configure the converters to acquire two signals at 1G sample/sec with 4k words of memory or one signal at 2G samples/sec with an 8k-word memory. You can expand the unit to contain 12 sampling modules with a total of 48 ADCs. A system with four channels and a 14-in. monitor costs \$22,500. Additional 4-channel modules, \$9950 each. Delivery, eight weeks ARO.

Analytek Ltd, 10261 Bubb Rd, Cupertino, CA. Phone (800) 366-5060; in CA, (408) 725-2560.

Circle No. 388

LITERATURE

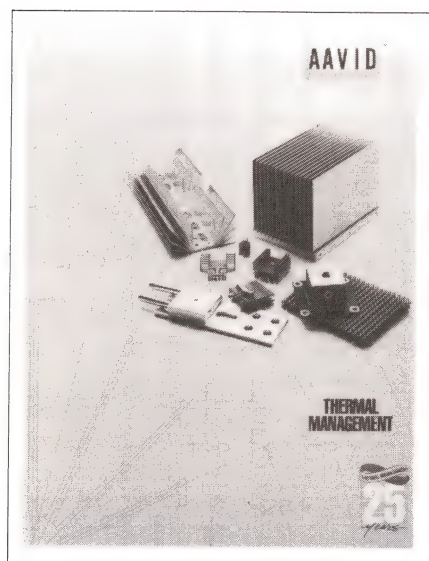

Heat sinks and extrusions surveyed

This 112-pg catalog describes the vendor's complete line of stamped and extruded heat sinks and accessories. The publication discusses a variety of shapes that handle various space requirements and heat-dissipation needs. The book contains a new parts-numbering system and highlights technical data on heat-sink selection, analyzing thermal performance, and labor-saving options. Among the thermal-management products described are capacitor clamps and brackets, "hockey-puck" clamps, spring clips, forced convection coolers, Quik Connect dual terminals, mounting insulators, washers and grounding lugs, and thermal-conductive adhesives and compounds.

Aavid Engineering Inc, Box 400, Laconia, NH 03247.

Circle No. 351


Two books detail two versions of Turbo Pascal

Turbo Pascal DiskTutor and *Object-Oriented Turbo Pascal: A new paradigm for problem solving and programming* provide comprehensive tutorials to help you learn object-oriented programming with the vendor's Turbo Pascal. *Turbo Pas-*

cal DiskTutor includes an updated version of Turbo Pascal 5.5, programming examples on disk, and a written tutorial providing complete instructions for learning Turbo-Pascal programming on your own. This version sells for \$39.95. The second book, *Object-Oriented Turbo Pascal*, is aimed at classroom instruction and costs \$9.95. A supplemental instructor's manual and a tutorial disk containing programming examples are available separately.

Borland International Inc, Box 660001, Scotts Valley, CA 95066.

INQUIRE DIRECT

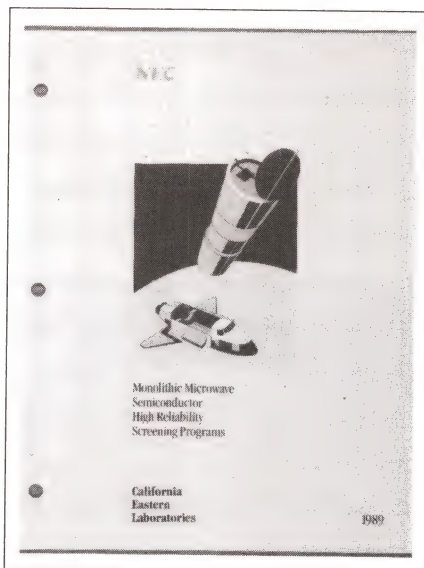

Screening procedure eases selection of ICs

The company's brochure describes screening and qualification procedures for NEC silicon monolithic-microwave ICs (MMICs), GaAs MMICs, and high-speed digital GaAs ICs. Also included are circuit elements such as transistors and resistors that meet MIL-STD-883. Reliability data for both chips and packages is presented for four grades: NEC Grade B—high reliability; NEC Grade C—military; NEC Grade CX—military; and NEC Grade D—industrial. Through the use of detailed processing information and flow dia-

grams, the brochure makes it easy to select reliability grades and complete specification-control drawings.

California Eastern Laboratories Inc, 3260 Jay St, Santa Clara, CA 95054.

Circle No. 352

Publication describes digitizing oscilloscopes

This brochure presents the Model HP 54120 Series digitizing oscilloscopes and time-domain reflectometry (TDR). The 34-pg publication discusses state-of-the-art applications and measurements, the Series' performance for computer-aided test applications, TDR, and the inside workings of the scopes, as well as numerous accessories. The 4-color booklet features the latest model, the 34-GHz HP 54123T.

Hewlett-Packard, Box 2197, Colorado Springs, CO 80901.

Circle No. 353

Service solves DRAM "timing" problems

Doctor Design's SuperSpec, a subscription service, contains tables of composite specifications from 12 manufacturers for 80-, 100-, 120-, and 150-nsec, 1M-bit dynamic RAMs (DRAMs) operating in a 1-pg mode. The publication provides a composite specification that lists every timing parameter for each manufacturer and a worst-case composite value. The product also gives basic information about the working of DRAMs, their timing cycles, and their design parameters, and shows how to derive the DRAMs' composite specifications. The vendor supplies a 3-ring binder to hold the periodic updates. \$195.

Academic Press, Harcourt Brace Jovanovich, Publishers, 1250 Sixth Ave, San Diego, CA 92101.

INQUIRE DIRECT



Most X.25 controllers are real dummies. At Themis we taught ours to talk.

Themis network-proven software brings reliable WAN communications to the VME bus. Get your system talking X.25 in nothing flat!

Themis' X.25 controller cut its teeth on some of the world's toughest packet switching networks. Certified to the rigorous standards of Germany's DATEX-P network, the TSVME 541 with proprietary X.25 software from Themis has proven itself on every major European network.

And boy, can this fellow talk: 225 Kbps link level on each of two channels, or 400 128-byte packets/s at a 64 Kbps line rate. All three levels of the X.25 protocol (CCITT rev. '84) are supported.

Drivers for Unix, OS-9, VRTX kernel and Ready Systems Velocity 2.2 Network Environment make it easy to get your VME applications on-line. Plug and play with Sun® using Themis' Sun O/S drivers. For performers who prefer custom software, Themis has a robust, hardworking Bus Interface Protocol to make driver development a snap.

Get smart with X.25. Give Themis a shout.

Call (415) 734-0870, FAX (415) 734-0873, or
in Europe, 33 1 69.86.15.25, FAX 33 1 64.46.45.50

Americas: 6681 Owens Drive, Pleasanton, CA 94588
Europe: 29, Av. de la Baltique, 91953 Les Ulis Cedex-France



EDN's CHARTER

EDN is written for professionals in the worldwide electronics industry who design, or manage the design of, products ranging from circuits to systems.

EDN provides accurate, detailed, and useful information about new technologies, products, design techniques, and careers.

EDN covers new and developing technologies to inform its readers of practical design matters that will be of concern to them at once or in the near future.

EDN covers new products

- that are immediately or imminently available for purchase
- that have technical data specified in enough detail to permit practical application
- for which accurate price information is available.

EDN's Magazine Edition also provides specific "how to" design information that its readers can use immediately. From time to time, **EDN's** technical editors undertake special "hands on" engineering projects that demonstrate **EDN's** commitment to readers' needs for useful design information.

EDN's News Edition also provides comprehensive analysis and news of technology, products, careers, and distribution.

EDN

275 Washington St
Newton, MA 02158
(617) 964-3030

BUSINESS/CORPORATE STAFF

Peter D Coley
VP/Publisher
Newton, MA 02158
(617) 964-3030; Telex 940573
Ora Dunbar, Assistant/Sales Coordinator

Mark J Holdreith
Associate Publisher/
Advertising Sales Director
Newton, MA 02158
(617) 964-3030
Heather McElkenny, Assistant

Deborah Virtue
Business Director
Newton, MA 02158
(617) 964-3030

NEW ENGLAND
Chris Platt, Regional Manager
Clint Baker, Regional Manager
199 Wells Ave
Newton, MA 02159
(617) 964-3730

STAMFORD 06904
George Isbell, Regional Manager
8 Stamford Forum, Box 10277
(203) 328-2580

NEW YORK, NY 10011
Daniel J Rowland, Regional Manager
249 West 17th St
(212) 463-6419

PHILADELPHIA AREA
Steve Farkas, Regional Manager
487 Devon Park Dr, Suite 206
Wayne, PA 19087
(215) 293-1212

CHICAGO AREA
Greg Anastos, Regional Manager
Jack Johnson, Regional Manager
Hollis Gronset, Telemarketing
Cahners Plaza
1350 E Touhy Ave, Box 5080
Des Plaines, IL 60017
(708) 635-8800

DENVER 80206
John Huff, Regional Manager
44 Cook St
(303) 388-4511

DALLAS 75243
Don Ward, Regional Manager
9330 LBJ Freeway, Suite 1060
(214) 644-3683

SAN JOSE 95128
Walt Patstone, Regional Manager
Bill Klanke, Regional Manager
Philip J Branon, Regional Manager
James W Graham, Regional Manager
3031 Tisch Way, Suite 100
(408) 243-8838

LOS ANGELES 90064
Charles J Stillman, Jr
Regional Manager
12233 W Olympic Blvd
(213) 826-5818

ORANGE COUNTY/SAN DIEGO 92715
Jim McErean, Regional Manager
18818 Teller Ave, Suite 170
Irvine, CA
(714) 851-9422

PORTLAND, OREGON 97221
Pat Dakin, Regional Manager
Walt Patstone, Regional Manager
1750 SW Skyline Blvd, Box 6
(503) 297-3382

UNITED KINGDOM/BENELUX
Jan Dawson, Regional Manager
27 Paul St
London EC2A 4JU UK
44 01-628 7030
Telex: 914911; FAX: 01-628 5984

SCANDINAVIA
Stuart Smith
27 Paul St
London EC2A 4JU UK
01-628 7030
Telex: 914911; FAX: 01-628 5984

FRANCE/ITALY/SPAIN
Alasdair Melville
c/o Editions J C B
Bureau 443
14 Boulevard Poissonniere
75009 Paris France
(331) 45 23 22 04
Fax: (331) 42 46 84 43
Telex: 648245

WEST GERMANY
Wolfgang Richter
Sudring 53
7240 Horb/Neckar, West Germany
49-7451-7828; Telex: 765450

AUSTRIA/SWITZERLAND/BAVARIAN GERMANY
Hans Haller
Preysingstrasse 30
8000 Munich 80 West Germany
(49) 89 48 8054
Fax: (49) 89 47 080 73; Telex: 523297

ISRAEL
Asa Talbar
Talbar Media
5 Bnei Brit St
Jerusalem 95146 Israel
0222 8 083; Fax: 9722-247-403

FAREAST
Jack Kompan, Asian Director of Marketing
18818 Teller Ave, Suite 170
Irvine, CA 92715
(714) 851-9422; Telex: 183653

HONG KONG
John Byrne & Associates Ltd
1613 Hutchison House
10 HGarcourt Road
Central Hong Kong
Tel: 5-265474
Telex: 61708 WEDIN HX
Fax: 5-6106781

JAPAN
Kaoru Hara
Dynaco International Inc
Suite 1003, Sun-Palace Shinjuku
8-12-1 Nishishinjuku, Shinjuku-ku
Tokyo 160, Japan
Tel: (03) 366-8301
Telex: J2322609 DYNACO

KOREA
Seo Jeong-Gwon
Doo Bee International Ltd
Center Bldg
1-11, Jeong-dong
Choong-ku, Seoul Korea
02-776-2096
Fax: 02-755-9860
Telex: K27117 DOOBEE

**SINGAPORE/MALAYSIA/INDONESIA/THAILAND/
THE PHILIPPINES/AUSTRALIA/NEW ZEALAND**
Asia Pacific Media House PTE Ltd
Peter Cheong
100 Beach Rd
#24-03 Shaw Tower
Singapore 0718
Tel: 2915354; Telex: RS 50026 MESPLY

TAIWAN
Acteam International Marketing Corp
6F, No 43, Lane 13
Kwang Fu South Rd
Mailing Box 18-91
Taipei, Taiwan ROC
760-6209 or 760-6210
Telex: 29809; FAX: (02) 7604784

PRODUCT MART
Joanne Dorian, Manager
249 West 17th St
New York, NY 10011
(212) 463-6415

INFO CARDS
Donna Pono
Newton, MA 02158
(617) 558-4282

CAREER OPPORTUNITIES/CAREER NEWS
Roberta Renard, National Sales Manager
103 Eisenhower Parkway
Roseland, NJ 07068; (201) 228-8602

Janet O Penn, Eastern Sales Manager
103 Eisenhower Parkway
Roseland, NJ 07068; (201) 228-8610

Paula Compton, Western Sales Manager
18818 Teller Ave, Suite 170
Irvine, CA 92715; (714) 851-9422

Diane Philipbar, Sales Assistant
103 Eisenhower Parkway
Roseland, NJ 07068; (201) 228-8608

Wendy A Casella, Nan E Coulter, Aileen B Turner,
Advertising/Contracts Coordinators; (617) 964-3030

William Platt, Senior Vice President, Reed Publishing USA
Cahners Magazine Division
Terry McDermott, President, Cahners Publishing Co
Frank Sibley, Senior Vice President/General Manager,
Boston Division
Tom Dellamaria, VP/Production & Manufacturing

Circulation: Denver, CO: (303) 388-4511
Eric Schmierer, Group Manager

Reprints of **EDN** articles are available on a custom printing basis at reasonable prices in quantities of 500 or more. For an exact quote, contact Joanne R Westphal, Cahners Reprint Service, Cahners Plaza, 1350 E Touhy Ave, Box 5080, Des Plaines, IL 60018. Phone (312) 635-8800.

Now You Can Make Important Component Selection Decisions Faster and Easier than You Ever Imagined!



INTRODUCING CAHNERS CAPS ON THE SUN-3™ FAMILY OF WORKSTATIONS.

THIS NEW, PRODUCTIVITY-
BOOSTING ENGINEERING
TOOL AUTOMATES,
ACCELERATES, AND
OPTIMIZES THE SELECTION
OF INTEGRATED CIRCUITS
AND SEMICONDUCTORS.

**CAPS WILL CHANGE THE WAY
YOU WORK!**

Imagine having up-to-date information on more than 425,000 devices from over 375 manufacturers worldwide at your fingertips.

Think about instantly accessing crisp, clear, unabridged images of manufacturers' datasheets, with the same text, tables, and graphics found in the printed versions.

Consider applying the power of menu-driven parametric searches that can identify devices which conform to your specifications.

This is CAPS. It's new. It's different. And it gives you all the information you need to make critical component selection decisions.

Available on a subscription basis and updated every month, CAPS comes complete with a four-disc CD-ROM reader, ready to install on your Sun® engineering workstation.

Learn more about how CAPS can take the drudgery out of your component selection process. Call or write:

CAHNERS
CAPS
Computer Aided
Product Selection

Cahners Technical Information Service
275 Washington Street
Newton, Massachusetts 02158-1630
Telephone: 617-558-4960
Facsimile: 617-969-6949
Telex: 940573
Toll-free: 1-800-245-6696

CIRCLE NO. 123

The Fine Cultured SMD Transformers

ISDN has revolutionized global communications. By enabling transmission of digitalized information signals, we now enjoy benefits from G4 facsimiles to video telephones and high-speed personal computer communications.

Matching exchange and terminal equipment with intermediate circuits requires transformers capable of transmitting pulse signals with start-up and transient response characteristics.

To keep up with state-of-the-art miniaturization,

the DC-DC converters and AC-DC isolation chokes that support communications equipment must provide not only improved performance, but also thinner, more compact configurations. On the leading edge of technological breakthroughs, TOKIN has developed an extensive line of surface mount transformers, for applications from

DC-DC converters to pulse transformers.

But we don't stop there. TOKIN **SMD (Surface Mount Devices) Transformers** can be designed for a vast range of functions and purposes, from high density mountings, to low height installations, DC-DC converters and pulse

transformers. All part of our never-ending search for the best materials, most innovative designs and the ideal magnetic circuit.

TOKIN. The cutting edge in transformer technology.

Call us now.

Features


- Thin, compact configurations are ideal for high-density mounting
- Flawless magnetic circuit designs offer high-inductance characteristics
- SMD discrete combined-use multi-terminal structure

Applications

- DC-DC converters, pulse transformers, various ISDN response equipment and communications equipment

Shapes and Dimensions

FEY9.1/7.3	FEY12.8/11.5	FED 6	FED 11.6	FEP 7T

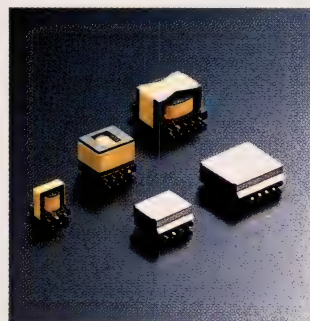

TOKIN

Tokin Corporation

Hazama Bldg., 5-8, Kita-Aoyama 2-chome, Minato-ku, Tokyo 107, Japan
Phone: 03-402-6166 Fax: 03-497-9756 Telex: 02422695 TOKIN J

Tokin America Inc.

155 Nicholson Lane, San Jose, California 95134, U.S.A.
Phone: 408-432-8020 Fax: 408-434-0375

Chicago Branch

9935 Capitol Drive, Wheeling, Illinois 60090, U.S.A.
Phone: 312-708-8802 Fax: 312-708-8804

Tokin Electronics (H.K.) Ltd.

Room 806 Austin Tower, 22-26A Austin Avenue, Tsimshatsui, Kowloon, Hong Kong
Phone: (3) 679157-9 Fax: (3) 7395950

Taiwan Liaison Office

7-F-2, No. 200, Sec. 3, Hsin-Yi Road, Taipei
Phone: (02) 7059310-1 Fax: (02) 7015650

München Liaison Office

Elisabethstraße 21, 8000 München 40, Bundesrepublik Deutschland
Phone: (089) 271 75 22 Fax: (089) 271 75 67
Telex: 5 24 537 tokin d

You can reach our agents by phone: Denmark (03) 63 3830; France (1) 45-34-7535; Italy (0331) 67-8058; Spain 729-1155; Switzerland (01) 830-3161


EDN PRODUCT MART

This advertising is for new and current products.

Please circle Reader Service number
for additional information from manufacturers.

Best value in a programmer you will ever find . . . anywhere

For example, the model shown here is fully Universal and is stand alone or remote controlled and offers these features: Programs & Tests ANY Logic, Memory or Micro device type in ANY package type up to 128 pins • Performs Functional and Signature Tests • Has 40 programmable pin drivers standard • Has Serial, Hi Speed Parallel and Handler ports • Super Fast Batch & Set modes • Device Library updates by Floppy Disk (two free) • SGAPL Logic Compiler & R/C software included • IC MANUFACTURER APPROVED • Many other features . . . \$2,750.00

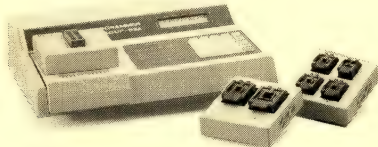

FREE Demo Disk and Benchmark™ will guide you in making the right selection (even if it is not ours)

**SYSTEM
GENERAL**

SYSTEM GENERAL Corporation
510 South Park Victoria Drive
Milpitas, CA 95035

Tel: 408-263-6667 • Fax: 408-262-9220

CIRCLE NO 325



**MY
FIRST
PAL
DESIGN**
Primer for
Primary
PAL
Designers

FREE! Logical's 40-pg. booklet is not intended to be a manual, but rather a guide through the basics--to help break the ice when you start your first PAL design. Easy to read diagrams make this a must for first-timers. For your free copy, ask for Sharon.

305-974-0967

**LOGICAL
DEVICES, INC.**

CIRCLE NO 326

VMEbus Signal/Image Acquisition and Processing

- **ICS-100** — 4-Channel Data Acquisition, Digital Filtering and Analog Output Board.
- **ICS-105** — 256-Channel Versatile Digital Filter Board.
- **ICS-200** — 384-Tap High-speed FIR Filter Board.
- **ICS-220** — Image Acquisition, Processing and Display Board.

— SunOs Drivers Available —



INTERACTIVE
CIRCUITS AND
SYSTEMS LTD.

Call Toll-Free 1-800-267-9794
or 613-749-9241

CIRCLE NO 327

A NEW Way To DEVELOP & TEST PC CARDS


Innovative PC extender card.

- Works with 8/16 bit buss.
- Allows to insert and remove tested cards without turning power off.
- Saves testing and debugging time - no rebooting and reloading of the test program.
- Overcurrent sensing and protection.
- 3" x 3" breadboard area with decoded I/O address for expansion.
- Hardware and software control and status interface.
- Takes 8 bits of I/O space at any of 14 different locations.
- Buss signals available at the top edge connector and at pin header.
- More

Call for information:
1 - 415 - 254 - 5400

AZCOM • 12 Rose Lane # 104 • Orinda, CA • 94563

CIRCLE NO 329

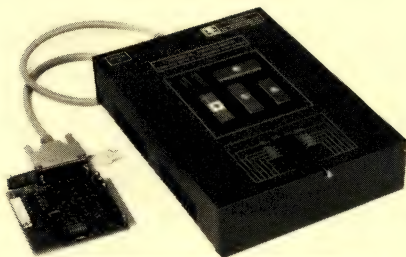

**PC BASED UNIVERSAL
DEVICE PROGRAMMER**

\$595-845

- Programs EE/EPROMs, PALs, GALs, IFLs, EPLDs, MICROS, BIPOLARS.
- Software driven pin drivers. DiA generated programming voltages (8 bit DACs used to generate voltages from 5.25V with 0.1V resolution for all 40 pins)
- Upgradable for virtually any future programmable devices up to 40 pins.
- Self substituent operation. No additional modules or plug-in adapters required.
- Includes user friendly MEMORY BUFFER FULL SCREEN EDITOR.
- Commands include: Fill, Move, Insert, Delete, Search, ASCII or HEX entry.
- Friendly Menu-Driven interface. Device selection by P/N and manufacturer.
- Supports 8/16/32 bit; data word formats.
- Programming algorithm: Normal, Intelligent I&II, Quick Pulse Programming.
- Verify operation performed at normal & worst case operating voltage.
- Functional test: JEDEC standard functional testing for logic devices.
- TTL Logic functional test for 74xx/54xx series devices.
- File formats accepted: JEDEC (full), JEDEC (kernel), Straight Hex, MOS Technology, Motorola Hex, Intel Hex, Tektronix Hex.
- Customer support via voice line, fax & dedicated BBS. Full 1 year warranty.
- Base price (\$595) includes Interface card, cable, Memory device library and 1 year free updates. Additional Device Libraries (Logic, Micros, Bipolars) \$95ea.
- Library updates can be received via floppy or Customer Support BBS.

MC / VISA / AMEX

Call today for datasheets!



B&C MICROSYSTEMS INC.
355 West Olive Ave, Sunnyvale, CA 94086 USA
TEL: (408) 730-5511 FAX: (408) 730-5521

CIRCLE NO 328

Don't Get Zapped!

High inrush current can **destroy** your sensitive VAX CPUs and peripherals in less time than it takes to flip a switch.

THE SOLUTION?

Power up with **Z-LINE** TPC 115-10 MTD™ the smallest power distribution and control system available.
POWER UP WITH — — —



Our proprietary **Multiple Time Delay™** circuitry sequences your power-up to **protect** your systems from the spikes and surges, EMI & RFI, that **destroy** your hardware and **erase** your data. And our remote on/off and emergency shutdown **gives** the power control back to you.


All Pulizzi Engineering MTD™ controllers are compatible with DEC and UPS systems.
PRICES FROM \$436 TO \$305

DON'T WAIT UNTIL IT HAPPENS, CALL TODAY!

PULIZZI ENGINEERING INC.
3260 S. Susan Street, Santa Ana, CA 92704-6865
(714) 540-4229 FAX (714) 641-9062

CIRCLE NO 330

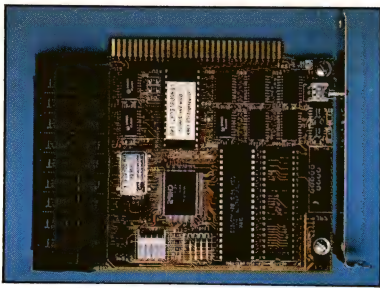To advertise in Product Mart, call Joanne Dorian, 212/463-6415



TURBO XT CPU BOARD

- PC BUS, 4.2" x 5.4" (4 Layer)
- Compatible with MS-DOS 2.0 - 3.X
- Dual speed (4.77 MHz/10 MHz) CPU
- Up to 2 Meg DRAM on board (SIMMs)
- Includes EMS 4.0 Memory Manager
- Processor: V20 Coprocessor: 8087
- \$320 qty. 1; \$160 qty. 10

295 Airport Road
Naples, FL 33942



1-800-634-0701 **TEMPUS TECH, INC.**

CIRCLE NO 331

A-BUS™

DATA ACQUISITION AND CONTROL

**Low Cost A/D, Motion Control, Relays,
D/A, Digital I/O, Counters...**

Sample Applications:
Read sensors:
voltages, light levels,
temperatures, keypads,
touch-tones; Switch
electrical devices;
Automate experiments;
Test equipment.

Some products:
RE-140: Relays, 8 SPST.....\$142
FA-154: 12-bit 8-channel A/D, 10µs.....\$179
IN-141: 8 Optoisolated inputs.....\$65
AD-142: A to D, 8 bit, 8 channel.....\$142
SC-149: Stepper Motor Controller, 4 Axis, with
microprocessor.....\$299


**Bus adapters for: PC/XT/AT & compatibles: Apple
II; Tandy and others. Or use RS-232 serial
adapters for remote applications**

Call for catalog: (203) 656-1806
Mon-Fri 9-5 Eastern time (or Fax 203 656-0756)

ALPHA Products
"Innovation through Application"
242-E West Avenue, Darien, CT 06820

CIRCLE NO 332

ECONOMICAL MINIATURE GEARHEAD

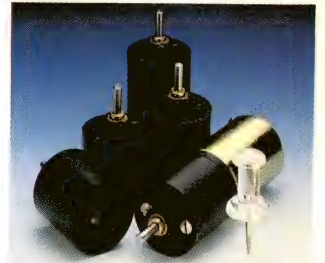


Sample quantities of a new series of economical precision gearheads are now available for immediate delivery. Micro Mo brand 16-22mm diameter gearheads will fit System Faulhaber brand as well as many competitive motors. Sintered and ball bearing versions are available in ratios from 9:1 to 5,752:1 with efficiencies of up to 81%. Such products are ideal for OA, instrumentation, pumps and monitoring devices, and precision modeling.

Micro Mo ELECTRONICS INC.

742 2nd Avenue South, St. Petersburg, Florida 33701 USA
Phone: 813/822-2529 / Telex: 807-982

CIRCLE NO 333

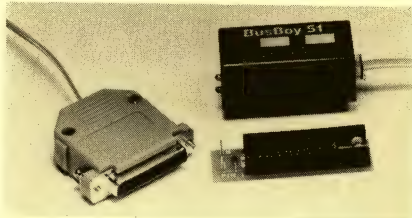

HARDWARE DEBUGGER

The BusBoy51 is a new in-circuit debugging tool for 8051 based boards. Useful in both prototype and production testing, it will help isolate wiring errors and component failures. The BusBoy 51 is menu driven with a serial interface to the operators terminal. It provides preprogrammed tests for 8051 memory and I/O, detecting stuck and shorted address or data bits. The BusBoy 51 is powered by the target system and autobauds. Use the BusBoy 51 to verify prototypes, test failed boards to isolate the memory or buffer chip responsible, final check production boards for proper memory and I/O operation.


BusBoy C51	\$389.00	51H	\$349.00
------------	----------	-----	----------

CALL (315) 478-0722 FAX (315) 475-8460

Logical Systems Corporation
P.O. Box 6184, Syracuse NY 13217-6184 USA
TLX 6715617 LOGS

CIRCLE NO 334

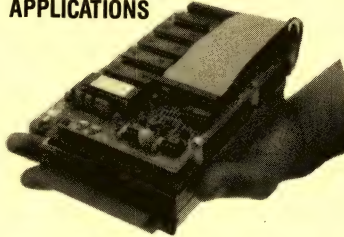COMPLETE DEVELOPMENT SYSTEM FOR MACHINE CONTROL APPLICATIONS



TINY188 is a low cost "PC somewhat compatible" engine for OEM controller applications. A selection of high level languages is available in ROM.

DDS188 An optional development board with EPROM programmer, floppy disk controller and added memory, removes to lower target system cost.

Prices start at \$269 each/\$129 at 1,000.

Vesta Technology, Inc.
(303) 422-8088

CIRCLE NO 335

Combine Your Product Mart Ads

In EDN's Magazine
and
News Editions for
higher impact and a
lower rate.

CIRCLE NO 336

27C512 AND 27C1001* IN-CIRCUIT EPROM EMULATOR

Emulate JEDEC 28-pin and 32-pin EPROMs (27C64, 27C128, 27C256, 27C512, etc.).

\$475/\$625*

Intelligent monitor in firmware allows you to download the output of your assembler or compiler directly into target EPROM socket at rates to 38.4K bits/sec via PC COM port

- Accepts Intel extended hex, Motorola S, TI, and straight binary formats.
- Examine, fill, modify, copy, search, upload, memory dump commands in firmware.
- 100 ns access time standard—faster available.
- Reset target processor from keyboard.
- PC based communications software included.

Call or write for detailed product information and prices.



Developed and
manufactured in the USA

Phone (214) 242-0450
FAX (214) 245-1005
1301 N. Denton Drive
Suite 204
Carrollton, TX 75006



CIRCLE NO 337

UNIVERSAL PROGRAMMER

@programs

E(E)PROM,

PAL,EPLD,

GAL,PEEL,FPL,

BIPOLAR,

8748/51 SERIES.

@tests TTL/CMOS

D/S RAM.

\$585 Complete. (u.s. only)

- programs E(E)PROMs upto 2Mbits and 16 Bit wide.
- 16Bit- and 32Bit- WORD SPLIT & 4-GANG adaptor.
- programs PALs (22V10) from AMD,MMI,TLS,SAMSUNG.
- supports PALASM,UCPL,ABEL,ORCAD JEDEC files.
- supports VERIFICATION using TEST VECTORs.
- programs GALs & FPLs from LATTICE,SGS,NS,SIGNETICS.
- supports RALs in GAL (16V8,20V8) devices.
- programs EPLDs from INTEL,ALTERA,ATMEL,CYPRESS.
- programs PEELs from ICT,HYUNDAI,GOULD(253,273).
- programs BIPOLAR PROMs.
- programs SINGLECHIPS 8748,8751,87C51 SERIES including 87C451,87C751,63701X/V,63705V with adaptors.
- tests ICs (TTL,CMOS) & MEMORYs (upto 1MB).
- with USER-DEFINABLE TEST PATTERN GENERATION.
- High-Speed,Parallel Interface & S/W Upgradable for New Parts.

XELTEK

1-800-541-1975 (Toll Free Order)

473 SAPENA CT. #26

TEL: (408) 727-6995


SANTA CLARA,

FAX: (408) 727-6996

CA 95054

COD,VISA,MC,AMEX

CIRCLE NO 338

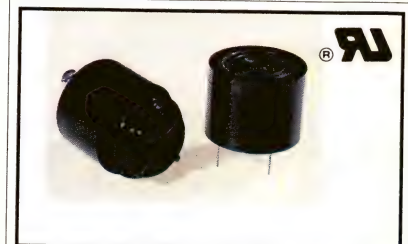

Chime and Warble Tone Piezo Alarms

Improved chime tone piezo alarm faithfully reproduces pleasant sound of small bell with attention getting output to 93dB @ 2ft. 1 or 2 chimes, per sec. Optional volume control; warble tone alarm has more aggressive but not abrasive 2Hz, 2 tone warble to 95dB @ 2ft. Alarms have low, 2200 Hz center freq. 5 Vdc-220 Vac, PC or panel mount. Opt manual shutter vol. control. Recog. components U.L. listed.

USA made by

Floyd Bell, Inc.

Box 12327, Columbus, OH 43212
614-294-4000 FAX: 614-291-0823

CIRCLE NO 339

To advertise in Product Mart, call Joanne Dorian, 212/463-6415

LOW BUDGET SPECIALS

19" COLOR SUPER VGA MONITORS
 LIKE NEW -- 6-MONTH WARRANTY \$800.00
 USED -- 3-MONTH WARRANTY \$600.00
 USED WITHOUT CASE \$300 TO \$500.00
19" COLOR SONY 1280X1024 \$1600.00

THESE SONY TRINITRONS
 HAVE A FULL 6-MONTH PARTS
 AND LABOR WARRANTY.
 LIMITED QUANTITY.

16" Ikegami 64 kHz 1280X1024
 New \$899.00

16" Panasonic 64 kHz
 Used \$599.00


14" Ikegami TTL VGA chassis, New, 1-year warranty \$249.00

19" PHILIPS 1024x800 48 kHz GRAYSCALE . . \$350.00
 NEW, 1-YEAR WARRANTY. MAY BE ORDERED FOR VGA AT
 NO EXTRA CHARGE. IN VGA MODE, WILL RUN 800X600X256
 GRAYSCALE, OR 1024X768X16 GRAYSCALE ONLY.

CALL US ABOUT OUR LARGE VARIETY OF GRAPHIC CARDS!

194 Main Street Marlborough MA 01752

CIRCLE NO 340

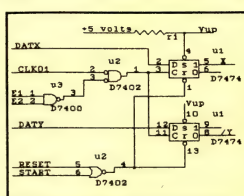

SuperCAD™
 Schematic entry
 Software
 for the IBM PC &
 Compatibles
 ONLY

\$99.00

COMPLETE PACKAGE

- ★ Easy-to-use schematic entry program for circuit diagrams, visible on-screen and pull down menus
- ★ Supports popular graphic standards, mice and printers
- ★ Powerful editing and drawing commands
- ★ Extensive digital, analog and discrete part libraries
- ★ In-depth, readable instruction manual
- ★ Can be used for flow charts and timing diagrams
- ★ Software includes part building, and netlisting
- ★ A compatible P.C. board layout software (\$99) and routing software (\$99) available

Write or call for demo disk:


MENTAL AUTOMATION, INC.

ORDERS/INFORMATION:

Send check or money orders to:

Mental Automation, Inc., Dept. S-9, 5415 136th Place S.E.,
 Bellevue, WA 98006 or call (206) 641-2141
 Visa/MasterCard orders accepted!
 Dealer inquiries welcomed.

CIRCLE NO 343

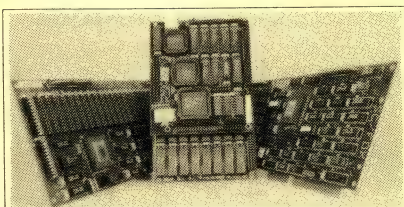

SC/FOX™ High-Speed Embedded Systems Controllers

SC/FOX PCS32 (Parallel Coprocessor System) 32 MIPS,
 70 MIPS burst, general purpose PC/XT/AT/386 32-bit plug-in
 board, 64K-1M byte 0-wait state memory, uses 32-bit SC32
 RISC microprocessor.

SC/FOX SBC (Single Board Computer) 18 MIPS, 60 MIPS
 burst, uses 16-bit Harris RTX 2000, for stand-alone or embedded
 operation, 100x160mm, 1 serial, 1 printer port, 32K-512K bytes
 0-wait state memory.

SC/FOX PCS (Parallel Coprocessor System) 15 MIPS, 50
 MIPS burst, general purpose PC/XT/AT/386 plug-in board, 32K-
 1M byte 0-wait state static memory, multiple board operation,
 uses Harris RTX 2000.

SC/FOX SCSI I/O plug-on PCS or SBC daughter board with
 SCSI, floppy, serial, and parallel ports, and driver software.


Ideal for embedded real-time control, data acquisition, and signal
 processing. Forth development software included. OEM pricing.

SILICON COMPOSERS INC (415) 322-8763
 208 California Ave., Palo Alto, CA 94306

CIRCLE NO 346

EDN Product Mart Provides Consistent Results

CIRCLE NO 341

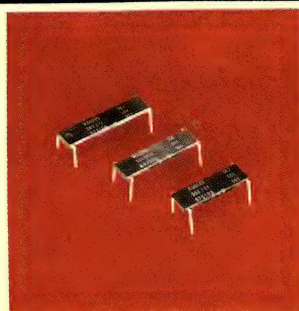

MICRO/Q 2000

FOR A DECOUPLING CAPACITOR THAT SAVES
 SPACE, DEFEATS NOISE, IS SUITABLE FOR
 MILITARY APPLICATIONS AND BEATS
 HUMIDITY, HEAT AND COLD:

ROGERS MICRO/Q® 2000


Rogers Corp., 2400 S. Roosevelt,
 Tempe, AZ 85282. 602/967-0624

CIRCLE NO 344

DATA ACQUISITION CONTROLLER

Now for the first time the 7200 combines intelligent
 hardware and software with high resolution analog
 I/O. Everything you need is on one STD Bus card.
 Easy to use STD BASIC III software supports all
 on-card hardware. Ideal for data acquisition,
 positioning, and motion control. Program
 development software available for PC.

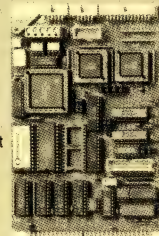- 12-bit, 8 channel A/D
- 12-bit, 2 channel D/A
- Supports 2 MB on bus
- 32 TTL I/O lines
- 1 RS-232 serial port
- 1 RS-232/422 serial port
- Keypad port
- Battery-backed RAM
- Watchdog timer
- EEPROM programmer



Call **303-430-1500** for more information.


OCTAGON SYSTEMS CORPORATION
 6510 W. 91st Avenue
 Westminster, CO 80030, Fax: 303-426-8126

CIRCLE NO 342

"Best Value" in PCB Design

Tango™ sets the pace in PC-based circuit board design
 with an easy-to-use, pop-up menu interface and
 powerful features including 1 mil resolution,
 full SMT support, DRC, Gerber and
 PostScript™ output, fast high-
 completion autorouter, and pho-
 toplot previewing. Configure
 your personal PCB design station
 from our selection of entry-level
 and expert tools, starting at
 just \$595.

Tango™

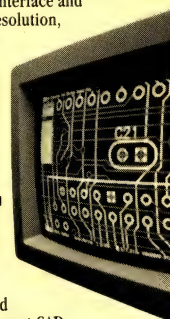

See for yourself why engineers rated
 Tango the "Best Value" in PCB design at CAD
 Showdown '89. Rich functionality, one year's
 updates, free tech support and BBS, plus our 30-day
 guarantee. Call today.



FREE EVALUATION PACKAGE

800 433-7801 619 554-1000 619 554-1019 Fax

ACCEL™ Technologies ■ 6825 Flanders Drive ■ San Diego, CA 92121 USA
 International prices may vary. Contact us for the distributor nearest you.

CIRCLE NO 345

MODEM COMPONENTS



- TELEPHONE LINE INTERFACE,
 DAA
 DOC, FCC, INTERNATIONAL
- ERROR CORRECTING AND
 DATA COMPRESSION
 MNP LEVEL 5
 X.25 LAP
- COMPLETE MODEM MODULES
 PRE-APPROVED
 2400, 1200 BPS
 AT COMPATIBLE



CERMETEK MICROELECTRONICS
 1308 BORREGAS AVE.
 SUNNYVALE, CA 94089

FAX # (408) 752-5004
 TEL # (408) 752-5000


CIRCLE NO 347

VISION 16 IMAGE CAPTURE

Vision 16 Cards:

LOW-COST

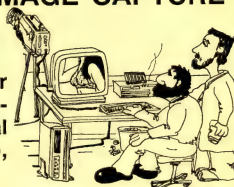solution to your
 imaging needs --
 works with Crystal
 3D, Lumena, Rio,
 Picture Power.



Board and Colorcheme I software list for
 \$1495.00 --

**Special OEM discounts for EDN
 readers: Please Call!!**


We also have 19-inch Ikegami
 monitors, perfect for image capture, at a
 Special OEM Price!

194 Main Street Marlborough MA 01752

CIRCLE NO 348

To advertise in Product Mart, call Joanne Dorian, 212/463-6415

Touch!

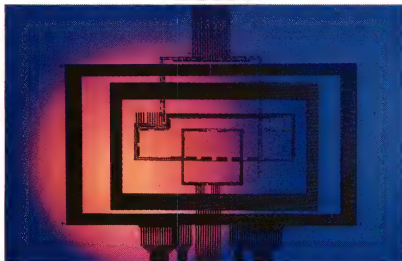

With monthly production of 50,000 units, we represent the world's largest matrix touch-panel manufacturer. And with 50-day delivery for custom parts, we may be the fastest. Our matrix, analog resistive and TekTouch sensors are ideal for any application.

We've got the best touch. Send drawings of your projects for a quotation and we'll prove it.

The Graphics Technology Company, Inc.
5524 Bee Caves Road
Austin, Texas 78746
FAX: (800) 962-3860
Phone: (512) 328-9284



CIRCLE NO 349

48 CHANNEL 25 MHz LOGIC ANALYZER



\$1595.00 + POD PRICE


- 48 Chnls @25MHz x 4K word deep/12 Chnls @100MHz
- 16 Trigger words/16 Level Trigger Sequence
- Storage and recall of traces/setups to disk
- Disassemblers available for: 68000, 8088, 8086, 80286, 6801, 6811, Z80, 8085, 6502, 6809, 6303, 8031

NCI □ 6438 UNIVERSITY DRIVE,
HUNTSVILLE, AL 35806
(205) 837-6667

CIRCLE NO 350

TAKE THE FAST TRACK

80C286 AT CMOS SINGLE BOARD COMPUTER

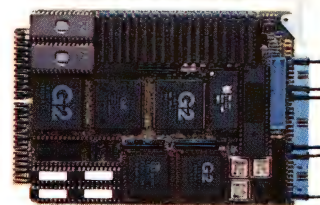


The TEK224 integrates a PC/AT type computer on a single STD Bus card. It features an 80C286 at 16Mhz with zero-wait state, 2 Mbytes of system memory, two serial ports, one parallel port, and consumes less than 6 watts.

P.O. Box 455
Ste-Thérèse (Québec)
Canada J7E 4J8
Tél.: (514) 437-5682
Fax: (514) 437-8053

TEKNOR
MICROSYSTEMS INC.
The right connection

CIRCLE NO 751

Worstcase at its Best!

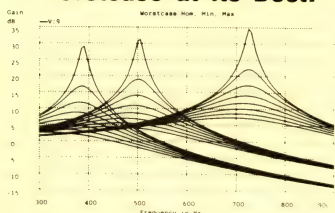


Analog Circuit Simulation

ECA-2 Electronic Circuit Analysis offers the best Monte Carlo and Worst-Case analyses with the capability to concurrently plot random samples or Min/Max/Nominal values.

- AC, DC, Transient
- Fourier, Temperature
- Sine, Pulse, PWL, SFFM, and Exponential generators
- Interactive/batch modes
- Full nonlinear simulator
- Over 500 nodes
- Multiple plots

• 2 to 50 times faster than SPICE

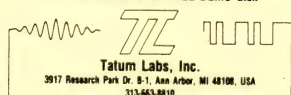ECA-2 2.50 IBM PC or Mac \$775
Call 313-563-8810 for FREE DEMO disk



Tatum Labs, Inc.
3917 Research Park Dr. B-1, Ann Arbor, MI 48106, USA
313-563-8810

CIRCLE NO 752

IEEE 488

*Easiest to use,
GUARANTEED!*

- IBM PC, PS/2, Macintosh, HP, Sun, DEC
- IEEE device drivers for DOS, UNIX, Lotus 1-2-3, VMS, XENIX & Macintosh
- Menu or icon-driven acquisition software
- IEEE analyzers, expanders, extenders, buffers
- Analog I/O, digital I/O, RS-232, RS-422, SCSI, modem & Centronics converters to IEEE 488

Free Catalog & Demo Disks
(216) 439-4091

IOtech

IOtech • 25971 Cannon Rd. • Cleveland, OH 44146

CIRCLE NO 753

Communicate Weekly

to the electronics
OEM through
EDN's Magazine
and News Editions
Product Mart

CIRCLE NO 754

EZ-WRITER™

(E)EPROM Multiprogrammer™

**DATA I/O 212* Performance
For Only \$995.**



100% USA
Made

DC Model
Available

- Supports (E)EPROMs up to 40-pins.
- Stand-alone or Remote.
- 40-pin Micros Opt.
- SET/GANG 4 (E)EPROMs Opt.
- Parallel port for Fast Up/Down Load.
- 256K bytes, expandable to 16 megabits.

BYTEK 1-800-523-1565
In Florida (407) 994-3520
Fax: (407) 994-3615

* DATA I/O is a registered trademark of DATA I/O Corporation

CIRCLE NO 755

PLD designs?

LOG/iC is simply optimal!

Prove it to yourself...
Call (800) 777-1202
for free evaluation.




**adams-macdonald
CORPORATION**
800 Airport Road • Monterey,
CA 93940 • Fax (408) 373-3622
Telex 882141 • Tel. (408) 373-3607

ISDATA

CIRCLE NO 756

PROTOTYPING ADAPTORS

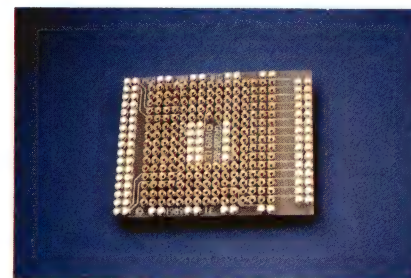

BY THE HUNDREDS

Our line of prototyping adaptors for VLSI devices including PGA, PLCC, LCC, ZIP, DIP, and Plastic Quad Flatpak is the most extensive available in the industry. These devices allow easy prototyping of these difficult to handle devices. Pins and sockets used are gold plated and of the highest quality. Parts are available in soldertail or with 3 level wirewrap pins. All types of wirewrap panels are covered.

IRONWOOD ELECTRONICS
P.O. BOX 21151, ST. PAUL, MN 55121
(612) 431-7025

CIRCLE NO 757

To advertise in Product Mart, call Joanne Dorian, 212/463-6415

WANTED

LAS Bug #880285



Timing Error

Exterminate him with the 8 ns resolution the Logic Analysis System

4k to 64k memory depth
16 level triggering with pass counter
40 to 320 channels
A complete Logic Analyzer on a Card
Interactive software under Microsoft™ Windows
Source code in C for automatic testing



701 River Street
Troy, NY 12180
(800) 367-5906
(518) 274-0755
FAX (518) 274-0764

CIRCLE NO 758

LOW COST Data Acquisition Cards for PC/XT/AT



12 Bit A/D & D/A [PCL711S] \$295

- A/D converter: 8 single-ended channels; Uses AD574 device; Conversion time is less than 25µsec; Input range: ±5V; Software Trigger Mode only.
- D/A converter: 1 channel; 12 bit resolution; 0 to +5.10V Output Range.
- Digital I/O: 16 In/Out (TTL compatible); External Wiring Terminal Board incl.
- Utility Routines and Demo/Sample Programs for BASIC and Quick-BASIC.

12 Bit A/D & D/A [PCL812] \$375

- A/D converter: 16 single ended inputs; Uses AD574; Conversion time less than 25µsec; Built-in programmable pacer; Input Ranges: ±10V, ±5V, ±1V.
- D/A converter: 2 channels; 12 bit resolution; Output Range 0-5V.
- Digital I/O: 16In/Out (TTL compatible); Programmable Counter/Timer (8254).
- DMA and interrupt capability. Utility software and sample program in BASIC.

Fast 12 Bit A/D/A [PCL718] \$895

- A/D converter: 16 single ended or 8 differential channels; 12 bits resolution; Programmable scan rate; Built-in Interrupt and DMA control circuitry. Conversion speed 60,000 samples/sec (standard), 100,000 samples/sec (optional).
- Input Ranges: Bipolar: ±10V, ±5V, ±2.5V, ±1V, ±0.5V; Unipolar: 10.5, 5.2, 1V.
- D/A converter: 2 channels; Resolution: 12 bits; Settling time: 5µsec; ±5V.
- Digital I/O: 16In/Out (TTL compatible); Programmable Counter/Timer (8254).
- Software: Utility software for BASIC & QuickBASIC included. Sample prgm. Supported by LabDAS, ASSYST, LABTECH, Uniscope.

6 Channel 12 bit D/A [PCL726] \$495

- Output Ranges: 0 to +5V, 0 to +10V, ±5V, ±10V, or sink 4-20mA.
- Settling time: 70µs. Linearity: ±10bit. Voltage output drive capacity: ±5mA.
- Digital I/O: 16 digital input and 16 digital outputs (TTL compatible).

MC / VISA / AMEX

Call today for datasheets!



B & C MICROSYSTEMS INC.
355 West Olive Ave, Sunnyvale, CA 94086 USA
TEL: (408) 730-5511 FAX: (408) 730-5521

CIRCLE NO 759

Z-1000B UNIVERSAL PROGRAMMER



- PROGRAM THOUSANDS OF DIFFERENT DEVICES
- NO PERSONALITY MODULES REQUIRED
- DESIGNED FOR EASE OF OPERATION
- STAND ALONE AND MS-DOS DRIVEN
- SELF CALIBRATING
- QUICK FLIP LCC AND SMT ADAPTERS



SUNRISE ELECTRONICS, INC.
524 South Vermont Avenue, Glendora, California 91740
(818) 914-1926

CIRCLE NO 760

Consistency
is
key
to the power of
EDN Product Mart

CIRCLE NO 761



Dynamic C For Real-Time Embedded Systems Z80/Z180/HD64180



A new idea!
An integrated C development environment with editor, compiler and source level debugger. Memory-resident on your host PC. Compiles, while downloading to the target, at 25,000 source lines per minute. Complete, low-priced system includes an IC180 in-circuit emulator and Dynamic C software. Ask for a Free Demo Disk.

1340 Covell Blvd. • Davis, CA 95616
(916) 753-3722 • Fax: (916) 753-5141

CIRCLE NO 762

E/EPROM PROGRAMMER

\$895

Lifetime FREE software updates (1st in the industry)



- EP-1140 includes: software, cable, user's manual, FREE software updates (via BBS), toll-free technical support, one-year warranty and an unconditional thirty-day money back guarantee
- Programs 24-, 28-, 32- & 40-pin E/EPROMs
- Supports 874X & 875X series microcontrollers
- Connects to a standard parallel port
- Currently supports parts to 4 Megabit
- 32-pin model, EP-1132, available for \$695

The Engineer's Programmer™

CALL TODAY 800-225-2102


BP MICROSYSTEMS

713/461-9430 FAX 713/461-7413
10681 Haddington, #190, Houston, TX 77043

CIRCLE NO 763

Create a DISKLESS PC IT'S EASY...IT'S SIMPLE..... THERE'S Nothing to it!!!


PROMDISK™ III IBM PC DISK EMULATOR CARD

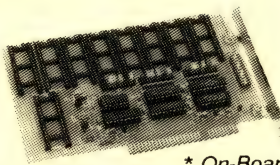

- * On-Board BIOS ROM
- * IBM PC/XT/AT Compatible
- * Mix EPROMs, EEPROMs, SRAMs
- * Emulates up to 1.024Mbyte Drive
- * Occupies 32K PC address space
- * Supports popular Byte-Wide chips
- * Includes PROMDISK™ III Software

For Information Call or Write:
MICRO COMPUTER SPECIALISTS, INC.
810-208 Los Vallecitos
San Marcos, CA 92069
(619) 744-8087

CIRCLE NO 765

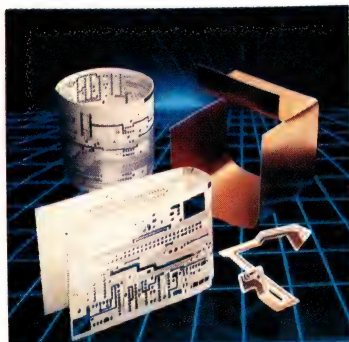

WE'RE BENDING THE RULES FOR CIRCUIT DESIGNERS

BEND/FLEX™, the bendable board material flexible enough to bend into any multi-plane shape. Eliminates stiffeners, flex-hardboard connectors. May reduce cost of two- and three-plane interconnect systems by as much as 30%!

Rogers Corporation. One Technology Dr.,
Rogers, CT 06263. (203) 774-9605.

CIRCLE NO 764

8051



MetaLink™...Originators of the PC Based 8051 Emulator

We have more 8051 emulators than anyone in the world: 8031, 8051, 8032, 8052, 8344, 8044, 80C152JA/JB/JC/JD, 83C152JA/JC, 80C452, 80C51FA, 8051S, 8053S, 80512, 80532, 80513, 80C517, 80C521, 80C541, 80C321, 8053, 8XC154, 8XC451, 8XC552, 8XC562, 8XC852, 8XC751, 8XC752, 80C537, CMOS, EPROMs, OTPs

Call or write for Free demo diskette

1-800-METAICE®

MetaLink Corporation

MetaLink Corporation P.O. Box 1329, Chandler, AZ 85244-1329
(602) 926-0797 FAX: (602) 926-1198 TELEX: 498050 MTLNK
*Price is U.S. list




PC BASED EMULATORS

- Source Level Debug for PL/M and C
- Source Level trace
- Debug with symbols, not HEX data
- Source Level disassembly with in-line assembler
- Interchangeable probe cards
- Up to 128K emulation memory
- 20 MHz real-time emulation
- Up to 4K trace buffer
- Performance analyzer
- TRUE 8051 Emulation including all I/O ports, idle, power down, DMA, and WatchDog timers at NO additional cost
- Breaks set symbolically
- Fully documented
- Serially linked to PC
- OEM supplier to 8051 IC manufacturers
- Unlimited FREE technical support
- From \$1495*

NOW
8XC552 & 8XC517
SUPPORT

CIRCLE NO 766

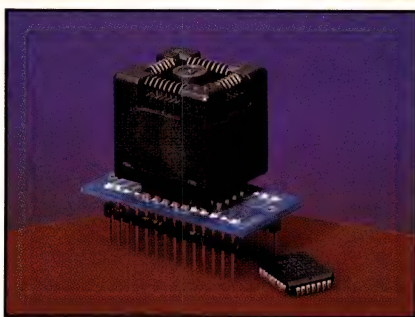To advertise in Product Mart, call Joanne Dorian, 212/463-6415




PAL/PROM Programmer Adapters

- Any EPROM programmer designed for DIPs can be converted to accept LCC, PLCC, and SOIC sockets in seconds!
- To program, just insert an Adapt-A-Socket™ between the programmer's DIP socket and the circuit to be programmed.
- Designed to fit all types of EPROM programmers, including Data I/O 120/121A, Stag, Logical Devices, etc.
- Quick turnaround on custom engineering services, if needed. For a free catalog, contact:

Emulation Technology, Inc.
2368-B Walsh Ave. Santa Clara, CA 95051
Phone: 408-982-0660 FAX: 408-982-0664



CIRCLE NO 767

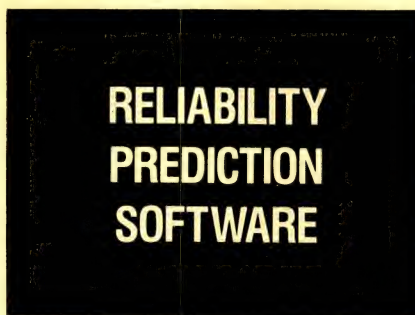

RELIABILITY PREDICTION SOFTWARE

ARE YOUR PRODUCTS RELIABLE?

The RelCalc 2 Software Package predicts the reliability of your system using the part stress procedure of MIL-HDBK-217E, and runs on the IBM PC and full compatibles. Say goodbye to tedious, time consuming, and error prone manual methods! RelCalc 2 is very easy to use, and features menu windows, library functions, global editing for what-if? trials, and clear report formats. Try our Demo Package for \$25.

T-CUBED SYSTEMS, 31220 La Baya Drive #110, Westlake Village, CA 91362. (818) 991-0057 • FAX: (818) 991-1281

CIRCLE NO 768

TRANSMISSION-LINE PROBLEMS?



Interactive Transmission-Line Simulator

Designing digital systems? With today's fast edges, chances are good you've got transmission-line problems.

LineSim is a new tool just for transmission-line design.

It features:

- a push-button schematic
- two PCB-impedance calculators
- models for major device families
- an oscilloscope display
- a totally interactive environment

LineSim shows you your signals when it makes the most sense: before you build boards. And it'll teach you more about how transmission lines work than a whole pile of dusty books.

30-day money-back guarantee.


\$595

Requires IBM PC with EGA.

HyperLynx

P.O. Box 3578 Redmond, WA 98073-3578 (206) 869-2320

CIRCLE NO 769

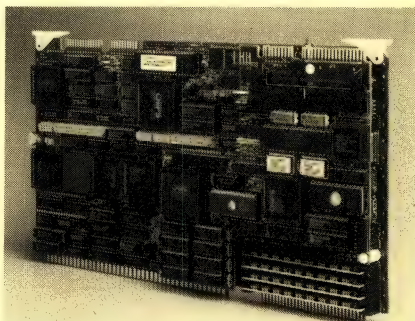

MULTIBUS™ AT-COMPATIBLE SBC

Multibus I is now IBM PC/AT™ compatible with MAT286™ our newest single board solution. MAT286 includes all of the functions of a 10 MHz AT motherboard, plus 2 serial ports, a parallel port, two SBX expansion-module interfaces, up to 512K EPROM/EEPROM/DRAM, and up to 4M of parity-checked, dual-ported DRAM. A piggy-back card, MATxSYSIO, adds EGA, floppy, and SCSI interfaces. Embed all the guts of an AT, two SBX modules, and more, into two Multibus slots!


Phone (408) 253-0250 or write for more information.

Single Board Solutions, Inc.

20045 Stevens Creek Blvd, Cupertino, CA 95014

Multibus is a registered trademark of Intel Corp.
MAT286 and MATxSYSIO are trademarks of Single Board Solutions, Inc.
IBM and PC/AT are trademarks of International Business Machines Corp.

CIRCLE NO 770

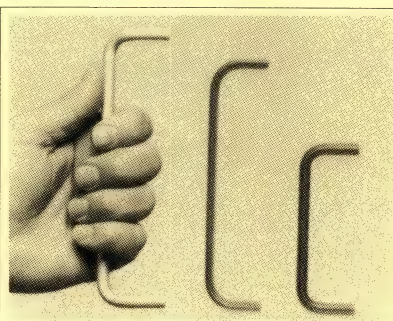

HANDSOME HANDLES

RAF offers a line of handles with a high-tech in round, oval, and round offset shapes with matching ferrules. These precision-made, dimensionally accurate handles are available in a wide variety of sizes, materials, and finishes. They are part of more than 35,000 items in stock.

For a catalog write or call:

RAF Electronic Hardware, Inc.

95 Silvermine Road, Seymour, CT 06483

Tel. (203) 888-2133, FAX (203) 888-9860

CIRCLE NO 771

WANT ATTENTION FROM OVER 139,000 ENGINEERING SPECIFIERS?

EDN PRODUCT MART

CIRCLE NO 772

An Industry First.

E-T-A's Series 1110 is the **ONLY** full feature circuit breaker that fits standard fuse holder panel cutouts. **PLUS** offers ON/OFF switching. 100% quality tested and available in ratings 0.05 through 16 amp.



E-T-A CIRCUIT BREAKERS

7400 N. Crounse Rd., Chicago, IL 60648
Phone: (708) 647-8303 Fax: (708) 647-7494

CIRCLE NO 773

DOS IN EPROM

Or any other code, for that matter! PromKit allows you to create Eproms that look like read-only disk drives in your PC-compatible systems. Use PromKit even if you're not a programmer. Just use PromKit to convert any disk into EPROM images for your Prom blaster! Copy system files, batch files, data files, or anything else you want. Use Proms for read-only, SRAMS for read-write! Includes source code in C. Over 180 pages, including disk, only \$179.

FREE We'll include a free copy of the pocket-sized **XT-AT Handbook** by Cholsner and Foster with each PromKit if you mention this ad when you order. Of course, this \$9.95 value is also available by itself. Or buy five or more for only \$5.00 each.

800-462-1042
519-271-9526 in CA

Annabooks


12145 Alta Carmel Ct Suite 250-262

San Diego, California 92128



Money-back guarantee

CIRCLE NO 774

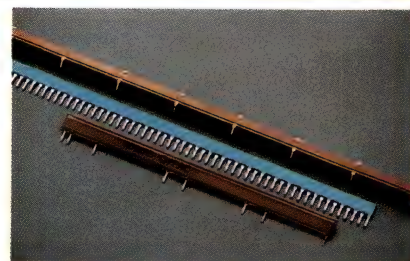

SAVE SPACE WITH Q/PAC® COMPONENTS

- Provide built-in capacitance
- Eliminate decoupling capacitance
- Gain 4-layer board quietness with 2-layer economy
- Vertical or horizontal mounting


Send for Rogers Q/PAC® Application Bulletin.

Rogers Corp., 2400 S. Roosevelt St.
Tempe, AZ 85282 602/967-0624

CIRCLE NO 775

To advertise in Product Mart, call Joanne Dorian, 212/463-6415

JE680 Universal Programmer

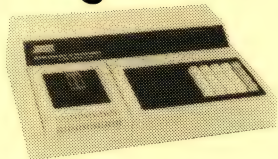


- Programs PROMs, EPROMs, EEPROMs, PALs, GALs, RALs, EPLs and PLDs
 - Stand-alone or computer controlled modes w/MS-DOS menu-driven software
 - JEDEC standard supported
 - Parallel and RS232C interface ports
 - Optional 40-pin MPU module available
- Listing of programmable devices and 80-page catalog available upon request!

JE680 Universal Programmer.....\$1799.95

Jameco 1355 Shoreway Road, Belmont CA 94002
Phone (415) 592-8097
FAX (415) 592-2503

CIRCLE NO 776

6800/6809 Micro Modules

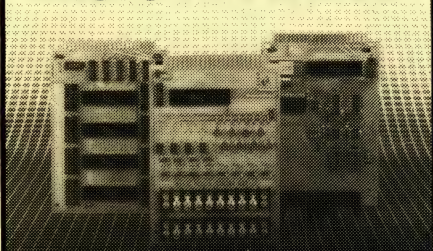

OEM 6800/6809 MICROCOMPUTER MODULES for dedicated control and monitoring. Interfaces for sensors, transducers, analog signals, solenoids, relays, lamps, pumps, motors, keyboards, displays, IEEE-488, serial I/O, floppy disks.

Wintek Corp.
1804 South Street
Lafayette, IN 47904
317-742-8428
800-742-6809

CIRCLE NO 777

Professional 8086 ROM Development

with C_thru_ROM and ROM-DOS

C_thru_ROM works with Microsoft C or Turbo-C to comprise a complete ROM development package: comprehensive debugger, remote debugging, startup code, full 80x86 locator, ROMable library, etc.

C_thru_ROM, \$495

ROM-DOS, a ROMable operating system, provides functionality of DOS 3.2 less networking. Runs PC programs and EXE files. Supports AUTOEXEC and CONFIG.SYS. Uses only 29K ROM and little as 6K RAM. \$6 each in quantity.

ROM-DOS Developer's Kit, \$495

Call for info and demo disk

1-800-221-6630

Datalight, 17505 - 68th Ave NE, Bothell WA, 98011
(206) 486-8086, fax (206) 486-0253

CIRCLE NO 778

Now on Sun!

Facts about 425,000 ICs and Semiconductors at Your Fingertips

Cahners CAPS is the newest component search and selection tool for electronic design engineers:


- PC-driven, CD-ROM-based
- Includes unabridged manufacturers' datasheets
- Represents more than 400 manufacturers worldwide

Call toll-free: 1-800-245-6696

CAHNER'S CAPS 275 Washington Street
Newton, MA 02158-1630
Telephone: 617-558-4960
Facsimile: 617-969-6949
Telex: 940573

CIRCLE NO 779

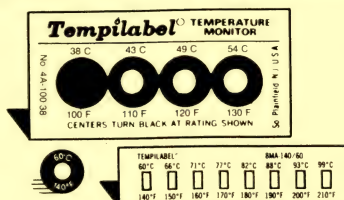WRITE OR CALL FOR SAMPLE
Low Cost Tempilabel® Temperature Monitor.



How to put a low cost temperature gauge on everything.


Label's center spot turns black when surface to which it is affixed reaches specified temperature. Single- or multi-spot labels with pre-determined increment of ratings: 100°F (38°C) to 600°F (316°C). 1% accuracy guaranteed. 1 thru 8 ratings on each monitor with various increments. Self-adhesive, removable.

TEMPIL DIVISION, Big Three Industries, Inc.
2901 Hamilton Blvd., South Plainfield, NJ 07080
Phone: (201) 757-8300 Telex: 138662

CIRCLE NO 780

Analog Circuit Simulation

SPICE FOR THE MACINTOSH

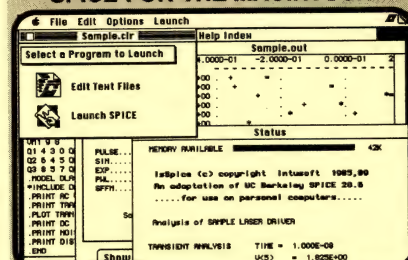

Intusoft introduces the NEW II ISpice/MAC. The only Spice program to run on all Macintoshes (Plus, SE, SE/30 and Mac II) in as little as 1 megabyte of RAM. The simulatable circuit size is only limited by the amount of RAM. Coprocessor (\$210) and Non-coprocessor (\$95) versions are available. Also available is PreSpice/MAC (\$175) which contains extensive model libraries, the IsSpice netlist editor and ICAPS, an easy to use menu system especially adapted for the MAC environment.


P.O. Box 6607
San Pedro, CA 90734-6607

intusoft (213) 833-0710
30 Day Money Back Guarantee

Macintosh is a registered trademark of Apple Computer

CIRCLE NO 781

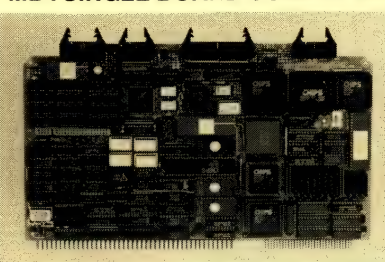NEW ZX-286/PCAT MB I SINGLE BOARD COMPUTER



Featuring:

- 100% IBM compatibility
- AT and SBX connectors
- 7 DMA channels
- 16 vectored interrupts

For a free, full-line catalog call 1-800-4MB-2DAY
(In California call 1-415-828-3000)

ZENDEX

6780 Sierra Court, Dublin, CA 94568

CIRCLE NO 782



Software to release your creative genius

ELECTRONIC ENGINEERS CALL FOR YOUR FREE MAC & MSDOS CATALOG

- AC/DC circuit analysis
- Active & passive filter design & analysis
- Engineering graphics
- Signal processing
- Logic simulation
- Root locus analysis
- Microstrip design
- Thermal analysis
- Statistics/ More

BV Engineering
Professional Software




To order call toll free 1-800-229-0283
2023 Chicago Ave., Ste. B-13, Riverside, CA 92507

CIRCLE NO 783

Telecom Design!

CALL PROGRESS TONE GENERATOR

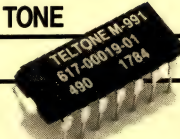

M-991 generates precise dial tone, busy tone, reorder tone, ringing, and other call routing tones for use in telephone systems, test equipment, callback security and other telecommunications systems.

- 14-pin CMOS DIP
- Single 5V power supply
- 3.58 MHz time base
- Combinations of all standard frequencies



For more info call: **1-800-426-3926**
(In Washington State: 206-827-9626)

TEL TONE®

10801-120th Avenue NE, Kirkland, WA 98033

CIRCLE NO 784

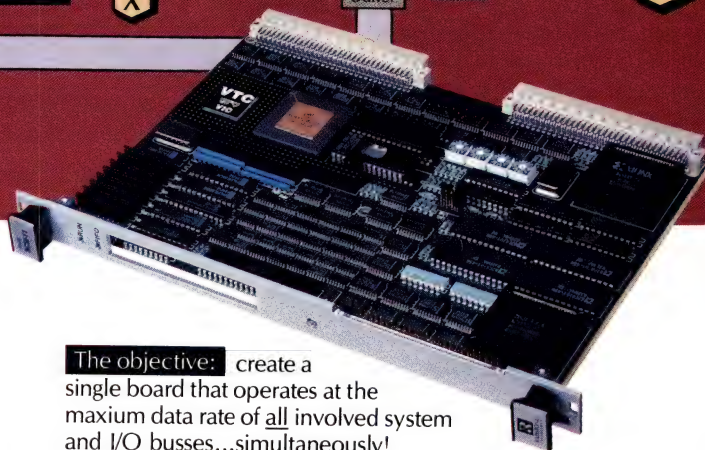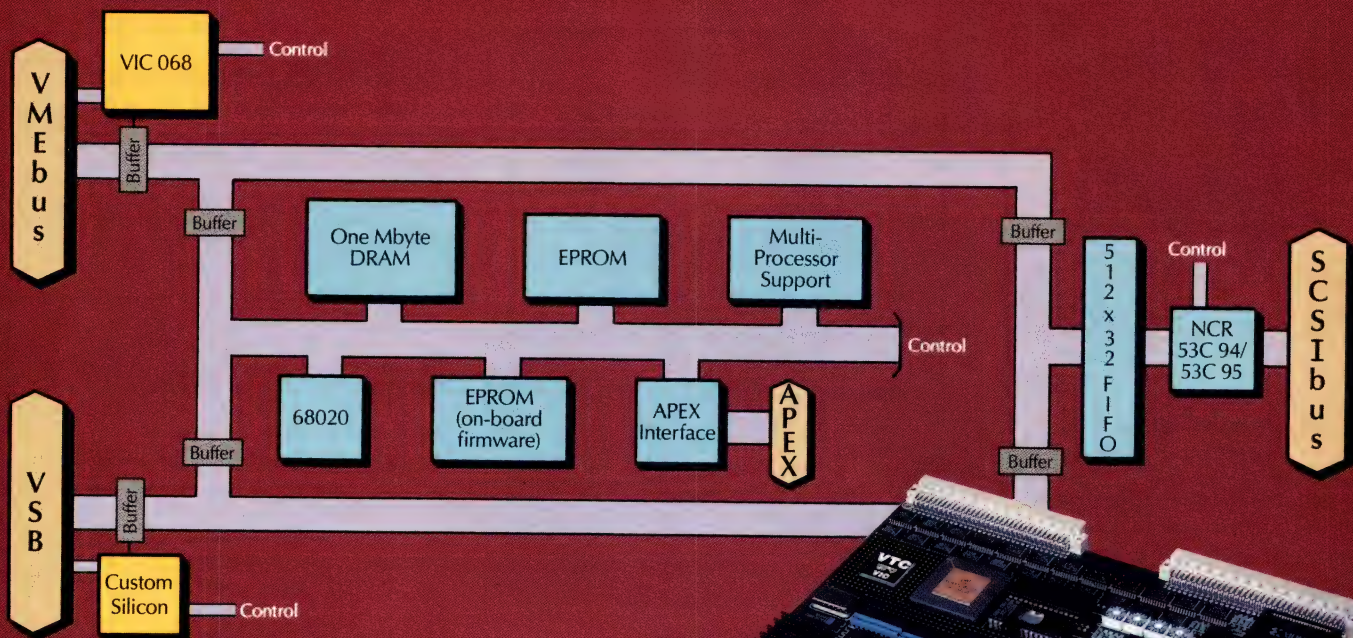To advertise in Product Mart, call Joanne Dorian, 212/463-6415



**At last... a real
40 Mbyte/sec.
data management
system on one
VME board.**

The SCSI-11 from Radstone.

Face it. Your real system problem is fast data access and transfer. Now there's a board that eliminates bottlenecks in those areas to let your VME system deliver peak performance.

The objective: create a single board that operates at the maximum data rate of all involved system and I/O busses...simultaneously!

The solution: Radstone's "Freeflow Architecture" SCSI board that let's you use up to four different busses—SCSI, VME, VSB and our APEX auxiliary bus. This gives you an I/O processor that not only supports SCSI, but dual SCSI, Ethernet, IEEE 488, floppy, parallel I/O and just about anything else your system might need.

The Ultimate SCSI Package

Only Radstone's SCSI-11 offers you:

- The fastest sustained transfer rate available— 40 Mbytes/sec. across the VMEbus
- The first controller board in the industry with the VIC 068 VMEbus Interface Chip
- Sustained 5 Mbyte/sec. transfer rate across the SCSI bus
- A full master/slave VSB interface with its own sustained 30 Mbytes/sec. DMA transfer rate
- 68020 Microprocessor
- 1 Mbyte Quad-ported DRAM
- APEX (Advanced Processor EXtension bus) to add the functionality you want—Ethernet, second SCSI, IEEE 488, floppy, parallel I/O...or your own.

Commercial through Mil-Spec

Radstone offers an entire family of SCSI interface boards for applications from commercial through full Mil-Spec. Plus the industry's best selection of commercial, ruggedized and military VME processor, memory, communications, I/O and controller boards, development systems and software. Radstone has your VME system solution now. Call us for the details.

UK Water Lane, Towcester, Northants, NN12 7JN, (0327) 50312
USA 20 Craig Road, Montvale, NJ 07645-1737, (201) 391-2700
France 'Miniparc', 6 avenue des Andes, 91940 Les Ulis, (1) 64.46.04.03
Germany Bahnhofstraße 38, D-6090 Rüsselsheim (061 42) 6 80 04

See us at Buscon West '90 Booth #419

R
RADSTONE
TECHNOLOGY

The new headhunters

Jay Fraser, Associate Editor

They've been called personnel consultants, executive recruiters, and headhunters. They've also been called a variety of unprintable names. Depending on your point of view, they're either the people who help professionals advance their careers through judicious job changes or the people who raid companies and steal some of their best talent. Almost no one feels neutral about them.

Headhunters work differently than ordinary employment counselors. Employment counselors start with people who are looking for work and try to find jobs for them.

Headhunters start with positions that are open and try to find qualified people to fill them.

*They're knowledgeable.
They're professional.
They're looking for you.*

The client companies pay the headhunters' fees. The standard fee is 10% of the candidate's first-year salary, but that can go higher, especially if the position is for a high-ranking corporate executive whose salary is in six figures.

Headhunters acquired an unsavory reputation in the high-tech industry during the late '60s and early '70s. In those boom times new companies were being started every day and established firms were expanding rapidly. Qualified engineers were in short supply, and companies were willing to pay high prices to anyone who could bring them in. That situation attracted some people to the recruiting profession who were much more interested in fast money than in career guidance.

Some shady operators were known to run want ads for jobs that



Jim Lambrenos

didn't exist so they could build up a stock of resumes. Others would get a company telephone book and cold call all the engineers in it, trying to lure them away. Some headhunters didn't interview candidates or check references. They just sent dozens of semiqualfied people to companies, hoping a few would be hired.

"Probably the thing that upset client companies the most was recruiting firms that were placing a candidate with a company, collecting the fee, then three or four months later taking that person out and moving him to another company," says Bob Read, who owns and operates a franchise of Management Recruiters in Redwood City, CA. "You've only got to do that a couple of times to lose all credibility with a client."

In 1969, Read, who has a degree in civil engineering from Iowa State University, went to a recruitment firm in San Francisco hoping it could find a position for him. He ended up going to work for it. "It's now 20 years later, and I'm still looking for the right position," he says with a smile. At one time he was the manager of eight recruitment offices in the Bay Area, and he has seen the profession change dramatically over the last two decades.

Early years of headhunting

"For the first three or four years that I was in the industry people would ask me what I was doing, and I'd say, 'Well... er... um... I'm a consultant or I'm this or I'm that'—anything but a headhunter," says Read.

However, with the shake out in the high-tech industry in the late '70s came a shake out in the ranks of the recruiters. Today's headhunters are much more professional and knowledgeable, and the word

"headhunter" has lost most of its unpleasant connotations.

"We've cleaned up our image an awful lot in the last ten years," Read adds. "Look at the people we're attracting to this industry now."



One of those people is the former president of the American branch of Acorn Computers, Harvey Lawner. He earned his BS in computer science at City College of New York and worked for Digital Equipment Corp, Data General, and Sony before taking over at Acorn. After he had been there three years, the parent company in Great Britain decided to close its American subsidiary. Lawner had to find another position. A friend suggested that he try recruiting. He did, and he was surprised by the demands of the job.

"People think that what we do is simple, but it's quite the contrary. It's probably the most difficult thing that I've ever done," says Lawner, who is now a senior partner at Logix, a recruiting firm in Waltham, MA.

The job is demanding, Lawner continues, "because I'm dealing with people, and people are consistently inconsistent. I can show you how a workstation performs, and it'll do what it's supposed to do, but I can't control people. I can't create chemistry between two people. I can't make decisions for people. I've found this job to be a lot more strenuous and stressful than working at Acorn Computers."

Special problems with engineers

In addition to the difficulties a headhunter might run into trying to recruit any professional, engineers often present special problems. Many engineers won't change jobs simply for more money. They want to work on projects that involve the most advanced technology or offer the opportunity to develop new products. Understanding the importance of job satisfaction to engineers is one of the keys to being a successful high-tech recruiter.

David Scardifield, president of Omnisearch Inc in San Mateo, CA, is specially qualified to recruit engineers. He has a bachelor's degree in electrical engineering from Reading Technical College in Reading, England, and he has held various management positions in companies such as Honeywell and Telex Computer Products. He often dealt with headhunters when he was trying to find engineers.

"A lot of times when I was looking for field engineers I had a difficult time finding a recruiter who really understood what they were," he says. "They would send me design engineers or they would send me bench technicians. I began to see there was a market niche there for a recruiting company."

Tired of working for large corporations, Scardifield wanted to strike out on his own. "I looked at what kinds of things I might do where

the fruits or failure would be right at my own doorstep. I enjoyed the people side of technical management, and it looked to me like there was an opportunity to do headhunting in a little bit different way.

"I worked for a recruiter for a year to learn the business, then started my own company, specifically to find field engineers and engineering managers," he continues. "I did it for about a year, and I was quite successful at it. Then the companies I was doing that for began to ask me to find other kinds of people, and that's how I got into the rest of the business."

The new breed

Not all headhunters are engineers, of course, but Read, Lawner, and Scardifield exemplify the new breed. Their educational backgrounds and their firsthand knowl-

edge of the high-tech industry have helped them immeasurably in their careers as recruiters. They speak the same language as the people they deal with, so they can tell precisely what an employer or a candidate is looking for. They can also tell if someone is stretching the truth on a resume. A good headhunter can save everyone time and money.

As the high-tech industry changed, the headhunter's job changed with it. It's no longer enough to simply find viable candidates and arrange interviews. As Read says, "Recruiters have had to become much more sophisticated and concerned with the service aspects of this business."

The service aspects may include giving candidates advice on how to write their resumes, how to present themselves to their prospective em-

ployers, and how best to leave their present jobs.

Sometimes after employees announce they're leaving, their companies will make a counteroffer. It might be a raise, a bonus, a promotion, incentives to go to school, even tenure. If the employees aren't prepared for a counteroffer, it might catch them off balance.

"I usually cover those things during the recruiting process," Scardifield says, "so the candidate has already thought it through."

"Counteroffers aren't usually effective," he adds, "because why didn't the company make that offer to the person without having to be pushed to it. Most people see that."

Other advantages for clients

Experienced recruiters can provide another advantage to both client companies and candidates—

What to do when a headhunter calls

Listen carefully. It won't cost you anything to listen. Even if the job the headhunter proposes isn't right for you, you'll gain information about the current marketplace. In addition, letting the headhunter know what you're interested in may lead to a better offer in the future.

Check on the headhunter's reputation.

- Ask your friends and colleagues about the recruitment firm and if they've ever had dealings with it.
- Call the state labor office or the Better Business Bureau where the recruitment firm is located and find out if any complaints have been made against it.
- Ask the headhunter if he or

she belongs to any of the national organizations—the National Association of Corporate and Professional Recruiters (Louisville, KY), the Association of Executive Search Consultants (Greenwich, CT), or the National Association of Personnel Consultants (Arlington, VA). All three promote ethical standards for the profession and deal with complaints against their members.

Insist on confidentiality. If you give your resume to a headhunter, you have a right to know where he or she is going to send it. Recruiters have been known to mail out resumes to dozens, even hundreds of companies. This

only increases the chances that news of your job hunting will get back to your boss. Tell your recruiter that you want to know in advance where your resume will be sent and insist that all efforts on your behalf be kept strictly confidential.

Arrange a personal meeting.

If possible, meet with the headhunter face to face and talk about his or her experience, contacts, and plans for you. You should have a good rapport with your recruiter, just as you do with your doctor or lawyer. The recruiter's manner and appearance should also meet with your approval. Remember, this person will be representing you.

PROFESSIONAL ISSUES

their network of contacts. If a headhunter has placed people successfully they will refer others to him or her. After being in the business for years some recruiters no longer have to make cold calls or run newspaper ads to find qualified candidates. The candidates come to them.

Dealing with an established recruiting firm has one more advantage for a candidate. Because the firm is going to be around for a long time there shouldn't be any pressure on someone to take a job he or she isn't really suited for.

The image of headhunters has also been improved by the growth of professional organizations, which set ethical standards for their members. The three major national organizations are the National Association of Corporate and Professional Recruiters, the Association of

Executive Search Consultants, and, by far the largest with more than 2300 member firms, the National Association of Personnel Consultants (NAPC).

Read is a past president of the California Association of the NAPC and now serves on the national board of directors. In his home state he has been active in promoting legislation, such as the licensing of career counselors, that he believes has benefited both candidates and client companies.

"There are probably more candidates who got caught in the problems than companies," says Read. "Candidates would put their faith in a recruiter and be told information that wasn't true. It would take them down the wrong path. You can't legislate morality, but you can set up a system that clients and candidates can go to and find consis-

tency as to what can be expected from our members."

High-tech recruiting is relatively young, but it has already passed through its childhood and its boisterous, rowdy adolescence. It has now entered its adulthood. As the industry matured most of the fly-by-night operators departed and the new breed of headhunters emerged. Lawner sums up in simple terms why they have been successful. "You have to understand what you're doing, like any other business. I think understanding your trade, understanding the service you provide, and providing that service to its completion is really what it's all about."

EDN

Article Interest Quotient
(Circle One)

High 509 Medium 510 Low 511

1,239,580 Filters

Lowest prices in America
on small quantities

0.1 Hz to 500 MHz

1,239,580 standard filter types □ Miniature and subminiature sizes □ Passive and active types □ Telemetry filters □ Gaussian, Butterworth, Chebyshev designs □ Call or write for free catalog today.

TTE

TTE, Inc.
11652 W. Olympic Blvd.
Los Angeles, CA 90064
(213) 478-8224



CIRCLE NO. 25

HI-CAL DESIGN INC.

Now you can
have a . . .

Free Prototype Board

HI-CAL DESIGN announces a
new concept in design services.

Now you can receive a prototype
board with every design we do
for you. No waiting...no fuss!

We also specialize in direct
HPGL Photoplotting.

H HI-CAL DESIGN INC.

1324 Buffalo Road • Rochester, NY 14624
(716) 235-3350 • 800-722-2763

CIRCLE NO. 26


End the connector compromise...

1. LIF RACK & PANEL CONNECTORS

2. MULTIPIN WITH 8-200 AMP CONTACTS

3. MIL-C-28748A RELIABILITY

...in electronic
power
supplies

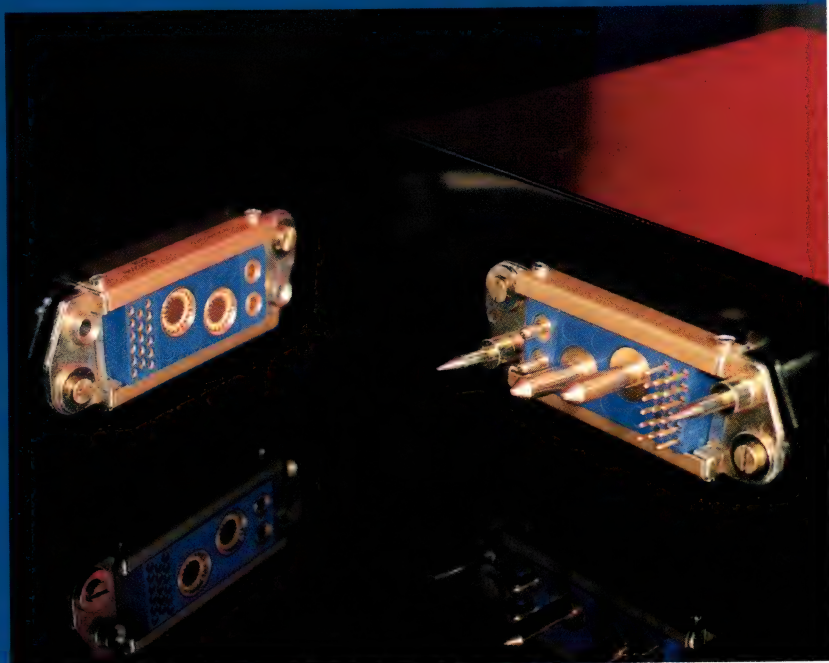

Only Hypertronics ends the compromise in power supply connectors for backplane subassemblies—in military, computer and other electronic systems—by combining Low Insertion Force (LIF) power, signal and MIL spec reliability in a single rack & panel connector.


Our modular design gangs power contacts, rated from 15 to 200 amps, with low-insertion-force signal contacts. Combine these design alternatives with high current/small size performance of the Hypertac® contact—for unique cost and space efficiency.

And now our L Series connectors have been proven to MIL-C-28748A performance standards.

Now you can have it all...in rack & panel

connectors for power and signal applications ranging from power supply to portable disc drives. End the connector compromise by calling 1-800-225-9228, toll free.

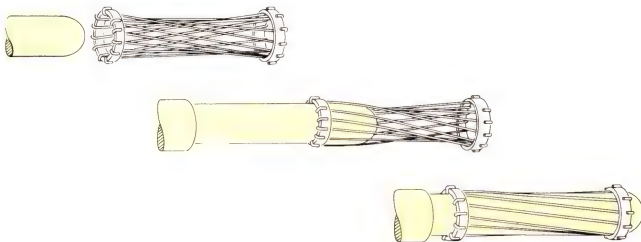HYPERTAC®:
Inserting pin into hyperboloid sleeve.



HYPERTRONICS CORPORATION

"New Horizons in Connectors"

16 Brent Drive, Hudson, MA 01749 (508) 568-0451 FAX (508) 568-0680

CAREER OPPORTUNITIES

1990 Recruitment Editorial Calendar

Issue	Issue Date	Ad Deadline	Editorial Emphasis
Magazine Edition	Feb. 15	Jan. 25	Digital ICs, Computer Systems, Interconnect Technology, Sensors
News Edition	Feb. 22	Feb. 2	CAE/Hardware, Telecom, Regional Profile: No. California
Magazine Edition	Mar. 1	Feb. 8	Computer-Aided Engineering/ASICs, Computers & Peripherals, Digital ICs/Microprocessors, Semicustom ICs
News Edition	Mar. 8	Feb. 15	Analog/ICs, Automotive Electronics, Special Supplement: RISC/Microprocessors
Magazine Edition	Mar. 15	Feb. 22	Analog ICs, Components, Engineering Software, Special Design Project #1
News Edition	Mar. 22	Mar. 2	Optoelectronics, Peripherals, Regional Profile: New York, Pennsylvania & Connecticut
Magazine Edition	Mar. 29	Mar. 8	Software Special Issue—Interface ICs, Software/Programming/Microprocessors/ASICs, April Fools Section, Special Design Project #2
News Edition	Apr. 5	Mar. 16	IC/Logic ICs, Distribution, Special Supplement: Distribution
Magazine Edition	Apr. 12	Mar. 22	Communications Special Issue—Communication ICs, Communication Systems, Microprocessors, Special Design Project #3
News Edition	Apr. 19	Mar. 30	ICs/Graphics Controllers/Microprocessors, Industrial Automation, Regional Profile: So. California
Magazine Edition	Apr. 26	Apr. 5	Computer Boards/Microprocessors, Power Sources, Sensors/Transducers, Special Design Project #4, Electro Show Issue
News Edition	May 3	Apr. 12	CAE/Board Layout, Education, Special Supplement: ASICs, Electro Show Issue
Magazine Edition	May 10	Apr. 19	Analogy Technology Special Issue—Analog ICs, Analog Instruments, Digital ICs/Microprocessors/ASICs, Special Design Project #5
News Edition	May 17	Apr. 27	ICs/Memory ICs, Test & Measurement, Regional Profile: Massachusetts & New Hampshire
Magazine Edition	May 24	May 3	Microprocessors, Computers & Peripherals, Semicustom ICs/ASICs, Components, Sensors & Transducers
Magazine Edition	June 7	May 17	Software, Design Tools, Microprocessor I/O Chips, μ P Support Chip Directory
News Edition	June 14	May 24	Peripherals/Input Devices, Software, Special Supplement: EDA
Magazine Edition	June 21	May 31	Computer-Aided Engineering, Computers & Peripherals, Power Semiconductors, Semicustom ICs/ASICs
News Edition	June 28	June 8	ICs/RISC/Microprocessors, Image Processing, Regional Profile: Oregon & Washington
Magazine Edition	July 5	June 14	Product Showcase—Volume I: Hardware & Interconnect, Power Sources, ICs & Semiconductors, Software
News Edition	July 12	June 21	Analog/Communication ICs, ASICs, Special Supplement: Automotive Electronics, Regional Profile: Washington, D.C.
Magazine Edition	July 19	June 28	Product Showcase—Volume II: CAE/ASICs, Computers & Peripherals, Components, Test & Measurement
Magazine Edition	Aug. 2	July 12	Digital ICs/Microprocessors, Computer-Aided Engineering, Computers & Peripherals, Test & Measurement, Technical Article Database
News Edition	Aug. 9	July 20	CAE/Software, Aerospace, Special Supplement: Defense
Magazine Edition	Aug. 20	July 30	Military Special Issue, Vision/Image Systems, ICs & Semiconductors, Memory Technology, Software
News Edition	Aug. 23	Aug. 3	Electromechanical, Opportunities in Non-EOEM, Regional Profile: New Mexico, Arizona

Call today for information:

East Coast: Janet O. Penn (201) 228-8610

National: Roberta Renard (201) 228-8602

HONEYWELL AND YOU: A WINNING COMBINATION FOR THE 90s AND BEYOND.

Honeywell in Phoenix offers a variety of career opportunities in our Commercial Flight Systems Group. Our continuing growth has created the following positions:

Systems Design Engineer — In this area, you will be involved in guidance and control systems analysis and hardware/software design trade-offs. Specification designs, including guidance, navigation and control algorithm development, as well as systems integration and installation, flight test and customer liaison activity, are a part of these positions.

System Software Development — This area involves development of flight software for advanced guidance and control systems for aircraft using modular and structured programming techniques. You will be involved with algorithms and development of real-time programs in both assembly (8086 family Z8002, 68000) and high order languages such as Pascal, "C," Ada and PLM/86, with subsequent integration with hardware.

Electronics Engineering — These positions involve the development of new processor/bus architectures and specifications to support fault tolerant/redundant airborne

applications. To qualify, you should have experience with embedded multiprocessor-based avionics systems.

Display Systems — These positions offer systems, software and hardware opportunities with CRT/LCD display technology. You should be familiar with digital hardware design and/or real-time programming. Systems functions include overall system definition and design and customer interaction.

To qualify for the positions listed above, you should have a BSEE degree or a BS degree in computer science and at least three years of experience.

Manufacturing Engineering — These positions offer support of new product transitions to production, on-going operations sheet and tooling requirements and implementation of floor work teams. You will interface with a number of functional areas and assist in the implementation of shop floor control, SPC and JIT systems. To qualify, you should have an engineering degree in mechanical, manufacturing, industrial or a related engineering discipline, with two or more years of experience in manufacturing engineering or a related product engineering role supporting electro-

mechanical or circuit card assembly. Experience in surface-mount technology, SPC and/or JIT implementation is a plus.

Quality Engineering — To qualify for this position, you should have a BS degree in an engineering curriculum. A minimum of two to five years of experience in quality engineering/assurance, reliability and/or product engineering is required. You should have strong communications skills and computer applications experience. Customer interface experience is preferred.

Additional opportunities are available in:

- Avionics Systems Simulation
- CAE Engineering
- Artificial Intelligence
- VAX Systems Administration

Make a career move. Honeywell offers you a competitive salary and benefits package and the opportunity to live in the year-round outdoor lifestyle of Phoenix. Send your resume and salary history, in confidence, to Honeywell, Commercial Flight Systems Group, Professional Employment (IEEE-E842), P.O. Box 21111, M/S I-17C, Phoenix, AZ 85036.

Honeywell

HELPING YOU CONTROL YOUR WORLD

Equal Employment Opportunity/Affirmative Action Employer
U.S. citizenship required for some positions

ENGINEERING CAREER OPPORTUNITIES

Join an expanding High Tech R&D/Product Engineering firm specializing in State-of-the-Art microprocessor based designs. We encourage employee initiative and creativity and offer opportunities for continued development of analytical and technical ability.

...

MANUFACTURING ENGINEER/ELECTRONICS, SMT

Looking for the right person to help us develop our fledging production facility. Requires: BS/BSEE degree & 6+ years experience.

- 2 years supervisory experience in general electronics assembly and testing techniques, including hand soldering, wire-wrapping, cable and mechanical assemblies, automatic pick & place machinery, IR reflow, and solder paste screening.
- Knowledge of industry standards for component qualification, quality assurance, and testing.

...

ANALOG DESIGN ENGINEER

Requires BS/BSEE and 5+ years experience in analog design.

- Semi-custom Analog Chip Design
- PSPICE Simulation
- DC to 50 MHz Analog Design

...

COMPUTER SCIENCE/SW ENGINEER

Requires BS/BSEE/CS and 2+ years experience.

- OS/2 and Presentations Manager
- Intel Microprocessors

Qualified candidates should forward a resume with salary history to:



Annapolis Micro Systems, Inc.

190 Admiral Cochrane Drive
Annapolis, MD 21401

(301) 841-2514

FAX: (301) 841-2518

Knock, Knock.

In EDN's
Magazine
and News
Editions,
opportunity
knocks all
the time.

EDN Magazine
Edition
News
Edition



COMMUNICATIONS PROFESSIONALS

II Morrow Inc., a wholly owned subsidiary of United Parcel Service, is a leading manufacturer of quality Navigation and Communication Systems. Dramatic growth in R&D since becoming the technological arm of UPS in 1987, has enabled us to continue developing new applications that promise to significantly impact the small package delivery industry. We're seeking Communications Engineering Professionals to join our dynamic R&D Communications Group in designing and developing an advanced data modem with application to narrowband mobile radio.

RF ENGINEERS

Requires communication experience in successfully bringing a product to market in a commercial environment.

COMMUNICATION SYSTEMS ENGINEERS

Commercial radio communication background required.

SOFTWARE ENGINEERS

Requires a BSCS/BSEE/BS in closely related field. Must have a background in application software for mobile digital product application, and Assembler and PASCAL experience.

MOBILE COMMUNICATIONS ENGINEER

Functional areas of responsibility will include the design of modem hardware (digital, analog, hybrid), generation and implementation of signal processing algorithms in DSP, simulation of digital communication systems. Requires an MSEE with 4 years of relevant experience in the mobile industry. (Position #71)

Located one hour south of Portland, Oregon in the spectacular Pacific Northwest, you'll enjoy a quality of life that includes a relatively low cost of living, year-round outdoor activities and excellent schooling. We offer an excellent compensation package and significant growth potential. Send your resume in confidence to: **II Morrow Inc., Recruiting Dept., (Position name or number), P.O. Box 13549, Salem, OR 97309. PRINCIPALS ONLY PLEASE.** An Equal Opportunity Employer.



SENIOR COMMUNICATIONS ENGINEER

You will be responsible for conducting trade-off studies in synchronization, analyzing interference problems, filter design, complex simulation for performance prediction in fading channels and hardware implementation of various subsystems. Requires a PhD in Communications and 5 years of experience or an MSEE with 8 years in the communications/mobile communications industry. (Position #72)

RF TECHNICIANS

You will develop state-of-the-art radio products for mobile communication and signaling systems. RF background required.

FIELD SERVICE TECHNICIANS

You will direct technical support, installation and training for UPS users of II Morrow digital communication systems. FCC License and/or Naber certification required. Requires travel.

TECHNICAL WRITERS NATIONAL OPENINGS

TO \$55,000

COMMERCIAL WRITERS

Opportunities exist for **Hardware and Software Writers** exp'd writing user, application, program, operating system, maintenance, or installation documentation for any of the following:

Mainframes	UNIX	LAN
Compilers	'C'	SNA, X.25
Workstations	VAX	Telephony
PC's	Databases	CAD

MILITARY/GOVERNMENT WRITERS

ENGINEERING WRITERS exp'd writing manuals, test procedures, or component documents for elec warfare or communication systems.

Writers/Trainers to write manuals, develop courseware, and instruct classes on military systems.

Software Writers exp'd writing sw development docs., application manuals, etc.

Call **Michael Dunn** (collect) at (215) 667-7700 or send resume to



**SUITE 402
150 MONUMENT ROAD
BALA CYNWYD, PA 19004**

All positions are **DIRECT CAREER OPPORTUNITIES** with all fees and interviewing expenses paid by client companies

Microcircuit Engineers

Will serve as the resident microcircuit expert to support the NASA Standard Parts Program. Responsibilities will include the development of evaluation reports and making presentations on microcircuits and related devices to NASA representatives. Requires a BS degree in electrical engineering or physical science with at least six years related experience. Must have solid knowledge of process problems in active devices, manufacturing process controls, screening methods, SPC, failure mechanisms and solid state physics. Individuals who have had experience with JEDEC and/or DESC and have some knowledge of military specifications are preferred. Writing skills and the ability to make platform presentations are of particular importance.

All prior Unisys employees with appropriate skills are encouraged to apply.

Unisys offers competitive salaries and comprehensive benefits. For immediate consideration, please send your resume to: **Unisys, Goddard Space Flight Center, Code 310.1, Dept EDN 1/18, Greenbelt, MD 20771.** An affirmative action employer, committed to work force diversity.

UNISYS

Be Famous In Real Time

We are! Ready Systems is the leading developer and worldwide vendor in software development tools for the fast-growing real-time embedded microprocessor systems market. Our large customer list continues to grow as we provide embedded system software designers with an integrated and comprehensive development environment. Our tools span the major phases of software development from CASE to simulation to compilation and debug through to real-time operating systems.

If your professional background includes microprocessors and real-time applications, consider these opportunities.

- Product Marketing Managers
- Software Development
- Applications Engineers

For immediate consideration, please send your resume to: Ready Systems, Professional Staffing, Dept. EDN, 470 Potrero Avenue, Sunnyvale, CA 94086. EOE/AA.



**READY
SYSTEMS**

Real-Time Challenge
For The Real World.

Professional Profile

Announcing a new placement service for professional engineers!

To help you advance your career, Placement Services, Ltd. has formed the EDN Career News Databank. What is the Databank? It is a computerized system of matching qualified candidates with positions that meet the applicant's professional needs and desires. What are the advantages of this new service?

- It's absolutely free. There are no fees or charges.
- The computer never forgets. When your type of job comes up, it remembers you're qualified.
- Service is nationwide. You'll be considered for openings across the U.S. by PSL and its affiliated offices.

- Your identity is protected. Your resume is carefully screened to be sure it will not be sent to your company or parent organization.
- Your background and career objectives will periodically be reviewed with you by a PSL professional placement person.

We hope you're happy in your current position. At the same time, chances are there is an ideal job you'd prefer if you knew about it. That's why it makes sense for you to register with the EDN Career News Databank. To do so, just mail the completed form below, along with a copy of your resume, to: Placement Services, Ltd., Inc.

IDENTITY

Name _____
Home Address _____
City _____ State _____ Zip _____
Home Phone (include area code) _____

PRESENT OR MOST RECENT EMPLOYER

Parent Company _____
Your division or subsidiary _____
Location (City, State) _____
Business Phone if O.K. to use _____

EDUCATION

Degrees (List)	Major Field	GPA	Year Degree Earned	College or University

POSITION DESIRED EXPERIENCE

Present or Most Recent Position _____ From _____ To _____ Title _____
Duties and Accomplishments _____ Industry of Current Employer _____
Reason for Change _____

PREVIOUS POSITION

Job Title _____
Employer _____ From _____ To _____ City _____
State _____ Division _____ Type of Industry _____
Salary _____ Duties and Accomplishments: _____

COMPENSATION/PERSONAL INFORMATION * (optional)

Years Experience	Base Salary	Commission
Bonus	Total Compensation	Asking Compensation
Min. Compensation	Date Available	
<input type="checkbox"/> I own my home. How long? _____ I rent my home/ apt. <input type="checkbox"/>		
<input type="checkbox"/> Employed <input type="checkbox"/> Self-Employed <input type="checkbox"/> Unemployed		
<input type="checkbox"/> Married <input type="checkbox"/> Single	Height _____ Weight _____	
Level of Security Clearance	I Will Travel	
<input type="checkbox"/> U.S. Citizen <input type="checkbox"/> Non-U.S. Citizen	<input type="checkbox"/> Light <input type="checkbox"/> Moderate <input type="checkbox"/> Heavy	
<input type="checkbox"/> WILL RELOCATE <input type="checkbox"/> WILL NOT RELOCATE <input type="checkbox"/> OTHER _____		
My identity may be released to: <input type="checkbox"/> Any employer <input type="checkbox"/> All but present employer		

EDN Databank

265 S. Main Street, Akron, OH 44308 216/762-0279

A DIVISION OF
PLACEMENT SERVICES
LTD., INC.

Engineering in the 1990s

EDN's editors predict how your job will change in the coming decade.

In the 1990s your job and your responsibilities as an engineer or engineering manager will expand dramatically. The days will soon be gone when you simply hand a design to the people in manufacturing and let them take it from there. In the years ahead you'll be much more involved in financial and manufacturing decisions. You'll follow your designs through the entire manufacturing process and into field service. You'll even be dealing with the customer-relations department and sometimes with the customers themselves.


Your new cradle-to-grave responsibility for your designs will help you in your work. Today few engineers know, or are told, the overall implications of what they do and how they affect their company's profitability. In the next decade, you'll learn firsthand the effects of your decisions on a product's life cycle, and you'll use that knowledge to improve future designs.

Because it will be practically impossible for them to undercut their Asian rivals on price, US companies will place new emphasis on service. You'll be meeting customers to explain the subtleties of your designs, how you ensure quality control, and what you do to produce a reliable product. This change in your responsibilities means you'll have to polish your interpersonal skills.

One vision of the decade ahead conjures up a nightmare in which engineers are chained to their workstations and confined to very small areas of specialization. We believe this scenario is ridiculous. You'll probably have to become familiar with a larger number of computer systems and software packages, but the storage, modeling, analysis, and communications capabilities of your workstation will let you take on larger and larger projects at higher and higher levels of abstraction. Instead of narrowing, your horizons will broaden.

Workstations will become much more sophisticated in the 1990s. For example, instead of telling you only whether a design will work or not, your new CAE and electronic design automation (EDA) tools will give you much more detailed information on how to change your designs to better meet your projects' goals. You'll be freed from repetitive, time-consuming tasks and have more time for creative thinking and experimentation. CAE and EDA are going to reverse Thomas Edison's rule: Engineering will become 90% inspiration and 10% perspiration.

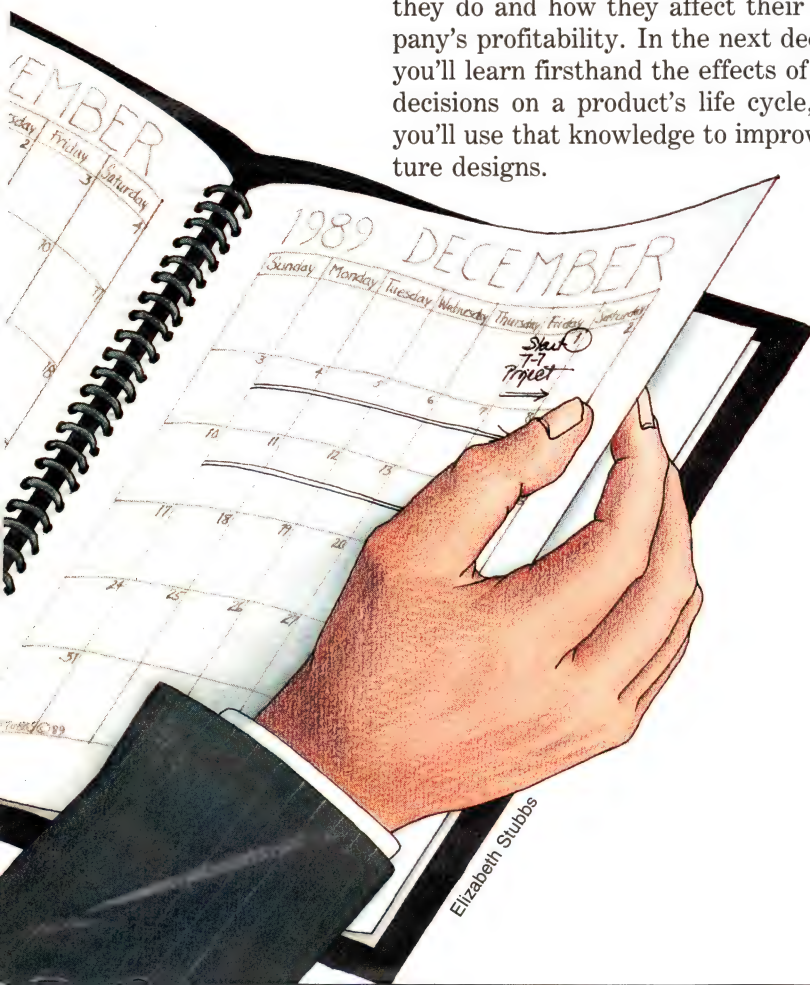However, no matter how sophisticated computers become, they will never be able to replace that old standby—the prototype. It's just not worthwhile to develop computer programs that can simulate the operation of complete and complex systems. You'll






BUSCON/90-WESTSM

FEBRUARY 13-16, 1990
LONG BEACH CONVENTION CENTER
LONG BEACH, CA

...THE BEST IN THE WEST

BUSCON '90 West promises to be the most comprehensive industry event on the west coast in 1990. All elements of board and system level technology from virtually every leading vendor in the industry will be on display along with the technical personnel to show you how it all works.

And the updated BUSCON West seminar program offers insight into the latest trends and technical developments presented by the people who are making it all happen. Be part of it. Mark your calendar now for BUSCON '90 West, February 13-16, 1990, Long Beach Convention Center, Long Beach, CA.

☐ Yes, I want more information about attending BUSCON '90 West

☐ I am interested in exhibiting

Name

Title

Company

Address

City State Zip

Phone

Send to: Conference Management Corporation
200 Connecticut Avenue, Norwalk, CT 06856-4990
Telephone: (203) 852-0500, Fax: (203) 838-3710



EDN011890

BW19

LOOKING AHEAD

still be getting your hands on real hardware.

Engineering will continue to require a mixture of hardware and software skills. Although software seems to dominate many of today's projects and products, in the next decade there will be a definite movement back to hardware design. In many designs it's already easier to change the hardware than the software.

Hardware design will change, too. Manufacturing processes will incorporate new techniques and methods, and you'll be called upon to improve the reliability of your designs. To do that you'll have to become even more involved with reliability engineering and failure analysis.

Soon computer-aided software-engineering tools will progress beyond their current disjointed state, and software engineers will become more like systems designers. You'll be working on "abstract" problems the way IC engineers now work with block diagrams and equations instead of the actual transistors and physical layouts on silicon chips. You'll be defining problems in conceptual terms rather than plotting instruction-by-instruction design strategies. The use of object-oriented programs and object-oriented languages such as C++ will change the way you think about programs and how you solve software problems.


Computer-aided software engineering will have an impact on the software engineer's job similar to the impact CAE has already had on the hardware engineer's. Software engineers will function in the same way systems design integrators do now. They'll start with definitions of "software requirements" and broad goals.

If you're an analog engineer, your job will also change. You'll find yourself working more as a device engineer does, building and analyzing ultrafast ICs. The use of simulation will grow, but you'll continue to test your designs through experimentation. As far as we can see, device models will never be accurate enough to do away with it.

Unfortunately, the ranks of analog engineers will shrink; they are already retiring faster than they are being replaced. Digital engineers will have to try to solve some analog problems—a situation that seldom delights digital engineers.

In the 1990s, your job as an engineer or engineering manager will be much broader and will require a broader vision. You'll have to be able to see beyond components and circuits, beyond systems and networks. You'll have to be able to see the entire life cycle of what you design; how it will be manufactured, marketed, and serviced; and how it will affect people's lives.

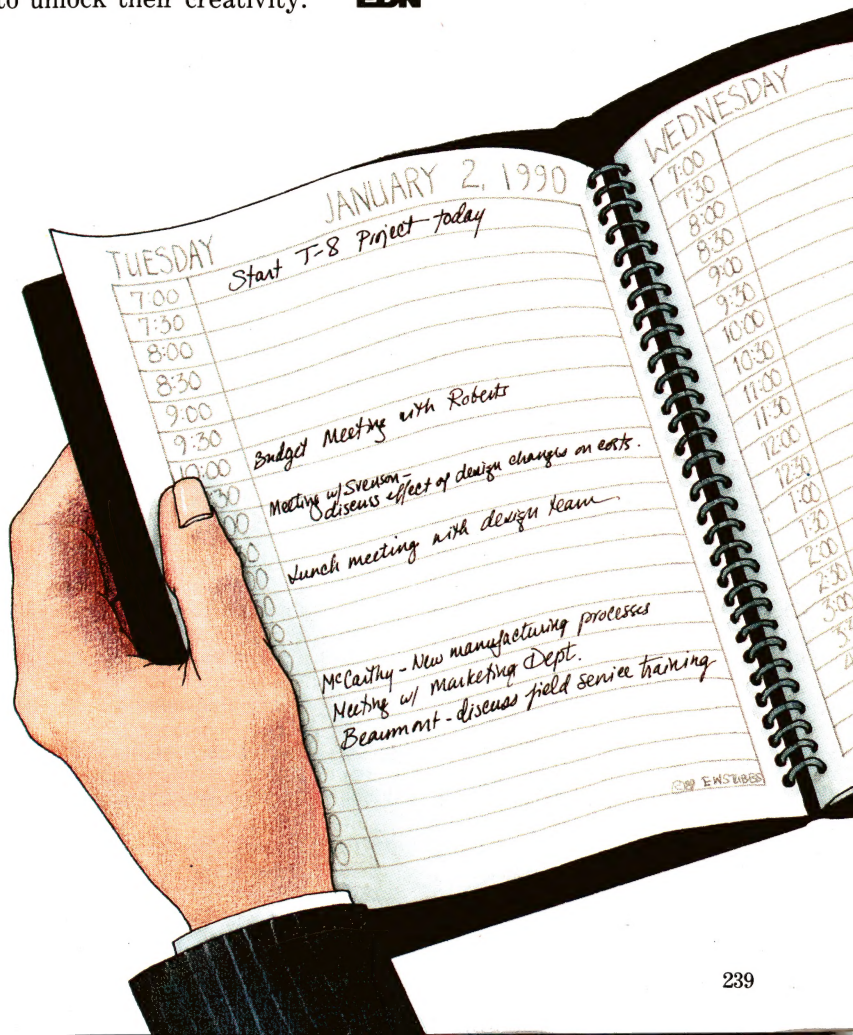Engineers who can't develop this vision will be relegated to support functions. They'll use design tools, but they'll only implement other people's designs. The engineers who will be successful in the next decade will be those who use their engineering training as a key to unlock their creativity. **EDN**



EDN's INTERNATIONAL ADVERTISERS INDEX

Academic Press	35	Hi-Techniques	86	Siemens AG**	63
ACCEL Technologies Inc	221	HyperLynx	224	Siemens Corp*	203
Adams-Macdonald Corp	222	Hypertronics Corp	231	Signetics Corp	101, 103
Advanced Micro Devices	12-13	IERC	142	Silicon Composers	221
Advance Power Supplies Inc	131	Industrial Devices Inc	202	Siliconix Inc	4
AEG Corp	40	Intel Corp	167-169	Silicon Logic	208
Aerospace Optics	81	Interactive Circuits and Systems Ltd	219	Single Board Solutions	224
Alpha Products	220	International Rectifier	C3	Spectrum Software	212, 221
American Automation	90-93	Intusoft	225	Sunrise Electronics Inc	102, 223
American Research and Engineering	62	IOtech Inc	222	System General	219
AMP	44-45	Ironwood	222	Tatum Labs	222
Ampro Computers Inc	34	ITT Cannon	64	T-Cubed Systems Inc	224
Analog Devices Inc	58	Jameco Electronics	225	TDK Corp of America	206
Analytek Ltd	32	Keithley Systems	73-75, 115	TEAC Corp**	76
Annabooks	224	Kepeco Inc	199-200	Teknor	222
Applied Microsystems Corp	48-49	Kontron Elec**	88-89	Tektronix Inc	28-29, 137
Aromat Corp	42-43	Lattice Semiconductor Corp	6	Teltona Corp	225
AT&T Technologies	150	Linear Technology Corp	181-182	Tempil Div	225
Augat	170-171	Littelfuse	191	Tempustek	220
Avantek	78	Logical Devices Inc	219	Teradyne Inc	30-31
Avocet Systems Inc	94	Logical Systems Corp	220	Themis Computer	215
Azcom	219	Macrochip Research	220	Thomas and Betts Corp*	204
B&C Microsystems	219, 223	Marshall	50	Tokin Corp	218
Bitwise Designs Inc	223	MathSoft Inc	40	Toshiba America Inc	106-107
BP Microsystems	223	Mental Automation	221	Transera	194
Brooktree Corp	109-112	Mentor Graphics Corp	10-11	TRW LSI Products Inc	23
Burr-Brown Corp	163	MetaLink Corp	223	TTE Inc	230
Buscon West '90	240	Micro Computer Specialties Inc	223	Vesta Technology Inc	220
BV Engineering	225	Micro Mo Electronics Inc	220	Vicor	14-15
Bytek Corp	222	Micron Technology Inc	195	VTC Inc	96
Caddock Electronics Inc	127	MicroStar Labs	62	Wandel & Goltermann	118-119
CAD Software Inc	176	Micro/Sys	116	Wavetek	3
Cahners CAPS	217	Microtek	192	Western Graphtec	149
Cahners Exposition Group	198	Minc Inc	210	Wintek Corp	225
Capital Equipment Corp	72	Mini-Circuits Laboratories	26-27, 179	Xeltek	220
Cermetek	221	Mitsubishi Electronics America Inc	51-56, 197	Xilinx	129
C G Instruments	38	Mitsumi	84	Yamaha LSI	66
Chomerics Inc	183	Mizar Inc	143	Zendex	225
C&K Components Inc	82	Motorola Semiconductor Products Inc*	16-17, 88-89	Ziatech Corp	1
Connor Peripherals	8	Multibus Manufacturers Group	145-148	Zilog Inc	117
Cypress Semiconductor	46	National Instruments	71	Z-World	223
Dale Electronics Inc	25	National Semiconductor Corp	130		
Data I/O Corp	C4	NCI	222		
Datalight	225	NEC Corp	114		
Data Translation Inc	83	NEC Electronics Inc	139		
Datel	142, 186	Octagon Systems	221		
Dialight Corp, A Cambridge Electronic Industries Co	165	OKI Semiconductor	36-37		
Digital Electronics Corp	132	Ontario Ministry of Industry Trade & Technology	141		
Digital Equipment Corp*	185	Orbit Semiconductor	41		
Eastman Chemical	99	OrCAD Systems Corp	87		
EG&G Vactec Inc	190	Personal CAD Systems Inc	144		
Electronic Solutions	2	Phillips Components Inc	174-175		
Emulation Technology Inc	224	Power Trends Inc	205, 207, 209		
E-T-A Circuit Breakers	224	Precision Monolithics Inc	108		
Floyd Bell	220	Pulizzi Engineering	219		
Fujitsu Component*	189	Pulse Engineering	188		
Fujitsu Microelectronics Inc	C2	Qualidyne Systems Inc	34A-D		
F & W Communications	221	Radstone Technology	226		
Gespac Inc	39	RAF Electronic Hardware Inc	224		
Graphics Technology	222	Rayovac	196		
Grayhill Inc	161	Rogers Corp	85, 221, 223-224		
Harris Semiconductor	172-173	Samtec Inc	104-105		
Heurikon Corp	57	SBE*	63		
Hewlett-Packard Co	18-19	Seagate Technology	33		
Hewlett-Packard Components	20				
Hi-Cal Design	230				
Hitachi America Ltd*	76				

Recruitment Advertising 232-236

Annapolis Micro Systems
Honeywell-Commercial Flight
Systems Group
Judge Inc
II Morrow Inc
Unisys Shipboard & Ground
Systems Group




*Advertiser in US edition

**Advertiser in International edition

This index is provided as an additional service. The publisher does not assume any liability for errors or omissions.

IRF730	IRF530	IRF350	IRF460
IRFBG30	IRL540	IRFP360	IRF9140
<u>HEXSense®</u>	<u>FULLPAK</u>	IRFP440	IRFAC50
IRCZ24	IRFIZ24	IRFP448	IRFAE50
IRCZ34	IRFI530	IRFP450	IRFAF40
IRC530	<u>SOT-89</u>	IRFP460	IRFAF50
IRC540	IRFS1Z0	IRFP9140	IRFAG50
IRC640	<u>D-PAK</u>	IRFP9240	<u>TO-39</u>
IRC634	IRFR014	IRFPC40	IRFF024
IRC730	IRFR024	IRFPC50	IRFF110
IRC830	IRFR120	IRFPE40	IRFF120
IRC840	IRFR220	IRFPE50	IRFF130
<u>HEXDIP™</u>	IRFR310	IRPFF40	IRFF420
IRFD1Z0	IRFR320	IRFPG50	IRFF9010
IRFD014	IRFR420	<u>TO-3</u>	IRFF9110
IRFD024	IRFR9014	IRF140	<u>TO-240AA</u>
IRFD110	IRFR9024	IRF150	IRFK2H250
IRFD120	IRFR9120	IRF240	IRFK2H450
IRFD210	<u>TO-18</u>	IRF250	IRFK4H350
IRFD9010	IRFF044	IRF244	IRFH145
IRFD9024	IRFP054	IRF254	IRFK6H150
			IRFK6H450

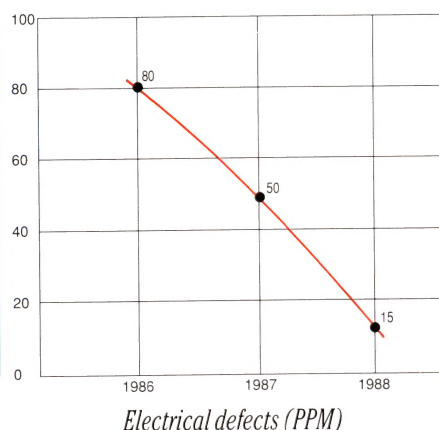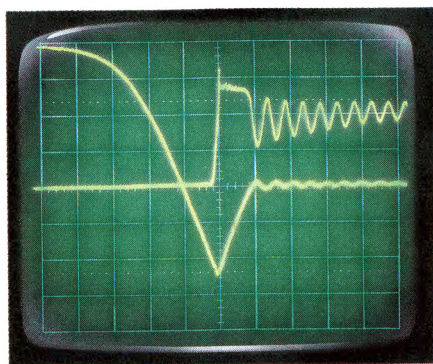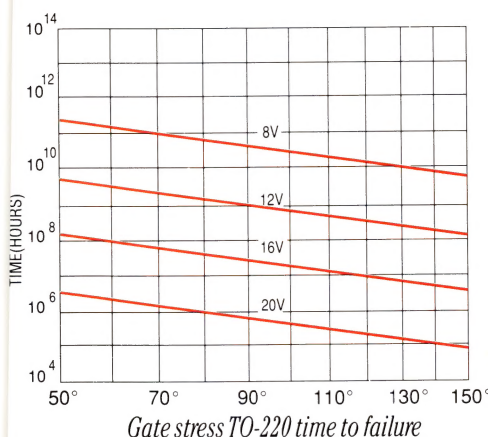They can copy these numbers. But they can't copy these.



As IR HEXFETs® hold their lead in power MOSFETs, our competitors become bolder and bolder in attempting to duplicate our success.

They're using our part numbers. And in some cases, they've even put "IR" in front of them. They've thought of everything. Except performance, ruggedness and reliability.

The numbers *in the charts* tell the story. You'll find them in our guaranteed avalanche ratings. Our quarterly reliability reports, the most comprehensive

in the industry. In AOQLs you can take right past incoming inspection to your production line.


And in our Generation III HEXFET process that's optimizing cell density and providing unparalleled performance per square inch.

The bottom line: If you're buying FETs, make sure they're IR, as in International Rectifier. Or you just might get a signed and numbered copy.

IR INTERNATIONAL RECTIFIER

WORLD HEADQUARTERS: 233 KANSAS ST., EL SEGUNDO, CA 90245 U.S.A. (213) 772-2000, TWX 910-348-6291, TELEX 472-0403
EUROPEAN HEADQUARTERS: HURST GREEN, OXTEY, SURREY RH8 9BB, ENGLAND TELEPHONE (0883) 713215, TELEX 95219

CIRCLE NO. 128

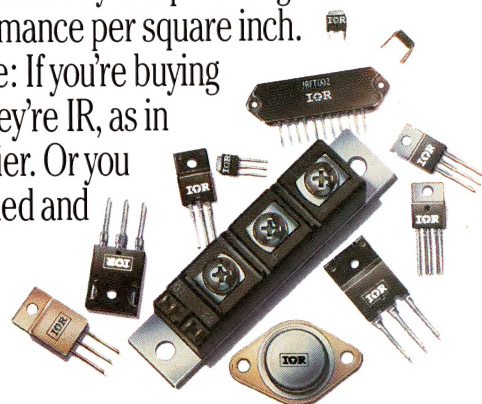



THE UNISITE PROGRAMMER: BECAUSE STATE-OF-THE-ART IS A STATE OF CHANGE.

PROGRAMMING TECHNOLOGY THAT SUPPORTS ADVANCED DESIGNS— TODAY AND TOMORROW.

The UniSite™'s universal programming technology is the fastest and easiest way to keep up with new devices and packages. Its software-configured pin driver system provides a single site for programming any DIP device up to 48 pins, including PLDs, PROMs, IFLs, FPLAs, EPROMs, EEPROMs and microcontrollers.

The optional ChipSite™ module supports logic, memory and micro-controllers in the most popular surface-mount packages—PLCCs, LCCs and SOICs. Or add SetSite™ to gang program up to eight 40-pin EPROMs, or set program a single file into multiple EPROMs.

INSTANT ACCESS TO NEW DEVICES.

The UniSite's device algorithms and system software are stored on 3 1/2"



micro diskettes, which are updated several times per year. To update the UniSite, simply load new master diskettes.

FAST, EASY PROGRAMMING. Menu-driven operation with step-by-step prompts makes programming simple. For added convenience, you can operate the UniSite from an ASCII ter-

minal or from a PC using the provided terminal emulator. On-screen help messages are available throughout operation.

To speed parts selection, the UniSite provides a built-in list of devices by manufacturer name and number. You can also save your most frequently used programming parameters and jobs for instant recall.

DESIGN FREEDOM FOR TOMORROW.

When leading-edge designers need to use the latest devices, they need the programming freedom only the UniSite provides. Call Data I/O® today, and ask about the UniSite. Because state-of-the-art never stops changing.

1-800-247-5700

Data I/O Corporation 10525 Willows Road N.E., P.O. Box 97046, Redmond, WA 98073-9746, U.S.A. (206) 867-6899/Telex 15 2167
Data I/O Canada 6725 Airport Road, Suite 302, Mississauga, Ontario L4V 1V2 (416) 678-0761
Data I/O Europe World Trade Center, Strawinskylaan 633, 1077 XX Amsterdam, The Netherlands +31 (0)20-6622866/Telex 16616 DATIO NL
Data I/O Japan Sumitomoseimei Higashishinbashi Bldg., 8F, 2-1-7, Higashi-Shinbashi, Minato-Ku, Tokyo 105, Japan
(03) 432-6991/Telex 2522685 DATAIO J

©1989 Data I/O Corporation

CIRCLE NO. 129

DATA I/O
Corporation